

Upgrading Your PC: Is It Worthwhile?

# SILICON CHIP

\$4.95 JANUARY 1996

NZ \$5.95 INCL GST

AUSTRALIA'S **DYNAMIC**  
ELECTRONICS MAGAZINE

SERVICING - VINTAGE RADIO - COMPUTERS - SATELLITE TV - PROJECTS TO BUILD



**BURP  
CHARGING  
NICAD  
BATTERIES**

## Build A Magnetic Card Reader

Read the code on your credit  
card & use it to operate a  
solenoid latch

# Surround Sound Mixer & Decoder For Camcorders

ISSN 1030-2662




01

PRINT POST APPROVED - PP255003/01272



# Especially For Model Railway Enthusiasts

Order Direct  
From  
**SILICON CHIP**

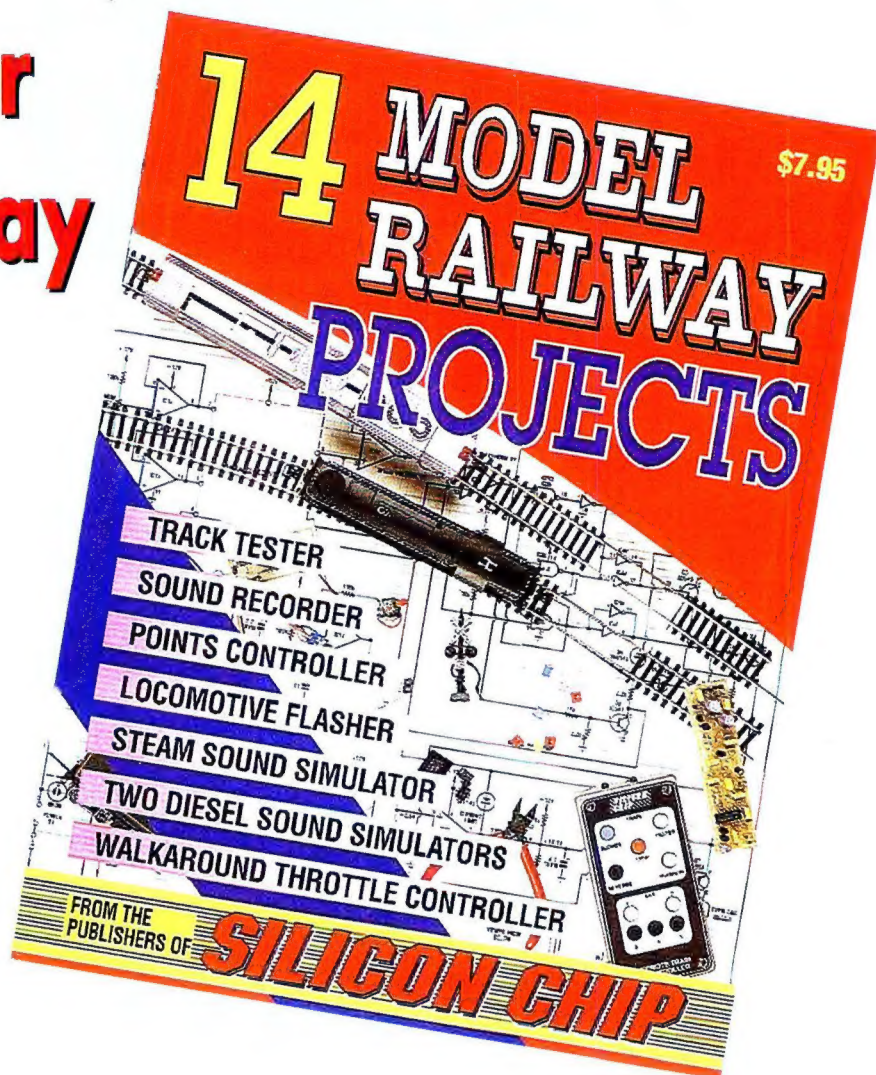

Order today by phoning (02) 9979 5644 & quoting your credit card number;  
or fill in the form below & fax it to (02) 9979 6503; or mail the form to  
PO Box 139, Collaroy, NSW 2097.

This book has 14 model railway projects for you to build, including pulse power throttle controllers, a level crossing detector with matching lights & sound effects, & diesel sound & steam sound simulators. If you are a model railway enthusiast, then this collection of projects from Silicon Chip is a must.

**Price: \$7.95  
plus \$3 p&p**

*Yes!* Please send me \_\_\_\_\_ copies of 14 Model Railway Projects

Enclosed is my cheque/money order for \$\_\_\_\_\_ or please debit my

☐ Bankcard ☐ Visa Card ☐ Master Card

Card No.

Signature \_\_\_\_\_ Card expiry date \_\_\_\_/\_\_\_\_

Name \_\_\_\_\_ Phone No (\_\_\_\_) \_\_\_\_\_

PLEASE PRINT

Street \_\_\_\_\_

Suburb/town \_\_\_\_\_ Postcode \_\_\_\_\_



# Contents

## FEATURES

### 4 LIVING WITH ENGINE-MANAGED CARS

We take a look at some of the do's and don'ts when it comes to maintaining a modern engine-managed car. Also, is it worthwhile changing the chip or are there better ways of increasing engine performance? – by Julian Edgar

### 10 RECHARGING NICAD BATTERIES FOR LONG LIFE

Nickel cadmium and nickel metal hydride batteries often don't last very long before requiring replacement. One solution is to use "burp charging" which is claimed to greatly extend battery life – by Horst Reuter

### 53 SATELLITE WATCH

A new column that gives you satellite reception reports for Australia and New Zealand – by Garry Cratt

THE DO'S AND DON'TS OF LIVING WITH  
ENGINE-MANAGED CARS – PAGE 4

## PROJECTS TO BUILD

### 22 SURROUND SOUND MIXER & DECODER

Build this unit and add depth and realism to your home videos. It provides realistic surround sound mixing and even includes a simple decoder – by John Clarke

### 40 BUILD A MAGNETIC CARD READER & DISPLAY

Check out what's written on the magnetic stripe on your credit card. This unit could also be used as the basis for an electronic door lock, restricting access to those with "authorised" cards – by Mike Zenere

### 54 THE RAIN BRAIN AUTOMATIC SPRINKLER CONTROLLER

Comes as a kit and controls up to eight solenoids plus a master solenoid. You program it yourself to selectively water any area of your garden as little or as often as you like – by Graham Blowes

### 70 IR REMOTE CONTROL FOR THE RAILPOWER Mk.2

Provides complete freedom of operation and has pushbutton control for everything. An optional speed meter is also included – by Rick Walters

## SPECIAL COLUMNS

### 32 COMPUTER BITS

Upgrading your PC; is it worthwhile? – by Geoff Cohen

### 80 SERVICEMAN'S LOG

The complaint seemed simple enough – by the TV Serviceman

### 86 VINTAGE RADIO

Converting from anode bend to diode detection – by John Hill

## DEPARTMENTS

### 2 PUBLISHER'S LETTER

### 3 MAILBAG

### 16 CIRCUIT NOTEBOOK

### 63 PRODUCT SHOWCASE


### 69 ORDER FORM

### 92 ASK SILICON CHIP

### 94 NOTES & ERRATA

### 95 MARKET CENTRE

### 96 ADVERTISING INDEX

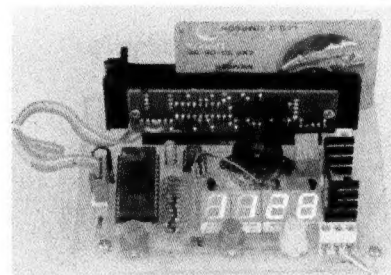

BUILD A MAGNETIC CARD READER  
& DISPLAY – PAGE 40



8-STATION SPRINKLER  
CONTROLLER – PAGE 54



IR REMOTE CONTROL FOR THE  
RAILPOWER MK.2 – PAGE 70



**Publisher & Editor-in-Chief**

Leo Simpson, B.Bus.

**Editor**

Greg Swain, B.Sc.(Hons.)

**Technical Staff**

John Clarke, B.E.(Elec.)

Robert Flynn

Rick Walters

**Reader Services**

Ann Jenkinson

**Advertising Enquiries**

Leo Simpson

Phone (02) 9979 5644

**Regular Contributors**

Brendan Akhurst

Garry Cratt, VK2YBX

Marque Crozman, VK2ZLZ

Julian Edgar, Dip.T.(Sec.), B.Ed

John Hill

Jim Lawler, MTETIA

Philip Watson, MIREE, VK2ZPW

Jim Yalden, VK2YGY

Bob Young

**Photography**

Stuart Bryce

SILICON CHIP is published 12 times a year by Silicon Chip Publications Pty Ltd. A.C.N. 003 205 490. All material copyright ©. No part of this publication may be reproduced without the written consent of the publisher.

**Printing:** Macquarie Print, Dubbo, NSW.

**Distribution:** Network Distribution Company.

**Subscription rates:** \$49 per year in Australia. For overseas rates, see the subscription page in this issue.

**Editorial & advertising offices:** Unit 34, 1-3 Jubilee Avenue, Warriewood, NSW 2102. Postal address: PO Box 139, Collaroy Beach, NSW 2097. Phone (02) 9979 5644. Fax (02) 9979 6503.

ISSN 1030-2662

# PUBLISHER'S LETTER

## Crystal balling the telephone



With the advent of the new year and the new century being not far away, it is timely to think about products that could appear in the near future. After all, with people being so conscious of computers, cellular phones, video and pay TV, the Internet and so on, it is common topic of conversation: "what will be next big consumer product?" No-one really predicted that cellular phones would be as popular as they have become and it is my opinion that another telephone derived product will be the next big seller.

An obvious derivative, to my mind, is a small computer combined with a fax machine. Perhaps it would be called a "fax terminal" or something similar. This would have a typewriter keyboard and LCD screen and probably not much storage but you could type a message on the screen and then send it to another person's fax machine. It could also receive fax messages but would not normally print them out, unless you wanted it to. Perhaps it would send a short voice message as well. You could also use it to pay bills and do all the things that a fax machine can do now. Such a machine is feasible now. It could be in many homes within five years.

Another more expensive product would be a home telephone exchange and burglar alarm system. Most small businesses have a phone system now, with three or four incoming lines and up to eight extensions. They can transfer calls, allow conferencing and operate as an intercom. Currently priced at around \$2000 to \$4000, such systems are becoming cheaper all the time. Five years ago, equivalent systems were priced at around \$8000 or more and are now just starting to be installed in larger homes where their convenience is really appreciated – no more shouting to call people to the phone, no more running to answer the phone and so on.

Such a system could be extended to provide a full home security system, with computer interfacing as well. You could be able to connect a computer modem to any handset so that any member of the household could connect to the outside world. How long before we see such a product marketed I wonder?

Further into the future, with the advent of highly compressed video and optical fibres, it seems likely that video phones are just a matter of time. It is not hard to envisage several or most rooms of a household having a video terminal which will do everything: provide entertainment, phone and computer services, the whole bit.

There are more variants on this theme but essentially they are all derivatives of the humble telephone. Who would have thought we want or need more telephones?

**Leo Simpson**

### WARNING!

SILICON CHIP magazine regularly describes projects which employ a mains power supply or produce high voltage. All such projects should be considered dangerous or even lethal if not used safely. Readers are warned that high voltage wiring should be carried out according to the instructions in the articles. When working on these projects use extreme care to ensure that you do not accidentally come into contact with mains AC voltages or high voltage DC. If you are not confident about working with projects employing mains voltages or other high voltages, you are advised not to attempt work on them. Silicon Chip Publications Pty Ltd disclaims any liability for damages should anyone be killed or injured while working on a project or circuit described in any issue of SILICON CHIP magazine. Devices or circuits described in SILICON CHIP may be covered by patents. SILICON CHIP disclaims any liability for the infringement of such patents by the manufacturing or selling of any such equipment. SILICON CHIP also disclaims any liability for projects which are used in such a way as to infringe relevant government regulations and by-laws.

Advertisers are warned that they are responsible for the content of all advertisements and that they must conform to the Trade Practices Act 1974 or as subsequently amended and to any governmental regulations which are applicable.



# MAILBAG

## Old house wiring is often dangerous

I would like to comment on your Publisher's Letter, November 1995, on the subject of house wiring safety. Congratulations for raising this subject. You state the house was built before 1950. This is significant. You express surprise that the study power point was not earthed. At the time the house was wired, unless the room was considered an earthed situation, the wiring regulations did not require earthing of the power point. This would also apply to most bedrooms.

It was not until the 1960 wiring rules that earthing was mandatory. I was employed as a Supply Authority Inspector from 1966 until retirement. While working in a country power station in the 1950s, we received pages of interpretations on the wiring rules, including three pages explaining where earthing was required or not.

I could never understand the type of thinking that permitted and perpetuated non-earthing of power points. It is virtually a booby trap for someone. The installation of a circuit breaker switchboard with old wiring would have been a good first move towards a complete rewire.

**R. Brownjohn,**  
Charlton, Vic.

## Pinking vs pingping: which is correct?

I notice that in his article on "Knock Sensing" (SILICON CHIP, December 1995), Julian Edgar refers to the term "pinging" as "a light, barely observable knock". Although this term is widely used, it is not correct.

In a package put out by the ABC a few years ago, called "Know Your Car", the speaker refers to this phenomenon as "pinking". I thought that this was a language problem at the time, so I checked and found that he was correct. I double checked today in the Macquarie Dictionary and see that it seems to be still right. This may not be really impor-

tant but I feel that Julian would appreciate the point. I would also like to thank him for his many interesting and informative articles.

**L. Cook,**  
Numurkah, Vic.

*Comment: the Macquarie Dictionary gives both terms as descriptive of knocking. We prefer "pinging" as it seems to be the most widely used in the trade. "Pingping" is also more precise in terms of onomatopoeia – it imitates the actual sound.*

## Oxygen sensor is the hard way

Your fuel injector article in November was interesting but, given the simple way the mixture or "burn" of the typical aircraft piston engine is sensed, controlling it by exhaust oxygen seems to be the hard way. Especially with lower-powered, carburetted mills, exhaust gas temperature (EGT), metered with a simple thermocouple, is often used to gauge the burn. The latter is leaned out until EGT peaks, indicating maximum combustion heat and least fuel flow at the extant throttle setting.

If cylinder head temperature, sensed by a couple on the hottest jug, is too high, the burn is richened to cool it down. (On larger mills, the mixture control is usually set to auto lean). Jug temperature alone can be used but either ploy optimises shaft horsepower for the fuel used. Although such a mill may run with near-constant parameters for some hours (easing the problem), why wouldn't EGT controllers work as well for autos?

**G. Lindley,**  
Redfern, NSW.

*Comment: your remarks about the ease of monitoring exhaust temperature are no doubt correct but the reason for monitoring exhaust oxygen content is to obtain the best compromise between carbon monoxide on the one hand and nitrogen oxides (NO<sub>x</sub>) on the other. Simply maximising exhaust temperature will lead to excessive nitrogen oxide production.*

# SATELLITE SUPPLIES

## Aussat systems from under \$850

SATELLITE RECEIVERS FROM \$280


LNB's Ku FROM ..... \$229

LNB's C FROM ..... \$330

FEEDHORNS Ku BAND FROM .... \$45


FEEDHORNS C.BAND FROM ..... \$95

DISHES 60m to 3.7m FROM ..... \$130

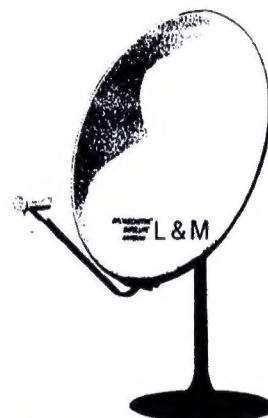

**LOTS OF OTHER ITEMS  
FROM COAXIAL CABLE,  
DECODERS, ANGLE ME-  
TERS, IN-LINE COAX AMPS,  
PAY-TV DECODER FOR  
JAPANESE, NTSC TO PAL  
TRANSCODERS, E-PAL  
DECODERS, PLUS MANY  
MORE**

**For a free catalogue, fill in & mail  
or fax this coupon.**

 Please send me a free catalog  
on your satellite systems.

Name: \_\_\_\_\_

Street: \_\_\_\_\_

Suburb: \_\_\_\_\_

P/code \_\_\_\_\_ Phone \_\_\_\_\_

**L&M Satellite Supplies**

33-35 Wickham Rd, Moorabin 3189  
Ph (03) 9553 1763; Fax (03) 9532 2957



# ***The do's & don'ts of*** **Living with** **engine-managed**


**While over the last few years we've covered in detail the technical make-up of current cars' electronic engine control systems, a more general treatment of what the average owner should and should not do with their car has been lacking. Here's the remedy!**

By JULIAN EDGAR

In general, the engineers employed by the car manufacturers really do know best – they're the people who have worked with the investment of millions of dollars in developing the technology. This means that the maintenance schedule laid out in the owners' manual should be followed to the

letter. It doesn't, however, necessarily mean that the official dealer needs to do the servicing of the car.

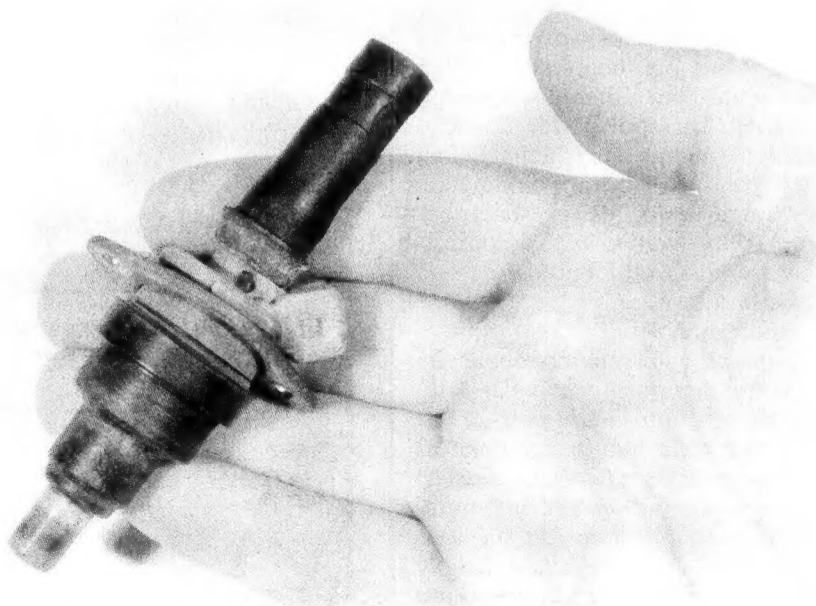Many dealer mechanics in my experience are quite ignorant about the cars for which they're supposed to be experts and do quite illogical things in response to perceived problems.



**Injector blockage can be avoided by regularly replacing the fuel filter. In addition, injector removal and back-flushing every 50,000km or so can be a worthwhile service precaution.**

An example of this is where, during a routine service, a dealer-trained mechanic instigated an ECU self-check investigation because he thought that the exhaust note of my car 'sounded funny'. Given that the car runs a modified 75cm diameter exhaust with free-flow mufflers, it wasn't surprising that the exhaust note was non-standard! But checking this by using the self-diagnosis function of the ECU...?

Having said this, there are some mechanics who really do take their marque to heart and have an incredibly detailed knowledge about their cars. If you find such a mechanic stick with him (or her) but unfortunately they are few and far between.

## **General maintenance**


The frequently advertised invitations to use oil additives or "upper cylinder lubricant" can generally be ignored – unless specified in the official maintenance schedule. However, the occasional use of an in-tank injector cleaning additive can be a worthwhile addition to the manufacturer's recommendations. Also, about every 50,000km or so, the injectors can be removed and back-flushed to clean their inbuilt filters.

However, note that injector problems are much more likely to occur if the fuel filter is not changed at the recommended service intervals. I've not bothered having the injectors removed for cleaning in any of my six EFI cars (some with more than 170,000km on the clock) but note that I have regularly changed the fuel filter.

Most engine-managed cars use high combustion pressures to achieve efficiency (and so fuel economy) gains.



# cars

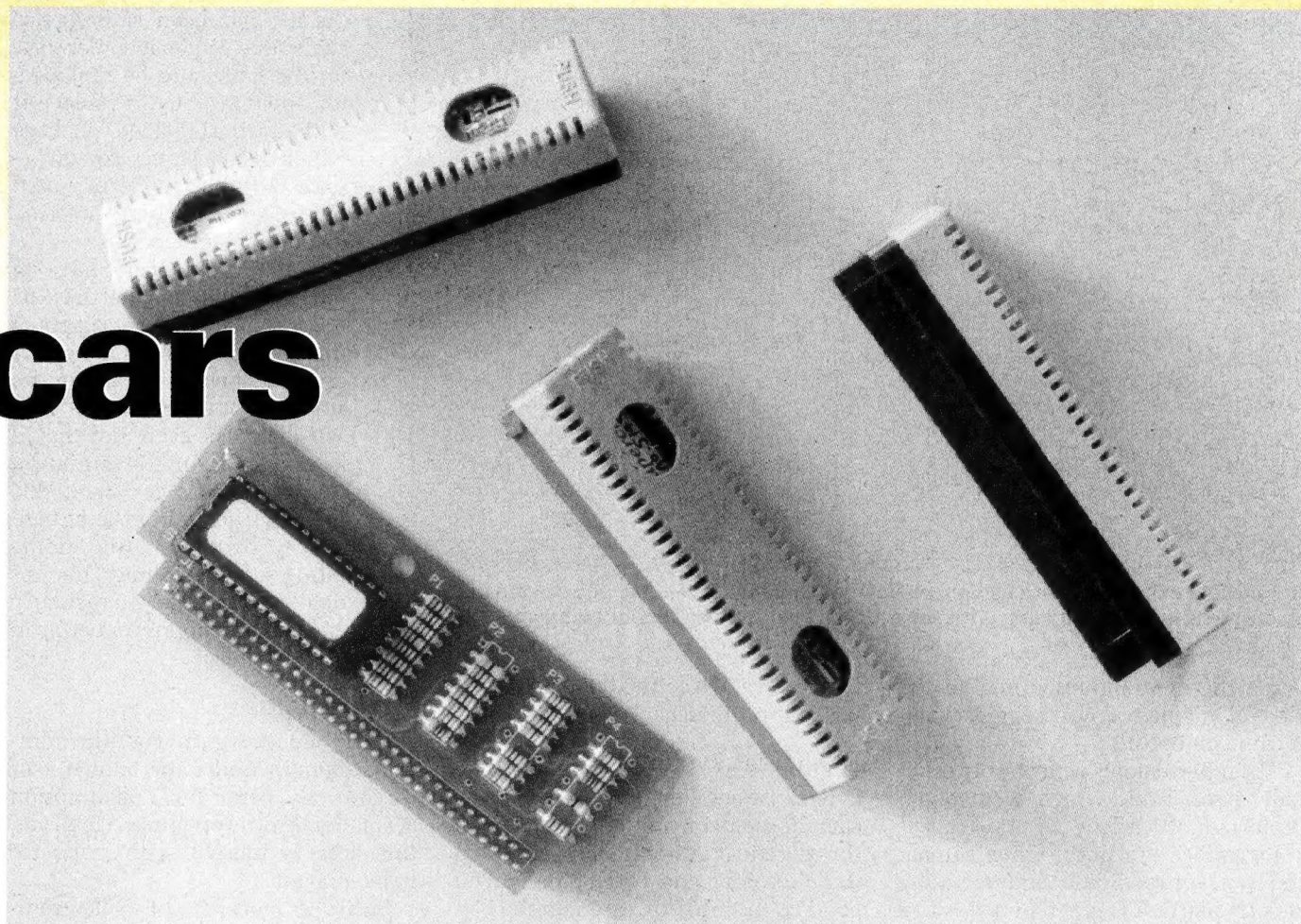


Firing the spark with high cylinder pressures requires a high-energy ignition system and these do not respond happily to high tension leads which are losing their insulation integrity. The best replacements for worn leads are usually the original equipment products – unless they are terribly expensive. But surely a set drawn from

the plethora of aftermarket leads would give better results? An example tells an interesting story.

I once covered the building of a very powerful Nissan FJ20 turbo four cylinder engine. Having a standard power of 200bhp, this particular race unit used a new turbo, was run on methanol using fully-programmable

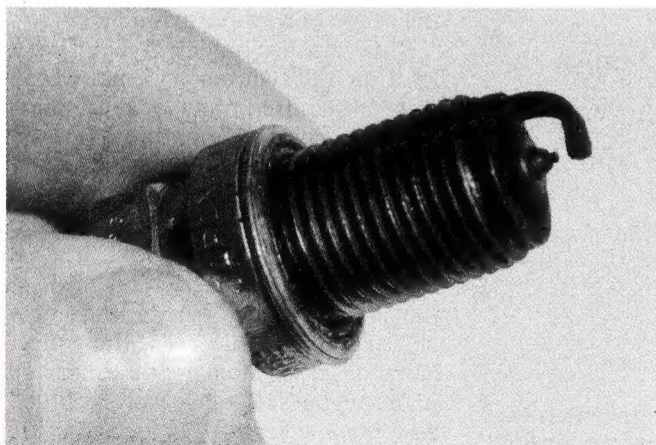**Changing the ECU's main memory chip is unlikely to give any noticeable improvement in power, with independent tests showing that losses are as likely as gains.**

engine management and ended up producing just over 400bhp! Some very high-tech spark plug leads were initially tried but were soon discarded



Many current cars require a spark plug change only every 50,000 or 100,000 kilometres. Reducing the quality of the replacement plug will result in poor performance.



High energy ignition systems place great demands on the ignition leads. Experience has shown that the original equipment leads are often the best.





**A modified exhaust system using free-flow mufflers will result in power gains in electronically managed cars, with the average peak-power benefit being about 10%.**

when the dyno-mounted engine put on a full display of pyrotechnics when it came on boost!


The replacements were the old original Nissan leads which went on to perform faultlessly.

Likewise, be careful when replacing spark-plugs. Some manufacturers specify platinum-tipped plugs, with a service interval of 50,000 or 100,000 kilometres. When they come due for replacement they will be expensive but they will also go on to perform for

the next 50,000 or 100,000 kilometres without problems!
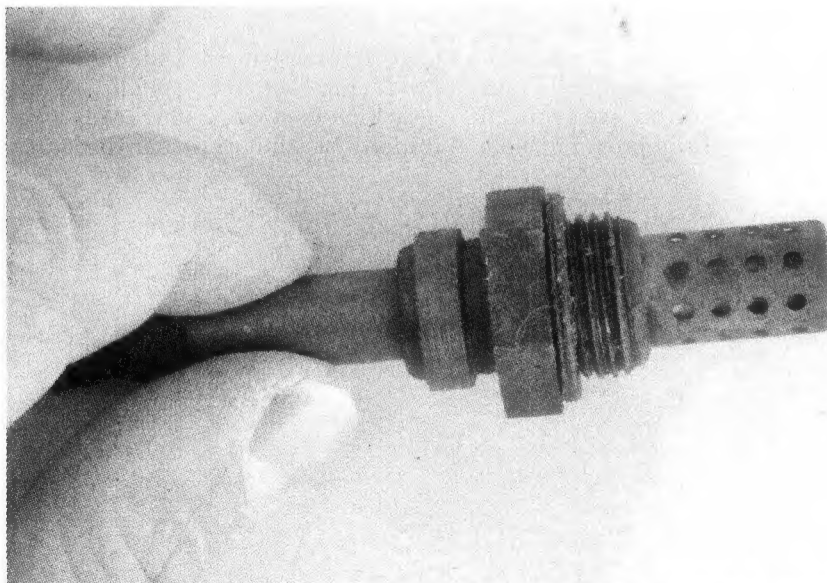
### Electrical system

Because engine-managed cars place a larger-than-conventional demand on the electrical system, make sure that the alternator and battery remain in good condition. Corrosion on the battery terminals can result in more than just poor headlight performance and it can be illuminating to feel the temperature of the battery terminals after



**One reason that frequent tune-ups are no longer required in modern cars is the presence of an exhaust gas oxygen sensor. This constantly indicates the air/fuel mixture strength to the ECU. The changes made to injector pulse widths as the result of this information allows the system to take into account changing parameters such as engine wear.**

the car has been running for some time. When it comes time for the battery to be replaced, it's advantageous to replace it with a similar-sized package which has a larger capacity – especially if you live in a cold environment where starting loads will be high.

If your car does not have an on-dash indication that the ECU has logged a problem (that is, if there is no “Check Engine” or equivalent warning light), make sure that you perform an ECU self-diagnosis each time the oil is changed. In the situation where it has a problem, this prevents the car from being constantly driven in limp-home mode – which may be undetectable unless you regularly check fuel economy or performance figures.

### Engine mods

Everyone likes getting a little additional oomph under the bonnet – or its corollary, better fuel consumption at smaller throttle openings. However, this area is fraught with traps for naive players.

Basically, modification of electronically engine managed cars can be divided into four different categories: (1) chip changes in otherwise standard engines; (2) inlet and exhaust changes; (3) turbocharger boost pressure changes (obviously, only in turbo engines); and (4) major mechanical modifications (porting, cams, compression ratio and so on).

The last item on the list can result in substantial gains in engine power but its detailed examination is beyond the scope of this magazine.

Chip changes (which give different ignition and fuel maps to that which exist as standard) may look attractive but in general give little or no real benefit. In fact, in some cases the performance can actually be worsened! Chassis dynamometer testing of a variety of ECU chips installed in a VR V6 Commodore gives a good guide to the changes made by installing a new chip alone. In this case, the power gains or losses at each 500 RPM step in the engine's rev range were recorded and then averaged. The results are shown in Table 1, the comparison being against the standard Holden chip.

As can be seen, there was a greater



**Table 1: Chip Substitution Results**

Chip	Average Gain Or Loss Across Rev Range
A	1.6% loss
B	1.7% loss
C	1.0% gain
D	1.9% loss
E	0.6% gain
Standard Chip + PULP	1.9% gain


overall power gain (1.9%) made by simply filling the tank with premium unleaded petrol (PULP) while retaining the standard chip! And a gain of just 1.9% is quite trivial. In short, making just a chip change (in a car which doesn't use forced induction) is likely to make no discernible difference to its performance. This is not the case when mechanical modifications have been made, where the fuel and ignition requirements may well have changed from standard.

Intake and exhaust changes can improve power and economy. Fitting extractors and a larger exhaust system will improve peak power output by approximately 10% in most late-model cars. Fuel economy will also be improved, with a gain of 10-20% realisable in country running. Incidentally, the noise output of the exhaust will also increase but this may not be discernible from within the cabin.

Changing the air filter in the standard box – as is advocated in numerous magazine advertisements – will gain very little power and in some cases will actually reduce power. Chassis dyno tests undertaken on both a late-model Falcon and a late-model Commodore showed, if anything, power reductions with a top aftermarket filter installed in the box. And that was in comparison with a dirty standard filter!

Ducting cold outside air to the filter's air box will improve power in many EFI cars. Using plastic stormwater pipe and fittings (painted black) is an efficient and cost-effective way of doing this. If a new air pick-up point is used, more frequent changing of the air filter element may be needed, as a greater quantity of dust is ingested. However, power gains of 5% are easily achieved in this way for under \$50.

Lifting turbo boost pressure by 20-

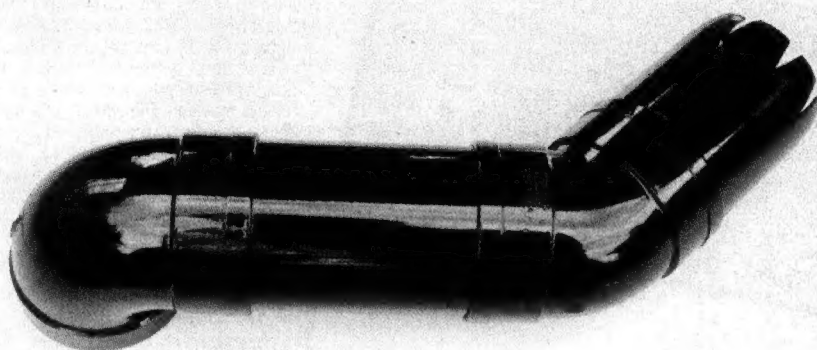

Ducting cold air into the standard air filter box can result in power gains of 5% for less than \$50. The trade-off is the requirement for more frequent air filter changes as more dust is usually ingested.



A cold air intake duct can be made from plastic stormwater pipe and fittings, painted black with a spray-can. The hole saw was used to cut a path through the inner guard.

30% in turbo cars will invariably result in an increase in engine power, with no negatives to speak of. If you undertake this course of action, fuel with an appropriate octane rating (for example, premium unleaded) will usually need to be used but there will be no other costs while an agreeable increase in power will be realised. Note that there is usually no need for ECU software changes – sufficient latitude has been built into the fuel system to cope with this type of increase in power.

## Conclusion

The electronic side of current cars is usually much more reliable than the old-tech equivalent systems. This

generalisation isn't always the case, of course but most engine-managed cars will run reliably for 150,000km+ without even the need for a traditional tune-up.

Incidentally, if paying large amounts for a tune, ask what is actually being done. In most current cars there's no need for plug changes, points regapping, mixture adjustment and so on and so a "full tune" can sometimes involve just an oil and filter change, together with a quick visual once-over.

In terms of gaining more power easily, in non-turbo cars the fitting of a good exhaust and extractors will give the best cost/benefit. In turbo cars, fit the modified exhaust and also lift turbo boost a little.

SC




# OATLEY ELECTRONICS

PO Box 89, Oatley, NSW 2223  
Phone (02) 579 4985 Fax (02) 570 7910  
Bankcard, Master Card, Visa Card &  
Amex accepted with phone & fax  
orders. P & P for most mixed orders:  
Aust. \$4-\$10; NZ (airmail) \$10. Orders  
by EMAIL: [oatley@world.net](mailto:oatley@world.net)
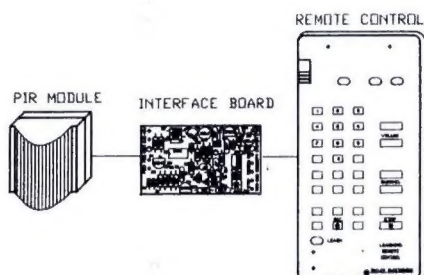
## DOMESTIC VCR TIME LAPSE RECORDING KIT

Commercial time lapse video recorders can cost thousands of dollars! This kit can achieve the same results with a standard IR remote controlled domestic VCR. The kit incorporates a ready made PIR detector module and learning remote control combination which can trigger any domestic IR remote controlled VCR to RECORD human activity within a 6m range with a 180 deg view. Starts VCR recording at the first movement and ceases recording a few minutes after the last movement has stopped. Just like commercial CCD-video recording systems costing \$1000+. No connection needed to your existing VCR. Includes small PIR



detection module which can be remotely placed, control kit, IR learning remote control and instructions: **\$80 (K48)**, \$65 when purchased with a CCD camera (this price also applies to previous purchasers of our CCD cameras, proof required).

## SIREN USING SPEAKER

Uses the same siren driver circuit as in the "Protect anything alarm kit". 4" cone/8Ω speaker is included. Generates a very irritating sound that is useful to far greater distances than expensive piezo screamers. Has penetrating high and low frequency components. Based around a 40106 hex Schmitt trigger inverter IC. Output has frequency components between 500Hz and 4KHz. Current consumption is about 0.5A at 12V. PCB: 46 x 40mm. As a bonus, we include all the extra PCBs as used in the "Protect anything alarm kit": **\$12**

## IR SWITCH/SECURITY REMOTE/REPEATER

Uses a commercial coded IR transmitter and a receiver kit. UP TO 15M RANGE!! IR transmitter has one button and is powered from 9V. Size 115 x 33 x 22mm. The transmitter uses a UM3750 (which is a combined coding and decoding chip). The receiver uses a receiving module to pick up the 40KHz IR signal. This demodulated code is simply detected and not decoded. The detected level switches a 4013 wired as a toggle flip flop. The 4013 switches a transistor which switches on a relay. We also show the circuit to enable these components to be used as a high security IR remote. This uses the UM3750 IC in the transmitter board as a decoder, while a second IR transmitter is used. The relay is only energised provided correct code is received. UM3750 has 12 coding inputs. You program

your own personal code into the transmitter and receiver UM3750. Note: you need to purchase two IR transmitters & one receiver kit to make this high security remote. We also show how to make an IR remote repeater. This works with most remote controls. The output of the receiver module is connected to the IR LED driving circuit of the IR transmitter. This re-transmits, giving an extension in range of up to 15m. You will need to purchase one transmitter & one receiver to make this IR repeater.

1 transmitter + 1 receiver: **\$18**. 2 transmitters + 1 receiver: **\$28 (K66)**.


## FM TRANSMITTER MK1 KIT

Ref: EA Nov 93. Our smallest FM transmitter kit. Typical range is about 50m. Stable design, although not as stable to handling as our MkII kit. Has high audio sensitivity. Circuit has two transistors. The complete transmitter PCB (miniature electret microphone included) is the size of an "AA" battery and it is powered by a single "AA" battery. We use a two "AA" battery holder (included in kit) for the case and a battery clip (shorted) for the switch. Estimated battery life is over 500 hours. PCB: 46 x 15mm: **\$12 ea. or 3 for \$33 (K10)**.
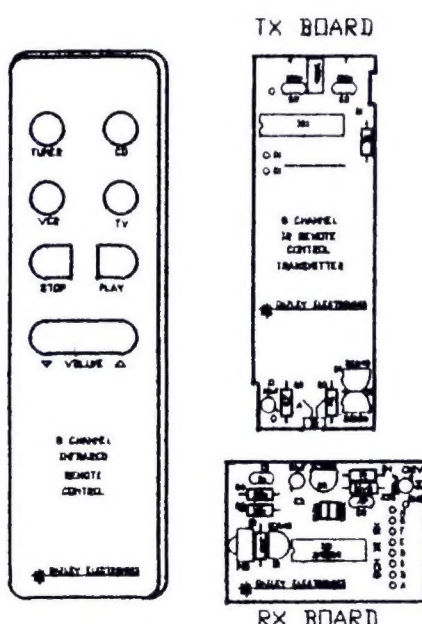
## FM TRANSMITTER KIT MKII

Ref: SC Oct 93. This low cost FM transmitter features pre-emphasis, high audio sensitivity (easily picks up normal conversation in a large room), a range of around 100 metres and excellent frequency stability. The specifications are as follows: tuning range: 88-108MHz, supply voltage 6-12V, current consumption @ 9V: 3.5mA, pre-emphasis: 75µs, frequency response: 40Hz to greater than 15kHz, S/N ratio greater than 60dB, sensitivity for full deviation: 20mV, frequency stability with extreme antenna movements 0.03%, PCB dimensions 25 x 43mm. Construction is easy and no coil winding is necessary as the coil is pre-assembled in a shielded metal can. The solder masked and screened PCB also makes for easy construction. The kit includes a PCB and all the on-board components, an electret microphone and a 9V battery clip. **\$12 ea. or buy 3 for \$33**.

**LOW COST 8 CHANNEL IR REMOTE CONTROL**  
AN EIGHT CHANNEL REMOTE CONTROL TRANSMITTER AND RECEIVER FOR A TOTAL OF \$36!! This kit




converts a brand new compact CD IR remote control, into an IR remote using a multichannel encoder IC. We simply use the commercial housing and 8 keys, and replace the existing transmitter PCB with our PCB. The receiver employs a high quality, high sensitivity IR receiver module (up to 15m RANGE!) and a matching decoding IC. There are 8 outputs. Two of these are toggling outputs. The other six are momentary outputs (ie output is on only whilst corresponding transmitter button is pressed). To convert the TTL momentary outputs to drive a relay, or a latching relay, you could use our "4ch relay kit": Information follows. The system also features a Customer Code with 4 combinations making it possible to use up to four systems in the same room/layout, or the possibility to extend the total number of channels to 32! Transmitter PCB: 89 x 30mm. Receiver PCB: 48 x 34mm.

**Transmitter kit: \$18. Receiver kit: \$18.**

The above mentioned 4CH RELAY KIT was published in SC (Circuit Notebook) Aug 95. This kit drives any of four relays according to logic level input voltage to any of the four inputs. The relays can be arranged for either toggling operation or momentary operation whenever a "one" logic level is inputted. Very low "stand-by" current. Four LEDs indicate when each relay is switched on. The relays have a contact current rating of 2A. 12V operation. PCB: 100 x 100mm: **\$25 (K68)**.
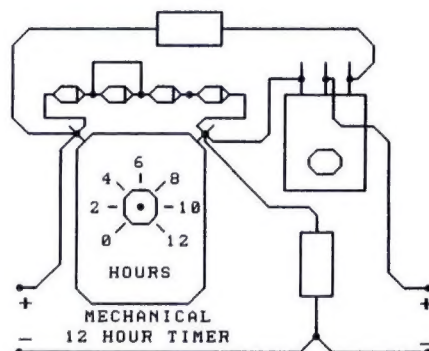
## BATTERY CHARGER WITH MECHANICAL TIMER

Simple kit which is based on a commercial 12 hour mechanical timer switch which sets the battery charging period from 0 to 12 hrs. Timer clock mechanism is wound-up and started by turning the knob to the desired time setting. Linear dial with 2hrs. timing per



45 deg of rotation, eg 270 deg rotation for 12hr. setting. The contacts on the timer are used to switch on a simple constant current source. Employs a power transistor and 5 additional components. Can easily be "hard wired". We supply a circuit, a wiring diagram, and tables showing how to select the charging current: changing one resistor value. Ideal for most rechargeable batteries. As an example most gel cells can be charged at a current which is equal to the battery capacity rating divided by 5-10. Therefore if you have a discharged gel cell that has 5Ah capacity and are using a charge current of 500mA, the timer should be set for about 11 hours (which includes 10% overtime), or 5.5 hours @ 1A. This circuit is suitable for up to approximately 5A, but additional heatsinking would be required at currents greater than 2A. Parts and instructions are only supplied in this kit. Includes a hobby box with aluminium cover that doubles up as a heatsink, timer switch, large knob, power transistor and a few other small components to give you a wide selection of charge current. You will also need a DC supply with an output voltage which is greater by about 2V than the highest battery voltage you need to charge. As an example a cheap standard car battery charger could be used as the power source to charge any chargeable battery with a voltage range of 0-15V:

**\$15**



## 27MHz RECEIVERS

Brand new military grade 27MHz single channel telemetry receivers. Enclosed in waterproof die cast metal boxes, telescopic antenna supplied. 270 x 145 x 65mm 2.8kg. Two separate PCBs: receiver PCB has audio output; signal filter/squelch PCB is used to detect various tones. Circuit provided: **\$20.**

## LIMITED SPECIALS

New 6J7 and 6AV6 valves: **\$6 ea. or 10 for \$40** (Mix OK) \* New large (150 x 150 mm face) square professional moving iron 1500A AC current meter movements with mounting hardware, need current transformer which is not supplied, basic movement 5A for 750A reading: **\$18** \* One only used Tektronix 434 dual trace 25MHz storage CRO: **\$590** \* Two only brand new military grade FLYING INTERCOMS made by MARCONI MARINE, two headsets plus two matching control units, incredible quality: **\$330 for the lot** \* Three only FLUKE 803B Differential AC-DC voltmeters: **\$65.**

## CCD CAMERA

Very small PCB CCD Camera including Auto Iris lens: 0.1Lux, 320K pixels, IR responsive, has 6 IR LEDs on PCB. Slightly bigger than a box of matches!: **\$180.**

## VISIBLE LASER DIODE KIT

A 5mW/670nm visible laser diode plus a collimating lens, plus a housing, plus an APC driver kit (Sept 94 EA). **UNBELIEVABLE PRICE: \$40.** Suitable case & battery holder to make pointer as in EA Nov 95 \$5 extra.

## 12V-2.5 WATT SOLAR PANEL KITS

These US made amorphous glass solar panels only need terminating and weather proofing. We provide clips and backing glass. Very easy to complete. Dimensions: 305 x 228mm, Vo-c: 18-20V, Is-c: 250mA. **SPECIAL PRICE: \$20 ea. or 4 for \$60.** A very efficient switching regulator kit is available: suits 12-24V batteries, 0.1-16A panels, \$27. Also available is a simple & efficient shunt regulator kit, \$5.

## SOLID STATE "PELTIER EFFECT" DEVICES SPECIAL

We have reduced the price of our peltiers! These can be used to make a solid state thermoelectric cooler/heater. Basic information supplied: 12V-4.4A PELTIER DEVICE: \$25. We can also provide two thermal cutout switches, and a 12V DC fan to suit either of the above, for an additional price of \$10.

## LEARNING - UNIVERSAL REMOTE CONTROL

These Learning IR Remote Controls can be used to replace up to eight dedicated IR Remote Controls: **\$45.**

## HELIUM - NEON LASER BARGAIN

Helium Neon 633nm red laser heads (ie tubes sealed in a tubular metal case with an inbuilt ballast resistor) that were removed from equipment that is less than 5 years old. These are suitable for light shows. Output power is in the range of 2.5-7.5mW. Heads are grouped according to output power range. Dimensions of the head are 380mm long and 45mm diameter. Weight: 0.6kg. A special high voltage supply is required to operate these heads. With each tube we will include our 12V Universal Laser power supply kit MkIV (our new transformers don't fail). Warning: involves high voltage operation at a very dangerous energy level. **SUPER SPECIAL: \$80 for a 2.5-4.0mW tube and supply. \$130 for a 4.0-6.5mW tube and supply.** This combination will require a source of 12V @ at least 2.0A. A 12V gel battery or car battery is suitable, or if 240V operation is required our Wang computer power supply (cat number P01) is ideal. Our SPECIAL PRICE for the Wang power supply when purchased with matching laser head/inverter kit is an additional \$10.

## ARGON-ION HEADS

Used Argon-Ion heads with 30-100mW output in the

blue - green spectrum. Head only supplied. Needs 3Vac @ 15A for the filament and approx 100Vdc @ 10A into the driver circuitry that is built into the head. We provide a circuit for a suitable power supply the main cost of which is for the large transformer required: \$170 from the mentioned supplier. Basic information on power supply provided. Dimensions: 35 x 16 x 16cm. Weight: 5.9kg. 1 year guarantee on head. Price graded according to hours on the hour meter. We had no serious problems with any of these heads as they were used at a very low current in their original application. Argon heads only, 4 to 8 thousand hours: **\$350.** Argon heads only, 8 to 13 thousand hours: **\$250.**

## MASTHEAD AMPLIFIER SPECIAL

High performance low noise masthead amplifier covers VHF-FM UHF and is based on a MAR-6 IC. Includes two PCBs, all on-board components. For a limited time we will also include a suitable plugpack to power the amplifier from mains for a total price of: **\$25.**

## COMPUTER CONTROLLED STEPPER MOTOR DRIVER KIT

This kit will drive two 4, 5, 6 or 8 wire stepper motors from an IBM computer parallel port. The motors require a separate power supply (not included). A detailed manual on the computer control of motors plus circuit diagrams and descriptions are provided. Software is also supplied, on a 3.5" disk. PCB: 153 x 45mm. Great low cost educational kit. We provide the PCB and all on-board components kit, manual, disk with software, plus two stepper motors of your choice for a special price. Choose motors from M17/M18/M35. **\$44.** Kit without motors is also available: **\$32.**

## LOW COST IR ILLUMINATOR

Illuminates night viewers or CCD cameras using 42 of our 880nm/30mW/12 degrees IR LEDs. Power output (and power consumption) is variable, using a trimpotentiometer. Operates from 10 to 15V and consumes from 5mA up to 0.6A (at maximum power). The LEDs are arranged into 6 strings of 7 series LEDs with each string controlled by an adjustable constant current source. PCB: 83 x 52mm: **\$40 (K36).**

## VHF MODULATOR FOR B/W CAMERAS

(To be published, EA) Simple modulator which can be adjusted to operate between about channels 7 & 11 in the VHF TV band. This is designed for use in conjunction with monochrome CCD cameras to give adequate results with a cheap TV. The incoming video simply directly modulates the VHF oscillator. This allows operation with a TV without the necessity of connecting up wires, if not desired, by simply placing the modulator within about 50cm from the TV antenna. Suits PAL and NTSC systems. PCB: 63 x 37mm: **\$12 (K63).**

## SOUND FOR CCD CAMERAS/UNIVERSAL AMPLIFIER

(To be published, EA). Uses an LM386 audio amplifier IC & a BC548 pre-amp. Signals picked up from an electret microphone are amplified & drives a speaker. Intended for use for listening to sound in the location of a CCD camera installation, but this kit could be used as a simple utility amp. Very high audio gain (adjustable) makes this unit suitable for use with directional parabolic reflectors etc. PCB: 63 x 37mm: **\$10 (K64).**

## LOW COST 1 to 2 CHANNEL UHF REMOTE CONTROL

(To be published, SC) A single channel 304MHz UHF remote control with over 1/2 million code combinations, which also makes provision for a second channel expansion. The low cost design has a 2A relay contact output. The 1ch transmitter (K41) can be used to control one channel of the receiver. To access the second channel when another transmitter is purchased, the other transmitter is coded differently. Alternatively, the 3ch transmitter kit (K40) as used with the 4ch receiver kit is compatible with this receiver and allows access to both channels from the one transmitter. Note

that the receiver uses two separate decoder ICs. This receiver operates from 10 to 15Vdc. Range is up to about 40m. 1ch Rx kit: **\$22 (K26).** Expansion components (to convert the receiver to 2 channel operation; extra decoder IC and relay): **\$6.**

## ONE CHANNEL UHF TRANSMITTER

AX5326 encoder. Transmit frequency adjustable by trimcap. Centred around 304MHz. Powered from 12V lighter battery. LED flashes when transmitting. Size of transmitter case: 67 x 30 x 13 mm. This kit is trickier to assemble than the 3ch UHF transmitter: **\$11.**

## NEW CATALOGUE

Our new catalogue will be available in January 96. Ask for a FREE copy to be included with your next order.

## THREE CHANNEL UHF TRANSMITTER

The same basic circuit as the 1ch transmitter. Two buttons, allows up to 3 channel operation. Easier to assemble than the 1ch transmitter and has slightly greater range. Size of transmitter case: 54 x 36 x 15mm: **\$18.**

## MAGNETIC CARD READER

Commercial class unit that will read some information from most plastic cards, needs 8 to 12V DC supply such as a plugpack. Draws about 400mA. Power input socket is 2.5mm DC power type. Weight: 850g. 220 x 160 x 45mm: **\$70 (Cat G05).**

## VISIBLE LASER DIODE MODULES

Industrial quality 5mW/670nm laser diode modules. Consists of a visible laser diode, diode housing, driver circuit, and collimation lens all factory assembled in one small module. Features an automatic power control circuit (APC) driver, so brightness varies little with changes in supply voltage or temperature. Requires 3 to 5V to operate and consumes approx 50mA. Note: 5V must not be exceeded and there must be no ripple on the power supply, or the module may be instantly destroyed. These items may require licensing. Overall dimensions: 12mm diameter by 43mm long. Assembled into an anodised aluminium casing. This module has a superior collimating optic. Divergence angle is less than 1milliradian. Spot size is typically 20mm in diameter at 30 metres: **\$65.** This unit may also be available with a 635nm Laser Diode fitted.

## CYCLE/VEHICLE COMPUTERS

BRAND NEW SOLAR POWERED MODEL! Intended for bicycles, but with some ingenuity could be adapted to any moving vehicle with a rotating wheel. Could also be used with an old bicycle wheel to make a distance measuring wheel. Top of the range model. Weather and shock resistant. Functions: speedometer, average speed, maximum speed, tripmeter, odometer, auto trip timer, scan, freeze frame memory, clock. Programmable to allow operation with almost any wheel diameter. Uses a small spoke-mounted magnet, with a Hall effect switch fixed to the forks which detects each time the magnet passes. Hall effect switch is linked to the small main unit mounted on the handlebars via a cable. Readout at main unit is via an LCD display. Main unit can be unclipped from the handlebar mounting to prevent it being stolen, & weighs only 30g. Max speed reading: 160km/h. Max odometer reading: 9999km. Maximum tripmeter reading: 999.9km. Dimensions of main unit: 64 x 50 x 19mm: **\$32 (Cat G16).**


## EMAIL WEBSITE

EMAIL address: oatley@world.net until Mar.96, oatley@ozemail.com.au from Feb.96.

WEB SITE address: over 300 kits plus our catalogue: <http://www.hk.super.net/~diykit>



New from Smart Fastchargers, this nicad and NiMH charger caters for a wide range of battery voltages and capacities and uses the patented Reflex charging method. It has eight buttons to set the rate of charge, a rotary switch to select the battery voltage and a LED bargraph to indicate the cell voltage. An audible beep, at one second intervals, gives an indication that the main charge is still in progress.

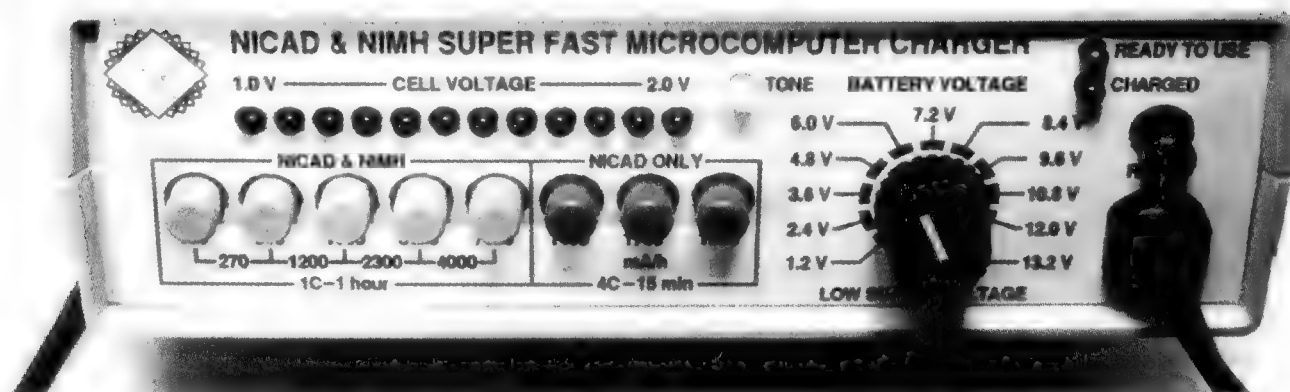

# Recharging nicad batteries for long life

Nickel cadmium and nickel metal hydride batteries are widely used in all sorts of portable equipment but they often don't last long before they must be replaced. One solution is to use "burp charging" which is claimed to provide many thousands of charge/discharge cycles.

By HORST REUTER\*

Battery powered equipment is undeniably practical – lightweight, portable and small, with no cables to drag around. But there is a price to pay for that convenience. Rechargeable batteries are costly to buy and often don't last long. The problem can usually be traced back to the type of charger used.

Unfortunately, most of the nicad chargers supplied with appliances at

present require manual termination; ie, the user has to switch off the charger and disconnect the battery. This makes it practically impossible to avoid overcharging the batteries, thereby reducing their life expectancy. The key to long life lies in the charging method.

In this article, a battery is defined as consisting of one cell or several cells connected in series. Internal cell im-

pedance is defined as the sum of the resistance of the internal connections and plates (both constant) and the degree of difficulty the ions encounter passing through the separators and electrolyte (variable).

## Nicad or NiMH?

From an environmental point of view it would be an advantage to change to NiMH batteries. Nickel Metal Hydride (NiMH) batteries are made without cadmium and are therefore less damaging to biological systems. At present, they have about 20% higher energy density than nicad cells (AA) and produce no memory effect (more about memory effect later).

However, typical NiMH cells have a higher internal impedance than nicad cells; 50mΩ instead of 10mΩ for 1200mAh cells. As a consequence,



NiMH batteries have lower maximum discharge currents. This means they are only suitable for low current appliances like handheld radios. The maximum discharge current is 3C for NiMH AA cells and 2C for NiMH button cells, whereupon the cell voltage drops to approximately 1.1V. "C" is defined as the current that equals the rated battery capacity. For example, charging a 1.2Ah battery with a 4.8A current is a 4C charge. The same 4.8A current applied to a 4.8Ah battery is a 1C charge.


In practice, the useful discharge currents for NiMH batteries are limited to less than 1C (the cell voltage remains above 1.2V). For currents above 1C, nicad batteries are superior. Fig.1 is a comparison of the load characteristics of one 1200mAh AA size NiMH cell, one 600mAh AA size nicad and one 1200mAh sub-C size nicad cell. The load was only applied for 5 milliseconds.

The tests showed that a fully charged 12V 1200mAh nicad battery as used in power drills delivers a maximum of 11.9V with a 10A load. Even a 12V 600mAh nicad battery delivers a maximum of 10.9V with a 10A load. However, a 1200mAh NiMH battery with the same load delivers only 7.65V.

NiMH batteries also differ from nicad cells in that the chemical reaction during charge is exothermic; ie, the charging process produces heat. The chemical reaction in nicad cells is endothermic; the reaction absorbs heat. However both battery types produce some heat during the main charge cycle because of internal impedance and both produce heat when overcharged. Overcharging creates heat and gas but does not produce any further energy storage in the cells.

The heat produced during the main charge in nicad cells due to cell impedance is absorbed in the endothermic reaction. In NiMH cells, the cell heating due to internal impedance is added to the heat of the exothermic reaction. When NiMH batteries reach the overcharge region, they are therefore hotter than nicads.

All available NiMH cells I have tested vented at around 43-45°C case temperature – much lower than for nicads. This means that charge termination at high charge rates is critical and cannot safely be achieved with delta V termination chargers. The case temperature should not exceed 40°C

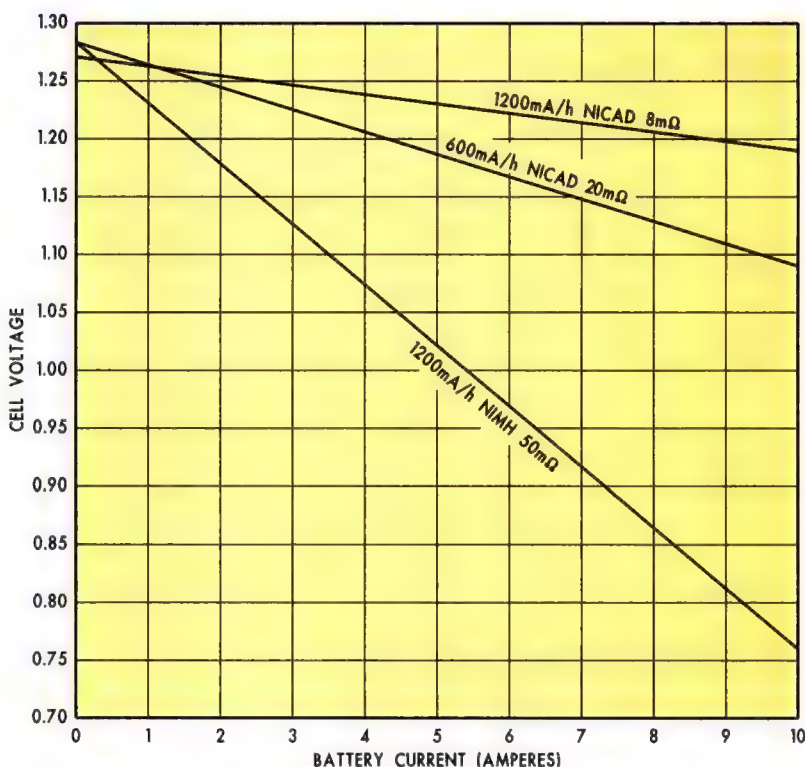


**Fig.1: a comparison of the load characteristics of a 1200mAh AA size NiMH cell, a 600mAh AA size nicad and a 1200mAh sub-C size nicad cell. The load was only applied for 5 milliseconds. This clearly demonstrates that the higher internal impedance of NiMH batteries limits their usefulness in delivering high currents.**

for NiMH cells and 45°C for nicads.

Delta V termination utilises the voltage drop at the beginning of the overcharge region of the cell voltage curve (see Fig.2). The magnitude of this voltage drop is generally not as well defined in NiMH cells as it is in nicad cells. It depends on factors like charge


current, ambient temperature, cell impedance, cell capacity, etc.

The situation can be worse in battery packs. Several unmatched cells may cause the battery voltage to reach only a very shallow peak if some cells reach their individual peaks while others are still charging. Even if the

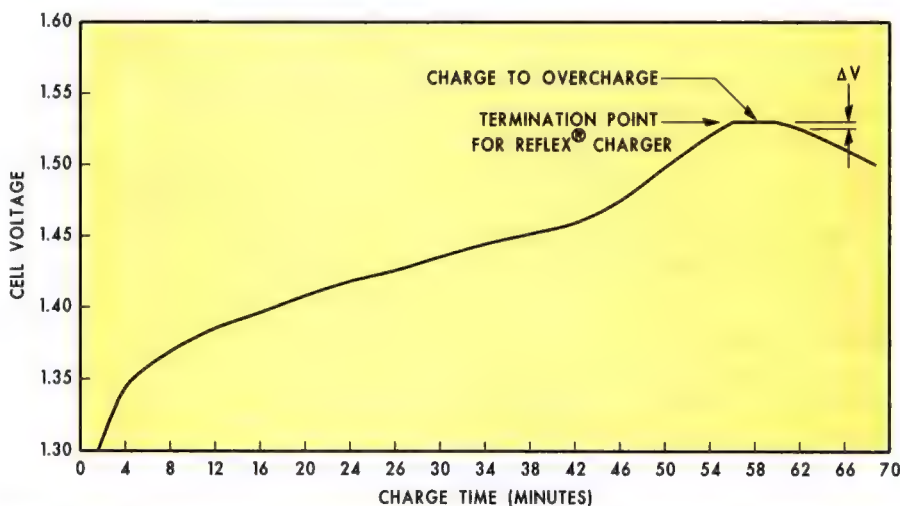

**Fig.2: delta V termination utilises the voltage drop at the beginning of the overcharge region of the cell voltage curve. The magnitude of this voltage drop is generally not as well defined in NiMH cells as it is in nicad cells. It depends on factors like charge current, ambient temperature, cell impedance, cell capacity, and so on.**



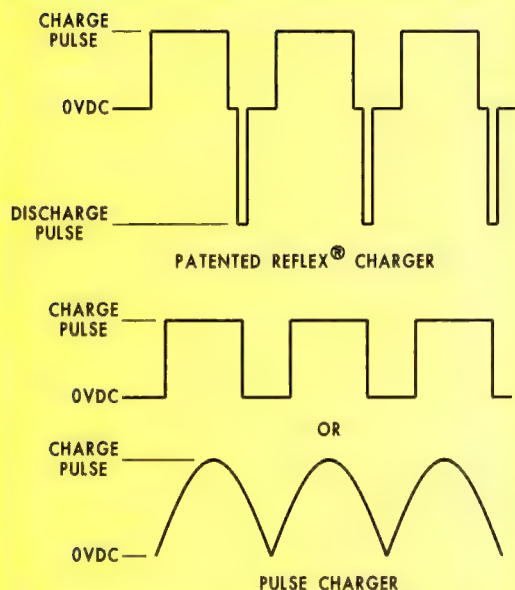

**Fig.3: the patented Reflex or “burp” charge method consists of a positive charge pulse followed by a high current, short duration discharge pulse. This is quite different from other chargers which have an essentially pulsed output but no discharge pulses.**

charger circuit is able to detect a very small voltage drop ( $<10\text{mV}$ ) at the very start of the overcharge region, the fact remains that we are already operating in the overcharge region.

Overcharging is not acceptable if we want to achieve maximum battery life for nicad cells. For NiMH cells it can be dangerous if used in combination with high charge currents. It can lead to venting and consequent loss of capacity and in extreme cases to cell explosion, due to a build up of gas pressure.

If NiMH cells are charged with delta V termination chargers, then this has to be done at the rate the manufacturer recommends, typically  $C/10$  ( $120\text{mA}$ ) for  $1200\text{mAh}$  cells. At this rate, any heat produced during charging and overcharging will be safely dissipated.

## Memory effect

Let's look at the major problem of nicad cells: memory effect. This is caused by charging a partially discharged battery and enhanced by slow charging and high operating temperatures. During charging, the negative plate loses oxygen and converts cadmium hydroxide to metallic cadmium, while the positive plate goes to a higher state of oxidation, changing the nickel

hydroxide to nickel oxyhydroxide. This process is reversed during discharge.

If each cell in the battery pack is discharged completely and then charged, the individual crystal sizes on the cell plates remain unaltered. However, if the cadmium is not completely converted back into cadmium hydroxide during partial discharge, on the following charge the cadmium hydroxide crystals will clump together, forming larger crystal structures.

Although it is not yet fully understood how this happens, scanning electron micrographs of batteries with and without memory effect clearly show the difference in crystal sizes.

The net result is that we are left with a smaller, less reactive surface area and therefore reduced capacity.

The clumping of crystals is mostly a slow process but is cumulative. However, as we will see later, it is reversible.

## End point voltage

The usual strategy to prevent memory effect is to discharge each cell to  $1.1\text{V}$  or  $1.0\text{V}$ , a level where very little useful energy is left. This is only partly effective with single cells and with new and well matched cells in

battery packs. Not all cells in a battery pack will age equally or charge and discharge equally at different operating temperatures. In the end, some cells will only be partly discharged when others are deep discharged.

At the final stage of the battery discharge, a sudden substantial voltage drop occurs. This can lead to reverse charging of the weakest cell in a battery pack of more than 12 cells and will still cause a clumping of crystals in all cells (except the weakest cell) during the next charge. The magnitude of memory effect in each cell depends on the depth of discharge.


Unlike some other types of cells, nicads can be totally discharged and then even shorted to avoid the memory effect but not without reducing life expectancy. The life expectancy of all types of batteries, including nicads, is partly dependent on the depth of discharge.

Hence, a total discharge will reduce life expectancy (up to a factor of 10 in cases of frequent total discharge). Totally discharging a battery to  $0\text{V}$  – unlike discharging a single cell – is a sure recipe for extremely short battery life due to cell voltage reversal.

Shallow discharge, less than 25% of total capacity, makes for long battery life but creates the conditions for memory effect. A  $1.1\text{V}$  or  $1.0\text{V}$  discharge voltage is only a compromise, not a magic value.


## Freezing cells

Another strategy to combat memory effect, the practice of freezing batteries to break up the clumping of the crystals, creates mechanical stresses in the cells. This can also lead to re-

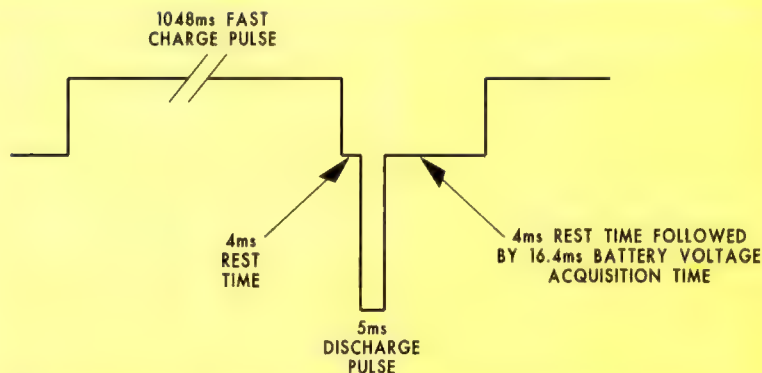

**Fig.4: the essential characteristic of the Reflex charging method is a high current charge pulse, followed by a short rest period and then an even higher discharge pulse for 5ms. The battery voltage is then measured before the next charge pulse.**



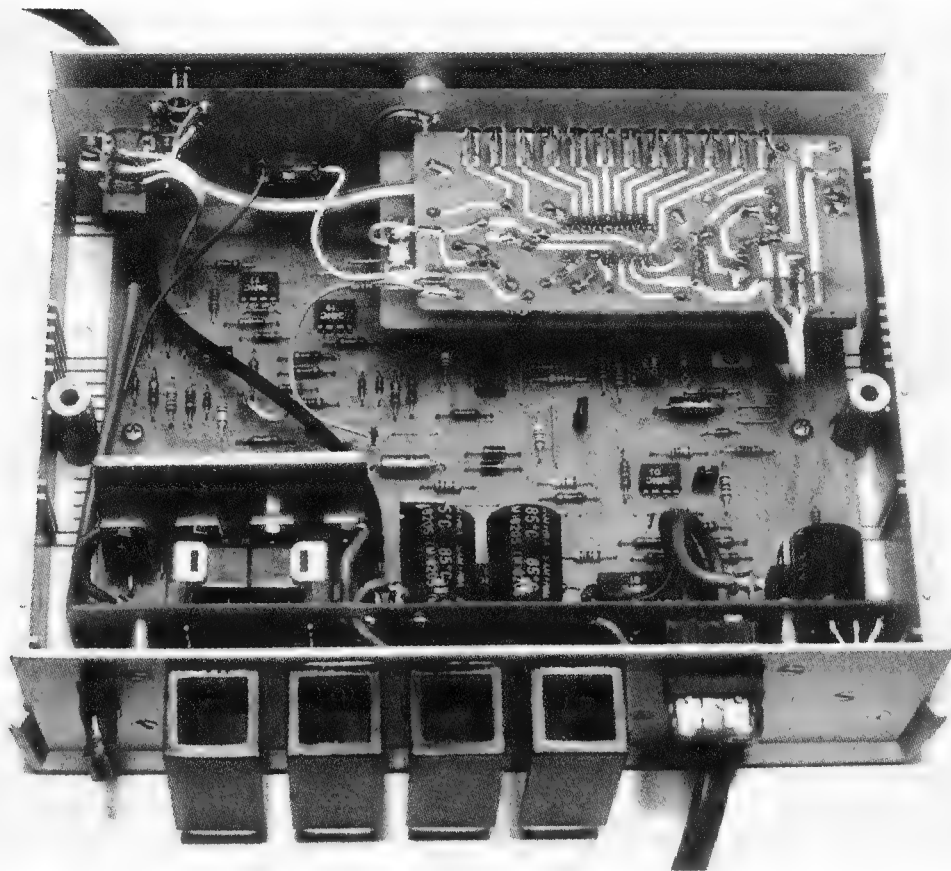

This is the view inside the prototype from Smart Fastchargers. It uses a total of three PC boards and can charge batteries at a rate of up to 9A.

duced life expectancy since a high degree of mechanical precision goes into the production of today's high capacity cells. It is also a time consuming method, since all cells in the battery have to be slowly warmed to above 10°C after freezing for efficient fast charging.

All these are makeshift solutions. The problem should be tackled at the roots, by using a charge method that will reduce crystal size in batteries where crystal clumping has occurred and avoids crystal clumping during the charging of partially discharged batteries.

Another area that needs improvement is the small number of recharge cycles suggested for most nicad batteries. In the case of some hand-held radios, the batteries are supposed to have only 300 recharge cycles. Batteries for other appliances are rated for 500 and 1000 cycles.

Theoretically, 5000 charge/discharge cycles are possible over a minimum life span of 10 years. One power hand tool manufacturer advertises 3000 cycles and 10 minutes charging time. This is achieved by using advanced charger technology and fast charge batteries. 3000 cycles repre-

sent approximately 6.5 cents per cycle as compared to 55 cents per cycle for the hand-held radio batteries (at presently quoted prices).

Another problem is the excessive time required to charge nicad and NiMH batteries with delta V termination chargers: generally between one hour for fast charge nicad batteries and 15 hours for standard nicad batteries and NiMH batteries. Only in exceptional cases, as with some chargers for battery powered tools, is it possible to achieve charge rates of less than one hour for nicad batteries.

### Burp charging

One overseas company has designed a fast charger that achieves an amount of recharge cycles close to the theoretical limit. This patented charger, well proven in industrial and military applications, is used to charge aircraft batteries, emergency standby batteries for hospitals, etc and operates fully automatically. It automatically detects the type of battery (nicad, NiMH, lead-acid, etc), battery capacity and voltage and adjusts itself accordingly.

These complex chargers use the patented Reflex or BURP charge method. This consists of a positive


charge pulse followed by a high current, short duration discharge pulse. This should not be confused with pulse or switchmode chargers which switch the charge current on and off but do not apply a discharge current – see Fig.3.

By using a charger circuit with the patented Reflex method incorporated in a licensed integrated circuit, it is possible to obtain a dramatic increase in the charge/discharge cycles of nicad batteries, to at least 3000 cycles if reasonable care is exercised. There is no need to run appliances until the batteries are flat to avoid the memory effect. It is now possible to recharge the batteries after each use. Partial discharge, as opposed to full discharge, will significantly increase the life of the batteries.

A microprocessor calculates and accurately terminates the applied charge by evaluating the inflection points on the charge voltage curve. The termination point varies according to the charging characteristic of the battery; it occurs just prior to the transition into overcharge (see Fig.2).

The circuit provides a fast charge, preceded by a series of soft start charge pulses. Then, if the battery is left in



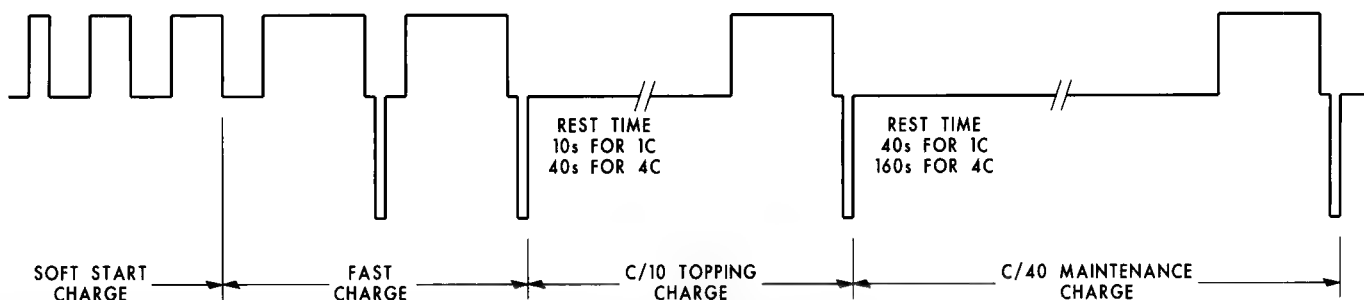

**Fig.5: the timing for soft start, fast, topping and maintenance charges. The charge/discharge pulse combination for the topping and maintenance modes remain the same as for the fast charge cycle; only the rest time is changed.**

the charger, the fast charge will be followed by a topping charge and a non-destructive indefinite maintenance charge.

All of the above can be done by one charger with an adjustable output current sufficient for batteries of 7000mAh capacity at the 1C (1 hour) charge rate or for 1900mAh capacity batteries at the 4C (15 minute) charge rate, taking the charge efficiency into account. To fully charge a battery, approximately 20% more charge than has been withdrawn has to be put back into the battery if charged at or above C/10 at 20°C.

The charge efficiency of batteries depends on charge current and ambient temperature. High or very low ambient temperatures and/or low charge currents decrease the charge efficiency; in extreme cases to a point where the battery cannot be fully charged.

### Soft start

Batteries can exhibit a high impedance during the initial stages of charging. The resulting voltage peak can be interpreted by the processor as a fully charged battery. However, with the soft start cycle, at first only short duration current pulses are applied to the battery. Starting at 200ms, the pulse width is gradually increased to approximately one second in duration. This gradual increase in pulse width takes place over a period of two minutes to avoid voltage peaks.

### Fast charge

During the main charge cycle, each positive current pulse is followed by a discharge pulse, as shown in Fig.4. The discharge pulse is 2.5 times the amplitude of the charge pulse. After the main charge, if the battery is left on the charger, it will be fed a topping

charge. This charge is at a current low enough to prevent cell heating but high enough to convert all active material in the cells to the charged state.

Due to higher temperatures and gas bubbles (see explanation further on), 100% charge cannot be achieved with fast chargers. Standard constant current chargers create heat and gas bubbles on the cell plates during charging. This results in less than 90% efficiency.

This version of the Reflex charger is approximately 95% efficient, since the termination method largely avoids cell heating and the charge/discharge pulse sequence removes most of the gas bubbles from the cell plates. The 2-hour C/10 charge tops up the battery if the time is available or 100% capacity is required.

### Maintenance charge

After the full charge and topping charge, the C/40 charge compensates for the internal self-discharge of the battery, at the same time preventing dendrite formation and maintaining the crystal structure. The battery can remain on the charger until used – there is no time limit. This charge cycle can be useful in standby applications, as in security installations.

Fig.5 shows the timing for soft start, fast, topping and maintenance charges. The charge/discharge pulse combination for the topping and maintenance modes remain the same as for the fast charge cycle; only the rest time is changed.

The removal of gas bubbles from the cell plates during charge keeps the cell impedance low, reduces operating temperature and allows higher charge currents for nicad and NiMH batteries. The following charge times can be achieved: fast-charge nicad batteries in less than 15 minutes at the 4C

rate, standard nicad and NiMH batteries in less than one hour.

As well, memory effect in batteries can be eliminated. This works even when the battery no longer holds any charge. It requires a minimum of three complete charge/discharge cycles. A typical case in practice involved a 4.8V 600mAh cellular phone battery pack. This had only 20% of its stated capacity, after it had been used over a period of six months with the supplied charger. After five charge/discharge cycles, it had recovered to approximately 95% of capacity.

The possibility to rejuvenate shorted nicad batteries is also a feature. Whenever a nicad battery has been stored charged and has then slowly self-discharged over a very long period of time at an elevated temperature, or has been charged at a low current over a long period, as in constant current trickle charging in standby applications, crystals on the cell plates can form crystalline fingers, or dendrites, which can propagate through the plate separators and across the cell plates.


In extreme cases, these crystalline dendrites can partially or completely short-circuit a cell. Such cells can be rejuvenated by this charger.

### Charger circuit

Fig.6 shows the block diagram of a charger using the patented Reflex charging method. The charger covers a battery voltage range from 1.2V to 13.2V at charge currents from 0.1A to 9.0A. The central part of the battery charger is basically a reduced instruction set microprocessor (RISC) to handle the complex calculations for the charge termination point.

The microprocessor uses an analog-to-digital converter (ADC) with 300μV resolution to convert the battery voltage, normalised to one cell by the input attenuator VR1. The ADC is followed by a filter to limit the effects caused by battery voltage jumps and ADC noise and to eliminate any large



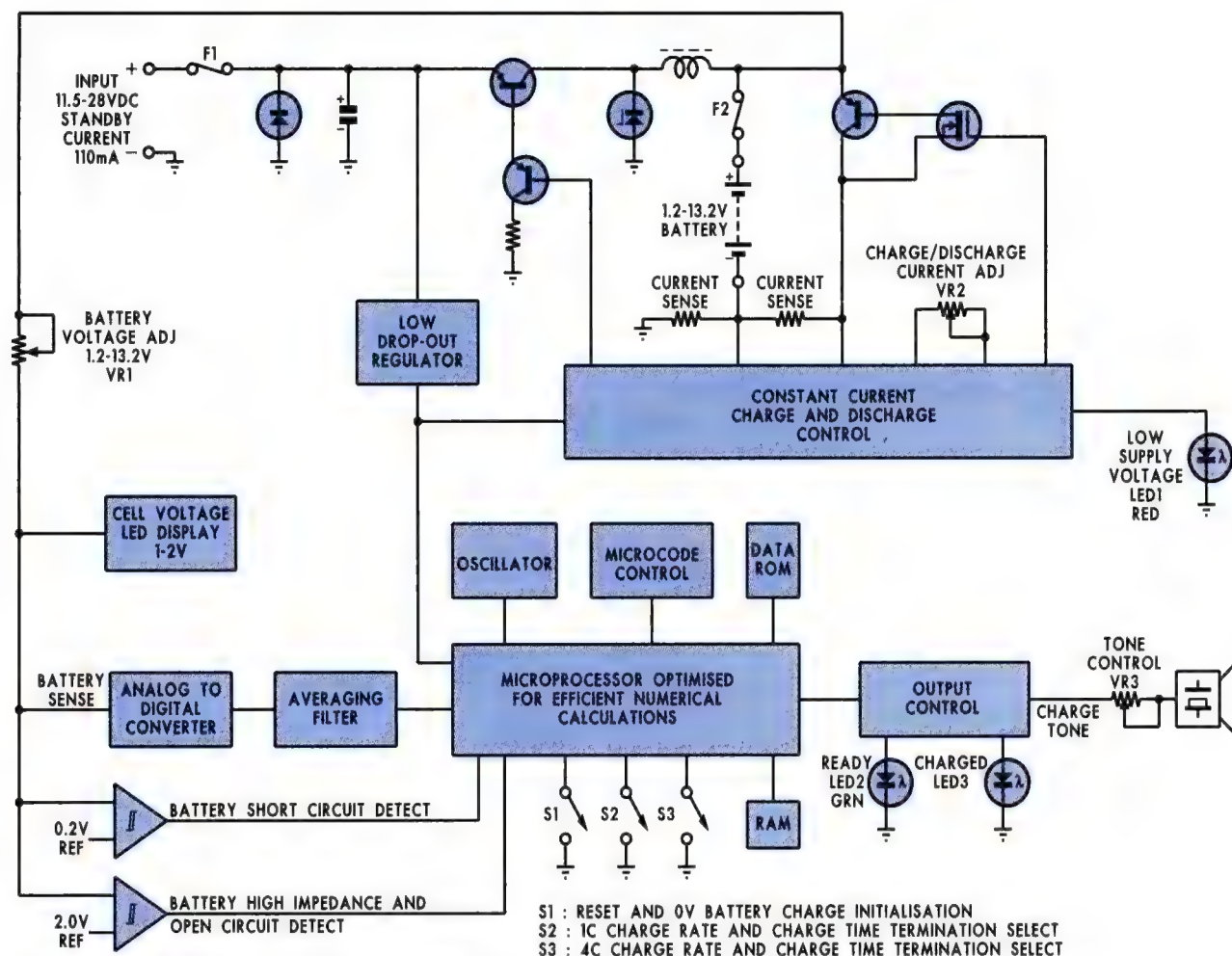

**Fig.6: the block diagram of a charger using a RISC microprocessor programmed with the patented Reflex charging method. The charger covers a battery voltage range from 1.2V to 13.2V at charge currents from 0.1A to 9.0A.**

aberrations in the battery voltage curve.

The microprocessor controls the charge, topping and maintenance modes. One input of the microprocessor controls the charge rates (1C or 4C) and is linked to the bank of push-buttons for selection of charge current.

One input resets the microprocessor to repeat a charge cycle or to charge shorted cells. In this case, the reset button has to be activated until the LED "cell voltage" display indicates acceptance of the charge current.

A battery voltage guard circuit avoids automatic charging of shorted batteries. This is necessary since the current required to kick start a shorted battery varies from case to case and should be controlled manually.

Another detect circuit avoids the automatic charging of batteries with a voltage or more than 2V per cell. This condition is due to high internal im-

pedance, as found in new batteries that have not been cycled and in some batteries which have been stored for several months. Charging these batteries would cause excessive heating.

The DC input to the charger can range from 11.5V to 28V, depending on the number of cells in the battery to be charged. Essentially, this is a minimum of 2V per cell plus an additional 2V. Hence a 6V battery (5 cells) requires a minimum of 12VDC to the charger while a 12V battery (10 cells) requires a minimum of 22VDC.

### Safety cut-off

In case the voltage sensing for end of charge does not work there is a time-out circuit which is set for 72 minutes at the 1C rate and 18 minutes for the 4C rate. In addition, there is a heatsink temperature sensor to interrupt the charge as a safety measure in extreme hot weather conditions.

The microprocessor controls three

output circuits and two LED indicators. The charge circuit is a switch-mode current source, adjustable from 0.1A to 9A with VR2 (a bank of push-button switches). The discharge circuit is a pulsed constant current sink adjusted to between 0.25A and 22.5A (2.5 times the charge current).

During the main charge cycle, a small piezo speaker emits a brief tone once a second, synchronised to the discharge pulses. This is a convenient audio cue to tell the user the battery is still in the main charge sequence. The tone control on the front panel actually adjusts the volume, so that the tone is not obtrusive.

Other details of the operation can be gleaned from the block diagram.


By this time this issue goes on sale, the charger will have been released for sale. For information concerning availability and price, contact Smart Fastchargers, R.S.D. 540, Devonport, Tas 7310. Phone/fax (004) 921 368.

**\*Horst Reuter is Technical Manager of Smart Fastchargers.**



# CIRCUIT NOTEBOOK

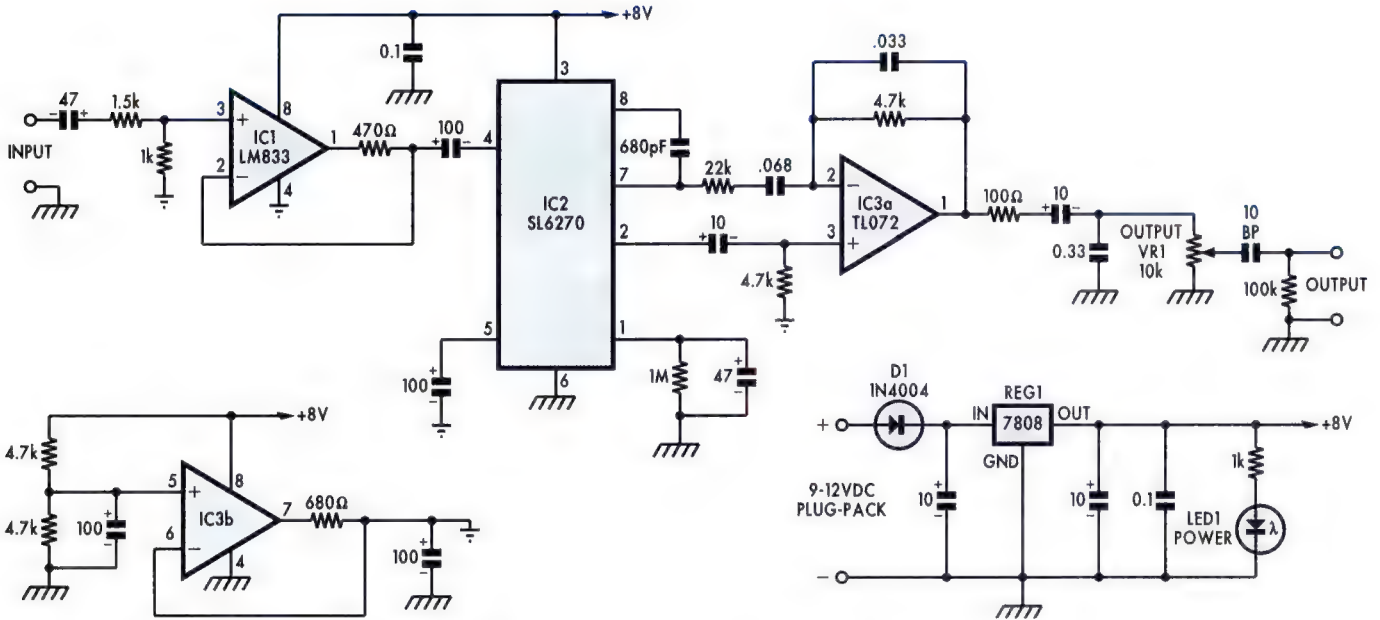**Interesting circuit ideas which we have checked but not built and tested. Contributions from readers are welcome and will be paid for at standard rates.**



## Automatic level control for line signals

This circuit adapts the Plessey SL6270 gain control chip to line levels. Intended for automatic level control of balanced microphones, the SL6270 was featured in the August 1995 issue. In this circuit, it will accept up to 1V RMS of signal before

clipping and will provide a constant output level for input signals between 14mV and 1V.

The 1.5k $\Omega$  and 1k $\Omega$  resistors at the input provide the necessary attenuation of the signal to prevent clipping within IC2. IC1 is simply used to buffer the signal and drive the 150 $\Omega$  input impedance at pin 4. The 470 $\Omega$  resistor in IC1's feedback path increases the

impedance seen by the op amp to  $600\Omega$  to prevent distortion.


The signal output at pin 2 of IC2 is AC-coupled to buffer amplifier IC3a. By virtue of feedback action, pin 2 of IC3a applies signal to the pin 7 input of IC2 where it is rectified and filtered to determine the gain. VR1 sets the output level.

## SILICON CHIP.
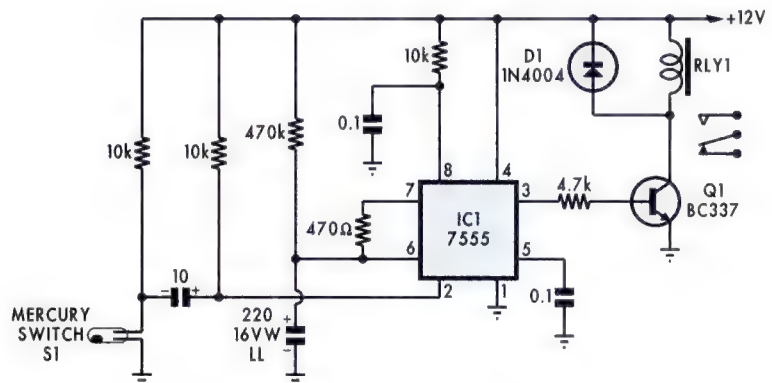
## Bilge pump timer uses a mercury switch

This circuit was designed to enable a mercury switch to replace the contacts in a float switch for a bilge pump. The mercury switch can be expected to last indefinitely compared with the limited life of mechanical contacts in a float switch. However, the mercury switch cannot be used to control the pump directly. Therefore it is used to initiate a 2-minute timer based on a 7555.

The mercury switch is mounted on the float switch lever in such a way that it closes when the water reaches a preset level. This momentarily pulls the trigger input (pin 2) low to start the timer. This takes pin 3 high to turn



on transistor Q1 which drives the relay. After two minutes or so, as determined by the 470k $\Omega$  resistor and 220 $\mu$ F capacitor at pin 6, the output at pin 3 will go low and Q1 will turn off. The relay must have adequate ratings

to handle the current drawn by the pump.

If you need a longer pumping time, increase the value of the 470k $\Omega$  resistor and vice versa.

## SILICON CHIP.




## PWM speed controller

This circuit can be used to provide a wide range of speed control for a 6V DC motor, with very little power dissipation in the controlling transistor.

Op amp IC1a forms a Schmitt trigger oscillator with a 45% duty cycle, as set by the voltage divider resistors at pin 3. The frequency is varied between 47Hz and 500Hz by VR1. The waveform at pin 6 of IC1b is a sawtooth and this is compared with the DC threshold voltage set by VR2 at pin 5.


With VR2 set for a low voltage, IC1b delivers short pulses; for a high setting, long pulses are delivered.

IC1b drives a Darlington transistor

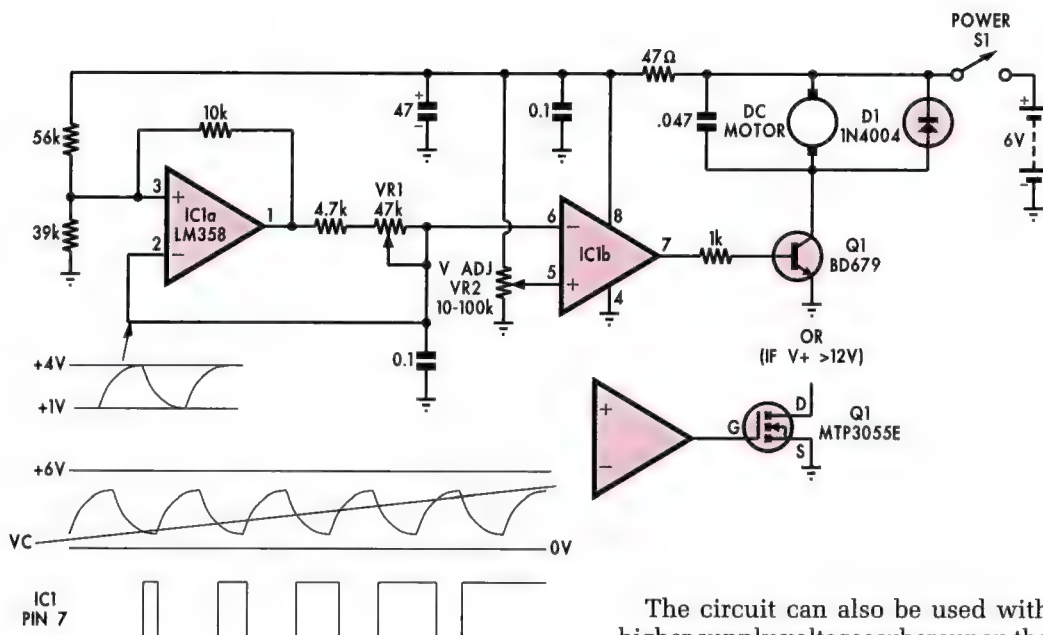

The circuit can also be used with higher supply voltages whereupon the bipolar transistor can be substituted with a Mosfet such as an MTP-3055E or BUZ71.

**M. Schmidt,  
Edgewater, WA. (\$30)**

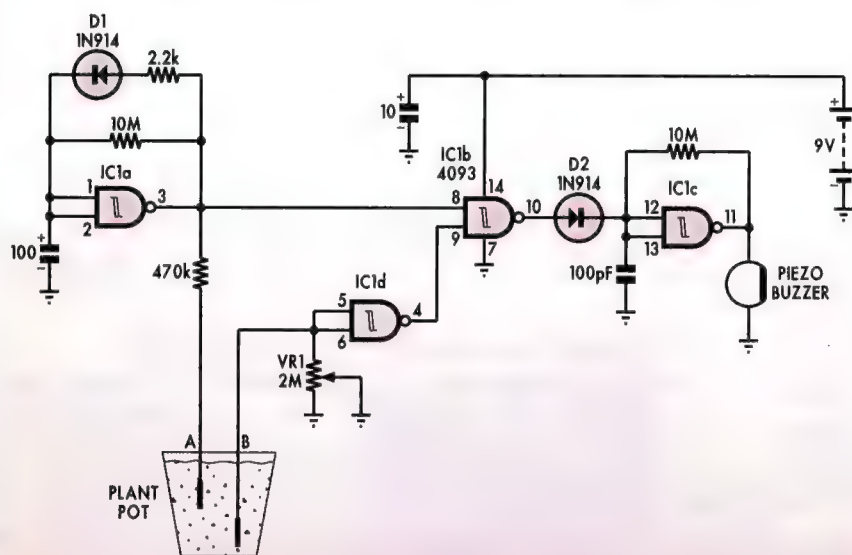

## Moisture monitor for pot plants

This circuit will sound a piezo beeper when your plants need a drink.


IC1a is a free-running Schmitt trigger oscillator which produces a brief positive pulse once every three minutes. This is fed to pin 8 of IC1b and to pins 5 & 6 of IC1d via a 470kΩ resistor and the pot-

plant pot. IC1d is connected to invert the pulses fed to pin 9 of IC1b. This gate's output remains high and inhibits an oscillator comprising IC1c, as long as the soil is moist and conducts.

When the soil is dry, IC1d's output goes high so that IC1b enables IC1c and the beeper sounds. VR1 acts as a sensitivity control.

**B. Avi,**  
**Rose Bay, NSW. (\$30)**

## DC amplifier for a centre-zero meter

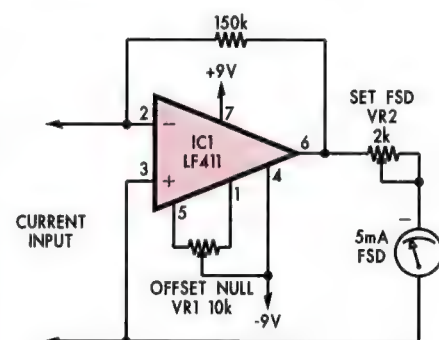

This circuit will allow a 5mA FSD centre-zero meter to be used where a 50 $\mu$ A meter movement would otherwise be required.

The circuit is based on an LF411 op amp which has been specified for its low drift. It operates as a current amplifier. VR1 is used to zero the meter when the input signal is zero, while VR2 adjusts the full scale deflection.

**SILICON CHIP.**

## Circuit Ideas Wanted

Do you have a good circuit idea? If so, sketch it out, write a brief description & send it to us. Provided your idea is original, we'll publish it & you'll make some money. Send your idea to: Silicon Chip Publications, PO Box 139, Collaroy, 2097.



# DICK SMITH ELECTRONICS

## All You Need Is Right Here!

**NEW**

### Range Of Knobs in a variety of colours



- Cat P-7126 15mm Push Fit Miniature Knob, Black \$0.85  
Cat P-7130 16mm Push Fit Miniature Knob, Red \$1.00  
Cat P-7132 16mm Push Fit Miniature Knob, Green \$1.00  
Cat P-7134 16mm Push Fit Miniature Knob, Yellow \$1.00  
Cat P-7136 16mm Push Fit Miniature Knob, White \$1.00

### Lighter Socket Plug

With in-built fuseholder,  
5A fuse and "Power On"  
LED indicator.

Cat P-1684

**\$3.95**



### Universal Camcorder Charger

Power supply and  
battery refresher suits  
most 8mm and VHS-C  
video cameras.  
Specially designed to  
safely recharge your  
camcorder batteries.  
Operates from car  
cigarette lighter  
socket or optional AC/DC  
adaptor. Refresh function  
provides 100% full  
charge. Normal and  
quick charge facilities.  
Cat M-9499

**\$39.95**

**SCOOP  
PURCHASE!**



**HURRY LIMITED STOCKS!**



### Audio Drive Belts Comes in packs of 10 Assorted sizes

Sizes include:  
25mm x 1.2mm x 1.2mm  
40mm x 1.2mm x 1.2mm  
44mm x 1.2mm x 1.2mm  
46mm x 1.2mm x 1.2mm  
49.5mm x 1.2mm x 1.2mm  
57mm x 1.2mm x 1.2mm  
82.5mm x 1.4mm x 1.4mm  
100mm x 1.6mm x 1.6mm  
105mm x 1.2mm x 1.2mm  
125mm x 1.2mm x 1.2mm

Cat H-6015

**\$4.95**

### Motorised Potentiometer


50k ohms log.  
Dual ganged.

Note: Pot is supplied with spline  
shaft and not straight solid shaft  
as illustrated.

Cat R-7830

**\$18.95**

**NEW**

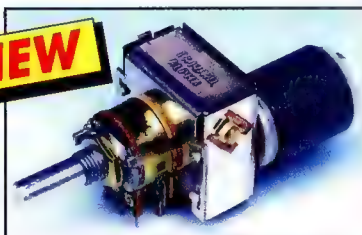

### Pressure Mat

Great as a customer warning in shops, or general home security,  
this pressure mat is almost impossible to detect under carpets or  
rugs. When an intruder steps on it, it triggers the alarm. With N.O.  
(Normally Open) contacts, it suits most systems.

Cat L-5270

**\$26.95**

**NOW AVAILABLE**



**NOW AVAILABLE**

### Fluke 76 True RMS DMM

This true-RMS Digital Multimeter  
is ideal for detecting peaking,  
nulling or trending with its fast,  
63-segment analog bar graph,  
4000-count digital display and  
40 times per second update rate  
- as fast as the eye can see.  
Also, the frequency counter  
shows frequency while  
simultaneously showing AC  
voltage levels on the analog bar  
graph! Other great features  
include 10A, 40mA, TouchHold,  
Audible Continuity/Diode Test  
and Auto Range Hold.

Cat Q-1608

**\$479**

**FLUKE**

On display at the following stores:

• York Street • Cannington • Brisbane City • Adelaide  
City • Bourke Street • Darwin • North Ryde • Hobart


May also be ordered from your nearest Dick Smith Electronics Store

**Don't forget your  
copy of BENCHMARK!  
Now available FREE  
in your nearest store.**



# Try Your Hand At These!

## DISCOVERY SERIES

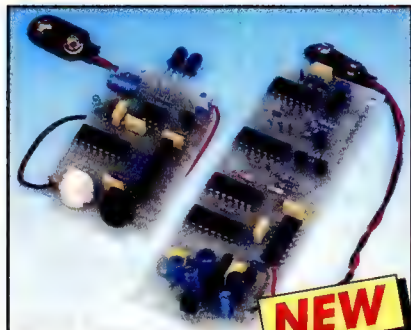


**NEW**

### Four Channel Infrared Remote Control

Build your own handy infrared remote control! It includes a small transmitter that can be constructed to fit in your hand, and a receiver with five outputs, all of which can directly drive relays. Both the transmitter and receiver have a selectable security code to prevent false triggering and operation by other transmitters. Kit comes complete with all components and PCBs which are solder masked and silk screened.

Cat K-2810

**\$39<sup>95</sup>**

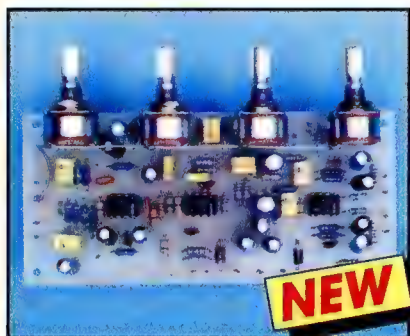

**NEW**

### Stereo Pre-Amp

This compact high quality module makes it possible to upgrade your bare power amplifiers into a complete audio system by adding volume, bass, treble and balance controls. The circuit is stereo with an extra input to both channels that can be used for either multi-channel mixing or gain control applications. Supplied with components, hardware and silk-screened, solder masked PCB.

Cat K-2811

**\$34<sup>50</sup>**

### With Bonus! DSE Soldering Station

Make a permanent and reliable connection! Features a fully variable temperature control from around 200 degrees to 500 degrees Celsius. With temperature meter and is approved by the Energy Authority. Comes complete with a lightweight iron fitted with a silicon non-burning cable, iron holder and cleaning sponge.

Cat T-2000

**\$159**



**BONUS**

### Helping Hands With Magnifier

Makes working on PCBs much easier!

Cat T-5715

### Hobby Tool Kit 28 Pcs With Case

A convenient collection of tools complete with a foam-lined plastic storage case. Includes 9-piece Hex Nut drivers and quality reversible ratchet handle, 6-piece Jewellers screwdrivers, sidecutters, pliers, plus 10-piece assorted screwdriver bits.

Cat T-4610

**\$29<sup>95</sup>**

**SAVE \$10**



**NEW**

### PC Driven EGO Analyser

This low-cost analyser is designed to monitor your car's engine performance by examining the Exhaust Gas Oxygen sensor (EGO sensor) directly. Supplied with software, the results will be displayed on your PC. Project is complete with all components, hardware, PCB, pre-punched silk-screened front panel, case and software.

Cat K-4214

**\$49<sup>95</sup>**

**EA Jan '96**

### ESR & Low OHM Meter

Measures the equivalent series resistance (ESR) which is often difficult to check with capacitance meters, so if you need to measure very low values of resistance, this project can save you lots of time and aggravation. Kit is supplied with all components, hardware, PCB, case and pre-punched silk-screened front panel.

Cat K-7204

**\$59<sup>95</sup>**

**NEW**

**EA Jan '96**



Availability: Our kits consist of many different parts from numerous suppliers. Whilst we have consulted closely with them and are satisfied with their ability to supply, sometimes problems can arise in obtaining all of the parts. This means there is a slight chance that availability may be delayed. Rainchecks are available, however, if you'd like to check beforehand, don't hesitate to contact your local store.



# Put These To Use!



**SCOOP PURCHASE!**

## Opto-Coupler H11A1Z

These industry-standard optoisolators consist of a GaAs Infrared LED and a silicon phototransistor. The devices are constructed with a high voltage insulation, double-moulded packaging process which offers 7.5kV withstand test capability. Available in standard 6-pin DIL plastic package format, it is a low-cost alternative to the popular 4N28 and 4N25 devices in a wide variety of circuits.

Cat Z-4810

**\$125**

## 12VDC Lighter Socket Extension Lead

This will be handy! With in-built fuseholder, 5A fuse, safety "Power On" LED indicator, dust & moisture-proof socket cap. Also includes 1-metre coiled cable that extends to approximately 2.8 metres.

Cat P-1681



**NEW**

**\$12<sup>95</sup>**

## 1.25 GHz Hand-Held Digital Frequency Counter

Ideal for measuring radio frequency transmissions and servicing stereos, videos, computers and cordless phones. This incredibly easy-to-use 10Hz to 1.25 GHz frequency counter has an 8-digit LCD display, data hold, relative management and data record (min, max & average). There's also selectable resolution, period measurement and more. Comes complete with telescopic antenna and BNC to alligator-clip test leads.

Cat Q-1322

**\$199**



**SAVE \$50**

**70% Less Than Regular 1/4 Watt Carbon Film Resistor Prices**

**NEW**

## 1/4 WATT CARBON FILM RESISTORS

Comes in a pack of 300+. Mixed values. With preformed and precut leads - the extra work's been done for you!

Cat R-7022

**\$445**

**THAT'S LESS THAN 1.5 CENTS EACH!**



**NEW**

## Miniature Toggle Switch

DP3T, 240V 2A.

Momentary both sides, centre off. With blue toggle cap.

Cat P-7689

**\$495**



**SCOOP PURCHASE!**

## Mini Speaker

At 8 Ohm and 0.2 W, it's just 38 mm.

Cat C-2209

**\$195**



**NEW**

## Apple Night Eyes Night Viewer

Designed for terrain urban viewing and orientation in the twilight, the Apple Nighteyes can be used by tourists, hunters, guard services for sea navigation and other tasks at night. The viewer makes it possible to observe in the natural night-sky background light as well as in the moon and stella light. Complete with a removable laser illuminator allows observation in total darkness. Also comes with soft carry case and shoulder strap. Nighteyes uses 2 x "AA" batteries.

Cat L-8150

**12 MONTH WARRANTY**

**\$999**

Available in selected stores only.

May be ordered if unavailable at your store.

### MAJOR DICK SMITH ELECTRONICS AUTHORISED STOCKISTS:

NSW: •Batemans Bay 725 030 •Bathurst 323 933 •Bowral 611 861 •Broken Hill 884 098 •Cootamundra 422 561 •Deniliquin 813 672 •Dubbo 828 711 •Goulburn 221 288 •Grafton 421 911 •Griffith 624 534 •Kempsey 631 134 •Leeton 532 800 •Moree 522 091 •Mudgee 723 895 •Murwillumbah 723 684 •Parkes 623 366 •Richmond 784 101 •Tuncurry 545 006 •Windsor 776 722 •Young 821 279 VIC: •Ararat 522 345 •Bairnsdale 525 677 •Benalla 622 710 •Colac 312 847 •Echuca 822 956 •Hamilton 72 2865 •Horsham 824 680 •Morwell 339 458 •Rosebud 822 225 •Shepparton 219 497 •Swan Hill 329 303 •Warragul 234 255 •Warrnambool 615 111 •Wonthaggi 721 411 QLD: •Ayr 831 566 •Boonah (0754) 632 606 •Bundaberg 521 785 •Caloundra (0754) 918 533 •Gympie (0754) 836 677 •Ingham 763 188 •Innisfail 612 014 •Kingaroy 625 777 •Mackay 511 723 •Maryborough 214 559 •Mossman 982 200 •Mt. Isa 433 475 •Pialba 283 749 TAS: •Burnie 319 222 •Devonport 248 322 SA: •Whyalla 454 764 WA: •Albany 412 077 •Bunbury 216 222 •Busselton 542 991 •Geraldton 211 278 •Mandurah 581 4940 •Margaret River 573 888

Stores Across Australia & New Zealand



# Time To Stock Up!


## WIA HAM Radio Callbook 1996

Lists call signs, names and address information for all the licensed amateur radio operators in Australia.

Cat B-2338

**\$15**

**NEW**

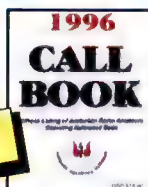

## Free Keyboard Template


## Microsoft Office Short Cuts Pack

All the Short Cuts Guide Books to the Microsoft Office program, plus a **FREE keyboard template** to Microsoft Office. Great for those who need memory joggers.

Cat B-8130

**\$29.95**

**NEW**

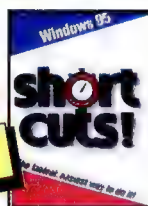

## Antennas & Techniques For Low-Band DXing

An in-depth treatment of antennas and operating strategies you need to span the continents on 40, 80 and 160 meters. Operating tips, antenna designs and software.

Cat B-2110

**\$39.95**

**NEW**




## Troubleshooting And Repairing VCRs 3rd Edition

With step-by-step details on home VCR maintenance and troubleshooting power supplies and logic circuitry problems.

Cat B-1640

**\$54.95**

**NEW**

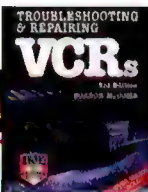


## Precision Knife Set

This 13-piece Precision Knife Set comes with three quality (varying size) knife handles and 10 spare blades in a variety of shapes and sizes. Comes in a handy plastic storage case.

Cat T-3618

**\$12.95**

**SAVE \$4**

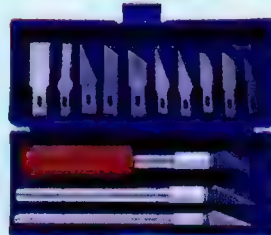

## Packet: Speed, More Speed & Applications

For packet enthusiasts interested in medium to high speed packet systems or applications that go beyond BBSs and Packet Cluster. Includes projects, special topics & references.

Cat B-2410

**\$26.95**

**NEW**



## Passport To Worldband Radio, 1996

What's on shortwave radio, the best and worst radios, how to get the most from your shortwave radio and more!

Cat B-2057

**\$34.95**

**NEW**




## With CD-ROM Upgrading & Repairing PCs 5th Edition

Scott Mueller's latest updated work is now more comprehensive than ever. It covers the Pentium Family and Intel Licensed processors. Contains a CD-ROM with a wealth of helpful information.

Cat B-6189

**\$79.95**

**NEW**

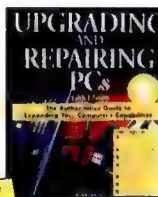

## Transformer 7.5 - 42.5 V @ 60 VA

Power Rating: 60VA  
Output Windings: 0 - 10 - 17.5V @ 1.4A  
0 - 17.5V @ 1.4V  
0 - 7.5V @ 1.4A  
Terminations: Solder lugs  
Dimensions: 65(h) x 79(w) x 70(d)mm

Cat M-6676

**\$19.50**

**SAVE 30%**



## PHONE, FAX & MAILORDER SERVICE

**AUSTRALIA:** Outside Sydney: **FREE Call (1800) 263 922**  
Sydney and Enquiries - (02) 9937 3366

Fax: (02) 805 1986 or write to

Dick Smith Electronics, Mail Orders, Reply Paid 160  
PO Box 321 NORTH RYDE NSW 2113

**NEW ZEALAND:** Phone: (09) 480 8049 or (09) 480 3331

Fax: (0800) 800 290 or write to

Dick Smith Electronics, Mail Orders Division, Private Bag 102-903  
North Shore Mail Centre, Auckland

All major Credit Cards accepted. Overnight Courier Available.

# DICK SMITH ELECTRONICS

**This magazine is now on sale at  
all of our New Zealand stores!**

NSW • Albury 21 8399 • Bankstown Square 707 4888 • Blacktown 671 7722 • Bondi 387 1444 • Brookvale 9905 0441 • Burwood 744 7299 • Campbelltown 27 2199 • Chatswood 411 1955 • Chullora 642 8922 • Gore Hill 439 5311 • Gosford 25 0235 • Hornsby 477 6633 • Hurstville 580 8622 • Kotara 56 2092 • Liverpool 600 9888 • Maitland 33 7866 • Miranda 525 2722 • Newcastle 61 1896 • North Ryde 9937 3355 • North Sydney (Greenwood Plaza) 9964 9468 • Orange 618 400 • Parramatta 689 2188 • Railway Square 211 3777 • Penrith (047) 32 3400 • Sydney City York St 267 9111 & Mid City Centre 221 0000 • Tamworth 66 1711 • Wollongong 28 3800 ACT • Belconnen (06) 253 1785 • Fyshwick 280 4944 VIC • Ballarat 31 5433 • Bendigo 43 0388 • Box Hill 9890 0699 • Coburg 9383 4455 • Dandenong 9794 9377 • East Brighton 9592 2366 • Essendon 9379 7444 • Frankston 9783 9144 • Geelong 232 711 • Highpoint 9318 6300 • Melbourne City Strand Central Arcade 9663 5320 & 246 Bourke St 9639 0396 • Richmond 9428 1614 • Ringwood 9879 5338 • Springvale 9547 0522 QLD • Alderley 3356 3733 • Booval 3282 6200 • Brisbane City 3229 9377 • Buranda 3391 6233 • Cairns 311 515 • Capalaba 3245 2870 • Chermiside 3359 6255 • Indooroopilly 3878 4944 • Maroochydore 791 800 • Mermaid Beach 5578 5600 • Rockhampton 27 9644 • Southport 5532 9863 • Toowoomba 38 4300 • Townsville 72 5722 • Underwood 3341 0844 SA • Adelaide City Pulteney St 232 1200 & Myer Centre 231 7775 • Elizabeth 255 6099 • Enfield 260 6088 • St Marys 277 8977 • Westlakes 235 1244 WA • Balcatta 240 1911 • Cannington 451 8666 • Fremantle 335 9733 • Perth City 481 3261 • Midland 250 1460 • Northbridge 328 6944 TAS • Glenorchy 732 176 • Hobart 31 0800 • Launceston 344 555 NT • Darwin 81 1977

\* STORES IN RED ARE OPEN SUNDAYS. STORES ACROSS AUSTRALIA AND NEW ZEALAND



# Surround Sound MIXER & DECODER



**PART 1 – By JOHN CLARKE**

*Build this unit and add depth, realism and effects to your home videos. It provides realistic surround sound mixing, while an inbuilt decoder provides the rear channel signal during playback if a surround sound processor is unavailable.*



**W**HILE HOME VIDEOS usually provide fairly bland viewing for all but a few doting grandparents and close relatives, this does not have to be so. Surround sound can capture the audience so that they become part of the action.

Adding surround sound will add a new dimension to your video recordings. It may even stir you into creating bigger and better movie productions, as you experiment with surround mixing.

As well as surround mixing, this Surround Sound Mixer & Decoder can also be used to mix normal stereo signals; ie, by using just the Left and Right channels. You can also mix in signals from two other sources via the A and B channels.

By adding the Centre and Surround channels, you will have surround processing. Signals from the A and B inputs can be mixed into any of the Left, Centre, Right and Surround channels using the L-R and the C-S pan controls. The resulting surround sound signal is encoded into the Left and Right channels and is subsequently decoded on replay.

To simplify the task of mixing, signal level meters are fitted to all four

output (L, C, R & S) channels. They comprise 10-LED displays with a -24dB to +3dB range in 3dB steps. In operation, they monitor the encoded Left and Right channel signals and the Centre and Surround channels.

### Surround sound playback


The encoded signals can be played

back in stereo or mono but in order to obtain surround sound, they must be replayed through a stereo VCR and decoder. While the mixer does incorporate a simple decoder, its main purpose is to provide the meter signals.

Ideally, for best sound effects, the L & R outputs from the VCR should be fed through a Dolby Pro Logic surround sound decoder. This

could be a commercial unit or you could use either of the two units described in SILICON CHIP (see Dec.94-Jan.95 and Nov.95-Dec.95). Fig.1(a) shows the basic scheme.

If you don't have a Dolby Pro Logic decoder, the basic decoder built into the Surround Sound Mixer & Decoder can be used instead. In this case, the L & R outputs from the VCR connect to the Left

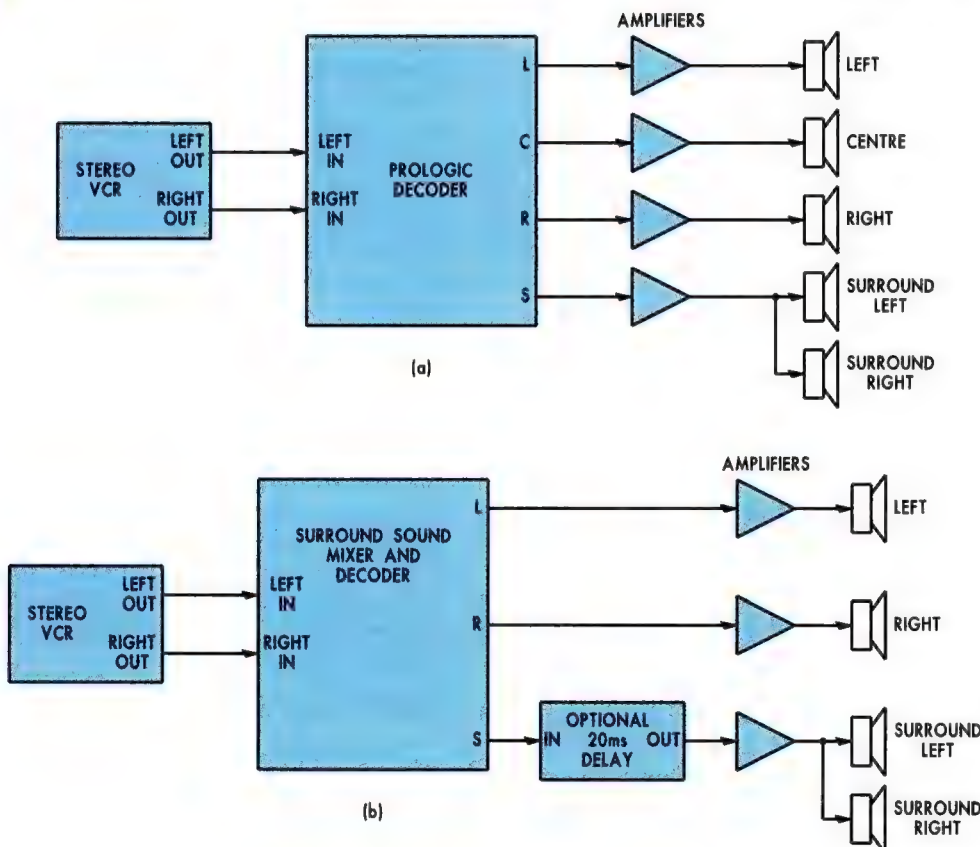


**Fig.1:** the encoded signals on the video tape can either be decoded using a Dolby Pro Logic unit as shown at (a), or fed through an internal decoder in the mixer itself as shown at (b). In the case of (b), the Centre (C) channel is not normally used, while the Surround (S) channel should ideally pass through a 20ms delay before being fed to its power amplifier.

## Main Features

- Surround sound encoding and decoding.
- Encoding similar to 4-channel Dolby® surround format.
- Encoded signals can be decoded by Dolby Pro Logic® and passive surround sound units, or by using the internal decoder in the mixer.
- Compatible with normal stereo and mono outputs.
- Separate Left, Centre, Right and Surround inputs, plus A and B channel inputs.
- A-channel panning between L-R and C-S.
- B-channel panning between L-R and C-S.
- Separate level controls for all inputs.
- Balanced or unbalanced microphone and line input options.
- Single output level control.
- LED level meters for the L, C, R & S channels (-24dB to +3dB).



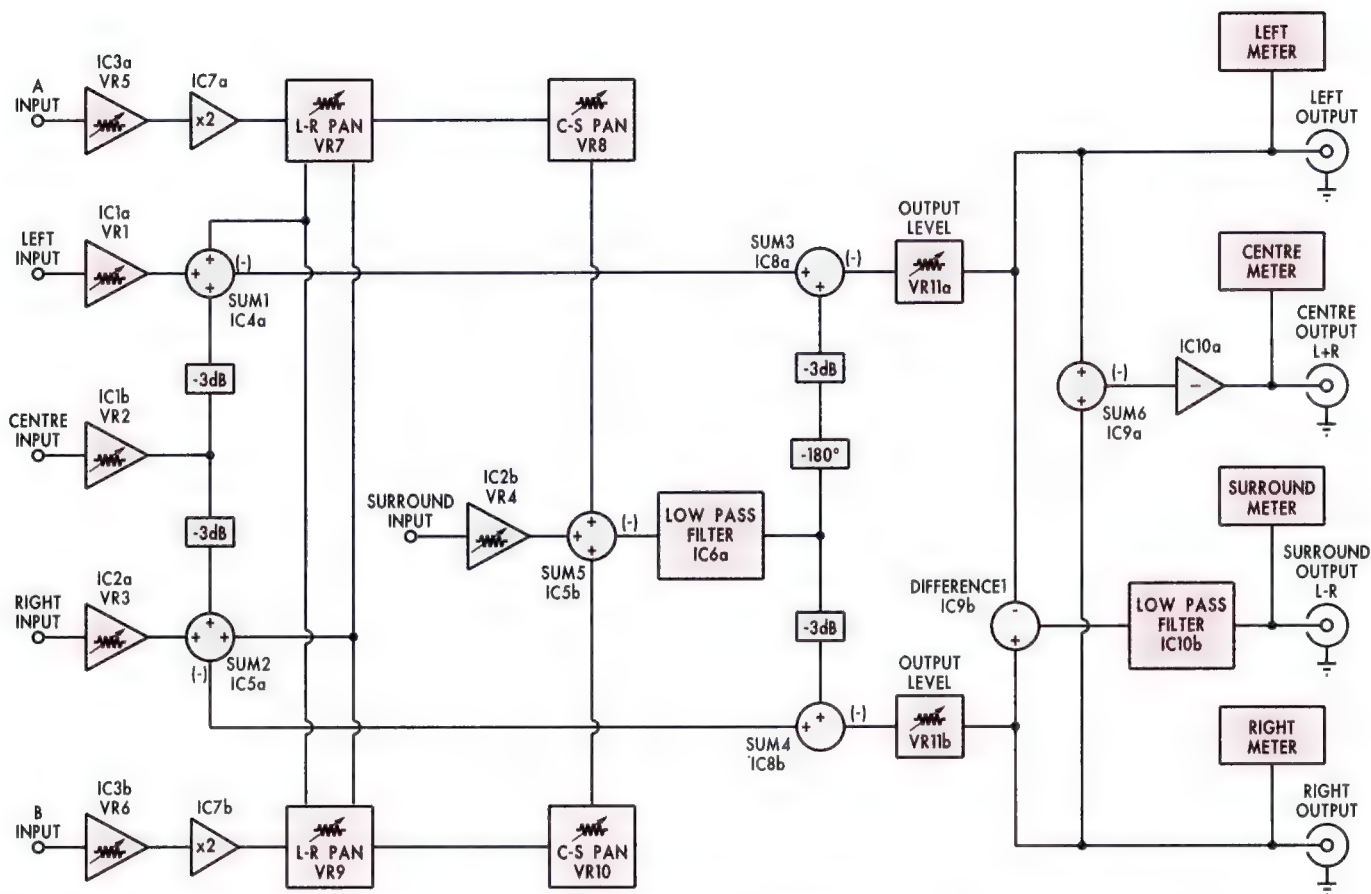

**Fig.2: block diagram of the Surround Sound Mixer and Decoder.** The various inputs are mixed in summing amplifier stages before being fed to the Left and Right outputs via level controls VR11a and VR11b. On playback, IC9a sums the Left and Right channels to provide the Centre output, while IC9b produces a difference output which is then filtered to provide the Surround output.

and Right channel inputs of the unit in the line mode – see Fig.1(b). The overall volume can then be controlled by the Output Level control, while the balance is adjustable using the individual Left and Right level pots.

Note that, ideally, the Surround channel output from the mixer unit should be passed through a 20ms delay (a suitable 20ms delay unit will be described in the February 1996 issue of *SILICON CHIP*). The Centre output is best left disconnected here, since it will have poor separation from the Left and Right channels.

Note also that the decoded sound will be nowhere near as realistic as from a Dolby Pro Logic unit. The decoder built into the mixer is very much a “poor man’s” approach to surround sound, although it can still give good effects.

In either case, separate amplifiers are required for the Left, Right, Surround and Centre channels in order to drive the loudspeakers. The Left and

Right channels are normally fed to an existing stereo amplifier, while a second stereo amplifier can be used for the Surround and Centre channels. Alternatively, some Dolby Pro Logic decoders have several audio amplifiers built in.

### Inputs & outputs

As shown on the main circuit diagram (Fig.3), each input has a stereo jack socket which can accept either a microphone or a line level signal, as selected by a toggle switch. Either a balanced or an unbalanced source can be used for the microphone input, while line level inputs must be unbalanced. If necessary, unbalancing can be achieved by using either a mono plug or a stereo plug wired with the ring connection to ground.

At the other end, the outputs are run to RCA sockets to provide the Left, Centre, Right and Surround (L, C, R & S) signals. For recording purposes, the Left and Right channels

only connect to the tape recorder (or VCR).

Although making a stereo recording is fairly straightforward, 4-channel recordings will require a fair degree of practice. Fairly obviously, you will need four microphones – one for each channel. For a concert, the Left, Centre and Right microphones should be spread across the stage. The rear channel microphone can either be placed behind the stage or within the audience, depending on the effect you want.

The A and B inputs can be used to add background sounds or music to one or more channels. And, if desired, you can produce the effect of movement between one channel and another by panning. There are four panning controls in all (two for the A input and two for the B input) and these provide panning between the Left and Right channels (Pan L-R) and between the Centre and Surround channels (Pan C-S).

### Block diagram

Fig.2 shows the block diagram of the unit. Starting at the left, there are six amplifiers for the Left, Centre, Right, Surround, A and B inputs. The



output levels from these stages are set by potentiometers VR1-VR6 respectively.

The Left amplifier output connects to summing junction SUM1 which comprises IC4a. This mixes in the Centre amplifier output after it has been attenuated by 3dB. Similarly, the Right amplifier output connects to summing junction SUM2 (formed by IC5a) and this also mixes in a -3dB Centre signal.

The A and B amplifier outputs are each amplified by two, using IC7a and IC7b respectively. This is done to compensate for losses in the following L-R pan circuit stages. The resulting L-R pan signals are then mixed into the SUM1 and SUM2 junctions.

Similarly, the Surround amplifier output is summed at SUM5 with the C-S (Centre to Surround) pan control outputs. The summed output is then filtered using low-pass filter stage IC6a, so that only signals below about 7kHz are fed to the following stages.

Following IC6a, the Surround signal is fed in two different directions. In one direction, it is first phase shifted by 180° (ie, inverted), then attenuated by 3dB and mixed at SUM3 with the signal from SUM1. In the other direction, it is fed straight to a 3dB attenuator (ie, no phase shifting) and then mixed at SUM4 with the signal from SUM2.

The process so far is similar to the encoding process used for Dolby Surround Sound recording, except that no noise reduction is used in the Surround signal path. This lack of noise reduction encoding circuitry is not important in this application, particularly as we wanted to keep costs down.

## Output level control

The SUM3 and SUM4 outputs are now fed to output level controls VR11a and VR11b, respectively. These are sections of a dual-ganged pot and are used to adjust the encoded Left and Right channel output levels. From there, the encoded signals are fed to the Left and Right channel output sockets. They are also used to drive the Left and Right signal strength meters.

In addition, the encoded Left and Right channel outputs drive summing circuit SUM6 and difference circuit DIFFERENCE1. The SUM6 output provides the Centre channel and is inverted (IC10a) before being fed to the output socket and to the Centre meter.

## PARTS LIST

1 sloping front console cabinet,  
170 x 213 x 31 x 82mm  
1 PC board, code 02302961,  
144 x 194mm  
1 PC board, code 02302962, 76  
x 105mm  
1 PC board, code 02302963, 72  
x 82mm  
1 self-adhesive front panel label,  
166 x 215mm  
1 self-adhesive rear panel label,  
165 x 78mm  
6 10kΩ log pots (VR1-VR6)  
4 10kΩ linear pots (VR7-VR10)  
1 10kΩ dual ganged pot (VR11)  
1 1kΩ horizontal trimpot (VR12)  
7 SPDT toggle switches (S1-S7)  
6 6.35mm stereo PC board  
mount switched sockets  
1 2 x 2-way PC-mount RCA  
panel socket (Altronics P0211)  
1 DC panel socket (to suit  
plugpack)  
1 12VAC 300mA plugpack  
4 knobs with blue insets  
2 knobs with red insets  
2 knobs with purple insets  
3 knobs with black insets  
15 cable ties  
1 15m length of single shielded  
cable  
1 1.5m length of yellow hook-up  
wire  
1 500mm length of red hook-up  
wire  
1 500mm length of green hook-  
up wire  
1 800mm length of blue hook-up  
wire  
4 9mm tapped spacers  
4 6mm untapped spacers  
4 3mm dia. x 12mm screws  
5 3mm dia. x 6mm screws

1 3mm nut  
74 PC stakes  
4 11-way pin headers (13mm  
long pins)

### Semiconductors

10 LM833 dual op amps (IC1-  
IC10)  
1 TL071, LF351 single op amp  
(IC11)  
4 LM3915 log. display drivers  
(IC12-IC15)  
1 7812T 3-terminal regulator  
(REG1)  
1 B104 1A bridge rectifier (BR1)  
4 BC328 PNP transistors (Q1-  
Q4)  
4 1N914 signal diodes (D1-D4)  
40 3mm red LEDs (LED1-40)

### Capacitors

1 2200μF 25VW PC electrolytic  
1 100μF 16VW PC electrolytic  
12 47μF 16VW PC electrolytic  
6 10μF 16VW PC electrolytic  
20 2.2μF 16VW PC electrolytic  
19 0.1μF MKT polyester  
2 .0027μF MKT polyester  
2 680pF ceramic  
6 220pF ceramic  
1 180pF ceramic  
1 100pF ceramic

### Resistors (0.25W, 1%)

4 1MΩ	8 4.7kΩ
4 100kΩ	12 2.2kΩ
19 22kΩ	4 1.2kΩ
4 16kΩ	8 1kΩ
2 20kΩ	4 680Ω
4 13kΩ	6 220Ω
1 12kΩ	4 150Ω
30 10kΩ	5 100Ω
2 8.2kΩ	

The DIFFERENCE1 output provides the Surround signal. This is rolled off above 7kHz by low pass filter stage IC10b before being applied to the output socket and metering circuitry.

## Circuit


Refer now to Fig.3 for the complete circuit details. Although it may appear quite complicated at first glance, there is in fact a considerable amount of duplication for the various inputs.

Let's begin by taking a look at the

input circuitry for the Left signal. This circuit is based on op amp IC1a which is wired in the balanced configura-

**Fig.3 (following pages): the input and summing circuitry is based on LM833 dual op amps (IC1-8), and these are also used in the decoding circuitry (IC9-10). IC11 is used to derive the split supply, while the four signal level meters are based on LM3915 display driver ICs.**



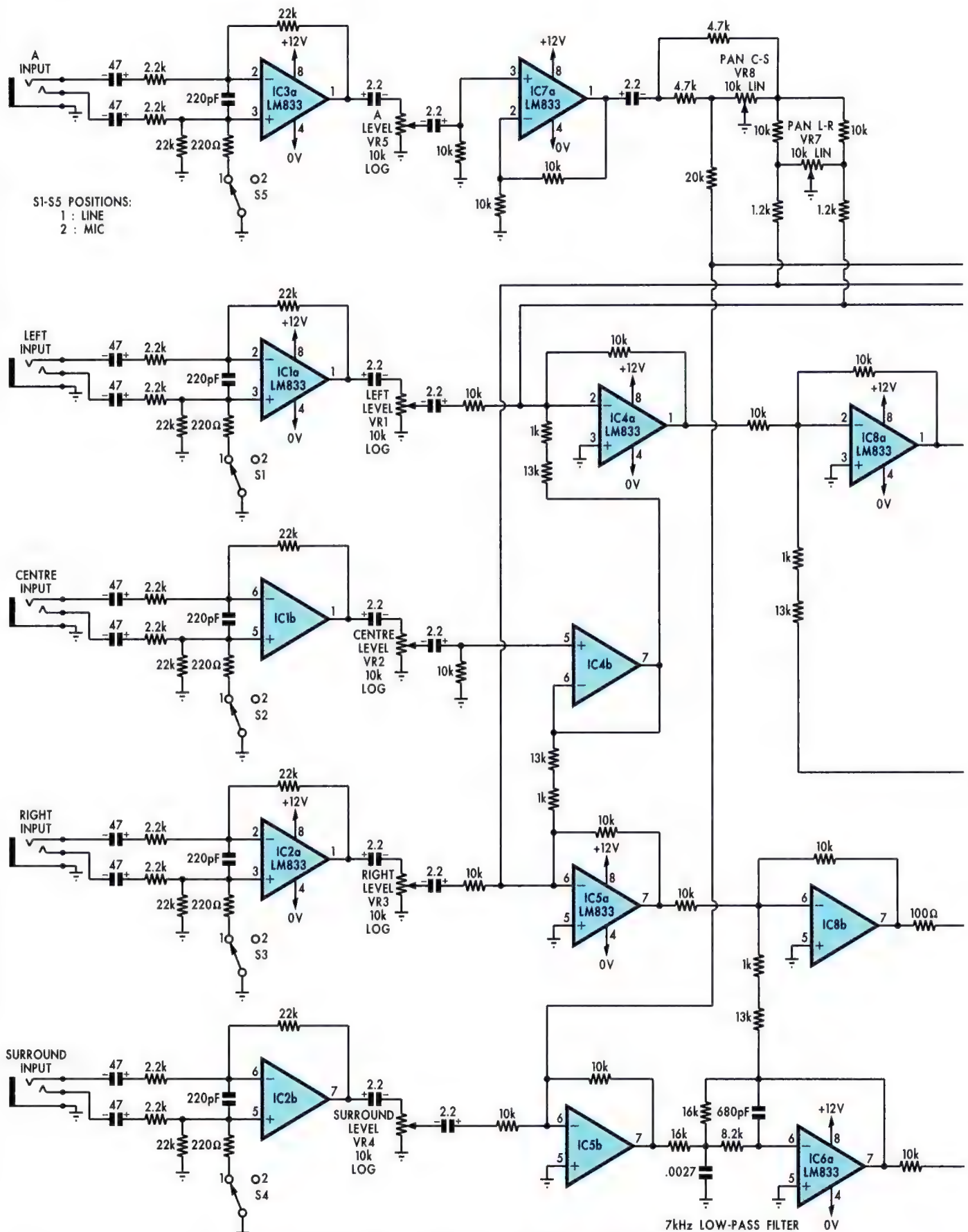

**SURROUND SOUND MIXER AND DECODER**







## Performance of Prototype

### Signal-To-Noise Ratio

Better than 84dB with respect to 1V output

### Frequency Response:

L, C, & R Channels: -1dB at 10Hz & 40kHz

A & B Channels: -3dB at 40Hz & -1dB at 40kHz

S Channel: -3dB at 7kHz

### Total Harmonic Distortion

0.01% at 1kHz and 300mV input

### Decoder Separation

Surround to Centre Channels: 42dB minimum at 1kHz

Left to Right Channels: 76dB at 1kHz

Left & Right to Centre Channel: 12dB

Left & Right to Surround Channel: 15dB

### Signal Handling

2V RMS maximum for line input

### Sensitivity:

Mic Input: 30mV for 300mV out. Line Input: 300mV for 300mV out.

tion. Assuming that S1 is in the MIC position, it has a gain of -10 for signals fed to its inverting input and +11 for signals fed to its non-inverting input (as set by the 22k $\Omega$  feedback resistor and the 2.2k $\Omega$  input resistors).

However, signals applied to the non-inverting input are first attenuated by 0.909 using a resistive divider (2.2k $\Omega$  & 22k $\Omega$ ) before being amplified. As a result, the overall stage gain for signals applied to the non-inverting in-

put is +10, which matches the gain for the inverting input. This gives good common mode rejection for balanced signals (eg, from a microphone).

For unbalanced signals, the inverting socket connection must be grounded externally by a mono plug (or by earthing the ring terminal of a stereo plug). This means that only signals at the socket tip will be amplified, with IC1a now operating as a non-inverting amplifier.

Assuming that S1 is closed (LINE), the input signal is attenuated by the 220 $\Omega$  resistor and the overall stage gain is +1. The output from IC1a appears at pin 1 and is fed to level control VR1.

IC1b, IC2a, IC2b, IC3a & IC3b are the input amplifiers for the Centre, Right, Surround, A and B channel inputs respectively. These stages are all identical to IC1a and their outputs feed level controls VR2-VR6.

Following VR1, the Left signal is fed to summing amplifier IC4a via a 10k $\Omega$  resistor. Similarly, the Right signal is fed via a 10k $\Omega$  resistor to summing amplifier IC5a. The Centre channel output at the wiper of VR2 is buffered using IC4b before being applied to each of these summing junctions via a 14k $\Omega$  resistance (made up of 13k $\Omega$  and 1k $\Omega$  resistors in series).

This arrangement effectively attenuates the Centre channel signal by 3dB with respect to the Left and Right signals. That's because IC4a & IC5a operate with a gain of -1 for the Left and Right signals, and a gain of -0.714 for the Centre signal.

Moving now to the Surround channel, the signal on the wiper of VR4 is coupled to pin 6 of IC5b, where it is summed with the Centre-Surround (C-S) pan signals (more on these shortly). The output of IC5b then drives IC6a. This op amp is wired as a 2-pole low-pass filter stage and rolls off frequencies above 7kHz.


TABLE 1: RESISTOR COLOUR CODES

	No.	Value	4-Band Code (1%)	5-Band Code (1%)
□	4	1M $\Omega$	brown black green brown	brown black black yellow brown
□	4	100k $\Omega$	brown black yellow brown	brown black black orange brown
□	19	22k $\Omega$	red red orange brown	red red black red brown
□	4	16k $\Omega$	brown blue orange brown	brown blue black red brown
□	2	20k $\Omega$	red black orange brown	red black black red brown
□	4	13k $\Omega$	brown orange orange brown	brown orange black red brown
□	1	12k $\Omega$	brown red orange brown	brown red black red brown
□	30	10k $\Omega$	brown black orange brown	brown black black red brown
□	2	8.2k $\Omega$	grey red red brown	grey red black brown brown
□	8	4.7k $\Omega$	yellow violet red brown	yellow violet black brown brown
□	12	2.2k $\Omega$	red red red brown	red red black brown brown
□	4	1.2k $\Omega$	brown red red brown	brown red black brown brown
□	8	1k $\Omega$	brown black red brown	brown black black brown brown
□	4	680 $\Omega$	blue grey brown brown	blue grey black black brown
□	6	220 $\Omega$	red red brown brown	red red black black brown
□	4	150 $\Omega$	brown green brown brown	brown green black black brown
□	5	100 $\Omega$	brown black brown brown	brown black black black brown







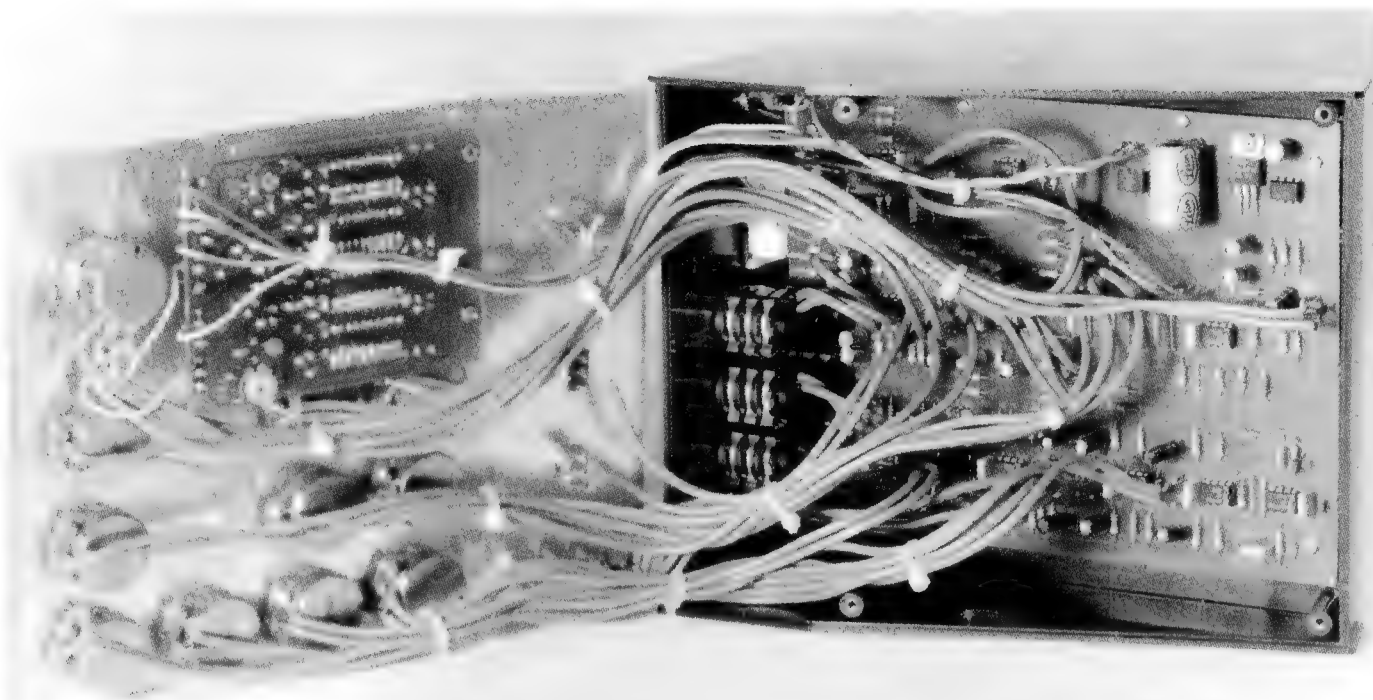

**The Surround Sound Mixer and Decoder is built into a compact console case with a sloping front panel. Note that there is a fair amount of internal wiring to be run, most of it between the main board and the front panel controls.**

level controls VR11a and VR11b. The encoded Left and Right signals are then coupled to their respective output sockets via 2.2 $\mu$ F capacitors.

### Panning

Now let's take a look at how the pan signals are derived.

In the case of the A input, the signal at the wiper of VR5 is first buffered and amplified by IC7a. This stage functions as a non-inverting amplifier with a gain of two. The output from IC7a is then applied to pan control VR8 via a 4.7k $\Omega$  resistor and to pan control VR7 via a second 4.7k $\Omega$  resistor and two 10k $\Omega$  isolating resistors.

VR7 is used to pan the "A" signals between the Left and Right channel summing amplifiers (IC4a and IC5a), while VR9 does the same for the "B" signals. Similarly, VR8 and VR10 (Pan C-S) pan the "A" and "B" signals between the Pan L-R controls and the input to IC5b.

In theory, VR7 and VR9 pan between the Left and Right channels, while VR8 and VR10 pan between the Centre and Surround channels. In practice, however, there is some interaction between these controls.

### Surround sound decoding

The internal decoding circuitry is

based on IC9a, IC9b, IC10a & IC10b and is normally only used on play-back – see Fig.1(b). IC9a and IC10a are used to derive the Centre channel. This is achieved by first adding the Left and Right channel outputs together in summing amplifier IC9a. The output of IC9a is then buffered by unity gain inverter IC10a and coupled to the Centre output socket.

A different technique is used to derive the Surround output. In this case, the encoded Left and Right channel outputs are fed to IC9b which is configured as a difference amplifier. This configuration is arrived at by feeding the Left channel to the inverting (pin 6) input and the Right channel to the non-inverting (pin 5) input.

The output from IC9b is simply the difference between the two input sig-

nals. This signal is filtered and inverted by low-pass filter stage IC10b and fed to the Surround output socket.

### Signal meters

As mentioned previously, the circuit contains four signal level meters which monitor the Left, Right, Centre and Surround outputs. These four meters are all identical, so we'll just look at the meter that monitors the Left output.

The circuit is based on IC12 which is a 10-LED display driver wired in dot mode. In operation, the incoming signal is first buffered by emitter follower stage Q1. It is then rectified by D1, filtered and applied to pin 5 of IC12.

The filter components on pin 5 consist of a 0.1 $\mu$ F capacitor and a 1M $\Omega$  resistor, connected in parallel. These give the meter a fast attack time and a slow decay response, so the meter effectively displays the peak average value.

As well as acting as a buffer, Q1 also compensates for the voltage drop across D1, since its emitter is always approximately 0.6V above its base. While this compensates fairly well, the balance is not perfect since there is more current through Q1's base-emitter junction than through D1. This slight imbalance is taken care of by using VR12 to set an offset voltage on pin 3 (RLO) of IC12. This jacks the pin

**TABLE 2: CAPACITOR CODES**

Value	IEC Code	EIA Code
0.1 $\mu$ F	100n	104
.0027 $\mu$ F	2n7	272
680pF	680p	681
220pF	220p	221
180pF	180p	181
100pF	100p	101



3 voltage up so that it equals the voltage at pin 5 when the input signal is tied to ground.

The full scale deflection value for the meter depends on the voltage on pin 7 and is set by the  $4.7\text{k}\Omega$  and  $680\Omega$  resistors. In this case, the voltage on pin 7 is set to  $1.64\text{V}$ , which corresponds to a peak value of  $3\text{dB}$  above  $774\text{mV RMS}$  (ie, LEDs 1-10 lit). As a result, the meter is calibrated for  $0\text{dBm}$ , which corresponds to  $1\text{mW}$  into  $600\Omega$ .

## Power supply

Power for the circuit is derived from a  $12\text{VAC}$  plugpack. This is fullwave rectified using BR1, filtered by a  $2200\mu\text{F}$  capacitor and applied to REG1 to derive a regulated  $+12\text{V}$  output.

IC11 is used to provide the circuit ground, so that the op amps are effectively fed from split supply rails. It does this by buffering the  $5.45\text{V}$  output from a voltage divider ( $12\text{k}\Omega$  &  $10\text{k}\Omega$ ) wired across the regulator output. The  $100\Omega$  resistor at IC11's output isolates the op amp from the following  $100\mu\text{F}$  capacitive load and prevents oscillation.

As a result, the  $+12\text{V}$  rail is  $6.55\text{V}$  above ground, while the  $0\text{V}$  rail is  $5.45\text{V}$  below ground; ie we effectively have split supply rails of  $+6.55\text{V}$  and  $-5.45\text{V}$ .


## Construction

Despite the circuit complexity, building this unit is quite straightforward. Most of the circuitry is contained on three PC boards: (1) a main board coded 02302961 ( $144 \times 194\text{mm}$ ); (2) a display driver board coded 02302962 ( $76 \times 105\text{mm}$ ); and (3) a LED display board coded 02302963 ( $72 \times 82\text{mm}$ ).

Begin the construction by checking the PC boards. In particular, check for any breaks in the tracks and for shorts between adjacent tracks. The board mounting holes should all be drilled to  $3\text{mm}$ , while a  $3\text{mm}$  hole is also required on the main board for the regulator (REG1) mounting screw.

Fig.4 shows the parts layout on the main PC board. Start by installing PC stakes at all external wiring points, then install the wire links (using tinned copper wire).

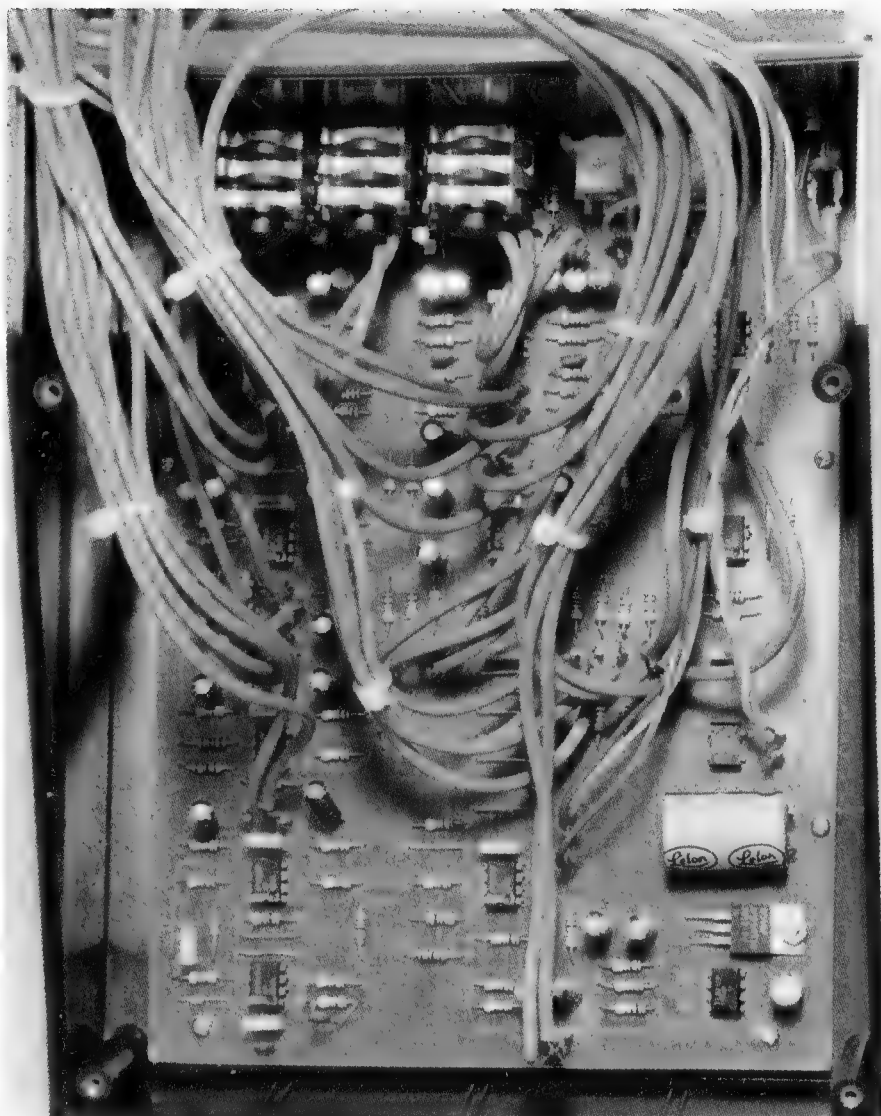The next step is to install the ICs. Note that these must all be oriented in the same direction. Note too that IC11 is a TL071 while the rest are all



**Make sure that all polarised parts are correctly oriented when building the main PC board. The  $2200\mu\text{F}$  capacitor (bottom, right) is installed on its side and is secured to the board using silicone sealant to prevent lead breakage.**

LM833s, so don't get them mixed up. The bridge rectifier (BR1) can also now be installed (orient it as shown), followed by 3-terminal regulator REG1. Secure REG1's metal tab to the PC board using a screw and nut.

The resistors and capacitors can now be mounted. Table 1 lists the resistor colour codes but it is also a good idea to check them with a multi-meter, as some colours can be difficult to decipher. Table 2 lists the capacitor codes. Make sure that the electrolytic capacitors are all correctly oriented and note that the  $2200\mu\text{F}$  capacitor is mounted on its side.

Use silicone sealant to secure the body of the  $2200\mu\text{F}$  capacitor to the board, to prevent its leads from flexing and eventually breaking.

As shown on Fig.4, three of the

$6.35\text{mm}$  stereo sockets are mounted directly on the main board. Install these now, along with the  $2 \times 2$  RCA socket package. The mounting clips on the underside of RCA socket package will have to be removed using side cutters before it is installed on the board.


That's all we have space for this month. Next month, we will resume with the parts layout diagrams for the display driver and display boards and give the complete wiring and testing details. We will also publish the full-size PC board patterns and the front-panel layout.

**Note:** "Dolby", "Pro Logic" and the Double-D symbol are trademarks of Dolby Laboratories Licensing Corporation, San Francisco, CA 94103-4813 USA.



# COMPUTER BITS

BY GEOFF COHEN  
gcohen@pcug.org.au

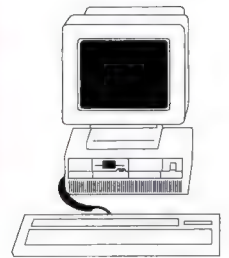

## Upgrading your old PC – is it worthwhile?

**Is it worthwhile upgrading your old PC or should you put the money towards a new one? The answer depends on the state of your old PC and the applications you wish to run.**

There are a swags of old 286, 386 and even 486SX PCs floating around now and a question I often get asked is "is it worthwhile upgrading my old PC to run Windows, or should I buy a new one?". The answer depends, of course, on what sort of PC you have and how much you want to increase the performance – and thus how much you are prepared to spend on the upgrade.

The options are: (1) do a minimal upgrade and recycle the old PC so the kids can run Windows (word processing and games); or (2) go for a full upgrade by replacing the motherboard, CPU and hard disc.

### Is it worth it?

First, you have to decide if it is

worthwhile upgrading your PC. If you have a PC with a mono screen, a hard disc smaller than 80Mb and less than 4Mb of RAM, upgrading the PC to run Windows (especially Windows 95) is not really an economic proposition. In addition, if you have a major brandname PC (IBM, Compaq, etc), you will need to check if the beast uses a standard size motherboard, with normal plug in cards. Many brandname computers use specialised components and cannot accommodate some of the standard parts used in clone PCs.

However, if you your PC has a minimum of a VGA card, a colour monitor and at least 4Mb of RAM, it may be worthwhile upgrading it. At the time of writing (November 1995), the cost

of upgrading to a 486DX2-66 motherboard (including the CPU) is around \$300.00, while a 545Mb hard disc drive and controller can be had for just \$280.00.

The cost of RAM is not too bad either, with the price of a 4Mb 72-pin RAM module currently around \$230.

### What should I upgrade to?

The answer to this question depends on what you want to do. Here are a couple of alternatives to consider:

**(1) Windows/games PC.** If you only want to run Windows 3.1 at a reasonable speed – eg, so that the kids can run Word and a few games – I would recommend upgrading to:

- (i) a 486DX2-66 CPU (these are so cheap it's not worthwhile using a slower CPU);
- (ii) 4Mb RAM; and
- (iii) an 80Mb or preferably bigger hard disc.

**(2) Microsoft Office/Windows 95 PC.** These programs require a bit more firepower than the system listed above. To run Microsoft Office the minimum system would be:

- (i) a 486DX2-66 or 486DX4-100/120 CPU, a Pentium being even better;
- (ii) 8Mb RAM for Windows 3.1 or 16Mb for Windows 95;
- (iii) a 540Mb, 850Mb or even a 1Gb hard disc.

In addition, a CD ROM drive is handy for installing programs like Office and Windows 95, as it saves having to install from multiple floppies.

I have noticed that there are still suppliers advertising Windows 95 systems with only 8Mb of RAM. I have tried this and it is very slow with Office 95. In fact, you need at least


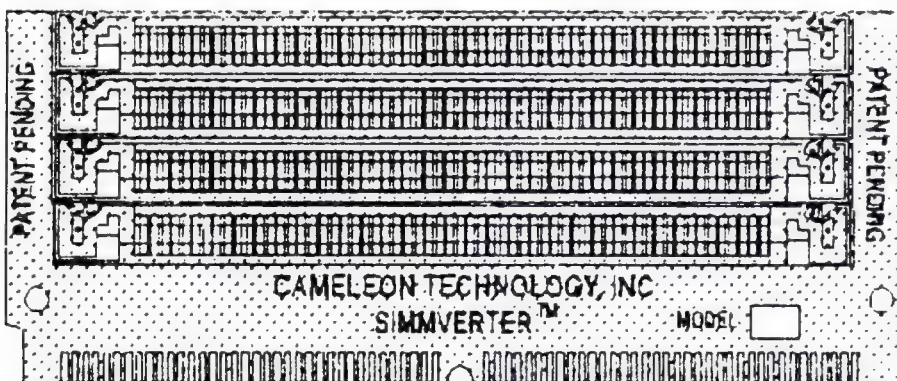


Fig.1: the SimmVerteR from Cameleon Technology accepts four 30-pin memory modules (either 4 x 1Mb or 4 x 4Mb) and effectively converts them to a single 4Mb or 16Mb 72-pin memory module that plugs into the latest motherboards.

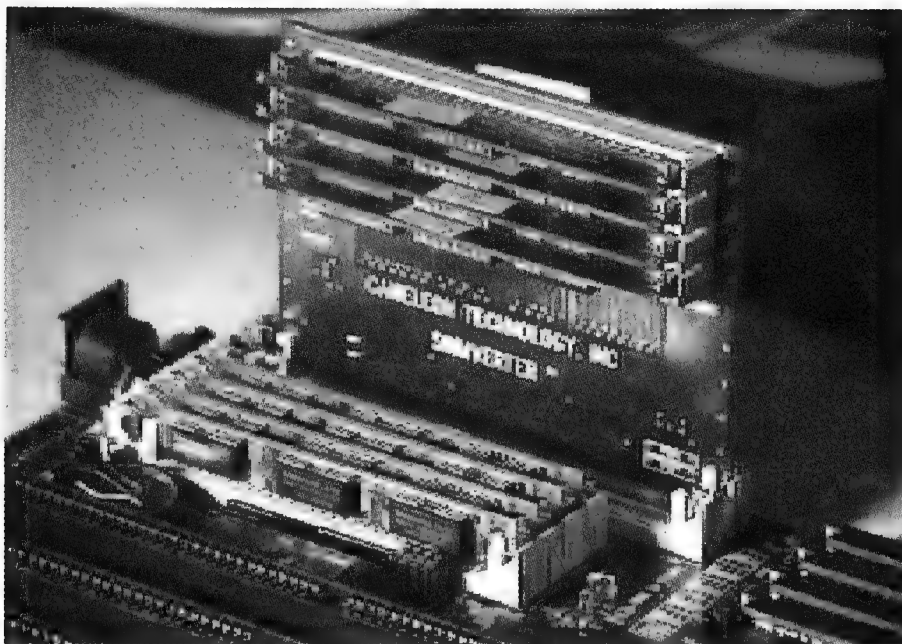



Some motherboards have two sets of 72-pin RAM sockets and four sets of 30-pin sockets. This photo shows a SimmVerter module, itself carrying four 30-pin SIMMs, plugged into one of the 72-pin sockets at the rear.

16Mb for a Windows 95 system if it is to operate at a reasonable speed.

### Using your old memory

A major problem used to be that while older motherboards used 30-pin SIMM RAM, the latest 486 and Pentium motherboards only have sockets for the new 72-pin SIMM RAM. This meant that upgrading to a new motherboard with 72-pin sockets necessitated throwing out (or selling cheaply) any existing 30-pin RAM, which was a tad annoying.

Fortunately, a new device is now available which overcomes this problem. It's called a "SimmVerter" and it effectively allows four 30-pin SIMMs (1Mb or 4Mb) to be converted to one 4Mb or 16Mb 72-pin SIMM module. All you have to do is plug four 30-pin SIMMs into the sockets on the SimmVerter. The SimmVerter itself then plugs into a 72-pin RAM socket on the motherboard.

SimmVerter's cost around \$30 each, which is far less than the cost of having to replace 4Mb of RAM. They are available in four different shapes so that you can easily accommodate four SimmVerter modules adjacent to each other, if necessary – see Fig.2.

Another approach is to see if there is any secondhand RAM available, either on the Net (eg, [aus.ads.for-sale.computers](http://aus.ads.for-sale.computers)) or in the Saturday paper. An important difference with

the Pentium is the need to fit 72-pin SIMMs in groups of two. I won't mention who fell for that trap the first time he installed a Pentium motherboard and used a single 8Mb SIMM, instead of two 4Mb SIMMs, and then complained that the !@#\$%^&\* thing wouldn't work.

If you want to improve Windows performance, the cheapest option is to increase your RAM. Upgrading from 4Mb to 8Mb makes the biggest difference and Word 6, for example, loads many times faster with this simple upgrade. Increasing the memory even further will provide even better per-

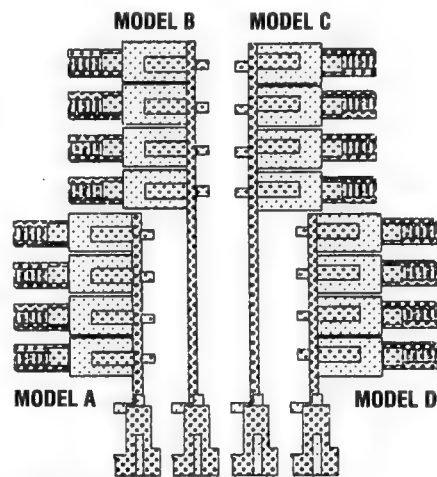


Fig.2: SimmVerter's come in four models (A, B, C and D) so that they can be fitted to adjacent memory sockets.

formance and allow more programs to be opened. 16Mb is a good size for Windows 3.1 and 32Mb for Windows 95.

### Parity or non-parity RAM

Most new motherboards have a CMOS option to enable or disable parity RAM, the default option being non parity in the motherboards I have tried. Unless the PC is going to be used as a network server, non parity RAM should be adequate, as a RAM test is performed every time the PC is switched on. In any case, I cannot remember the last time I had a faulty RAM chip – it was, at least, several years ago.

### Disc controllers

An upgraded disc controller card may be necessary if you are upgrading the hard disc. Assuming that you are going to stick with an IDE disc, you can purchase a multi-I/O card for around \$25. As well as running your floppy drives and two IDE hard discs, this will also generally provide two serial ports, a parallel printer port and a games port. If you have (or are upgrading to) a VESA motherboard, then you should buy a VESA multi-I/O card, as they are much faster than a standard ISA card.

Note, however, that most new Pentium PCI motherboards will already have the floppy, hard disc and I/O controllers on board. In that case, you don't have to worry about a separate I/O card.

### Hard discs

Depending on your requirements, you could stay with an existing 80-200Mb hard disc and buy a used 100-200Mb drive. However, a new 500Mb hard disc is only around \$200 and a minimum of 150Mb is needed to run the full Windows 3.1 and Microsoft Office suite of software.

If you are fitting a hard disc of 500Mb or above and have thousands of files, you need to consider how to partition it. For drives under 512Mb, a one byte file will take 8192 bytes. This increases to 16,384 bytes for 512-1024Mb drives, and so on.

In other words, the larger the logical drive, the larger the space that a one byte file effectively takes up and this wastes space. For example, if you have an 850Mb disc with 10,000 files, this will waste (on average) 10,000 x



## The ZIP Drive – 100Mb On A \$33 Disc



Most computer users don't consider backing up the large hard discs that are now being sold. There's an old saying that there are only two types of computer users: those who have lost data and those who will lose data. The truth is that backing up onto floppy discs is often too cumbersome, while tape drives have the capacity but are quite slow when it comes to retrieving files (unless you have a DAT tape drive).

### External drive

An external drive is the answer to backup problems. One interesting new device is the Zip drive which has recently been released by Iomega. This is a (relatively) cheap 100Mb removable disk drive which retails for around \$370, with the 100Mb discs selling for around \$99 for a pack of three. When installed, it is assigned a drive letter and is treated just like any other disc drive.

I have been using the parallel port version for several weeks now. It really is quite nifty – you just plug it into a parallel port, run GUEST.EXE

and copy to/from the ZIP disc. A SCSI version is also available for the same price and is reported to be three times faster than the parallel version. On the downside, the SCSI version isn't as portable and you have to buy a SCSI controller for it.

### Testing

I did some testing and found that large database files copied to the Zip drive at about 4.5Mb per minute. Alternatively, by using Norton Backup and saving to a logical disc drive, I was able to copy at an effective 8-10Mb per minute and fit over 250Mb (before compression) on one 100Mb disc. So, at just \$33 per disc, the Zip drive is good for archiving applications.

Assuming that it stands up to prolonged use, the Zip drive is a good product. I tested mine by copying files to and from it for over 20 hours without any problems. Zip drives are imported by PolaroidAustralia (1800 066 021) and are available from computer dealers and from Harvey Norman retail stores.

16,384/2 bytes, or around 80Mb.

However, if this disk was configured into two 425Mb partitions, you would save over 40Mb of space. So consider carefully how you should partition

the disc (using FDISK), before you actually start using it.

### Video cards

Even with a Pentium processor, the

speed at which Windows updates the screen may not be all that fast if an old ISA video card is fitted. Starting at around \$120, a VESA or PCI video card will speed things up considerably. Typical examples, using ATPERF for relative performance details, are:

Old ISA	2
VESA	12
PCI	20

Another item to consider, if you want to use high resolution (ie, 1024 x 768 or larger), is the amount of video RAM. A new video card should have a minimum 1Mb of RAM (preferably with sockets to accept more), or you can just bite the bullet and get a video card with 2Mb of RAM for even better performance.

### Installation

For timid souls, there are many computer shops and technicians who will upgrade your PC for a reasonable labour cost. If you are more adventurous, replacing a motherboard is a relatively straightforward job.

First, remove all cables from the PC (including the power cord) and remove the cover (this is usually done by removing a number of self-tapping screws). Once inside the PC, remove all the plug-in cards from the motherboard.

Depending on the age of the PC, the motherboard itself will probably be secured by two or more screws that will need to be removed. Once this has been done, the motherboard will then either lift or slide out.

The next step is to swap the nylon clips from the old to the new motherboard, after which the new motherboard can be installed in the case and the plug-in cards reinstalled. An important point to note here is that if you have two connectors that go to the power connector on the motherboard, the black wires should be next to each other when they are plugged in.

Another option that you may want to consider is a new case, especially if the old one is looking a bit tacky. A complete mini-tower case and power supply can be purchased for less than \$100 and would certainly improve the value of the PC if you wanted to sell it.

Finally, if you have any problems locating a SimmVerter, I purchased mine from The Logical Approach in Canberra – phone (06) 251 6511. **SC**



# RITRON QUAD SYSTEM

NOW WITH 8 MEG RAM

## UPGRADE TO POWER MULTIMEDIA COMPUTING TODAY!

Choosing the right system configuration has never been so easy - simply match your needs & budget to the choices here and you are well on the way to exploring the world of multimedia. Each & every system is powerful in its own rights and will handle today's complex & software applications quite easily.

### 4x QUAD-SPEED CD-ROM DRIVE

• Quad-Speed CD-ROM drive • 8 MEG RAM • 850 MEG H.D.D. • 1 MEG Video Card • 14" SVGA N.I. Mon- 1024 x 768mm 0.28mm D.P. • 1.44 3.5" F.D.D. • Ritron Mouse Pad • Mouse & Joystick • 101 Keyboard • 16-bit Sound Card • Magnetic Shielded Spkr • Workgroups for Windows 3.11 or Windows 95

• INCLUDE 7 FREE CD SOFTWARE TITLES: Microsoft- Works/Money/Encarta' 95/Dangerous Creatures/Golf & CD Sampler and Yellow & White Pages Phone Disc. • 20 Mbytes FREE SHAREWARE GAMES.



### 4 YEAR PARTS & LABOUR WARRANTY (FIRST 2 YEAR ON-SITE) MELB MET AREA 4 HOUR FREE TRAINING COURSE

CPU CHOICES	TAX EX	TAX INC
DX2-66	\$1650	\$1999
DX2-80	\$1710	\$2060
DX4-100	\$1800	\$2090
Pentium™ 60	\$1800	\$2090
Pentium™ 75	\$2050	\$2350
Pentium™ 90	\$2150	\$2450
Pentium™ 100	\$2295	\$2595
Pentium™ 120	\$2390	\$2740
Pentium™ 133	\$2620	\$2990

WITH HEX-SPEED CD-ROM DRIVE...\$250 extra FREE HOME DELIVERY & SETUP- MELBOURNE METRO AREA ONLY

# RITRON QUAD SYSTEM PRO

## UPGRADE TO POWER MULTIMEDIA COMPUTING TODAY!

This range of great systems offer higher performance levels with 8 Meg of RAM, a huge 1 GIG hard disk drive and the Quad-Speed CD-ROM drive. Video or animation files will play more smoothly ever before, off this CD-ROM drive. Internet connection is child's play with these powerful systems.

### 4x QUAD-SPEED CD-ROM DRIVE

• Quad-Speed CD-ROM drive • 8 MEG RAM • 1 GIG Hard Disk Drive • 1 MEG Video Card • 14" SVGA N.I. Monitor- 1024 x 768mm 0.28mm D.F. • 1.44 3.5" F.D.D. • Ritron Mouse Pad • Mouse & Joystick • 101 High Quality Keybrd • 16-bit Sound Card • Magnetically Shielded Spkrs • Workgroups for Windows 3.11 or Windows 95

• INCLUDE 7 FREE CD SOFTWARE TITLES: Microsoft- Works/Money/Encarta' 95/Dangerous Creatures/Golf & CD Sampler and Yellow & White Pages Phone Disc. • 20 Mbytes FREE SHAREWARE GAMES.



### 4 YEAR PARTS & LABOUR WARRANTY (FIRST 2 YEAR ON-SITE) MELB MET AREA 4 HOUR FREE TRAINING COURSE

CPU CHOICES	TAX EX	TAX INC
DX2-80	\$1769	\$2079
DX4-100	\$1820	\$2140
Pentium™ 60	\$1860	\$2100
Pentium™ 75	\$2080	\$2390
Pentium™ 90	\$2240	\$2590
Pentium™ 100	\$2390	\$2720
Pentium™ 120	\$2495	\$2810
Pentium™ 133	\$2690	\$3020

WITH HEX-SPEED CD-ROM DRIVE...\$250 extra FREE HOME DELIVERY & SETUP- MELBOURNE METRO AREA ONLY

## SOUND BLASTER VALUE I6/6X-I7



Combines SBlaster 16 Value with the Creative Hex Speed, Photo-CD compatible, Multi Session, CD-ROM drive & includes SBS30 stereo speakers plus 17 CDs software titles. GREAT VALUE!

## SB PERFORMANCE CD32/6X



Combines SBlaster 32 Plug and Play compliant audio card with the latest Creative Hex speed CD-ROM drive. Includes CS100 stereo speakers, Telex microphone and bundled with 23 software titles. GREAT VALUE PACK!

## Removable Cartridge ZIPPY DRIVE

"zippy" 13.5ms access speed-135MB cheap storage & backup. As fast as a hard drive \$399

## SYQUEST EZ135

4MB/SEC DRIVES EASY TO USE ON DISPLAY AT OUR CITY STORE

## UPGRADES & PERIPHERALS FOR YOUR SYSTEMS

### MULTIMEDIA UPGRADE KIT

Upgrading to multimedia has never been so easy - simply follow the installation instructions. All CD-ROM drives versions are Kodak PhotoCD™ compatible. Includes the same 16-bit Sound Card, Stereo Speakers and great Software titles: Microsoft- Encarta'95/Works/ Money/Golf/Dangerous Creatures & CD Sampler which previews over 55 MS titles, has 8 Windows games.

Quad-Speed Version ..... \$389  
Hex-Speed Version ..... \$499

### CD ROM DRIVES

DUAL-SPEED CD ROM DRIVE  
IDE INTERFACE ..... \$149  
PANASONIC QUAD-SPEED CD ROM DRIVE  
IDE INTERFACE ..... \$249  
PANASONIC 562/Panasonic Interface \$129  
NEW HEX-SPEED CD ROM DRIVE ..... \$399

### MEMORY

30 PIN SIMM	1-9	25+	100+
1M x 9-70 With Parity	\$65	\$63	\$57
4M x 9-70 With Parity	\$209	\$189	\$185
72 PIN SIMM FOR PENTIUM™			
4M X 8-70 No Parity	\$199	\$189	\$179
4M X 9-70 With Parity	\$235	\$239	\$229
8M X 9-70 No Parity	\$399	\$389	\$369
16M X 8-70 No Parity	\$799	\$779	\$729
16M X 9-70 With Parity	\$849	\$819	

MS OFFICE PRO CD UPGRADE/ \*CROSSGRADE- \$99021  
Access Word/PowerPoint  
Schedule+ Excel  
PLUS: MS PLUS- FREE!  
\$449

MS OFFICE STD CD UPGRADE/ \*CROSSGRADE- \$99022  
Access Word/PowerPoint  
Schedule+ Excel  
PLUS: MS PLUS- FREE!  
\$349

### SUPA MOTHERBOARD UPGRADES

486DX2-80# L.B No Cache	\$190
486DX2-80#256K Cache L.B NEW!	\$249
486DX4-100 No Cache PCB NEW!	\$279
486DX4-100#256K Cache L.B NEW!	\$289
PENTIUM™ 60MHz/256 C VESA/PCI	\$299
PENTIUM™ 75MHz/256 C PCI/ISA NEW!	\$599
PENTIUM™ 90MHz/256 C PCI/ISA	\$729
PENTIUM™ 100MHz/256 C PCI/ISA	\$799
PENTIUM™ 120MHz/256 C PCI/ISA	\$899
PENTIUM™ 133MHz/256 C PCI/ISA	\$1099

\*AMD CPU. #CYRIX CPU Without Asterisk- INTEL CPU @ Come with 160mb hard disk on me

### HARD DRIVES VOICE COIL IDE HD

Capacity	Av Access	Price	Tax Inc.
420M	12ms	\$293	\$240
540M	12ms	\$318	\$260
640M	12ms	\$330	\$270
850M	11ms	\$354	\$290
1.08GB	12ms	\$412	\$340
1.27GB	10ms	\$479	\$399
1 GB SCSI HD	10ms	\$561	\$460
1.6GB WESTERN DIGITAL	10ms	\$610	\$500
2.1GB SCSI HD	5400rpm	\$1220	\$1000
2.1GB SCSI HD	7200rpm	\$1220	\$1000
4.2GB SCSI HD	FASTSCSI 2	\$1952	\$1600

ALL DRIVES COME WITH 3 YEAR WARRANTY HARD DRIVE BRACKET...\$495

### NEW MONITOR RANGE

All these superb monitors on display at all stores

• 14" Interlaced 1024x768 (0.28mm Dot pitch)	\$349
• 15" XGA Digital MPRII 1280x1024	\$629
• 15" XGA Digital MPRII 1280x1024	\$699
• 17" XGA Digital MPRII 1600x1280 (0.25mm Dot Pitch)	\$1305
• NEW! 17" XGA Digital MPRII	\$1999

#15" & 17" Digital Monitor comes with Economy Management Software

### VERBATIM DISKS

DESC.	1-9	10+
3 1/2" DS/DS 1.44	\$17.95	\$17.95
3 1/2" DS/HD 2.25	\$19.95	\$17.95
3 1/2" DS/HD 2.25	\$19.95	\$17.95
5 1/4" DS/HD 1.44	\$14.95	\$13.95


## RITRON COMPUTER SYSTEMS

NOW WITH 640 MB H.D.D.

CPU TYPE.....	<b>GREAT VALUE!!</b>	TAX EX.	TAX INC
486DX2-80.....		\$1065	\$1299
486DX4-100.....		\$1099	\$1340
Pentium™ 60*....		\$1099	\$1341
Pentium™ 75*....		\$1395	\$1699
Pentium™ 90*....		\$1535	\$1872
Pentium™ 100*...		\$1720	\$2098
Pentium™ 120.....		\$1890	\$2305
Pentium™ 133.....		\$2050	\$2501

Keyboard #3 Slots VESA Local Bus  
Motherboard #14 SUPER VESA (1024 X 768)  
(0.28" DOT PITCH) Colour Monitor #VLB  
IMB VESA Cards are supplied in 486 machines  
AT NO EXTRA COST (Up to 1280 x 1024)  
Pentium systems now come with PCI Cards and  
should be bought with SMB of RAM

**FREE 3 HOUR  
TRAINING COURSE  
(MELB. ONLY) FOR  
ALL COMPUTER  
SYSTEMS INCLUDING  
MULTIMEDIA**



\*External 256K Cache 4 YEAR PARTS & LABOUR WARRANTY

## MULTIMEDIA SPEAKERS

Amplified Stereo Speakers for your multimedia systems • Magnetically shielded with Plug n Play feature.

### 120 watt PM.P.O.

• 4" woofer & 2" tweeter speakers • 220 H x 140 W x 180 D mm • Suit PC/Macintosh • C10181 \$99.95

### 50 watt PM.P.O.

• 198 H x 75 W x 95 D mm • Oval speakers • C10110 \$49.95 (Both speakers come with 6' length cord)

## NEW MOTHERBOARDS

OPTI895 GREEN PC Mainboard ..... \$189  
DX2-66 CPU installed ..... \$219  
DX2-80 CPU installed ..... \$229  
DX4-100 CPU installed ..... \$289

With 4 x 72 pin SIMM sockets 256K REAL CACHE

### 80486 GREEN Mainboard

DX2-66 CPU installed ..... \$179  
DX2-80 CPU installed ..... \$189  
DX4-100 CPU installed ..... \$229

With 2 x 72 pin & 4 x 30 pin SIMM sockets


## EPSON PRINTERS-NEW LOWER PRICES!

LX300 284 Cps Draft, 9 pin dot matrix	\$249
With colour option	\$349
LQ300 216 Cps Draft, 24 pin dot matrix	\$429
With colour option	\$529
Stylus Pro 720dpi full colour A4 NEW!	\$1399
Stylus Pro XL 720dpi full colour A3 NEW!	\$2899
Stylus 820 720x360dpi b/w A4 NEW!	\$419
Stylus Colour IIs 720x360dpi full colour A4 NEW!	\$549
Stylus Colour II 720x720dpi full colour A4 NEW!	\$719
EPL 9000 600dpi, 8ppm, laser, A3NEW!	\$3499

Stylus 820 Stylus Colour IIs Stylus Colour II
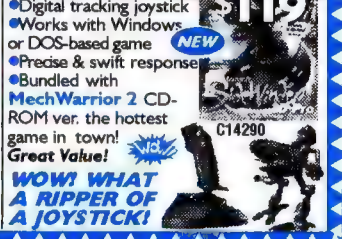
## MICROSOFT SIDEWINDER 3D PRO

• Digital tracking joystick • Works with Windows or DOS-based game • Precise & swift response • Bundled with MechWarrior 2 CD-ROM ver. the hottest game in town! Great Value! \$119



## RIE ROD IRVING ELECTRONICS

FOR THE SERIOUS COMPUTER USERS A.C.N. 005 428 437

ESTABLISHED SINCE 1977. 100% AUSTRALIAN OWNED. ALWAYS AHEAD WITH THE LATEST TECHNOLOGY & PRODUCTS.

HEAD OFFICE: 56 Renner Rd Clayton, Victoria, 3168 Ph: (03) 9543 7877  
MELB: 48 A'Beckett St. City Ph: (03) 9663 6151, Fax: (03) 9639 1641  
VERMONT: 190 Rooks Rd. Ph: (03) 9874 8888, Fax: (03) 9874 2288  
OAKLEIGH: 240C Huntingdale Rd. Ph: (03) 9562 8939, Fax: (03) 9562 8940  
NORTHCOLE: 423 High St. Ph: (03) 9489 8866, Fax: (03) 9489 8131  
BOX HILL: 1031 Maroondah Hwy. Ph: (03) 9899 6033, Fax: (03) 9899 0156  
ADELAIDE: 241-243 Wright St. Ph: (08) 211 7200, Fax: (08) 211 7273  
SYDNEY: 74 Panamatta Rd, Stanmore. Ph: (02) 519 3888, Fax: (02) 516 5024

BLUESTAR COMPUTERS: 271 Maroondah Hwy, Ringwood Vic (03) 9570 1800  
Fax: (03) 9879 3027 TRADING HOURS: Monday 9am - 5.30pm, Sat 9am - 1pm

City store open till 8pm on Fridays. Box Hill store open till 3pm on Saturdays.

Tax Exempt sales: RITRONICS WHOLESALE Ph: (03) 9643 2166 Fax: (03) 9643 2646

RIE BULLETIN BOARD Ph: (03) 9562 7877 For Specials, Info & Shareware E-MAIL: rie @ ozemail.com.au

MAIL ORDER: Ph: (03) 9543 7877 Fax: (03) 9543 8295 Mail Order Hotline 1-800 33 5757

Pentium™, OverDrive™ & Intel486™ are registered trademarks of the Intel Corporation SOGGI96



**FREE PACK & POST** FOR ALL ORDERS OVER \$25.00 & UNDER 3 KG. OFFER EXPIRES 31ST JANUARY 1996. **FREE PACK & POST**



**ROD IRVING ELECTRONICS PTY. LTD.**  
YOUR FIRST CHOICE IN QUALITY ELECTRONICS A.C.M. 005 428 437

ESTABLISHED SINCE 1977

**ROD'S HOTLINE**  
1-800-33-5757  
MAIL ORDER LOCAL CALLS: (03) 9543 7877

**ORDER YOUR COPY OF RIE'S 1995-96 ANNUAL CATALOGUE NOW! PACKED WITH NEW PRODUCTS!**

Or use our Mail Order Form to order products & we'll send you one FREE!

**SEND TO: FREE POST**

ROD IRVING ELECTRONICS P/L REPLY PAID 8888, BAG

CLAYTON SOUTH, 3169.

**196 PAGES!  
ONLY \$1.00**

MAIL ORDER  
CASH/CC  
VISA/MC

### FLASHING LED

CHEAP PROTECTION FOR YOUR CAR. EASY TO INSTALL AND WIRE UP.  
Flashing 12VDC LED alarm indicator. Small 5mm  
LED size in bezel housing.  
• Hole size: 7mm  
• Max panel thickness: 4mm

**\$15087  
\$4.95**



### ADAPTOR-SCSI TERMINATOR

50 pin IDC single sided internal SCSI terminators • Passive

**X15702  
\$24.95**



### ADAPTOR-SCSI TERMINATOR

50 pin IDC double sided internal SCSI terminators • Passive

**X15104  
\$39.95**



### SCSI ADAPTOR

Honda 30 pin plug to DB25 female • "T" shape

**X15706  
\$69.95**



**RIE-ALWAYS AHEAD  
WITH NEW PRODUCTS**

## INDOOR/OUTDOOR SPEAKERS

**3-WAY ACCOUSTIC SYSTEM WATER RESISTANT**

**25 WATTS RMS  
POWER HANDLING**

3 way speaker system in a water resistant ABS plastic cabinet. Ideal for patios, pergolas and boats or other potentially wet areas. Completely sealed enclosure houses a "4" woofer, midrange and tweeter drivers. Supplied complete with mounting brackets. The speakers are internally set up to be wired as either 4 or 8Ω.

- Speakers: 4" woofer treated paper cone, 2" cone midrange, 1/2" mylar dome tweeter
- Power: 25WRMS
- Impedance: 4 or 8Ω.
- Freq Resp: 100Hz to 16KHz
- Sensitivity: 92dB @ 1mW
- 1B2 (H) x 113 (W) x 110mm (D)
- Weight: 1.2kg each
- With mounting brackets

**C10189  
\$89.95  
GREAT  
VALUE AT  
\$69.95**

## GAS SOLDERING KIT

A multi-purpose unit that is available in this model as a gas soldering iron tool with solder tips. Can also be used as a: • Blow Torch • Hot Knife • Polyform Cutter or a Flat Flame depending on model purchased



**T12661  
\$24.95  
MORE VALUE-FOR-MONEY PRODUCT!**

## SECURITY KIT

Protect your investments in computers and other office equipment with this kit. Easy to install and comes with a heavy duty lock with 2 sets of keys.

- Contents:**
- 7ft length coated steel cable
  - 3 permanent adhesive-backed mounting plates
  - 1 padlock and 3 sets of keys

**IDEAL FOR HOME, OFFICE OR FACTORY SECURITY**



**BACK IN STOCK!  
A15206  
\$19.95**

ERRORS & OMISSION EXCEPTED.  
PRICES CHANGE WITHOUT NOTICE

## 50 WATT AMPLIFIED COMPUTER SPEAKER

Magnetically shielded speakers for monitor, drive an disc protection. Unique styling with space-saving compact size.

OVAL SPEAKER 50 x 90mm

- Power Output: 50 watt PM.P.O.
- Frequency resp: 20 - 20K Hz
- Speaker Impedance: 4 ohm
- Cord length: 6' to source
- Power: on/off
- Volume control
- Dimension: 198 (H) x 75 (W) x 95 (D) mm

**C10110  
\$59.95  
NOW  
\$49.95**



### MICRO SWITCH



- Single pole double throw
- Solder terminal • Standard size • Level action • Rated at 5A • 28 x 15mm

**NOW \$2.50 (S13248) \$2.95**


### MICRO SWITCH



- Single pole double throw • Solder terminal • Standard size • Rated at 5A • 28 x 15mm

**NOW \$2.50 (S13250) \$2.95**

### MICRO SWITCH

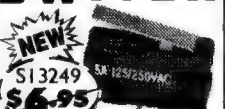

- Single pole double throw • Solder terminal • Miniature size • Rated at 5A • 20 x 10mm

**NOW \$2.50 (S13249) \$2.95**

### MICRO SWITCH



- Single pole double throw • Solder terminal • Miniature size • Rated at 5amp • 20 x 10mm

**NOW \$2.50 (S13247) \$2.95**

## SECURITY TORX DRIVER SET

Tool set with ratched handle and multiple bits. Supplied with security torx drivers and standard sized attachments. Total of 29 pcs.

- Ratchet handle
- Bit holder
- Socket adaptor
- 8 star bits T8/T9/T10/T15/T20/T30/T40
- 4 slotted bits 4/5/6 & 7mm
- 2 hex bits H3/H4
- 7 hexagonal sockets 4/5/6/7/8/9 & 10mm

**T12177  
\$29.95**

Contains 29 pieces & the handle to get torx bits



Illustration of bits is only indicative of comparative sizes and is not true to actual size.

### S1 2001

Miniature Rocker- on/off single pole single throw 250VAC- 10amp.

**1-9 10+  
\$1.95 \$1.50**



### S1 2002

Miniature Rocker- on/off double pole single throw 250VAC- 10amp.

**1-9 10+  
\$2.95 \$1.95**



### S1 2007

Miniature Rocker- with LED on/off single pole single throw 250VAC- 6 amp.

**1-9 10+  
\$3.95 \$2.95**



### S1 2003

Miniature Rocker- on/off single pole double throw 250VAC- 10amp.

**1-9 10+  
\$2.95 \$1.95**



### S1 2005

Miniature Rocker- on/off/on single pole double throw 250VAC 6amp.


**1-9 10+  
\$3.50 \$2.50**



### S1 3242

Miniature Rocker- with neon light on/off double pole single throw 250VAC- 10 amp.

**1-9 10+  
\$3.45 \$2.95**

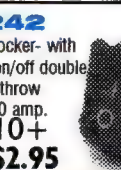


MINIATURE SWITCHES



**BACK TO SCHOOL ITEMS!!  
GREAT FOR EXPERIMENTATION  
& EDUCATION PURPOSES**

## BUDGET MULTIMETER

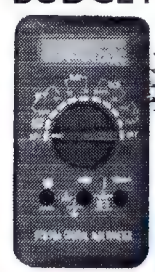

**Q91566** **EVERY HIGH SCHOOL STUDENT SHOULD HAVE ONE OF THESE**

**ONLY \$24.95**

**Keep one handy in your car! You never know when you need to test equipment while on the road!**

**ROD IRVING ELECTRONICS**  
**No.1 FOR VALUE-FOR-MONEY PRODUCTS**

Mid size digital multimeter with most standard ranges. Convenient for onsite jobs. 3.5 digital display. • 5 functions • 9 measuring ranges • Supplied with leads and instruction manual. 1 x GP 1604 (9Volt) battery included.

**SPECIFICATIONS:**

DC Voltage: 0-20, 200  
AC Voltage: 0-500  
Resistance:  $\times 2K\Omega$ ,  $\times 2000K\Omega$   
DC amps: 200mA, 10A  
Max DC volts: 200V  
Max AC volts: 500V  
Battery tester: 1.5 and 9V

# ANALOGUE MULTIMETER



Q91562

**19.95**

**NOW**  
**\$16.95**

Designed to measure AC and DC voltage, DC current, and resistance with accuracy and ease. can also be used as a battery tester. One AA cell (1.5V) provides power for resistance measurement. 65cm insulated test leads with plugs included.

**1562**

**SPECIFICATIONS**

DC Voltage: 0-2.5/10/50/250/500v

Impedance:  $\times 10\Omega$ ,  $\times 1k\Omega$

AC Voltage: 10/50/250/500v

DC Current: 500 $\mu$ A-10mA-250mA

Resistance: 2k ohms, 200k ohms

Battery Test: 1.5V 9V

Sensitivity: AC/DC voltage, 2,000 ohms/volt

Power: 1 x 1.5v AA cell

Size: 10 x 6.4 x 3.5cm (HWD)

## DIGITAL MULTIMETER Q13080



The ideal meter for technicians with a full 3½ digit LCD readout. Requires a 9V battery either alkaline or carbon. Expected life of carbon battery is 100 hours and 200 for the alkaline.

**\$59.95**

**SPECIFICATIONS**

DC Voltage: 200mV-2-20-200-1000 volts

AC Voltage: 200-2-20-750 volts

DC Current: 200 $\mu$ A-2mA-20mA-200mA-2A-20A

AC Current: 200 $\mu$ A-2mA-20mA-200mA-2A-20A

Resistance: 200 $\Omega$ -2k $\Omega$ -20k $\Omega$ -200k $\Omega$ -2M $\Omega$ -20M $\Omega$

Diode Test: Measures forward resistance in k $\Omega$  with a test current of 1.5mA max

Power: Requires 1 x 9V battery

## DIGITAL MULTIMETER



**Ideal for technicians with full 3½ digit LCD readout & continuity buzzer. 9V alkaline battery supplied. Expected life of battery is 200 hours.**

**SPECIFICATIONS:**  
 DC Voltage: 200mV/2/20/200/1000V  
 Basic accuracy: +/-0.5%  
 Input Impedance: 1M  
 Maximum output: 1000V DC  
 AC Voltage: 200/750V  
 DC current: 200A/2000A/20mA/200mA/  
 10A  
 Resistance: 200Ω/2000Ω/20kΩ/  
 200kΩ/2M  
 LCD Display: 15 x 46mm  
 Outer case size: 125 x 77 x 28mm

---

**Temperature measuring features:**  
 Range: -20° to 1370° C  
 Resolution: 1° C  
 Accuracy: ±3° ±2D (up to 150° C)  
 ±3% of rdg (over 150° C)

## DIGITAL MULTIMETER



The ideal meter for technicians with a full 3½ digit LCD readout. Requires a 9V battery either alkaline or carbon. Expected life of carbon battery is 100 hours and 200 for the alkaline.

### SPECIFICATIONS

DC Voltage: 200mV-2-20-200-1000 volts

AC Voltage: 200-750 volts

DC Current: 200 $\mu$ A-2000 $\mu$ A-20mA-200mA-10A

Resistance: 200 $\Omega$ -2000 $\Omega$ -20k $\Omega$ -200k $\Omega$ -2000k $\Omega$

Diode Test: Measures forward resistance in k $\Omega$  with a test current of 1.5mA max

Power: Requires 1x 9V battery

## ANALOGUE MULTIMETER



A pocket sized multimeter that includes 5 functions and 16 measuring ranges. Single knob function control makes it very simple to use. Comes complete with test leads and instructions and is ideal for the handyman - can be kept in the glove box of the car.

**SPECIFICATIONS**  
 DC Voltage: 0-2.5-10-50-250-500 volts  
 AC Voltage: 0-10-50-250-500 volts  
 DC Current: 0-500 $\mu$ A-10mA-250mA  
 Resistance: Rx10, Rx1 k (centre 3.6)  
 Battery Test: 1.5V 9V  
 Sensitivity: 2k ohms/volt DC/AC  
 Power: Requires 1 x AA battery

### JACOB'S LADDER DISPLAY



Without COIL K10695 **\$29.95**  
With COIL K10696 **\$59.95**

## 18 WATT SOLAR PANEL

12V VAC 16V (max) 18V Isc  
800mA (max) 1000mA



## SOLAR MOTOR KIT

This is a great starter kit consisting of a 0.9V 400mA solar cell and a small motor with a 48" wire. Great for beginner or just the curious!

**Z19040**  
**\$9.95**



## SOLAR EDUCATIONAL KIT



Now you can experiment with solar energy....the energy source of the future. Our solar educational kit is designed to let you build your own solar models.

This kit comes complete with:

- Solar cell module • Solar energy booklet explaining the whys and hows of solar energy.
- Small DC Motor • Screws and nuts • Wire with motor clips • Coloured spinner discs • Paper aeroplane and bird models • Plastic turnables with 4 sizes, 5/8", 1", 1 1/2", and 2" • Plastic fan-spinner

*The solar cell modules, when placed in direct sunlight or close to incandescent light bulbs, generate power similar to batteries. Discover for yourself how to harness the energy of flight and employ it in countless practical applications. Solar energy uses are limited only by your imagination.*

## PC-DRIVEN ELECTROCARDIOGRAM




This simple project will let you take your own electrocardiograph, and display it on a PC. With the software supplied, you can read, display, save to disk and print the electrical waveform generated by your own heart (or anyone else's). Powered by a 9V battery a safe, low cost way to

## A BUDGET PRICED "SHOESTRING" STEREO AMP

Power rating of around 15 watts per channel and impressive noise and distortion performance, this low-cost amplifier is ideal for small Hi Fi systems, "home theatre" installations, and a host of other applications. Uses readily available parts, offers a basic range of features and is easy to put together. Ideal for schools, college or University project or built to work as a multimedia amplifier.

**EA JULY '95**

**ERRORS & OMISSION EXCEPTED. PRICES CHANGE WITHOUT NOTICE**



**K10650**  
**\$99.95**



FREE PACK & POST FREE PACK & POST FREE PACK & POST FREE PACK & POST FREE PACK & POST

FREE PACK & POST FREE PACK & POST FREE PACK & POST FREE PACK & POST FREE PACK & POST

**ROD IRVING ELECTRONICS PTY. LTD.**  
YOUR FIRST CHOICE IN QUALITY ELECTRONICS A.C.N. 005 428 437

ESTABLISHED SINCE 1977  
ERRORS & OMISSIONS EXCEPTED. PRICES CHANGE WITHOUT NOTICE.  
WINDOWS IS A REGISTERED TRADEMARK OF MICROSOFT CORPORATION IN THE U.S. AND OTHER COUNTRIES

# SYQUEST PRODUCT RANGE ROUND-UP -

FOR EVEN MORE AFFORDABLE BACKUP AND FILES EXCHANGE BETWEEN COMPUTERS



**FREE PACK & POST FOR ORDERS WORTH \$25 OR MORE & UNDER 3KG - OFFER VALID ONLY UNTIL 31ST JANUARY 1996**

HERE'S A VERY ECONOMICAL WAY TO BACKUP FILES AND TRANSFER INFORMATION...

## INDUSTRY STANDARD 3.5" HIGH PERFORMANCE REMOVABLE CARTRIDGE HARD DISK DRIVE.

### FEATURES INCLUDE:

- ANSI ATA interface (IDE SCSI available as option) provides 14.5msec access time
- Offers primary and secondary storage in one drive.
- 64K intelligent read "Look Ahead" caching buffer.
- Data transfer rate at the host interface up to 4.0MB per second
- Data transfer rate from the head / media interface is up to 2.3 MB per second.
- Programmable power modes - sleep, stand-by idle and active
- 20,000 cartridge insertion cycles
- 100,000 start/stop cycles
- Ergonomic engineering for reliable and easy cartridge loading and unloading
- 100,000 hours MTBE with 100% duty cycle
- On-the Fly error correction
- 1-7 RLL modulation recording for maximum read window margins.
- Removable storage advantages - including unlimited capacity and off-line storage, data transportability, system sharing, data security and fast backup.

The 3.5" SQ3105 drive is designed for all laptop/desktop computers.

Our 3.5" drives provide universal interchangeability through the use of an embedded servo system and adaptive read channel, while including comprehensive self-diagnostic capabilities and programmable power-saving modes.



### AS USED BY

- Printers • Draughtsman • Architects • CAD Users
- Bureaus • Typesetting Bureaus • DTP-based design studio • Advertising Agencies • Computer-based Graphic Artist & others who has the need to exchange data quickly and easily.

Printing companies take note- these are the same removable media that you could be paying \$250.00 or more for. We will call at your place of business to advise for free. Call 543 2166. Ask for Kevin Glenton.

**WHILE STOCK LASTS!**



<b>105MB Cartridge C11880</b> (Compatible with the 270MB Removable Drive)		
<b>270MB Removable Cartridge C11888</b>	\$129.00	\$105.00
<b>270MB Removable Drive Mechanism IDE C11854</b>	\$599.00	\$531.00
(Read and writes 105MB cartridge format)	<b>SPECIAL PRICE</b>	\$519.00 \$425.00
<b>270MB Removable Drive Mechanism SCSI C11856</b>	\$599.00	\$531.00
	<b>SPECIAL PRICE</b>	\$519.00 \$475.00

## Stealth 64 DRAM

### The World's Fastest DRAM Graphics Accelerator

Diamond's Stealth 64 DRAM is the perfect choice for graphics performance. With 2MB of DRAM, the Stealth 64 DRAM displays 24 bit true colour up to 800 x 600 resolution and provides 65,536 colours at 1152 x 864 resolution.

**AMAZING WINDOWS PERFORMANCE** - With advanced 64-bit technology and affordable DRAM, the Stealth 64 DRAM, the Stealth 64 DRAM out-performs many VRAM accelerators in demanding applications such as, desktop publishing, graphic design and CAD.

**SUPER FAST DOS PERFORMANCE** - With extended VESA mode support in BIOS for high resolution and true colour modes, the Stealth 64 DRAM is perfect for the most demanding games and CAD applications.

### Product Specifications:

Controller: S3 Vision 864

Memory Configurations: • 1MB DRAM upgradable to 2MB  
• 2MB DRAM fixed

Horizontal Sync Signals: 31.5KHz - 81.5KHz


Vertical Refresh: 56Hz - 120Hz

Maximum Dot Rate: 135MHz Standard

Video Output Signal: Analog

Video Connector: DB-15

Feature Connector: VESA 26-pin header

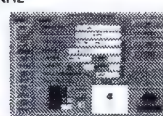

### RANGE AVAILABLE:

	MEG	CAT No.	PRICE
<b>DRAM</b>	1M	X18206	\$279
	2M	X18207	\$349
<b>VRAM</b>	2MV	X18208	\$529
	4MV	X18209	\$999

**EASE OF USE** - With Diamond's InControl Tools software, Windows is a breeze to use. Change resolutions at a keypress without restarting Windows. Increase the Windows desktop to over six times the standard size and move easily with real-time pan and zoom. Control monitor power consumption (DPMS) and image colour correction via a point and click interface.

## LATEST CPU PRICE

Intel CPU	AMD CPU
486DX2-66 OverDrive Chip ... \$189	486DX4-100 NEW! ... \$179
486DX4-100 OverDrive Chip ... \$249	486DX4-120 NEW! ... \$249
PENTIUM 60MHz ... \$199	
PENTIUM 75MHz ... \$319	<b>CYRIX CPU</b>
PENTIUM 90MHz ... \$449	486DX2-66 3.3V ... \$69
PENTIUM 100MHz ... \$499	486DX2-66 5V ... \$79
PENTIUM 120MHz ... \$599	486DX2-80 3.3V ... \$89
PENTIUM 133MHz ... \$899	486DX2-80 5V ... \$99
	486DX4-100 ... \$129

AVAILABLE ON ORDER THROUGH OUR STORES OR BY MAIL ORDER

## COMPUTER CARDS - HUGE RANGE!!

CAT NO.	DESCRIPTIONS	PRICE
X18075	1Meg 16bit VGA	\$159
X18196	Trident 9440 AGI VGA	\$169
X18004	IDE/SPG	\$39
X18005	High Speed I/O	\$59.95
X18013	IDE	\$29
X17072	ADAPTEC SCSI 16bit 1522A	\$189
X18161	*16bit ETHERNET NE2000 BNC	\$69
X18165	16bit ETHERNET RJ45 + BNC	\$79
X18169	16bit NE2000+	\$119
X18159	Ethernet 10 base T Connector	\$119
X18151	S.P.G.	\$25
X18190	Printer 2-Port Slot Lpt 1-2 Card	\$39
X18191	Printer Port Slot Lpt 1-2-3 Card	\$49
X18141	High Speed Serial Card 1-Port 16550	\$49.95
X18041	High Speed Serial Card 2-Port 16550AFN	\$69
X18143	High Speed Serial Card 4-Port 16550AFN	\$189
X18157	S.P.G with 16550 UART Chip	\$44.95
X18019	Games Card	\$19
C14260	SMART GAMES Cont	\$39.95
X18177	CD ROM Controller	\$45
	2.88 FDD Controller Card	\$125

Specifications subject to changes. \*X18161 without Boot Rom.

## VESA LOCAL BUS

X17078	VESA SCSI IDE FLOPPY MULTI I/O...	\$249
X18002	VESA MULTI I/O	\$39
X18099	VESA 1 Meg TRIDENT 9400	\$129
X18100	VESA CIRRUSS 5428	\$139
X18184	VESA PARADISE Bahamas 1Meg	\$349
X18186	VESA IDE Cache Cont	\$349
X17071	VESA SCSI 2, IDE, Floppy, Multi I/O	\$299
X18087	VESA WD Accelerator Video Card	\$209
X18167	VESA VGA S3 Accelerator	\$169
X18185	VESA ET-4000 TSENG LABS	\$199
X18149	VESA CLOUD9 VGA 2 MEG	\$449
X18047	VESA IDE ENHANCED MULTI I/O	\$119
X18182	VESA CACHED IDE MULTI I/O	\$280

## P.C.I.

X17900	PCI 1M VGA TRIDENT 9440	\$149
X18179	PCI IDE CONTROLLER	\$39
X18206	PCI VGA STEALTH 1MEG DRAM	\$279
X18207	PCI VGA STEALTH 2MEG DRAM	\$349
X18208	PCI VGA STEALTH 2MEG VRAM	\$529
X18209	PCI VGA STEALTH 4MEG VRAM	\$999
X18183	PCI VGA CIRRUSS LOGIC 5430	\$175
X18510	FULL - DUPLEX PCI ETHERNET	\$149
X18514	FULL - DUPLEX ISA ETHERNET	\$99


## AMIDiag \$159 NEW

From the makers of AMIBIOS®  
The first program with specific test for:

- PCI • PnP • EISA • Pentium™
- Packed with diagnostic features that test CPUs, video modes/ memory, motherboard functionality, COM ports, Sound Card, Speaker, Hard Disk, Floppy Disk Drive and Keyboard & Mouse. System information

features ISA/EISA I/O, INTR, DMA, RAM & ROM display, PCI & PnP I/O, INTR, RAM & ROM display. PCMCIA card details. Network configuration details. VGA and VESA VGA hardware, mode display. Network user list display. Power management setup display and much more! Requires AT 286, 386, 486, Pentium or higher processor.

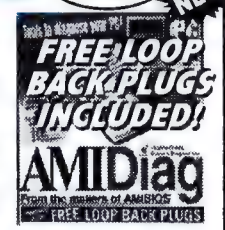FOR MORE INFO SEE FULL REVIEW IN THE NOVEMBER ELECTRONIC AUSTRALIA MAGAZINE ON PAGE 90.



PLEASE SEND ALL MAIL ORDERS TO:  
MAIL ORDER DEPARTMENT,  
ROD IRVING ELECTRONICS PTY. LTD.,  
LOCKED BAG 620, ROSEBANK MDC,  
CLAYTON SOUTH, VIC. 3169.


- ☐ MELBOURNE: 48 A'BECKETT ST. MELBOURNE 3000.  
• PH: (03) 9663 6151 • FAX: (03) 9639 1641  
• Mon-Thurs: 9.00-5.30pm • Fri: 9.00-8.00pm • Sat: 9.00-1.00pm
- ☐ VERMONT: 190 ROOKS RD. VERMONT 3133  
• PH: (03) 9874 8888 • FAX: (03) 9874 2288  
• Mon-Fri: 9.00-5.30pm • Sat: 9.00-1.00pm
- ☐ DAKLEIGH: 240C HUNTINGDALE RD. DAKLEIGH 3166  
• PH: (03) 9562 8939 • FAX: (03) 9562 8940  
• Mon-Fri: 9.00-5.30pm • Sat: 9.00-1.00pm
- ☐ NORTHCOE: 423 HIGH ST. NORTHCOE 3070.  
• PH: (03) 9489 8866 • FAX: (03) 9489 8131  
• Mon-Fri: 9.00-5.30pm • Sat: 9.00-1.00pm
- ☐ BOX HILL: 1031 MAROONDAH HWY. BOX HILL 3128.  
• PH: (03) 9899 6033 • FAX: (03) 9899 0156  
• Mon-Fri: 9.00-5.30pm • Sat: 9.00-3.00pm
- ☐ CLAYTON: 55 RENNIE RD. CLAYTON 3168.  
• PH: (03) 9543 7877 • FAX: (03) 9543 8266  
• Mon-Fri: 9.00-5.30pm • Sat: 9.00-12.00pm
- ☐ BLUESTAR COMPUTERS: 271 MAROONDAH HWY. RINGWOOD 3134.  
• PH: (03) 9870 1800 • FAX: (03) 9879 3027  
• Mon-Fri: 9.00-5.30pm • Sat: 9.00-1.00pm
- ☐ SYDNEY: 74 PARRAMATTA RD. STANMORE 2048.  
• PH: (02) 519 3888 • FAX: (02) 516 5024  
• Mon-Fri: 9.00-5.30pm • Sat: 9.00-1.00pm
- ☐ ADELAIDE: 241-243 WRIGHT ST. ADELAIDE 5000.  
• PH: (08) 211 7200 • FAX: (08) 211 7273 • Mon-Thurs: 9.00-5.30pm  
• Fri: 9.00-3.30pm • Sat: 9.00-5.00pm Sun: 10.00-4.00pm

FREE PACK & POST FOR ALL ORDERS OVER \$25.00 & UNDER 3 KG. OFFER EXPIRES 31ST JANUARY 1996. FREE PACK & POST

FREE PACK & POST FREE PACK & POST FREE PACK & POST FREE PACK & POST FREE PACK & POST



By MIKE ZENERE

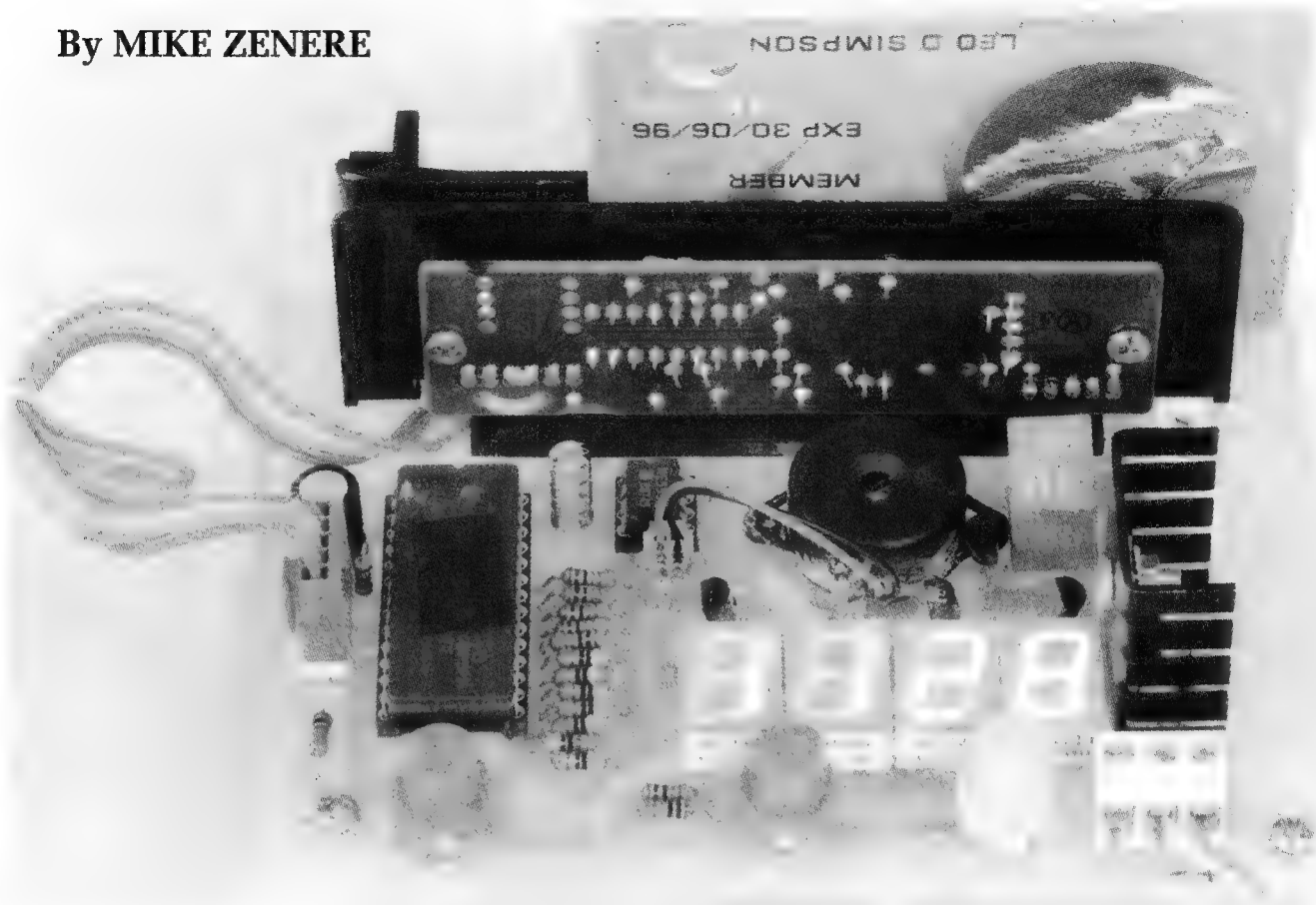

# Build a magnetic card reader & display

**Have you ever wanted to find out what's written on your credit card or other magnetic stripe cards? Now you can do it. This unit will enable you to read and display the contents of track two on any magnetic card and could be used as the basis for an electronic door lock.**

Magnetic cards have been around for many years and have found their way into many fields such as banking, security and vending machines. Most cards follow defined guidelines as to their construction and layout and are therefore very flexible to the designer.

Each card has three tracks but the most commonly used is track two.

Recalling data from the card has become relatively simple in the last few years with modern card readers. These generally have a single on-board chip to decipher the raw data from the

read head. This looks much like the record/play head in a cassette deck.

The on-board chip generally contains conditioning circuitry to pick up the signal, reject noise and provide a digital output. Most card readers interface via three wires which are Clock, Data and Card Valid.

Assuming that a microprocessor is hooked up to the card reader, a typical card read takes place as follows. When a card is swiped through the card reader, the Card Valid line goes low after eight or nine flux reversals, indicating that a valid card is present.

The microprocessor monitors the clock line and waits until the Clock



# Magnetic Card Standards

Most magnetic cards adhere to defined standards that describe the physical as well as electrical layout. The standards outline card size, magnetic stripe and track positioning, and format information.

The information is recorded onto the card using a technique known as Two Frequency Coherent Phase Recording or F/2F. This allows for serial recording of self-clocking data on each track. The data consists of data and clocking bits together. When a flux transition occurs between clock cycles, a "one" is obtained and when there is an absence of flux between cycles a "zero" is obtained.

Standard magnetic cards have three data tracks and each has its own subtle differences. Track 1 has a bit density of 210 bits per inch, giving it the ability to hold a total of 79 characters over the entire length of the card. Each character on this track is made up of six data bits and one parity bit, providing 64 different alphanumeric combinations to choose from. The card and track layout is shown in Fig. 1.

The remaining tracks, two and three, provide only numeric data and have a bit recording density of 75 bpi and 210 bpi respectively. The character set for these two tracks is

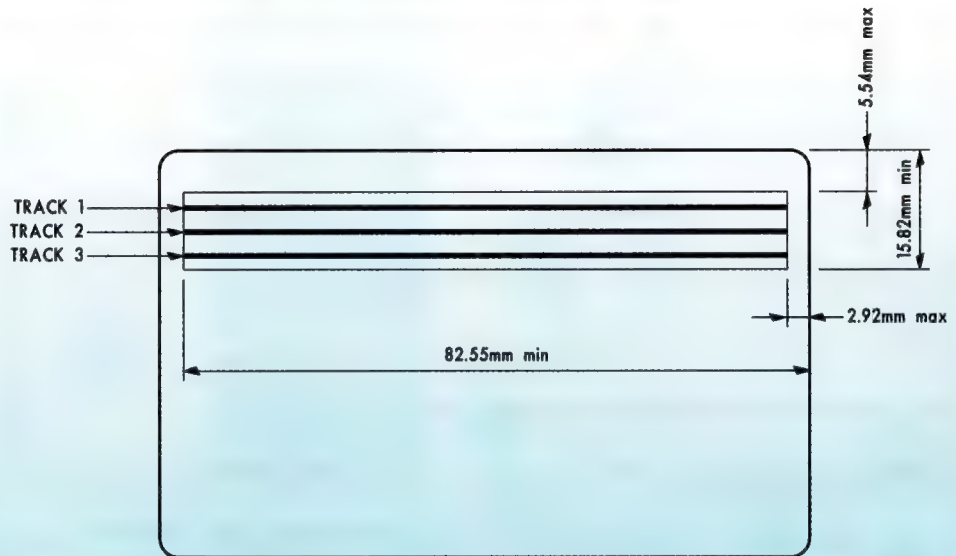


Fig.1: the track layout on a magnetic card. Track 1 can record alphanumeric data, while tracks 2 and 3 provide only numeric data.

encoded using 4-bit BCD with odd parity.

All tracks are recorded with the least significant bit first and the parity bit last. The higher density track three holds up to 107 numerics while track two holds only 40. The necessity for start and end sentinels and other separating characters reduces the above storage capabilities to a certain extent.

Reading or writing of data to the card generally follows the same path for all three tracks. First, leading zeros are encoded to indicate the presence of data and to provide synchronisation. Next, the start sentinel is encoded to indicate the start

of the actual data to be read, followed by the data, the end sentinel, LRC and finally, trailing zeros to the end of the card. The term LRC stands for "longitudinal redundancy check" and is used for horizontal error detection.

By far the most commonly used track is track two. Although holding less information than the others, this track has all the data required to do a banking transaction. If there is a need for the customer's name to be present, then track one is used as it is the only one that holds alphabetical characters. The third track is special in that data may be written or read during a transaction.

line goes low, indicating that data is present on the data line. The data bit is collected and temporarily stored until a succession of bits is gathered to make a 5-bit word, with four data bits and one parity bit. When the 5-bit word is obtained and stored, the cycle repeats itself until all the 5-bit characters have been read into memory. The processor can now go back over the data and analyse it for parity.

## Date rate & swipe direction

The data rate even for the high density tracks is quite low, allowing al-

most any microprocessor to sample and collect the data. Let's assume that the card is passed through the reader at around one metre per second.

This translates to around 9983 bps or 1426 7-bit characters per second, meaning that a new data bit is presented about every 100µs. Most card readers are capable of reading two of the three tracks in one swipe. Even allowing for this extra load, most microprocessors running at 1MHz or more will handle this with ease.

Although data is written onto the card in a particular format, there be-

ing a start and end sentinel, this does not limit the programmer to write software to read a card when swiped forwards or backwards. In a "backward read", the card data is simply read as usual and stored in memory but this time the last character is first and the first character is last. The program simply detects this by looking for the start and end sentinels and then corrects itself.

## Card reader

The card reader and display unit to be presented here is self-contained on



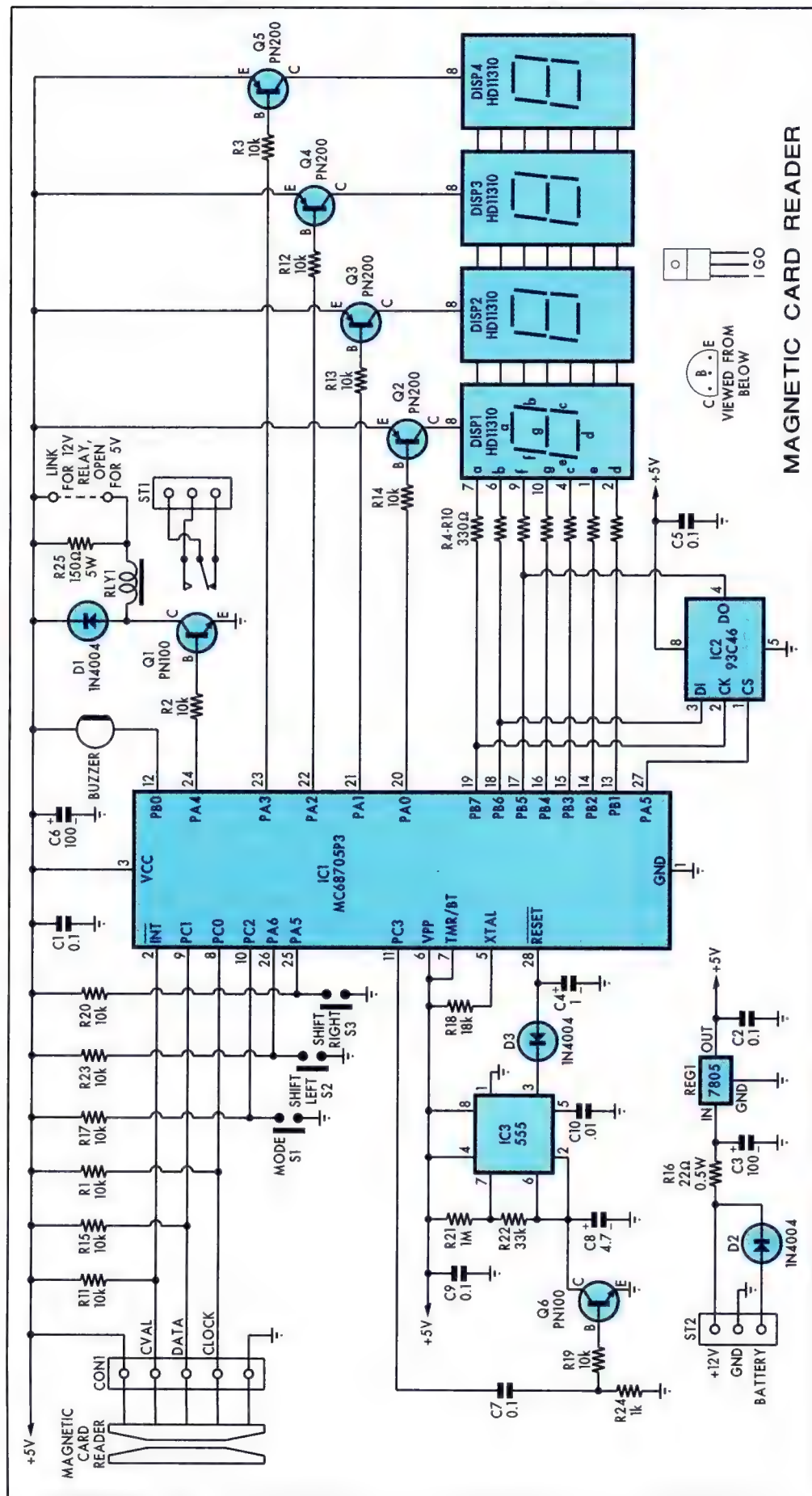


Fig.2: the circuit is based on a magnetic card reader module with its own on-board decoding. The data from this module is fed via three lines to the microprocessor (IC1) and this in turn drives a multiplexed 4-digit display. The track 2 contents of four cards can be stored in the EEPROM (IC2) and this data can be used as the basis of an electronic door lock. IC3 and its associated parts form a watchdog timer circuit and this automatically resets the microprocessor if signal activity from pin 11 ceases, indicating that the processor has "crashed".



a PC board measuring 128 x 101mm. As well as the card reader module with its integral PC board, there is a 4-digit display, a 28-pin 68705P3 microprocessor (IC1), a piezo buzzer and three pushbuttons. The circuit is shown in Fig.2.

The card reader and its integral PC board has all the circuitry necessary to decode and convert the raw data coming from the card being read. The data is transformed into logic levels and is then sent out via three serial lines to the processor. The card reader is connected to the logic board via a 5-way cable, with three of the lines for data and the other two for power.

The recording function of the circuit is performed by a small serial EEPROM, IC2. Once the unit is placed in the record mode and a card is swiped through, the data will be saved in the EEPROM.

Because timing is not critical in this project, a crystal for the microprocessor is not necessary. Instead, by placing an 18k $\Omega$  resistor from pin 5 to the +5V rail, an inbuilt oscillator is enabled, causing the processor to run at near full speed.

### Beeper & relay driver

A DC self-oscillating beeper is connected to port B, pin 12, on the processor. Port B can sink up to 10mA which is sufficient for this application and is pulled low to turn on the beeper.

The relay is driven by transistor Q1 which is controlled by the line from pin 24. This line is normally low and the relay is off. When a valid card is swiped through the reader, the processor port pin 24 goes high for a period of time and turns on Q1 which operates the relay.

The display consists of four 7-segment common anode displays multiplexed together. The cathodes are driven directly by port lines from the processor, while each display anode is driven by its respective PNP driver transistor (Q2-Q5).

The processor receives an interrupt every 5ms from an internal timer. Each time an interrupt is received, the processor switches off the current display digit that it is driving and turns on the next. In this manner, each digit is only on for 5ms before the next digit is updated. This gives each digit a total on-time of around 250ms per second; ie, a duty cycle of 25%.

The SHIFT LEFT and SHIFT RIGHT buttons are used to move the display laterally to enable the user to view the entire number.

### Construction

Begin assembly of the PC board by mounting the four standoffs, one at each corner. This done, install the diodes, resistors, links and capacitors. Note the polarity of the electrolytic capacitors and the diodes. Install the 7805 regulator and fit it with a small heatsink.

Next, install the transistors, the two small ICs and the socket for IC1 but do not install the processor until after the unit has been powered up and a voltage check performed. When installing the four 7-segment displays, their decimal points should be close to the edge of the PC board.

The remainder of the components can now be mounted, noting the orientation of the pushbutton switches. The card reader module is attached to the PC board with screws fitted from the underside. The back of the read head should face the outside edge of the board.

When all the assembly work is complete, apply 12V DC to the board and check that +5V is present at pins 3 & 6 of the socket for IC1, at pin 8 of IC2, pins 4 & 8 of IC3 and at the emitters of Q2-Q5.

If this checks out, remove the power, plug in the processor and connect the card reader module. Reapply power – the buzzer should beep four times and the display should read "OPER". The unit is now ready for a test drive.

Before you start, here are a few tips. The mode button is used to cycle through the various available modes. Each time you press this button, the next option appears on the display. The modes are OPER (operate), rEC (record), dEL (delete), pLAY and rEAd. When in the operate mode, the display blanks out after about 30 seconds to conserve power. If any button is pressed after this time the display will light and programming may continue.

### Initial set up

If this is the first power-up you will need to reset the memory of the EEPROM and this is done by holding down SHIFT LEFT and SHIFT RIGHT and applying power. The EEPROM will be cleared and the relay on-time will be set to three seconds.

## PARTS LIST

- 1 PC board, 128 x 101mm
- 1 magnetic card reader module
- 1 piezo buzzer
- 1 12V miniature SPDT relay
- 3 momentary contact pushbutton switches
- 1 5-way connector
- 1 2-way connector
- 2 3-way PC-mount insulated terminal blocks
- 4 PC standoffs

### Semiconductors

- 1 MC68705P3 programmed microprocessor (IC1)
- 1 93C46 EEPROM (IC2)
- 1 555 timer (IC3)
- 1 7805 5V 3-terminal regulator (REG1)
- 4 HD11310 7-segment red LED displays (DISP1-4)
- 3 1N4004 silicon diodes (D1-D3)
- 2 PN100 NPN transistors (Q1, Q6)
- 4 PN200 PNP transistors (Q2-Q5)

### Capacitors

- 2 100 $\mu$ F 16VW electrolytic
- 1 1 $\mu$ F 16VW electrolytic
- 4 0.1 $\mu$ F monolithic

### Resistors (0.25W, 5%)

- 1 1M $\Omega$       1 1k $\Omega$
- 1 33k $\Omega$       7 330 $\Omega$
- 1 18k $\Omega$       1 22 $\Omega$  0.5W
- 11 10k $\Omega$

### Miscellaneous

Screws, nuts, shakeproof washers, solder.

### Where to buy the parts

A complete kit of parts for the magnetic card reader is available from the author. This includes all electronic components except for the 12VDC power supply and a case. The price is \$75.00 plus \$7.50 for postage and packing.

Completely assembled and tested units are also available at an extra cost of \$20.00. The documented source code is a further \$8.00 for the print out.

Please make postal money orders payable to Mike Zenere, 83 Headingley Road, Mt. Waverley, Vic 3149. Phone (03) 9803 3535.

Note: copyright© of the PC board is retained by the author.







# JANUARY DEALS FROM JAYCAR

## 1 Amp AA NICKADS!!!

Yes, that's correct. They do exist, and we've got them at very low prices.

AA 1.2V 1A/HR Cat. SB-2440

AA 1.2V 1A/HR with solder tags Cat. SB-2441

NICKEL METAL HYDRIDES ARE ALSO AVAILABLE

AA 1.2V 1.1A/HR Cat. SB-2455

AA 1.2V 1.1A/HR with solder tags Cat. SB-2457



**NEW**

\$4.75ea

\$5.00ea

\$5.95ea

\$6.25ea

## JAYCAR ELECTRONICS IS NOW A

## QUALITY ENDORSED COMPANY!

Our Purchasing Dept, Warehouse, Wholesale Sales and Kit Department are now Quality Assured to AS9002.

Quality System

Quality Endorsed Company AS9002

## CAR AMPLIFIER 18WRMS X 2

OUTPUT POWER 18WRMS / CHANNEL


If your car stereo does not have enough grunt, and you don't want to spend a lot of money then this could be the unit. It

has high input gold RCA sockets as well as low inputs, an input gain control and power LED indicator. Outputs to speakers are by push terminals. This amplifier gives a genuine 18 watts

RMS per channel into a 4 ohm load. **Specifications:** •Supply voltage: 13.8VDC (12V) •Input sensitivity: 65mV to 2.5V adjustable •Output power: 18WRMS / channel 4 ohm •Distortion: 10% max volume •Frequency response: 25Hz to 20kHz •Dimensions: 85 x 103 x 41mm

Cat. AA-0415

**\$45.00**

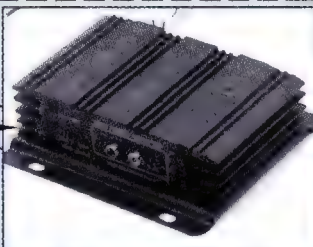

## CAR AMPLIFIER 30WRMS X 2

OUTPUT POWER 30WRMS / CHANNEL


If 18W RMS/channel is not enough, then look at this unit.

Features include high input gold RCA sockets, as well as low inputs, an input gain control and power LED indicator.

Outputs to speakers are by push terminals. Output power is a genuine 30 watts RMS per channel into 4 ohms. **Specifications:** •Supply voltage: 13.8VDC (12V) •Input sensitivity: 65mV to 2.5V adjustable •Output power: 30WRMS / channel 4 ohm •Distortion: 10% max volume •Frequency response: 25Hz to 20kHz •Channel separation: 50dB •Signal to noise ratio: 60dB •Idle current: 13mA •Max Current draw: 13A •Weight: 1kg •Dimensions: 150 x 103 x 41mm

Cat. AA-0420

**\$75.00**

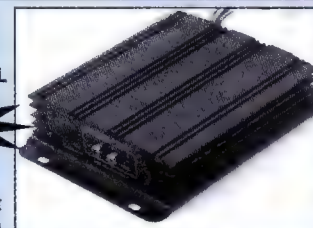

## Jaycar 2.8 Amp 24 to 12 Volt Reducer

New smaller model for 1996. Ideal for cellular phones. This reducer will drop 24 volts to 12 volts with continuous loads of 2.8 amps. It is fully protected (see specs) and is ideal for truckies running a 12 volt cellular phone on the 24 volt truck power. And the price is lower than last year.

Cat. MP-3058 **was \$49.95 NOW \$39.95**



## Jaycar 7.5 Amp 24 to 12 Volt Reducer

New model for 1996. This Switch Mode reducer will drop 24 volts to 12 volts with continuous loads of 7.5 amps. This unit offers very high efficiency - up to 90%, its much smaller physically than the one it replaces, and it has internal current limiting.


Cat. MP-3060 **was \$92.50 NOW \$69.95**



## CHEAP DISKS!!!

**NEW** Save even more on 3.5" HD IBM formatted disks. 100% error free and includes user labels. CAT XC-4740 **Don't pay \$19.95**

**Pkt 25 Only \$13.95**

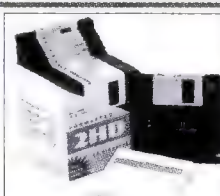

## PROGRAMMABLE REMOTE CONTROL

This remote control will "learn" the functions of other remotes. If your TV / stereo coffee table has a row of remotes, you can actually retire them all and just use this one. Also ideal if one of your remotes is "on the way out". Before it dies, buy one of these and it will learn the functions. Brand name replacement remote controls cost a fortune.

**Specs:** •Memory capacity: 150 commands


•Memory hold without batteries: About 8 minutes

•Suitable equipment: Most brands of infra red remote controllers for audio/video devices

•Effective range: 8 metres •Power source: 4 x AAA batteries (not supplied) •187(L) x 64(W) x 15(D)mm

Cat. AR-1710

**\$43.95**

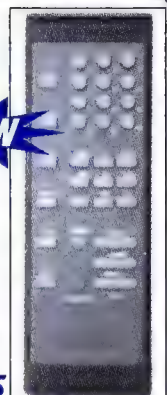

## LASER POINTER

If you need to point out objects or details that are

out of reach, then you need a laser pointer. Up until

now you have had to pay around \$140, but not at

Jaycar. Laser Pointer is small and easy to hold, and has

a push on switch for operation. Requires 2 x AAA batteries.

Supplied in a plastic case for storage. **Specifications:** •wavelength -

670nm at 50 metres, 650nm at 150 metres, 630nm at 300 metres •size -

140 x 18 x 15mm. Class 2 laser product. Do not store into beam.

Cat. ST-3100

**\$89.50**



## Planetary Gear Box Set

Automatic transmissions in cars use planetary gear clusters. They are simple, compact and strong.

This gear set made in Japan by TAMIYA is

sensational. Why? Firstly you can configure the

gearbox to 8 different reduction rates 4:1, 5:1, 16:1, 20:1,

25:1, 80:1, 100:1 and 400:1. A genuine MABUCHI RC-260

3VDC motor is included! (at 400:1 the gearbox gives a

massive 15kg/cm of torque!) Typically Japanese, it is

thorough. Absolutely everything is supplied including tubes of lubricating grease, mounting feet, two drive

attachment cranks and a beautiful brass double female coupling to connect to other (drive) shafts. You will

love this product! •Measures 100mm long x 28mm (dia of body), height including mounting feet 38mm.

Steel output shaft 4mm dia •Can be ganged for up to (max) 160,000:1 •Moulded out of sturdy ABS plastic

Cat. YG-2720

**NEW**



**\$39.95**

## JAYCAR NOW

## OPEN IN

## PERTH

## 4.5 DIGIT DMM SELLOUT



**FEATURES:** •Frequency

Counter •Transistor Test

•Capacitance •Data Hold

•Auto Power Off •Large Display •Overload

Protection •Diode Test •20A •19999

Count. See cat p 27 for details. Cat. QM-1330

**1994 Price \$129.50**

**1995 Price \$99.95**

**NOW ONLY \$79.95**






## Save on Breadboard for January

See catalogue page 130 for full details.

Cat	Description	Normally	Jan	Save
PB-8810	Distribution strip 100 hole	\$4.25	\$2.95	\$1.30
PB-8812	Terminal strip 630 hole	\$13.50	\$9.95	\$3.55
PB-8814	830 tie points	\$18.95	\$13.95	\$5.00
PB-8816	1660 tie points on plate	\$44.95	\$34.95	\$10.00
PB-8818	2420 tie points on plate	\$56.95	\$46.95	\$10.00
PB-8820	3220 tie points on plate	\$75.00	\$62.00	\$13.00

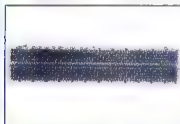

## SAVE ON CROS

### 25MHZ

**CRO** \$749

**2 PROBES** \$79

**\$828**

**Jan Pay \$699**

### 50MHZ

**CRO** \$1195


**2 PROBES** \$79

**\$1274**

**Jan Pay \$1095**



QC-1900

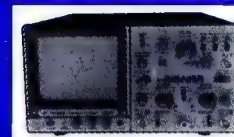


QC-1910

## Cable For 2 Disk Drives

This lead has one 3.55" floppy disk drive plug to 2 x 3.5" drive power sockets.

Cat. PL-0753

**\$5.95**

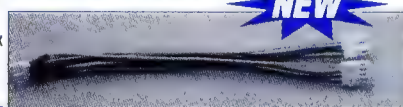


**NEW**

## 6 Core Phone Cable Sellout

SAVE A FORTUNE!

Our new cable is Austel approved. This stuff isn't. Limited quantity only. Austel approved cable is 0.75¢ metre or \$48 roll

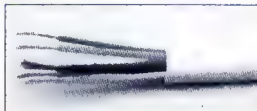This cable is **0.40¢** metre or **\$28** roll  
Cat. WB-1603



## MAJIC EAR

Majic Ear is an amazing aid to hearing that sits comfortably behind your ear and magnifies sound with superb clarity. If you have trouble hearing the TV, listening to the radio etc than Majic Ear will help. There is also 3 different earpieces so you can be assured of a perfect fit. There is an adjustable volume control and an on/off switch. Complete with battery and a spare. Don't put up with trouble hearing!!! Cat. QM-7230

**Cat Price \$29.50 NOW \$19.50**



## Ammonium Persulphate Bucket


Save a fortune. 2.5kg bucket.

**CAT PRICE \$29.95**

**Now \$22.95**

**SAVE \$7**

Cat. NC-4256

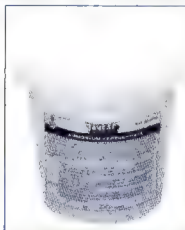

## DOLBY PRO LOGIC CENTRE SPEAKER KIT BARGAIN

Kit includes:

- 2 x 5" shielded woofers Cat CW-2102
- 1 x 1" shielded dome tweeter Cat CW-2006
- 1 x crossover network Cat CX-2613
- 1 x set box plans / wiring details

Value \$79.90

\$16.95

\$8.50

**\$105.35**

**Only \$89 SAVE OVER \$16 Cat. CS-2500**



## LED Display Bargain

LTS313AR / LT303 common cathode 0.3". Peak wavelength 700, IFMA10 .1V(VDC)650 Cat. ZD-1803



**CAT PRICE \$2 EACH**

**Jan 10 for \$10**

## TELEPHONE EXTENSION LEAD

This lead has a 15 metre length of telephone cable with a U.S. 4 pin plug on each end. Also supplied are two adaptors. One accepts the U.S. plug and converts it to an Australian plug. The other adaptor is from the U.S. plug to and Australian socket. So you can have any combination of U.S. plug to Aust plug, U.S. plug to U.S. plug or U.S. plug to Aust socket all 15 metres long. Adaptors cost \$6.50 each and the lead is \$12.95. That's over \$25 value. Austel approved.


Cat: YT-6050 **Cat Price \$13.95 JAN \$9.95**



## 12V 16W TWIN TUBE FLURO LIGHT

This fluro light runs off your 12V car power and plugs into the cigarette lighter. It has a magnetic base, so its easily attached to a van, and you can have one or both tubes on. Also ideal for lighting sheds, or houses without 240 volts.

Cat. ST-3025 **only \$24.95**

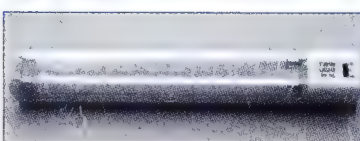

**NEW**

## SAVE ON VIFA JV80 - SUBWOOFER

QUOTE FROM ROB EVANS IN ELECTRONICS AUSTRALIA MAGAZINE.

"The JV80 performed extremely well in both our subjective and objective tests, and really did demon-strate how a refined driver such as the Vifa M22WR can deliver the goods in a correctly tuned enclosure".



AS REVIEWED IN ELECTRONICS AUST. JUNE 95

The driver has an impedance of 6 ohms, so could also be used in a car situation. The power handling is very large, for such a small driver being 150 watts nominal (RMS) a long term max rating of 300 watts (on for one minute, pause for two minutes) and a short term max power of 500 watts (on for one second, pause for one minute). We also recommend you use a polyswitch RXE300 Cat RN3472 \$10.95. To simplify, any amplifier between 30 and 200 watts can be used. Look at our new Subwoofer Amplifier Kit.

The enclosure is very small with a volume of 35 litres and only 600 x 270 x 300(D)mm. The cabinet is supplied prebuilt and is made from MDF in blackwood veneer. Grill is supplied with speaker cloth mounted.

### SPEAKER ONLY

VIFA M22WR 8" Cat. CW-2115

**Normally \$199.50**

**Jan Price \$179.50 ea**

**SAVE \$20**

### SUBWOOFER KIT

INCLUDES: •VIFA M22WR DRIVER •

PREBUILT CABINET •POLYSWITCH

**Catalogue Price \$349.45**

**Jan Price \$299**

**SAVE ALMOST \$50**

**ROAD FREIGHT ANYWHERE IN AUSTRALIA \$14. INSURANCE \$3**

## UNIDEN Cordless Phone Sellout!!!


We have a very small quantity of these phones left. See catalogue page 106 for full details.

**CAT PRICE \$229**

**Sellout**

**Price \$189**

**SAVE \$40 Cat. YT-7040**

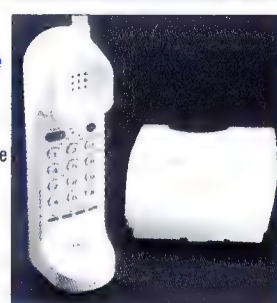

**GIFT VOUCHERS AVAILABLE**




## Mouse Station

Mouse station is ergonomically designed to rest your wrist and reduce the risk of Carpal Tunnel syndrome. As well as the padded wrist support, it includes a mouse pad and a slide out drawer at the rear. The drawer will hold 10 x 3.5" floppy disks plus pens etc. Total size 350(D) x 258(W)mm.

Mouse and disk not supplied.

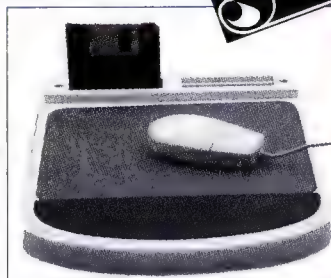Cat. XM-5098 **Catalog Price \$19.95**  
**FOR JANUARY \$13.95 Save \$6**



## AMAZING VALUE DMM'S FROM JAYCAR

BRILLIANT RANGE OF MULTIMETERS ALL OFFER UNBELIEVABLE VALUE FOR MONEY  
For full specs and the features associated with each model see our 1995 catalogue.

### Low Cost

- 3.5 Digit 12.5mm High Display LCD
- Transistor Test
- Diode Test
- 10 Amp Current



QM-1500 \$29.95

### Pocket

- 3.5 Digit
- Wrap around leads
- Small size
- One hand operation
- Continuity • Diode



QM-1520 \$34.95

### 30 Range

- Large Display
- Transistor Test
- 20 Amp
- Diode Test



QM-1300 \$49.95

### Temperature

- Frequency Transistor
- Diode, Continuity
- Capacitance
- Auto Power Off
- Large Display • 20A



QM-1320 \$69.95

### Auto Range

- 3.5 Digit
- 1999 Count
- Data Hold
- Bargraph
- Holster
- Diode • 10 Amp



QM-1530 \$89.95

## COMPUTER OPERATOR FOOT REST

This foot rest is designed for computer operators, and is suitable for anyone who sits at a desk.

The footpad measures 420(W) x 280(H)mm, and is ribbed.

The angle of the pad is easily adjustable (by your feet). Its simple to assemble and is grey in colour.

Cat. XC-5160

**Catalogue Price \$22.95**

**NOW ONLY \$12.95 Save \$10**



## Desktop Copyholder

Tilting bail, adjustable document clip and sliding rule.. Colour is black.

Cat. XC-5152

**Cat Price \$14.95**

**JAN \$9.95**

**Save \$5.00**



**Save \$50 On 0-15**

**VDC 25Amp**

**Adjustable**

**Regulated**

**Laboratory**


**Power Supply**

**NORMALLY \$349.50**

**SAVE \$50 Cat. MP-3088**

**JAN ONLY**

**\$299.50**

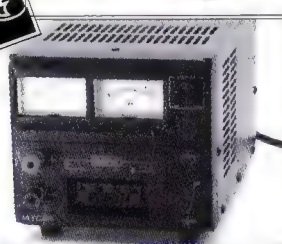

## Transistor 2SC2545 Giveaway

2SC2545 is a NPN ultra low noise device.

•Case is TO-92 •Diss @ 25°C is 400mW

•Vcb is 60V •IC is 100mA.

Cat. ZT-2400 **Cat Price \$2.95**


**Now 10 for \$2**

## 4 DIL Bridge Rectifier

A small bridge that fits into an IC socket. No is 1B4B42. Rated at 1A 100V.

Cat. ZR-1308

**\$1.20**

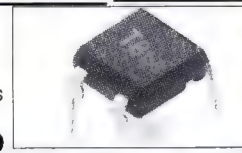

## 24 Hour Arlec Timer

Ideal for pumps, lights, heaters etc etc etc.

Cat. XW-0400 **was \$27.95**

**Now \$19.95**




## Save \$3 On 12V 13W Portable Fluro Light

Supplied with hangup clips. Power lead with alligator clips

and lighter plug. **NORMALLY \$19.95**

**JAN \$16.95 SAVE \$3**

Cat. ST-3020

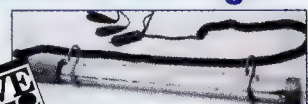

## AMAZING LIGHT GLOBE STROBE


That's right! A powerful high energy strobe light that will fit a standard 240V bayonet type light globe socket!! There are many uses for such a product. On the factory floor you can replace red warning lights with much more visible flashing ones. Replace some of the globes in your outdoor festoon party lights with dramatic effects. Ideal use in discos and advertising signs etc. Features: •xenon flash tube with all electronics in base •flashes approx 120 times / minute •visible for miles •only draws 1 watt average at 240V •easy installation - needs a bayonet type light socket •3 colours avail.

Cat YS3020 Clear / YS3022 Red / YS3024 - Blue

**Only \$19.95 ea or 10 up (mixed) \$17.95 ea**

**BULK USERS CONTACT OUR**

**WHOLESALE DEPT FOR SPECIAL PRICES**

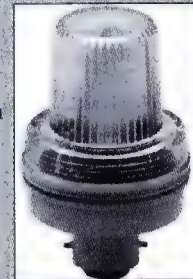

## CAR ALARM SENSATION

Amazing scoop purchase from Importers Distress allows you to save a fortune.

Road Alert RA-52 is a remote control car alarm, the siren (110dB) sounds inside the car - making it too unbearable for the thief to stay there. The RA-52 is a versatile portable alarm that can be armed / disarmed manually, or by the infrared remote control supplied. It will operate from a rechargeable 9v battery, or direct from the cars power, hard wire connected or through the cigarette lighter socket. All leads supplied.

This is a unique car alarm, that works extremely well, and is an ideal investment to help "Keep Your Car". Cat. LA-8950

**Retail Price was \$179**

**Distress Purchase Price \$79.50 JAN ONLY \$49.50**



**BUY 10 LESS 10%**



## STEREO INFRARED CORDLESS HEADPHONES

These are very similar to the mono ones shown above, but transmit in stereo. Use on your Hi Fi or stereo TV etc. To use, plug the transmitter into the headphones or output socket (lead supplied). Transmitter sits on top of your TV or stereo. Headphones have a separate volume control on each and require 2 x AAA batteries. Operating distance is up to 7 metres. Unit requires 12VDC mains adaptor. Use an existing one or purchase our cat MP-3006 \$15.50.

Cat. AA-2004




**\$79.95**

## FREECALL FOR PHONE ORDERS

**008 022 888**
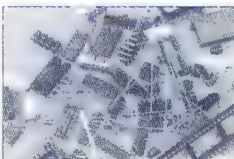
## Mixed Semi Pack

Contains a minimum 100 mixed, semi conductors for \$10. Includes ICs, transistors, diodes etc.



Cat. ZP-8990

**only \$10**

## SAVE \$40 ON OUR TOP OF LINE AC + DC TRUE RMS DIGITAL MULTIMETER

FEATURES INCLUDE: •4000 COUNTS •40,000 COUNTS MODE •ANALOGUE BARGRAPH •DUAL DISPLAY •0.08% BASIC DCV ACC •BACKLIGHT DISPLAY •TRUE RMS •DC VOLTAGE •(DC + AC) VOLTAGE •DC CURRENT •AC CURRENT •RESISTANCE •CONDUCTANCE •FREQUENCY •DUTY CYCLE •CAPACITANCE •DIODE ADAPTOR •AC ADAPTOR •DBM & DB •150US CONTINUITY •50MS RECORD •0.8MS CREST •SORT •DATA HOLD •STORE AND RECALL •RELATIVE ZERO •RELATIVE % CHANGE •RELATIVE PER UNIT •INPUT WARNING •SPLASH PROOF CASE •PROTECTIVE HOLSTER COMPLETE WITH TEST LEADS, BATTERY INSTALLED AND USERS MANUAL. SEE CATALOG FOR FULL DETAILS. CAT. QM-1460



## Multiturn Pot Sellout

Quality Japanese Sakae Brand. These are 10 turn glass filled with phenolic base. Stainless steel 1/4" shaft with screwdriver slot. Linear tracks rated at 3W @ 40°C. Some types have extremely limited quantities with stock only in our stores. Normally worth around \$14, some values are in our catalogue at \$5.95 and \$7.95. Grab these while we have them.

Cat. RP-3810

100Ω

Cat. RP-3812

200Ω

Cat. RP-3814

Cat. RP-3818

2KΩ

Cat. RP-3830



500Ω

100KΩ

**ONLY \$3.95 each**

## PROFESSIONAL ADJUSTABLE WIRE STRIPPER SELLOUT

Quality tool ideal for stripping coaxial cables. Will either strip in a circular motion or slice the sheath side ways. Simple cutting depth adjustment. If you strip a lot of cables, this tool is a must for your toolbox.

Cat. TH-1822

**WAS \$24.95**

**NOW \$10 SAVES \$14.95**



## METAL DESOLDER TOOL

**TOOL**

See cat page 88 for details.

**NOW \$12.95**

**WAS \$16.95 SAVE \$4** Cat. TH-1862



## 14,400 BPS DATA/FAX MODEM Internet Software Included!!!

**SPIRIT SWIFT**


This is a fully featured modem on a circuit card ready to plug straight into the motherboard of your PC. Why clutter your workspace when your modem can be inside your PC!!!

The Swift will send and receive faxes at the new V.17 standard of 14,400BPS as well as falling back to the slower speed of 9,600 BPS. This is a very clever modem which loses nothing to black box units.

SPIRIT SWIFT INCLUDES: •Spirit Swift fax modem •Winfax lite, DOSfax lite and Comit lite for DOS and Windows •2 metre phone cord •User manual •OzEmail Internet software  
SPECIFICATIONS: •ITU-T V.32bis, V.32, V.22bis, V.22 and Bell 212A compliant •14,400/12,000/9,600/7,200/4,800/2,400/1,200/300bps •ITU-T Group III, Class 2 send and receive fax at up to 14,400bps •HARDWARE ITU-T V.42bis and MNP 5 data compression •HARDWARE ITU-T V.42 and MHP 2,3 and 4 error correction •57,600bps effective throughput •Auto speed negotiation •Adaptive line speed •Hardware and software flow control •Data communications, internet and fax software included.

Cat. XM-5100

**only \$199!!!**

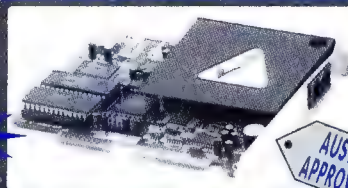

AUSTEL APPROVED

5 YEAR WARRANTY

## 1 Amp Regulated Switched Power Supply

Desktop type, with outputs of 6.9 and 12V DC. Includes 7 reversible plugs.

Cat. MP-3032

**only \$39.95**



## 500mA Regulated 3/4.5/6/7.5/9/12VDC

Cat. MP-3030

**\$29.95**

## Panel Meter Sellout

MU65 style which is the largest available in the range. Overall size 100(W) x 82(H)

**CAT PRICE \$24.50 EA**


**Now \$14.95ea**

**0-1MA**

Cat. QP-5040

**0-100UA**

Cat. QP-5042

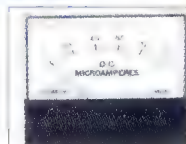

## Headphone Extension Lead Bargain!!!

Limited quantity. These leads should have been curly cord, but they arrived straight.

6.5mm stereo plug to stereo plug line socket. Length 2.8 metres. Curly cord ones sell for \$41.95. These are only \$4.95

Cat. WA-1004

**only \$4.95**



## 300 Watt Sinewave Inverter Sellout

See 1995 catalogue P109 for full details.

**CAT PRICE**

**\$699**

**January \$550**

**SAVE \$149**

Cat. MI-5030

**PRO Mic/Headset SALE!!!**

See catalogue page 59 for full details.

**CAT PRICE \$89.95**

**Jan**

**\$69.95**

**SAVE \$20**

Cat. AA-2022





## SAVE BIG \$\$\$\$\$\$ ON JV100 10" 3 WAY 5 SPEAKER KIT



Huge Power Handling - Amazing Sound  
See catalogue for full details or call into any  
Jaycar store for a demo.  
Buy in January and save big dollars.

### SPEAKER KIT

Normally \$1199 pair

**Jan \$999 pair Save \$200**

### FULL KIT WITH CABINETS

Normally \$1499 pair


**Jan \$1250 pair Save \$249**

**Quote from Leo Simpson Silicon Chip Magazine On JV100's**  
This speaker really performs, with prodigious power handling & beautiful bass down to below 30Hz. But as well as power handling & extended bass response, the system is very satisfying in its handling of all types of music with a smooth midrange & very clean treble reproduction.


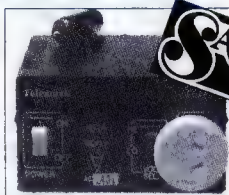
## 100 Watt Inverter Sellout!!!

Convert  
12VDC to  
240VAC  
and run  
products up  
to 100  
watts. See  
page 108 of  
catalogue  
for full details. Cat. MI-5035



**1994 PRICE \$134.95**  
**1995 PRICE \$89.50**

**Now Only \$69.50**

**BUY 10 LESS 10%**

## PART CASES CLEAROUT!

Prices reduced further.

### #1 - INTERLOCKING SINGLE PARTS DRAWER

Single or double drawers available. Size: 110(W) x 120(D) x 50(H)mm.

**Cat. HB-6300 Was \$5.95 Now \$3.25 Save \$2.70**

Some double drawer units available in very limited quantities. Cat HB-6301 was \$6.20 Now \$4.20

### #2 - 3 DRAWER PARTS CABINET

Size: 98(W) x 42(H) x 88(D)mm.

**Cat. HB-6323 Was \$5.95 Now \$3.25 Save \$2.70**



### #3 - SMALL TOOLBOX

Has 2 compartment trays. Total size 310(L) x 160(W) x 150(D)mm.

**Cat. HB-6330 Was \$17.95 Now \$13.95**

**Save \$4.00**


**CLEAROUT  
PRICES**

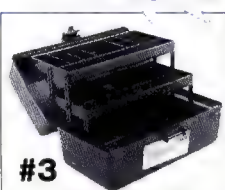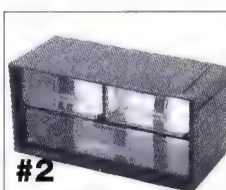

## Save \$10 on Probe DMM

•Logic test •Diode  
•Buzzer •Auto/manual  
range •Data hold. See 1995 catalogue P32 for full details. Cat. QM-1420

**WAS \$54.95**

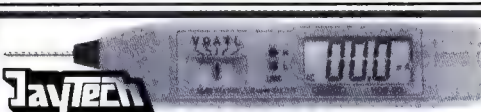

**Jan \$44.95**


**SAVE \$10**

## SAVE SAVE SAVE ON NICADS!!!!!!

	NORMAL	JAN	SAVE	CAT
9 VOLT NICAD 100MA	\$17.95	\$14.95	\$3	SB-2458
AAA - PKT 2 180MA	\$6.95	\$4.95	\$2	SB-2454
C NICAD 1.2A	\$5.95	\$4.95	\$1	SB-2459
C NICAD 2.25A	\$9.50	\$7.50	\$2	SB-2464
D NICAD 1.2A	\$5.95	\$4.95	\$1	SB-2460
D NICAD 5.1A	\$16.95	\$13.95	\$3	SB-2466



**SAVE!!**

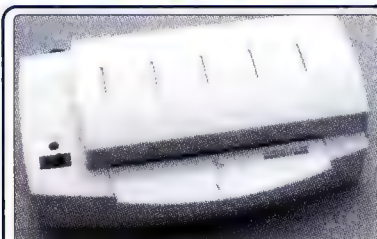

## A4 LAMINATING MACHINE

Protect catalogues, documents,  
etc up to A4 size (216 x 303mm).  
Operates on 240VAC.

**Save \$50 For January**



**Opposition Price: \$399**

**Jaycars Price: \$299**

**JANUARY PRICE \$249**

**Cat. XL-2510**

**A4 Laminating Sleeves Pkt of 25**

**Cat. XL-2512**

**\$24.95**



•Dual display •RS232 interface  
•Transistor •Capacitance •Auto  
hold •Data hold •10 memory  
•Bargraph •Min/max display  
•Relative offset •Logic •20 amp  
•20mHz frequency See catalogue  
page 29 for full details.  
Cat. QM-1240


**Cat Price**

**\$179.50**

**Jan**

**\$149.50!!**

**Save \$30!!**

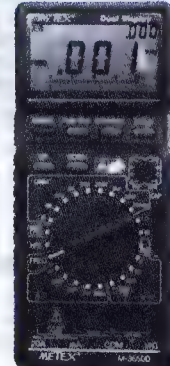


## BUY A SPARE!

**LOCKDOWN ANTENNA  
FOR EA-EB FALCON**

**Cat. AR-3256 was \$14.95**

**Save \$4.95**

**now only \$10**

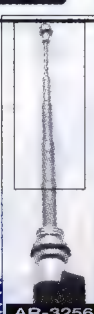

AR-3256



## More Kits GEIGER COUNTER

REF: Silicon Chip September '95  
Our Geiger Counter Kit will detect alpha, beta and gamma radiation and has an audible output. Kit includes PC Board, Case, Geiger Muller Tube, Speaker, Transformer Assembly and all specified components.

Cat. KC-5194

normally \$179.50 Save \$20  
**ONLY \$159.50**



## Jacobs Ladder High Voltage Display Kit

REF: Silicon Chip September 1995

Ever since scientists Tesla and Edison were able to generate really high voltages the Jacobs Ladder display has been creating awe. Best examples of a Jacobs Ladder can be seen in those early Frankenstein films, and the kit presented here produces a noisy ladder of sparks that look equally as nasty and dangerous - as indeed they are - along with the familiar smell of ozone! Kit includes PCB and electronic components. 12V auto coil required - not incl.

Cat. KC-5191



**\$29.95**

## 5 Band Equaliser Kit

**NEW** REFER: SILICON CHIP 12/95  
Live up your keyboard, guitar or music system with this low noise equaliser kit. Each band is centred on 63Hz, 250Hz, 1kHz, 4kHz and 16kHz with low distortion of .005% over the 20Hz to 20kHz range. S/N -97dB A-weighted @ 1VRMS. DC rectifiers and regulators on board - just add AC 30V C-T transformer use MM-2007. Two kits required for stereo. PCB, knobs and electronic components supplied.

Cat. KC-5197



**\$39.95**

## Engine Immobiliser Kit


REFER: SILICON CHIP 12/95

This simple yet effective circuit will immobilise your car if a thief tries to start it, providing you with cheap insurance and peace of mind. The unit allows the engine to be started but stops after 3.5 seconds - repeatedly stalling the engine and frustrating the would-be-thief. After several tries the thief is likely to decide the car has an intermittent problem and leave it. PCB, case, auto connectors and components supplied.


Cat. KC-5196



**\$24.95**

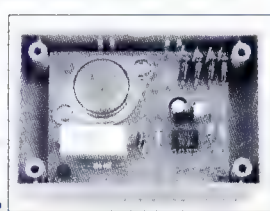

## Clock Movement

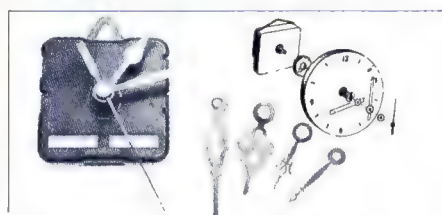

MAKE YOUR OWN CLOCK! FIX YOUR OLD CLOCK!

•Very compact 56 x 56 x 15mm •Self starting one second stepping motor •Uses 1 x AA battery that lasts 1 year •±15 second/month accuracy •Supplied with three sets of hands •Includes sweep second hand

Cat. XC-0100

**\$9.95**

MELODY MOVEMENTS ALSO AVAILABLE

Cat. XC-0106 Westminster Chimes

**\$21.50**

Cat. XC-0107 12 Melodies


**\$21.50**

## Ferrite Material & Applications

This is one subject that is very difficult to find any information on. Magnetic cores are the foundation for transformers, inductors and chokes used in so many of our electronic projects. This book is intended to be used by persons who want to (or have to) work with ferrite materials, but are not well versed in magnetics or ferrites and cannot justify outside consultation. Some of the problems addressed are:- • How to select the right type of material • How to identify an unknown material • How to measure material properties and much more. Written in 1991 by A. K. Johnson. Softcover, ringbinder. 82 pages 212 x 132mm.

Cat. BC-1125 Cat Price \$18.95

**JAN \$12.95 Save \$6**

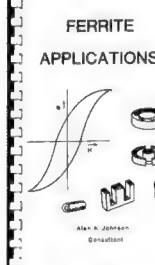

## Speaker / Microwave Wall Bracket

This bracket will accommodate a large range of things including speakers, microwave ovens, clothes dryers etc. The shelf has an adjustable depth from 375mm to 570mm, wall bracket length is 420mm maximum. Finished in black. Load capacity is 31kgs.

Cat. CW-2820

1994 Price \$37.50 1995 Price \$29.95

**NOW ONLY \$20 SAVE \$9**




## TV Wall Bracket with VCR Shelf

The VCR shelf attaches firmly underneath the platform, so that both the TV and VCR controls are close together. Finished in black epoxy polyester powder coating. The TV shelf expands width wise from 380mm to a massive 1150mm. Depth of shelf 260mm. VCR shelf expands from 350mm to 540mm. Load capacity is 50kgs. Cat. CW-2830

1994 Price \$79.95 1995 Price \$79.95

**NOW ONLY \$59.95**

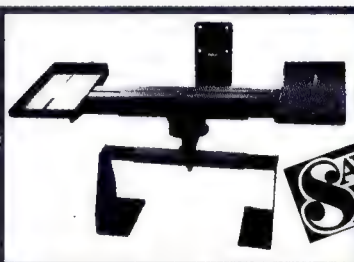

## Save \$10 on 10" Guitar Speaker

Power handling 65WRMS. Ideal for practice amp. See 1995 catalogue P50 for full details.

CAT PRICE \$57.50

**Jan \$47.50 SAVE \$10**

Cat. CG-2376



## 12" 4Ω Polycone Woofer

Power handling 200WRMS. Full specs see cat P63.

Cat. CG-2338

**WAS \$135**

**Jan \$99**

**SAVE \$36**



## Polyswitch Speaker Protectors

Save Money and protect your speakers. See cat P51 for details.

Cat.no	Part No	Price	Jan Special	Save	Trip Watts 4 ohms	Trip Watts 6 ohms	Trip Watts 8 ohms
RN-3460	RXE075	\$6.95	<b>\$4.95</b>	\$2.00	5.1	7.7	10.2
RN-3462	RXE090	\$7.25	<b>\$4.75</b>	\$2.20	7.3	10.9	14.6
RN-3464	RXE110	\$7.50	<b>\$5.20</b>	\$2.30	10.9	16.3	21.8
RN-3466	RXE160	\$7.95	<b>\$5.50</b>	\$2.45	23.0	34.6	46.1
RN-3468	RXE185	\$8.50	<b>\$5.50</b>	\$3.00	31.4	47.0	62.7
RN-3470	RXE250	\$9.95	<b>\$6.95</b>	\$3.00	56.3	84.4	112.5
RN-3472	RXE300	\$10.95	<b>\$7.50</b>	\$3.45	81.0	121.5	162.0
RN-3474	RXE375	\$12.95	<b>\$8.95</b>	\$4.00	126.8	190.2	253.6



## Plug In Rabbit Ears Antenna

Ideal replacement. Has two telescopic antennas in plastic base that plugs into a socket on the TV for mounting. Supplied with length of 300Ω cable and spade terminals. Antenna rods are adjustable and expanded length is 800mm. Surplus buy - priced well below normal.

Cat. LT-3120 **\$4.95**





## PIR MADNESS!!!


We have made a scoop purchase of a quantity of Micron Pulse count passive infrared detectors. The Micron PIRs are designed by an English company and manufactured in Asia. This unit is currently being sold to the installer market, at a price which is higher than what we can offer you. But remember, this is a once only deal, and cannot be repeated. Stock will not last. The Micron is the ultimate low cost/high performance PIR detector. The Micron circuit design has been tested at 20V/m over the frequency range 20 to 1000MHz proving that the Micron has ultra high RFI protection and complies with BS6667, part 3 and IEC Publication 801, Part 3. Knowing the Micron has passed these tests and by utilizing the selectable 1, 3 or 5 pulse count, once installed correctly you can leave the installation, confident that false alarms will not occur. Specifications:

- selectable 1, 3 or 5 pulse count
- operating voltage 9-16VDC
- current 17mA
- alarm contacts - NC
- operating temp -10° to 55°C
- pyroelectric detector dual element.

NORMALLY WOULD COST AROUND \$35 TO \$40

Cat. LA-5030

**ONLY \$25 OR 10 FOR \$200**

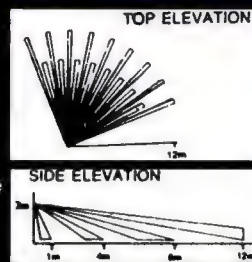

**NEW**

## HOME BURGLAR ALARM DEALS FROM JAYCAR

### DEAL 1



### Protect Your Home For Under \$200


You won't beat this deal anywhere. Check out what our opposition have available for \$249!!! All you need is a bit of labour and you have a reliable affordable alarm that offers you piece of mind.

INCLUDES:	NORMAL PRICE
1 x 4 sector Jaytech panel	\$109.50
2 x Jaytech pulse count PIRs	\$59.90
1 x mains power supply	\$21.50
2 x reed/magnet switches	\$11.50
1 x siren horn	\$24.95
2 x deterrent stickers	\$4.00
50 m of 4 core alarm cable	\$28.00
NORMALLY PAY	\$259.35

Cat. LA5450 **Pay Only \$199**



### DEAL 2

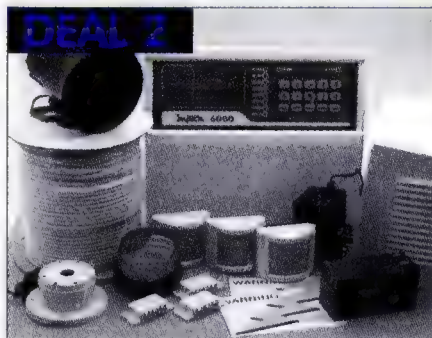

Ideal for larger homes. This system has our 6 sector panel and includes everything that a professional alarm installation company would install and charge around 800-\$1000. Save a fortune by doing it yourself.

INCLUDES:	NORMAL PRICE
1 x 6 sector Jaytech panel	\$139.50
1 x mains power supply	\$21.50
1 x 1.2Ah backup battery	\$28.50
3 x Jaytech pulse count PIRs	\$89.85
3 x reed/magnet switches	\$17.25
1 x strobe	\$19.95
1 x metal siren cover	\$28.95
1 x siren horn	\$24.95
1 x internal siren	\$19.95
2 x deterrent stickers	\$4.00
100 m of 6 core alarm cable	\$88.00
NORMALLY PAY	\$482.40

Cat. LA5455 **Pay Only \$349**



### DEAL 3




This system includes the brand new DSC 5 sector alarm panel with Austel Approved dialler. Connect it to an alarm company or it can phone you or your neighbours etc.

INCLUDES:	NORMAL PRICE
1 x DSC 5 zone alarm/dialler	\$279.00
3 x Bellmate 100 PIRs	\$119.85
1 x mains 3 wire power supply	\$24.95
1 x 6.5Ah backup battery	\$43.50
2 x reed/magnet switches	\$11.50
1 x strobe	\$19.95
1 x metal siren cover	\$28.95
1 x siren horn	\$24.95
1 x internal siren	\$24.95
2 x deterrent stickers	\$4.00
100 m of 6 core alarm cable	\$88.00
NORMALLY PAY	\$669.60

Cat. LA5460 **Pay Only \$599**



## ALARM CABLE BARGAIN

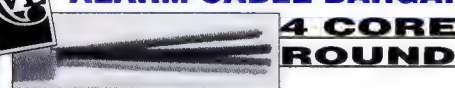

**4 CORE ROUND**

NORMALLY \$56 PER 100M ROLL  
**JAN \$29/roll** Cat. WB-1590

**6 CORE ROUND**

NORMALLY \$88 PER 100M ROLL  
**JAN \$45/roll** Cat. WB-1592

## LAST CHANCE - Burglar

### Alarm Window Tape & Blocks

Are discontinued. Grab the last of our stocks while they last!!!

**TAPE - 33M ROLL** Cat. LA-5050


**WAS \$19.95 NOW \$16.95**

### TERMINAL BLOCKS

For joining tape to alarm wiring.

**WERE \$1.25EA NOW \$1ea**

**or 10+ 90¢** Cat. LA-5060

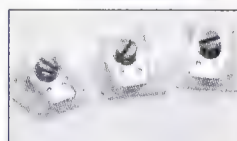


## BULK USERS

CONTACT  
OUR  
WHOLESALE  
DEPARTMENT  
FOR SPECIAL  
PRICING  
(02) 743 5222

## JayTech Digital Capacitance Meter



BRAND NEW MODEL!!! Has a unique tilting LCD display which allows you to read at any angle. General specs: •Display - 3.5 digit LCD •Range - 9 ranges 200pf to 20mf •Sampling time - 0.5 seconds •Accuracy - 0.5% ranges 200pf to 200mf ranges, 1.0% range 2,000uf, 2.0% range 20mf.

Cat. QM-1572 **\$99.50**

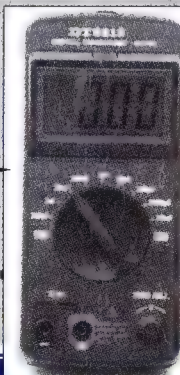
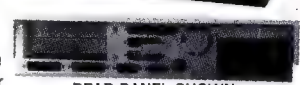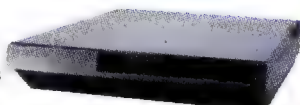
## BARGAIN COMPUTER CASE

Limited quantity. It consists of a metal base/rear panel and fawn coloured plastic top and sides. It measures 360(D) x 340(W) x 70(H)mm. There is a slot in the front panel (26H x 216W) which will accept 2 x 3.5" disk drives or hard disks. Brackets supplied for mounting. The rear panel has numerous cutouts for a myriad of things. These include D25 slot for printer, D25 slot for COM2, D25 slot for SCSI, D37 slot for ext floppy disk, round hole for keyboard, reset pushbutton hole, slots for fan, hole for expansion board 112W x 47Hmm and a hole for a power supply 86W x 53Hmm. Grab one while we have them. Mail order customers add an extra \$4 to P&P charges due to heavy weight (3kgs). Cat. HB-5100



REAR PANEL SHOWN

**only \$10**



## DOLBY PRO LOGIC KIT FOR UNDER



**DOLBY SURROUND**  
**PRO • LOGIC**

**ONLY \$379.00**



Yes, you can now buy the Dolby Pro Logic short form kit (KC-5175) and the enclosure kit (KC-5176) for \$199.

**SAVE \$40**

**\$199.00**

**\$69.50**

**\$44.95**


\$10 - \$24.99	\$ 4.00
\$25 - \$49.99	\$ 5.00
\$50 - \$99.99	\$ 7.00
OVER \$100	\$ 8.00

**RHODES**

- 129 York St • Ph: (02) 267 1614 • Fax: (02) 267 1951
- Mon/Fri: 8.30-6pm • Thurs: 8.30pm • Sat: 9-4pm
- 363 Hume Hwy Cnr Meredith St • Ph: (02) 709 2822 • Fax: (02) 709 2007 • Mon/Fri: 9-5.30 • Thurs: 8.30pm • Sat: 9-4 • Sun: 10-4pm
- 188 Pacific Hwy (Cnr. Bellevue Ave) • Ph: (02) 439 4795 • Fax: (02) 439 4895 • Mon/Fri: 9-5.30 • Thurs: 8.30 • Sat: 9-4 • Sun: 10-4
- 830 Hunter St (Cnr Stewart Ave) • Ph: (049) 653 799
- Fax: (049) 653 796 • Mon/Fri: 9-5.30 • Sat: 9-4pm
- 355 Church St (Cnr. Victoria Rd) • Ph: (02) 683 3377
- Fax: (02) 683 3626 • Mon/Fri: 9-5.30 • Thurs: 8.30pm • Sat: 9-4pm
- Sun: 10am-4pm
- 199 High St • Ph: (047) 21 8337 • Fax: (047) 21 8935
- Mon/Fri: 9-5.30 • Thurs: 8.30 • Sat: 9-4pm • Sun: 10-4pm
- 326 Newcastle St Northbridge • Ph: (09) 328 8252
- Fax: (09) 328 8982 • Mon/Fri: 9-5.30 • Sat: 9-4
- 8-10 Leeds St • Ph: (02) 743 5222 • Fax: (02) 743 2066
- Mon/Fri: 9-5.30



# SATELLITE WATCH

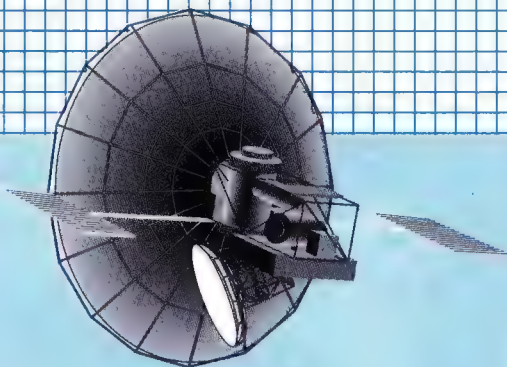

*Welcome to the first Satellite Watch column, where we will keep you updated with satellite signal reception reports for Australia and NZ.*

Compiled by  
**GARRY CRATT\***

• **INTELSAT - 70-66° E longitude, C band:**

This satellite is visible only from the west coast of Australia and carries Worldnet programming from the USA, CFI from Paris and various other itinerant signals.

• **GORIZONT - 19 - 96.5° E longitude, C band:**

This satellite carries the Russian "Network 1" programming on 1475MHz, with audio at 7.02MHz. An additional radio service is also carried at 7.5MHz. CCTV 4 Chinese television can be seen at 1325MHz and now carries a new English News service. Az Tv from Azerbaijan can be seen on an irregular basis at around 1800AEST and can be found at IF 1425MHz.

• **ASIASAT II - 100.5° E longitude, C band:**

Scheduled for launch last November, this will provide new programming for satellite enthusiasts. After months of delay caused by previous failures aboard the Long March launcher, this is the launch that will make or break Great Wall. Mooted to carry similar programming to ASIASAT I, this satellite will be visible over Australia and New Zealand with a small (2m) dish. At least five channels will be free to air, according to prelaunch press releases.

• **GORIZONT 25 - 103° E longitude, C band:**

Another Russian satellite carrying Network 1 programming, for a different time zone to Gorizont 19.

• **ASIASAT 1 - 105.5° E longitude, C band:**

Visible in the northern and north western parts of Australia, this satellite has a potential northern hemisphere audience of over a billion viewers and covers from India to the Middle East. Reports as far south as Albury (NSW) and the Barossa Valley area indicate sidelobe signals are visible in some parts of southern Australia. Programming carried includes Prime Sports, Star Movies, Zee TV and other pay services. Transponder frequen-

cies can be obtained by dialling the Hong Kong Info service number: 0011 852 172 777 01. Call charges are at normal IDD rates.

• **PALAPA B2P - 113° E longitude, C band:**

Presently visible only in the Northern part of Australia, this satellite was placed in an inclined orbit in November, to conserve station keeping fuel, whilst waiting the launch and subsequent replacement by PALAPA C1, a higher powered satellite covering all of Australia and New Zealand. Palapa C1 will now be launched by Lockheed Martin of the USA. Prior to this announcement in October, the launch was scheduled with Ariannospace but the launch company was unable to keep to the original schedule.

It is expected that all current users will transfer to the new satellite, now scheduled for launch in January 1996. Amongst signals on the B2P satellite is Australia's ATVI, the international arm of the ABC. Weekly program data can be obtained by polling fax # 055 29900.

• **JCSAT 3:** First observed early in October, this satellite has the capability to cover Australia and New Zealand with strong signals. Reports from the east coast of Australia, Japan, Hawaii and Noumea indicate the testing phase of this satellite is almost complete. It is expected that some programming could become available early in 1996.

• **RIMSAT G1 - 130° E longitude, C band:**

The orbit of this Russian Gorizont class satellite is only slightly inclined, making 24-hour small dish reception of RAJ TV, a Tamil language broadcast, a reality. RAJ TV operates at 1475MHz.

• **RIMSAT G2 - 142.5° E longitude, C band:**

Until September 12, this satellite carried the ATN network from India. Due to unresolved difficulties involving the satellite operator RIMSAT, the Russian government space agency and ATN, this transponder ceased operations temporarily during September but now appears to be operating on a permanent basis. The other full time transponder, operating at

1265MHz, carries EM TV from Papua New Guinea. This transponder operates LHCP (left hand circular polarisation) and carries a mix of Nine network (Australia) and local programming.

During late November, ATN changed format to two adjacent half transponders. Whilst continuing with the regular ATN broadcasts on IF 1465MHz, ATN PRIME will commence early December using an IF of 1480MHz.

• **OPTUS B1 - 160° E longitude, K band:**

This satellite carries outback TV in BMAC, as well as up to five interchange services in PAL. Interchange IF frequencies are: 1219, 1155, 1425 (all vertically polarised) and 1249MHz horizontal.

• **OPTUS B3 - 156° E longitude, K band:**

The latest Optus satellite came into operation last August. Presently, it carries several closed user group BMAC services, as well as the OTEN network (Victorian and NSW education departments) and several interchange services. IF frequencies are 1233, 1361 and 1094MHz. The Optus A3 satellite, until recently co-located at 156° E, is most likely part way through a planned drift back to 164°, where it could be used to replace the ageing A2 satellite, now in an inclined orbit.

• **PANAMSAT PAS-2 - 169° E longitude, C band:**

Although many services on this bird use either secure BMAC or MPEG 2, there are still some analog services that can be viewed by enthusiasts. CNN, NHK and CNBC Asia operate on 1153, 1113 and 1035MHz IFs. Recent itinerant users include the American ABC network and a number of news feeds from Osaka, Japan, during the recent ASEAN conference.

• **INTELSAT 511 - 180° E longitude, C band:**

This ageing satellite, now in an inclined orbit but due to be replaced during 1996, carries Deutsche Welle programming from Germany, RFO from Tahiti and Worldnet from the USA. In the last few months several services have migrated from Intelsat to other satellites, whilst some previous analog services (CNN, NBC) have gone to digital format. **SC**

\*Garry Cratt is Managing Director of Av-Comm Pty Ltd, suppliers of satellite TV reception systems.





# Rain Brain

By GRAHAM BLOWES

**This automatic sprinkler controller allows you to selectively water any area of a garden or nursery as little or as often as you like. It can control up to eight solenoids plus an optional master solenoid.**

**T**HE FIRST VERSION of this design was published in the July 1992 edition of SILICON CHIP. It was a popular project and I still get enquires from the original article.

About a year ago, I decided that an update was due. The most obvious thing that needed replacing was the microcontroller, as the NMOS 68705-P3 microcontroller was to be discontinued. The controller now uses a PLCC version of the popular 68HC-705C8. There was also some changes

made to the power supply, which now uses a switching IC.

While I was at it, I also decided to make a couple of changes to the front panel layout. First, I deleted the row of green LEDs that were used to indicate which solenoids were on. This function is now taken care of by the row of red LEDs – when a solenoid turns on, the appropriate LED flashes at a fast rate to provide the “on” indication.

I also added an extra button to the

front panel to make it easier to get back to the default mode. Apart from that, the layout of the front panel worked pretty well, so I kept it that way.

The PC board is also now a lot easier to put together than before. And finally, I’ve added three inputs – designated Rain 1, Rain 2 and Frost 1 – that enable almost complete automation of your garden!

Two of the inputs are for optional rain switches that enable the controller to turn off selected cycles if it is raining. This facility is especially important in a country like Australia, where many parts of the country suffer from low rainfall. Wasting water costs money, especially these days with the in-vogue user-pays principle, so turning off the sprinklers when it rains makes economical (and ecological) sense.

The third input is for a temperature sensor (again optional). This enables the controller to switch in extra cycles on a hot day. It even works in reverse; an extra cycle can be switched in if the temperature falls below a set trip point. The controller even stores the MIN and MAX temperatures (time stamped) for today and yesterday.

Each rain switch and temperature trip point can be set on a cycle by cycle basis. The default mode can display the time and date, or the time and current temperature. This facil-



## Main Features

(1). Uses a 16 x 1 liquid crystal display (LCD) to show time, date and sprinkler settings, plus all the various system menus.

(2). Controls up to eight solenoids plus a master solenoid.

(3). Each station can have up to four cycles on Program A and Program B, or eight cycles on Program C (Program C = Program A + B). Each cycle can operate with either the three-week built-in calendar or on a continuous schedule for up to 99 days

(4). Each station (and cycle) is completely autonomous, providing a possible 64 programmable start times per day (Program C).

(5). LED indication of station status. Continuously lit = auto mode on; fast flash = solenoid on; 1Hz flash = Rain Off mode.

(6). Manual on/off control for each solenoid. The run time of cycle 4 can be used to provide an automatic cut-off feature. This lets you manually

switch on a sprinkler and forget it. The sprinkler will then automatically turn off after the run time of cycle 4 has expired.

(7). Run time (per cycle): 1-99 minutes. The cycles can be joined so the maximum run-time (per solenoid) is: 8 x 99 minutes = 13 hrs, 10 mins.

(8). An EEPROM stores all settings, so settings are not lost if the backup battery fails. Battery backup is provided by a 3V lithium battery.

(9). A "Rain Mode" deactivates all automatic cycles while saving program settings.

(10). Two fully programmable Rain Switches (optional) allow any/all of the 64 cycles to be controlled by the immediate weather conditions automatically.

(11). An optional Temperature Sensor enables any/all of the 32 cycles of Program A (or B) to switch to another cycle if the programmed trip temperature is exceeded. This allows extra

cycles to be automatically added; eg, so that plants get extra water on a hot day! The sensor is accurate to  $\pm 0.1^{\circ}\text{C}$  and has a range from  $-20^{\circ}\text{C}$  to  $+60^{\circ}\text{C}$ .

(12). The controller stores the maximum and minimum temperatures sensed that day and the time at which these extremes occurred is also recorded. This information is accessed by pressing the "Cursor" button while in the Default Mode. The previous day's temperature extremes can also be displayed, as well as the current temperature!

(13). Uses the well proven MC68HC-705C8 microcontroller. A watch dog circuit ensures a proper reset is issued to the microcontroller if it "crashes" due to a mains glitch.

(14). All appropriate solenoids are enabled and the various cycles completed after a reset, or when power is restored after a power failure.

(15). Runs from a 10-24VAC or a 10-35V DC 1A plugpack supply.

ity is programmable via the "CONFIG" menu. More about that later.

### Main features

The original version allowed sprinklers to turn on every day, every second day, every third day, etc. While this system worked OK, it was a bit difficult to nail down exactly which days the sprinklers would turn on. To rectify this, the Rain Brain now has a 3-week cycle as well as the original method – the original method being useful for plants that require watering at a set interval, regardless of whether it is a weekend or not.

The "3-week cycle" method is based on a built-in calendar. It lets you choose exactly which days the sprinklers will turn on up to three weeks in advance! For example, you could program the unit so that solenoid 1 turned for two 1-hour cycles on Monday of the first week, Wednesday of the second week and Thursday of the third week.

All the facilities mentioned above are available to every single cycle, and are programmable via the "AUXILIARY FUNCTIONS" menu.

To cater for the extra facilities, the Rain Brain has twice the EEPROM capacity of the previous version. Each

of the eight stations can switch on as often as eight times a day (ie, there are up to eight daily cycles), or as little as once every 99 days! As before, each cycle can be programmed for an "on time" of 1-99 minutes.

A new feature allows you to choose from three standard programs, designated A, B and C. Programs A and B allow each station to be programmed for four cycles per day, while program C combines programs A and B to provide up to eight cycles per station per day. If this isn't enough, you can add optional extra memory plus a switch to select an alternative group of A, B and C programs.

The row of eight LEDs beneath the LCD indicates the status of the solenoids at a glance. If a LED is flashing quickly, this indicates that the solenoid is turned on. If a LED is steady, the station is active, meaning that it will switch on automatically once its "turn on" conditions are satisfied. And if all enabled LEDs are flashing slowly (1s on, 1s off), a rain switch has been activated.

A flash rate of 0.5s on, 0.5s off indicates the "RAIN OFF" mode. This means that all automatic cycles have been globally disabled (see later). This mode has precedence over the rain

switch inputs and the fast flash rate has precedence over them all.

Although these different flash rates may seem initially confusing, it all makes perfect sense when you start using the unit.

### Power requirements


The unit is powered by the usual 24V AC plugpacks associated with watering systems, or from voltages as low as 10V DC. As with the first version, flat batteries are not a problem, as all settings are stored securely inside an EEPROM. The controller reads the EEPROM when it is first turned on, so it knows exactly which mode it should be in (RAIN OFF or DEFAULT) and which sprinklers are active.

### Other uses

By this stage, you are probably already thinking of other uses for this versatile controller, apart from its primary use as a sprinkler solenoid controller. For example, those of you who have an interest in satellites can set the controller to switch on a tape recorder at the time it is due to pass overhead, even though you may be on holidays for a few weeks.

Alternatively, the unit could be used as a security light controller or



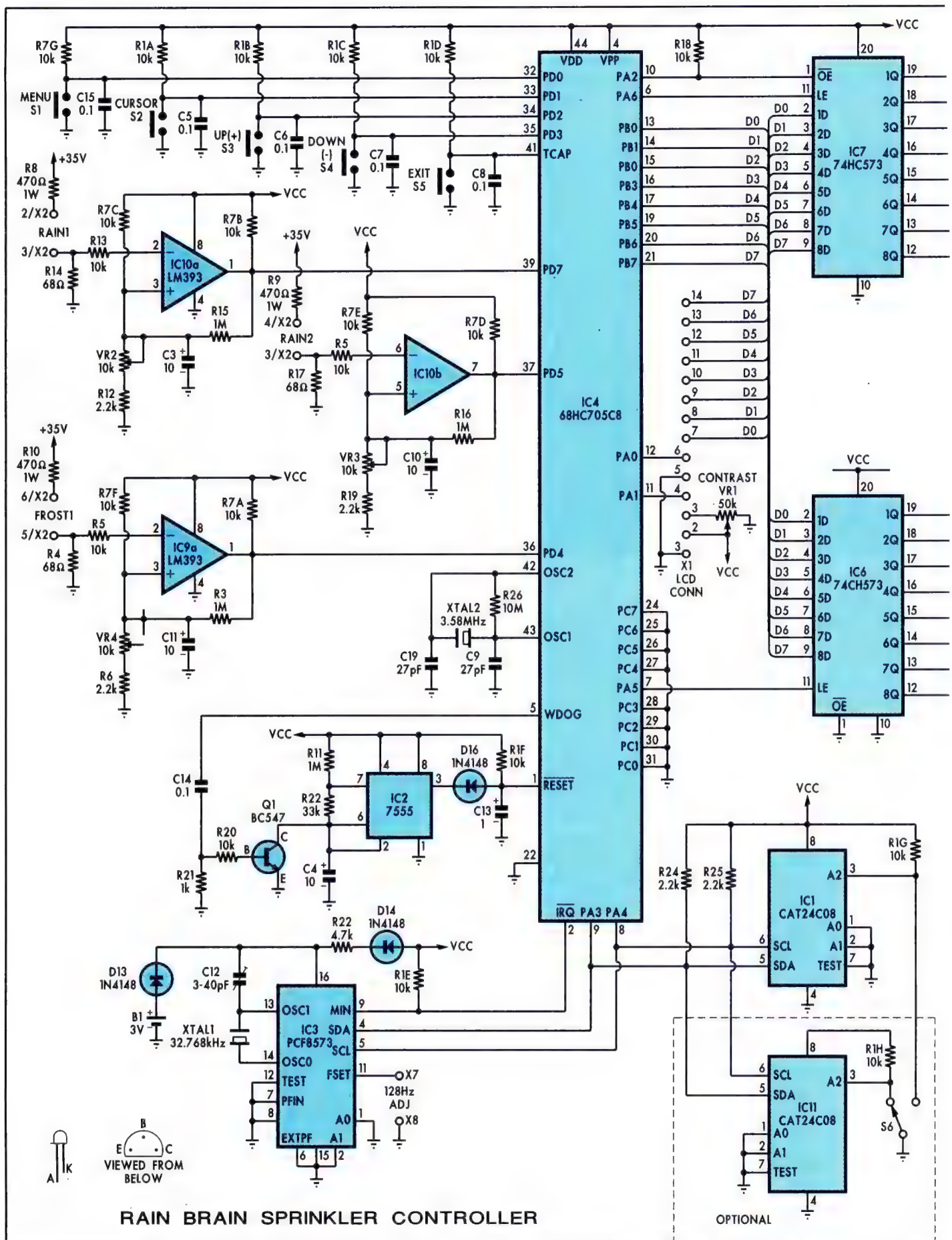



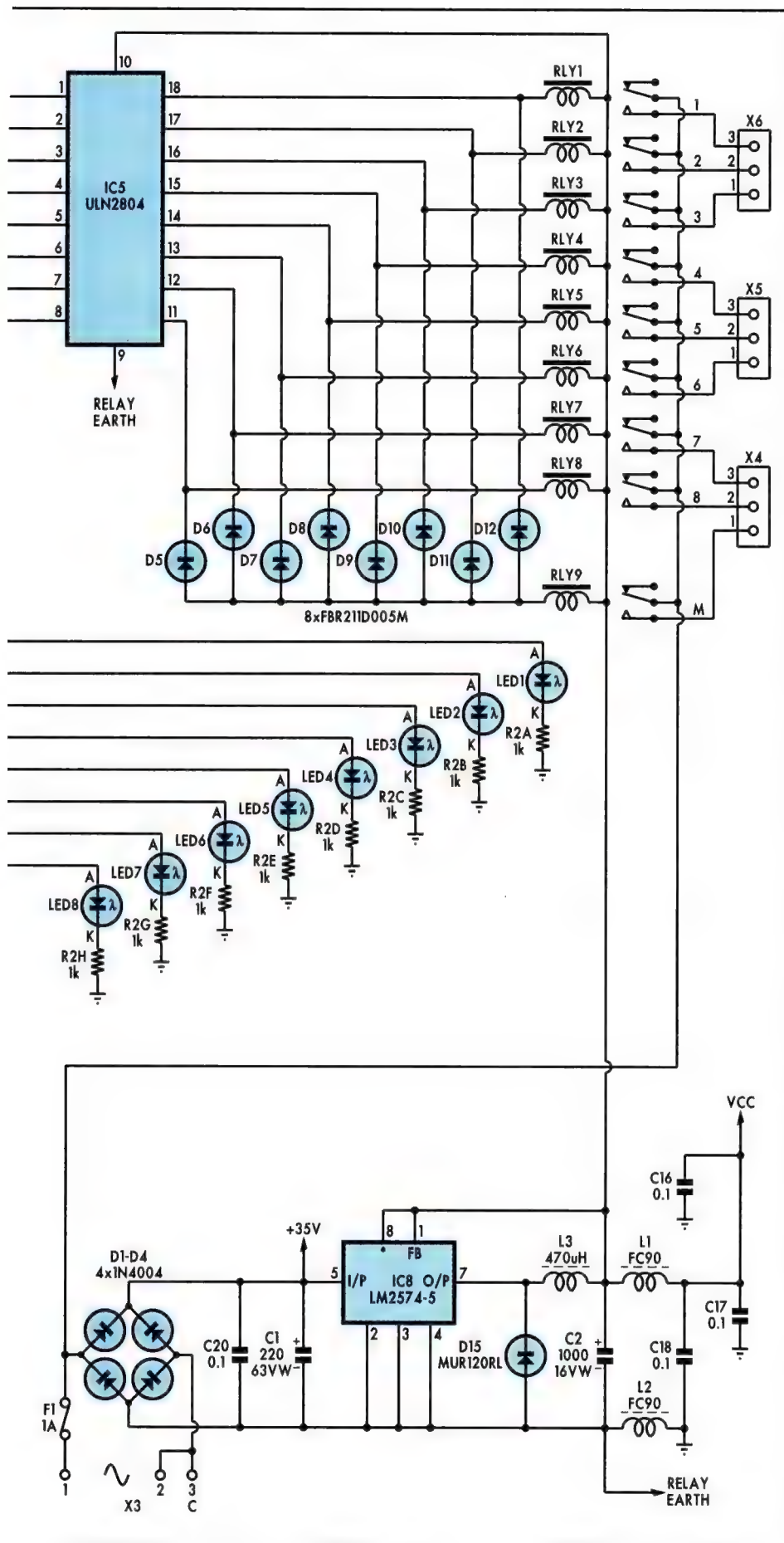


Fig.1 (left): the circuit is based on IC4, a 68HC705C8 microcontroller. IC3 is a real-time clock (RTC), while IC1 is an EEPROM and is used to store the programmed settings.

as a general-purpose timer. In these applications, the on-board relays can act as slaves to appropriately rated off-board relays, so that other equipment can be controlled.

## How it works

The circuit is fairly straightforward (Fig.1), with all the heavy work being done by the software in the microcontroller (IC4).

Starting with the power supply, diodes D1-D4 rectify the 24V AC input, which results in about 35V DC across C1. IC8 (LM2574-5) is from the "simple switcher" series from National Semiconductor and provides a very efficient method of providing a 5V rail to power the circuitry.

The resultant 5V across C2 is further decoupled by L1 and L2. These inductors attenuate any spikes generated by the solenoids as they switch on and off. Note that the relay driver (ULN2804, IC5) is supplied from the "noisier" 5V across C2.


C16, C17 and C18 are spread around the PC board to decouple the power supply. The circuit draws the following currents from a 24V AC plugpack under the following conditions: (1) all LEDs off = 26mA; (2) all LEDs on = 32mA; and (3) all LEDs and relays on = 88mA.

The microcontroller (IC4) uses a standard 3.58MHz crystal (Xtal2) as a timebase. A feature of this microcontroller is an internal watchdog function, called the Computer Operating Properly (or COP). I tried to get this to work but the maximum timeout period with this crystal is a bit over one second. This is a bit short and I eventually opted for a tried and tested alternative built around timer stage IC2.

The time function is supplied by real time clock stage IC3 (PCF8573), hereafter referred to as the RTC. This RTC chip interrupts the microcontroller every minute. Each time it receives an interrupt, the microcontroller reads the RTC and stores the time in an internal RAM buffer.

After this, it reads 12 bytes of



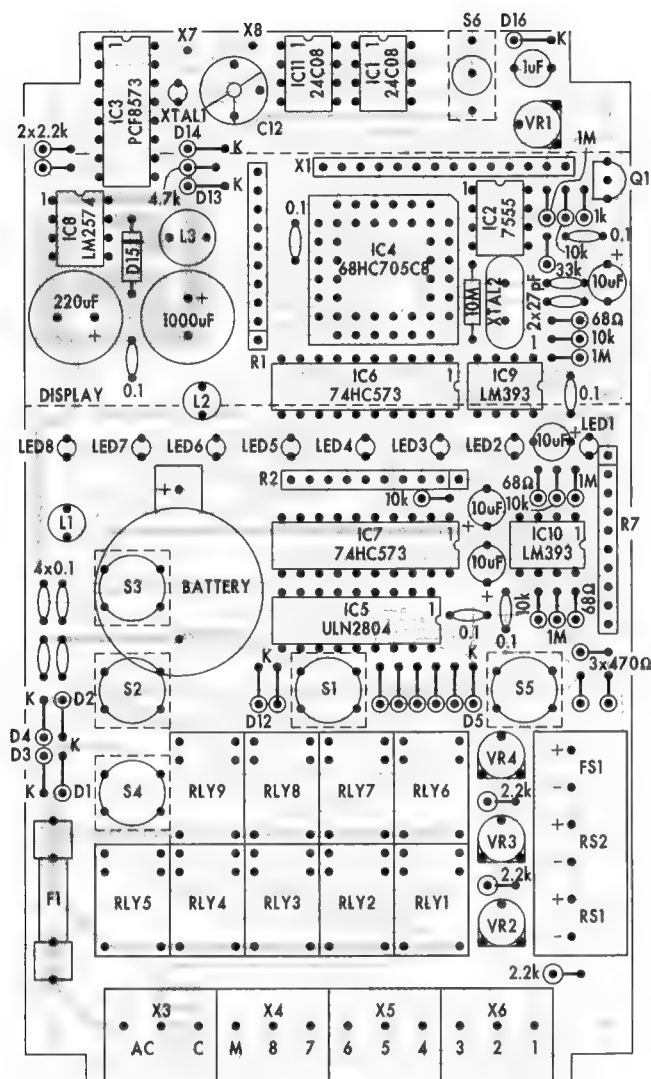

**Fig.2: install the parts on the PC board as shown here. Note that IC1, IC3, IC4 & IC11, the relays and the LCD should not be mounted until after an initial "smoke" test has been carried out (see text).**

EEPROM (IC1 or IC11) associated with cycle 1 of solenoid 8 and compares the stored start times with the current time and date. It then repeats the process 31 more times for the other cycles and solenoids (this process takes twice as long when program C is selected).

The LCD and the two 8-bit latches IC6 & IC7 (74HC573) share port B as a common data bus. When the microcontroller needs to send data to either latch, pin 11 of the required latch is pulsed high (by either PA5 or PA6). At reset, all port pins are initialised as inputs (high Z), therefore the OE pin (pin 1) of IC7 is held high by R18 until the latch is cleared and PA2 is made an output. This stops inadvertent operation of any relays until initialisation is complete.

The LCD data is validated by the E pin (pin 6, LCD connector). As the microcontroller is not required to read the internal RAM of the LCD display, the R/W pin can be tied low, which is write mode. VR1 is used to adjust the contrast of the display.

The two Rain Switch inputs (PD7 & PD5) are tested during the timer interrupt routine. Appropriate flags are

set if any of these inputs are activated. The temperature input (PD4) is read every minute, for one second exactly. During this time, writes to the LCD and LED flashing routines are disallowed, so as to prevent incorrect temperature measurements.

## Button switches

The button switches are connected directly to the microcontroller (PD0-PD4 & TCAP). An RC network attached to each pin provides a small amount of debounce, while the software does the rest.

Buttons S1-S4 (Menu, Cursor, Up, Down) are polled during the main loop, whereas button S5 (Exit) is connected to the TCAP input. The TCAP pin is an interrupt pin associated with the internal timer function. In this application, it is simply used to notify the microcontroller that the button was pressed in a manner similar to how a normal interrupt would be used.

## Watchdog timer

This circuit comprises a CMOS 7555 IC (IC2), configured as an astable multivibrator but normally prevented from oscillating. If IC4 is functioning correctly, PA7 (pin 5) is set to a logic 1 within the timer interrupt routine and cleared in the mainloop. The resulting waveform continually charges and discharges C14. This means that Q1 is continually turned on and off, which prevents C4 from charging up and thus disables IC2.

However, if the pulses from PA7 stop due to a spike causing the program to stop and/or crash, IC2 will begin to oscillate. After about 10 seconds, its pin 3 output will pull IC4's reset pin (pin 1) low via D16, thereby resetting the microcontroller. Note that the time-out period is set to 10 seconds to allow for the "dead time" during the EEPROM read cycle every minute. The timer interrupt interval is set to 5ms.

## The EEPROM

The EEPROM is an 8Kb device, internally organised as 1024 x 8 bits. Each cycle of each solenoid is allocated 12 bytes of the EEPROM (11 of these are used, with one spare). Another part of the EEPROM is set aside for storing "global" variables like the current year, the LED status, and whether "Rain Mode" is active or not.


Pin 3 (A2) of IC1 and IC11 is an address pin, which allows two of these chips to be connected onto the same I<sup>2</sup>C bus. The A2 pins are connected to either side of S6, which allows either of the EEPROMs to be switched into circuit.

The selected EEPROM is read at power up, to determine which mode it should be in (ie, "RAIN OFF" mode or just the Default mode) and which LEDs are active. At the next interrupt from the RTC (IC3), any cycle that satisfies the "On Time" conditions will be switched on. No settings will ever be lost!
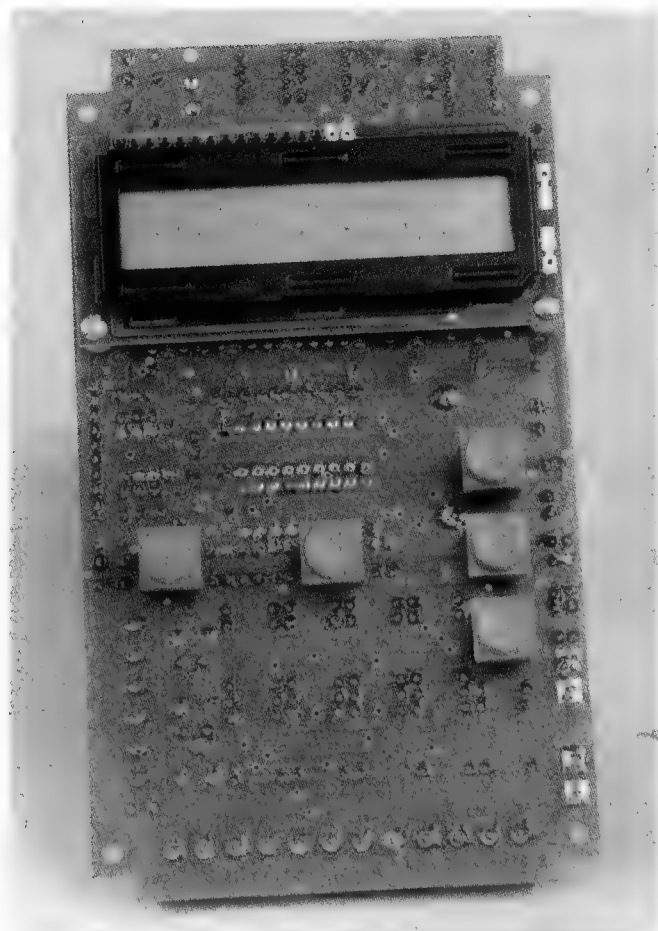
## Real time clock

The RTC chip (IC3) interrupts the microcontroller every minute, causing it to read the time. IC3 requires a 32.768kHz crystal (commonly called a "watch" crystal) for its internal dividers. The oscillator can be trimmed using C12 to provide very accurate time keeping. Note





The switches, the eight station indicator LEDs and the LCD are all installed on the reverse side of the board.

that the FSET pin (frequency SET) is brought out to a PC board pin to facilitate easy tuning using a frequency meter.

When power is lost from the main circuit, a 3V lithium battery (B1) cuts in and keeps IC3's oscillator going. The battery is held off via D14 and D13 when normal power is applied to the circuit. IC3 draws about 7 $\mu$ A when the power is off.

Note that if the HOURS or MINUTES setting is altered when setting the time, the seconds counter in the RTC will be reset. The DAY and MONTH settings do not cause the seconds counter to reset but the HOUR and MINUTE settings are written to. The YEAR and (P)rogram settings have no effect on the RTC.

### Rain/temperature inputs


The three input circuits are identical and are based on LM393 comparator ICs. VR2-VR4 are used to adjust the trip voltages, which can vary from about 0.9V to about 2V. Resistors R3, R15 & R16 (1M $\Omega$ ) provide hysteresis

to prevent the outputs from oscillating.

R8, R9 and R10 provide the current feed to the rain switches and temperature sensor circuit. The output circuits of the rain switch and temperature sensor act as constant current sinks. If the probes are wet, then the Rain Switch draws an extra 13mA compared to when the probes are dry. The current flows to ground via 68 $\Omega$  resistors R4, R14 & R17.

The extra current flowing when the probes are wet causes the voltage across these resistors to increase, which in turn causes the comparator to trip. Normally, the open collector outputs of the comparators are held high by 10k $\Omega$  pullup resistors. When they trip, the outputs turn on, thereby presenting a logic 0 to the microcontroller port pins (PD7, PD5 & PD4).

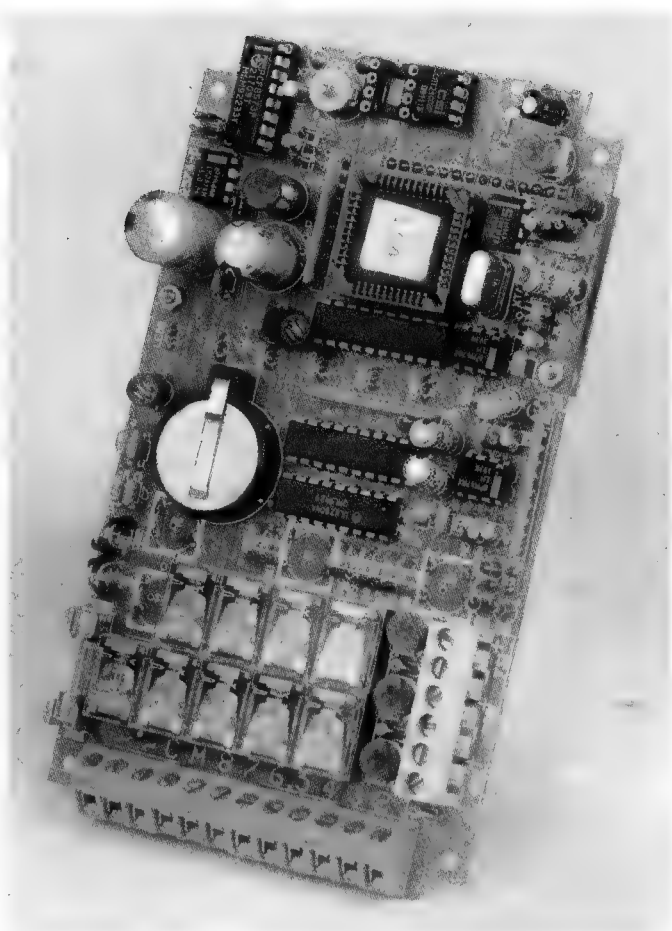The temperature input requires a frequency that is directly proportional to the temperature at a resolution of 50Hz/ $^{\circ}$ C. 1000Hz corresponds to 0 $^{\circ}$ C, 2000Hz corresponds to 20 $^{\circ}$ C and so on. When the temperature sensor is



The programmed data in the EEPROM is backed up by a 3V lithium cell. Take care with the orientation of IC4.

not connected, the temperature display will be -19.9 $^{\circ}$ C.


### Relay drivers & relays

IC7 drives IC5, a ULN2804 relay driver IC. This device has open collector outputs and can therefore be used to drive relays with an operating voltage different to that specified. To do this, the component side track marked "\*" (above the battery holder) must be cut. A wire running off to a separate power supply is then soldered into the via on the solder side, about 10mm below the "\*".

The controller can operate all of the specified relays at once if need be. Each relay draws about 41mA at 5V. This does not mean that all solenoids should be operated at once, however. This very much depends on the transformer that is used to power your sprinkler system. Most solenoids draw around 300mA when supplied by 24V AC.

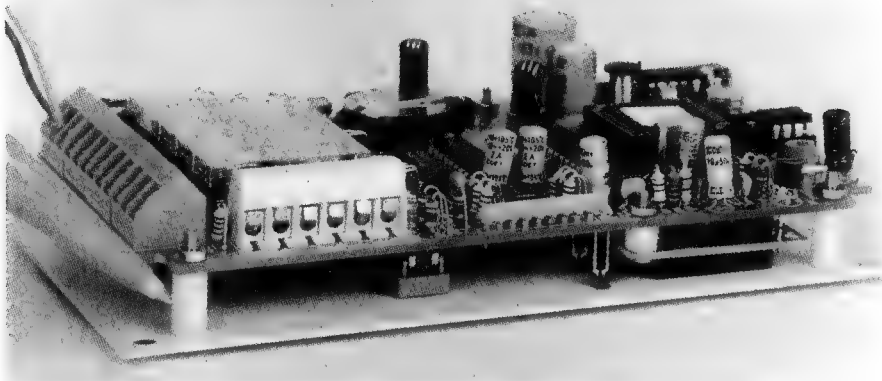Diodes D5-D12 form an 8-input diode AND gate. If any of the relays (RLY1-RLY8) is (are) switched on, then





The PC board is mounted on the front panel using 12mm spacers and machine screws and nuts. Similarly, the lower edge of the LCD module (near the LEDs) is secured to the PC board using 5mm spacers and machine screws and nuts.

the associated diode(s) will also be forward biased, thereby switching on RLY9 (the master relay). This relay can be used to switch on the master solenoid in a sprinkler system, or to start a pump in a rural situation.

## Manual operation

In addition to automatic operation, the solenoids can also be switched on manually. To do this, you simply select the solenoid with the Menu button, then press the Down button; the selected solenoid will immediately turn on, as indicated by the fast flashing LED. It will subsequently automatically switch off after the "Run Time" of cycle 4 (cycle 8 if program C) for that solenoid has expired.


If the "Run Time" is set to "00", then the solenoid will switch off at the next interrupt from the RTC. Note that this facility works whether the "RAIN OFF" mode is active or not.

## Construction

Construction of the Rain Brain is straightforward, since it is supplied as a complete kit. All the parts mount on a double-sided PC board with plated-through holes and a screened layout overlay, so that you can see at a glance where the parts go. As always, eyeball the PC board for any obvious faults before starting assembly.

Begin by fitting all the ICs and sockets (except the PLCC socket for IC4). The RTC IC (IC3) and the EEPROM(s) (IC1 & IC11) are the only ICs that require sockets. Do not use sockets for the other ICs. In particular, IC8 (LM2574-5) absolutely must be soldered to the PC board.

This done, fit the PLCC socket. This

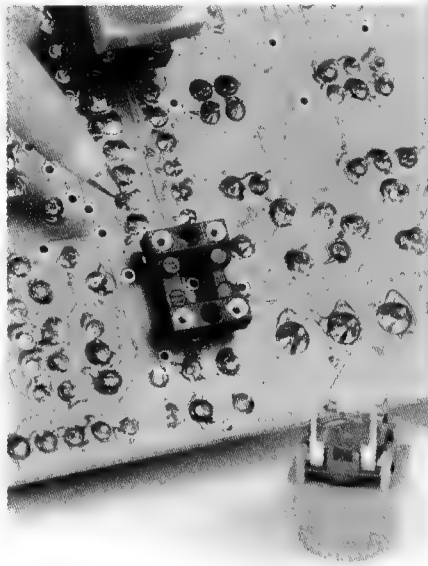

The five pushbutton switches are all mounted in modified 6-pin DIP sockets on the track side of the board. Note that two pins of each socket are removed – see text.

socket has one corner chamfered and this must match up with the screened overlay on the PC board. Also pin 1 on the PC board is square, and you will see a little ridge on the side of the socket that denotes pin 1. Do not plug the microcontroller in yet!

The three SIL resistor networks (R1, R2 and R7) should be installed next, noting that the pin with the dot goes into the square hole. Note that two of these resistor networks are 10k $\Omega$  types, while the other is a 1k $\Omega$  type so don't get them confused. All three can be either 9-pin or 10-pin types.

The following parts are mounted on the solder side of the board: LEDs 1-8 (discussed later), the five 6-pin DIP sockets, and the 14-pin SIL con-

necter for the liquid crystal display.

Pins 2 & 5 of the 6-pin DIP sockets (used to mount the push buttons) have to be cut out so that they won't interfere with the PC board (pushing the pins out with the hot soldering iron results a neater job). Solder in all five sockets, then turn the board over and fit the battery holder (don't fit the battery yet). This done, solder in the 14-pin LCD connector, remembering that it goes onto the solder side of the board (along with the five switch sockets).

Next, fit the four trimpots (VR1-VR4) and the trimmer capacitor (C12). Set VR2, VR3 and VR4 to midway, then install power supply components IC8, C1, C2, D15 and L3. Note that the cathode of D15 goes into the square hole.

The resistors can now all be installed. In particular, install R15 (1M $\Omega$  near pin 1 of IC10) so that its long lead goes into the top hole. The same goes for R16 (1M $\Omega$  below IC10), while R3 (1M $\Omega$  near pin 1 of IC9) should have its long lead to the left. The reason for this is that these long leads are used as test points when adjusting the comparator trip points.



The capacitors, diodes, the transistor and the two crystals can be fitted now. You will notice that all the diode cathode pads have square holes, as do all the positive pads of the electrolytic capacitors.

L1 and L2 have small lengths (2-3mm) of spaghetti sleeving fitted over their mounting leads so that they stand proud of the board. If only one EEPROM is to be installed, solder a link between the bottom two holes of S6 (marked SW1 on the screened overlay). This links the A2 pin of IC1 to ground.
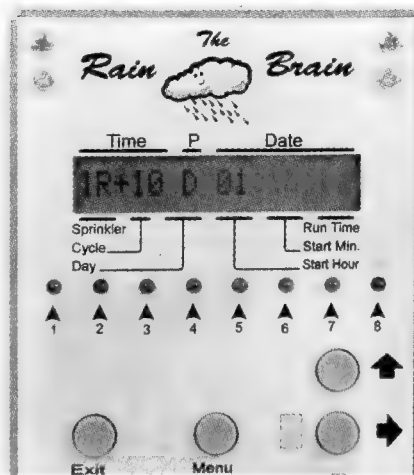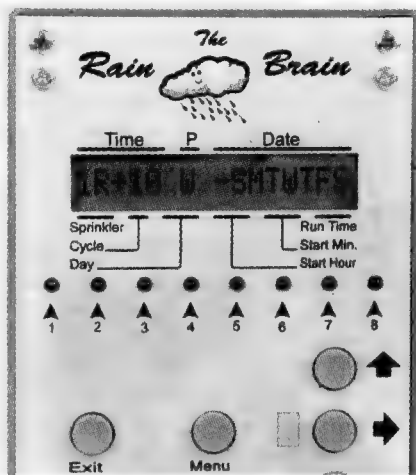
## Installing the LEDs

As mentioned earlier, the LEDs are mounted on the solder side of the board, so that they match up with clearance holes in the front panel. Insert each LED into its position, remembering that the cathode (short lead) goes into the square hole but do not solder any yet. This done, carefully fix the front panel to the PC board using 12mm spacers and machine screws and nuts – just install two spacers diagonally opposite each other, as this is only a temporary operation. Once the panel is on, manipulate the LEDs so that they fit into





These two photos show typical displays for the Auxiliary Functions menu. At left, rain sensor 1 has been enabled (1R), the temperature trip point is 10°C, the three-week cycle mode (W) has been selected, week 1 has been selected (—), and the sprinkler will turn on every day of this week. In the photo at right, the continuous schedule (D) mode has been selected and the sprinkler will turn on every day (01).

the appropriate holes, then solder them in from the component side and remove the front panel.

Now fit the fuse clips and the connector blocks to the PC board. Don't fit the LCD or the relays yet, as a smoke test needs to be done first!

### Smoke test

Before applying power, ensure that IC3, IC4, IC1, IC11 (if supplied) and the LCD have not been fitted. This done, connect a suitable power supply to the designated connectors and switch on.

Now check that 5V is present across the power supply pins of IC6 (or IC7); ie, between pins 20 & 10. If so, touch the top of each IC for a few seconds, particularly IC8. All the ICs should be cool to the touch. If all is well, switch off and plug in the rest of the ICs. Make sure that you install the microcontroller around the right way. The chamfered corner of the IC must match the chamfered corner of the socket.

### Installing the LCD

Before installing the LCD, the six tabs that secure the metal frame to the LCD board should be bent over slightly. This is to prevent possible contact with any of the leads protruding through the main PC board. Also check that none of the tabs is shorting to any of the fine tracks around the edges of the tab holes.

Next, turn VR1 clockwise until it stops, so that it is in the full contrast

position. This done, fit the LCD to the connector on the main board and force it down slightly so that it firmly grips the pins.

Now turn the power on, while making sure that nothing on the LCD board can short against the main board. You should be greeted with a message telling you to check the battery, a software version message for a second or two, and then the time and date display.

Assuming that all is well, the LCD can be permanently mounted. The lower edge of the LCD (near the LEDs) is secured to the main board using 5mm spacers and machine screws and nuts. Once these are fitted, judge the gap at the connector edge and solder

tack a pin. This done, check that the LCD board is parallel to the controller board, adjust it as necessary, then solder the rest of the pins.

By the way, all the LCDs are tested before they are packed into the kits, as are the microcontrollers. However, it is still nice to know that it works before soldering it in as it is an unpleasant job trying to unsolder them.

The five pushbutton switches can now be installed by fitting them to the previously installed DIP sockets (there's no need to solder them). Once they're in, the plastic switch caps can be clipped into position.

If you have purchased the additional memory kit, solder the wires to the toggle switch, then mount the switch in a convenient location on the side of the case. Make sure that this switch can not foul other parts on the main board when it is installed in the case.

Now the front panel can be refitted using the four 12mm spacers provided. This done, clip the lithium battery into its holder (positive side up), connect a power supply and switch on. The LCD should go through the same routine as above. Once the time has been programmed into the RTC, the battery flat message should not show at power up unless the battery is flat.

Note that, at this stage, the time display will have miscellaneous characters in the time and date fields.

### Memory initialisation

The next step is to put the memory into a known state. To do this, turn

### Where To Buy The Parts

Parts for the Rain Brain Sprinkler Controller are available as follows:

ITEM	PRICE	P&P
Rain Brain kit (excludes relays)	\$175.00	\$10.00
Relays - FBR211D005M (Price ea.; specify number required)	\$4.50	
Built & tested (relays extra)	\$225.00	\$10.00
Rain switch kit (Price ea.; specify number required)	\$25.00	\$2.00
Temperature probe kit	\$33.00	\$2.00
Optional memory kit	\$12.00	\$2.00
Optional super twist LCD with LED backlight upgrade	\$8.00	

Note 1: p&p is \$10.00 for Rain Brain kit plus any combination of other kits. Individual parts are also available (POA).

Note 2: Payment by cheque or money order to Mantis Micro Products. Send order to Graham Blowes, 38 Gamet St, Niddrie, 3402 Vic. Phone/fax (03) 9337 1917. For COD orders, you pay \$4.75 COD charge plus postage at the destination post office. The Post Office will notify you when the parcel arrives.



## PARTS LIST

1 double-sided PC board, code SPV6  
 1 plastic case with screened front panel  
 1 P1601 liquid crystal display (H1)  
 1 BH800 battery holder (BH1)  
 1 3V lithium battery (B1)  
 9 5V SPDT relays, FBR211CD005M (RLY1-9)  
 2 M205 fuse clips (FH1,FH2)  
 11A M205 fuse (F1)  
 2 ferrite (6-hole) inductors (L1,L2)  
 1 470µH inductor (L3)  
 1 50kΩ miniature horizontal trimpot (VR1)  
 3 10kΩ miniature horizontal trimpots (VR2-VR4)  
 1 44-pin PLCC IC socket  
 1 8-pin DIP socket  
 1 16-pin IC socket  
 5 momentary contact pushbutton switches plus plastic caps (S1-S5)  
 5 6-pin DIP sockets (for switches)  
 4 15mm x 3mm dia. machine screws plus nuts  
 4 12mm x 3mm dia. spacers  
 2 5mm x 3mm dia. spacers  
 1 14-way connector (X1, for LCD)  
 1 6-way terminal block (X2)  
 4 3-way terminal blocks (X3-X6)  
 2 PC pins (X7,X8)

### Semiconductors

1 CAT24C08P EEPROM (IC1)  
 1 LM7555 CMOS timer (IC2)  
 1 PCF8573P real time clock (IC3)  
 1 MC68HC705C8FN microcontroller (IC4)

1 ULN2804 8-channel driver (IC5)  
 2 74HC573 latches (IC6,IC7)  
 1 LM2574-5 5V switching regulator (IC8)  
 2 LM393 dual op amps (IC9,IC10)  
 1 BC548 transistor (Q1)  
 4 1N4004 silicon diodes (D1-D4)  
 11 1N4148 silicon diodes (D5-D14,D16)  
 1 MUR120RL fast recovery diode (D15)  
 8 3mm red LEDs (LED1-8)  
 1 32.768kHz crystal (Xtal1)  
 1 3.579545MHz crystal (Xtal2)

### Capacitors

1 1000µF 16VW electrolytic (C2)  
 1 220µF 63VW electrolytic (C1)  
 4 10µF 10VW electrolytic (C3,C4,C10,C11)  
 1 1µF 10VW electrolytic (C13)  
 10 0.1µF monolithic (C5-8,C14-18,C20)  
 2 27pF monolithic (C9,C19)  
 1 3-40pF trimmer capacitor (C12)

### Resistors (0.25W, 1%)

1 10MΩ 5 2.2kΩ  
 4 1MΩ 1 1kΩ  
 1 33kΩ 3 470Ω 1W  
 5 10kΩ 3 68Ω  
 1 4.7kΩ  
 2 10kΩ SIL resistor networks  
 1 1kΩ SIL resistor network

### Optional memory kit

1 CAT24C08P EEPROM (IC11)  
 1 8-pin DIP IC socket  
 1 SPDT switch (S6)

A "D" indicates that the date will be displayed in the default display. A "T" means that the temperature will be displayed instead of the date. Press the Down (↓) button to toggle from "D" to "T".

## Adjustments

The contrast pot (VR1) should already be set up. The range isn't very broad, so maximum is probably the best to start with (fully clockwise). The other pots (VR2-VR4) were originally set during construction.

Assuming that you are using the optional Mantis Rain Switches (available from the author), VR2 and VR3 can be further adjusted to set the trip voltages to 1.5V. This can be monitored by connecting the positive lead of your meter to the top lead of R15 for Rain Switch 1 (VR2), or to the top lead of R16 for Rain Switch 2 (VR3).

To adjust IC3's oscillator, connect a frequency meter to the pin marked "128Hz" (X7) and the ground lead to the GND pin (X8) nearby. Now tune C12 until a display of "128.0000 Hz" is obtained. Note that the frequency counters built into some multimeters will probably prove unsuitable, as they do not have the resolution required.

If a frequency meter is unavailable, check the time against a known good source and tweak the trimmer until the unit keeps good time.

## Installation

The case is not waterproof, so mount it on a wall in the garage or in some other sheltered location. If you must have it outside, the controller will have to be installed in a waterproof case.

You will have to drill two rows of five holes (5mm dia.) in the bottom of the case to provide access for the external wiring. Position one row close to the back of the case and the other row about 5mm away.

## Programming

At first sight, programming this controller may seem a little daunting but it only takes about 20 minutes to get the hang of things. If you can program a VCR, you can program this device.

We don't have space to include the programming instructions here but full instructions will be supplied with the kit. **SC**

off the power, hold down the Menu and Cursor (⇒) buttons, and turn the power back on. This time, the LCD will tell you to press the Menu button. Once this is done, the "Config" menu will be displayed. This consists of three options:

(1). "M" is memory initialisation. Press the Down (↓) button to initialise the memory. As each block of 16 bytes is initialised, a LED lights. The LEDs chase each other from left to right, eight times. This routine also acts as a fault locator. If more than one LED lights at the same time, then there is a short circuit on the port B data bus.

Each cycle is set to 00:00:00 which is actually a start time of midnight, with a run time of 00 minutes. All cycles and both rain switches are enabled. The temperature trip point is off. The 3-week cycle is active, with all days set to on (uppercase).

(2). Press the Cursor (⇒) button to move to the next option (A) which is the VR4 adjusting mode. This mode continually reads the temperature and displays the result. If VR4 is adjusted correctly, the display will show a steady temperature. How to do this is included as part of the temperature sensor kit.

(3). D is the default display setting.



# PRODUCT SHOWCASE

## Tektronix P5200 high-voltage differential probe

**The measurement of high voltage or AC mains voltage signals presents problems that are not easily overcome with standard dual channel oscilloscopes. One solution is to use a Tektronix P5200 high voltage differential probe.**

The attenuators of most general purpose oscilloscopes provide a maximum input sensitivity of 5V/division. With the screen displaying eight vertical divisions this means that the maximum input signal can only be 40V peak-to-peak with a direct probe or 400V peak-to-peak using a 10:1 divider probe. Larger signals can be displayed using the variable input control but then the amplitude measurement facility is lost.

If the signal to be measured is a mains AC waveform or other higher voltage which is not ground referenced then it can be displayed using a dual trace oscilloscope in the Add mode. Once again the maximum calibrated display voltage will be 400V peak to peak. As an alternative, some organisations adopt the practice of using an oscilloscope with its mains earth disconnected to display floating and mains voltages. This is a highly dangerous procedure with nothing to recommend it.

Displaying the mains voltage waveform using a regular probe with the tip connected to the active lead and the earth clip connected to the neutral is also a dangerous procedure. Transposition of the live and neutral connections to the probe is always a possibility and if this mistake is made then the best that can happen is a blown fuse and the worst is electrocution.

What is really required is an instrument with a differential input,

some level of signal attenuation and a single ended output signal to apply to the following measuring equipment. To cater for signals with fast rising wave fronts – eg; SCR circuits, switchmode supplies, etc – it should also have a wide bandwidth and fast rise time.

The Tektronix P5200 high voltage differential probe meets all these requirements and allows the aforementioned measurements to be made easily and safely. It is supplied with two sets of connectors and a 9VDC 1A plug-



**Table 1: Specifications**

Maximum applied voltage between either input and ground .....	1kV (DC + peak AC)
Maximum applied voltage between inputs .....	1.3kV (DC + peak AC)
Rise time .....	<14ns in 1/50 range
DC CMRR .....	>5000:1 at 500VDC
AC CMRR .....	60Hz >10000:1; 100kHz >300:1; 1MHz >300:1
Bandwidth .....	DC to 25MHz (-3dB) in 1/50 range
Maximum operating input voltage .....	1/500 differential 1.3kV (DC + AC peak); 1/500 common mode, 1kV (DC + AC peak); 1/50 differential, 130V (DC + AC peak); 1/50 common mode, 1kV (DC + AC peak)
Range accuracy .....	±3% between 20-30°C after 20 minute warmup.
Input impedance .....	8MΩ + 3.5pF between inputs; 4MΩ + 7pF each input to ground
DC output drift .....	±0.5mV/°C
Propagation delay .....	20ns
Operating temperature range .....	0-40°C



pack power supply. One pair of connectors are long reach plunger probes and the other pair are heavy duty, double insulated crocodile clips.

Its dimensions are 185mm (L) x 66mm (W) x 32mm (H). Two 500mm long input connectors are at one end of the case and these are terminated with shrouded plugs to fit the probe connectors. At the other end of the case is a 1500mm long output lead terminated with a moulded plug that carries an input socket for the plug-pack and a 300mm long coaxial lead terminated with a BNC male plug to supply output to the measuring instrument which will usually be an oscilloscope.

The face of the probe case features a pushbutton switch which provides 1/500 or 1/50 attenuation to the input signal. There are also LEDs for Power and Over Range and a table showing the effective volts/division of the combined probe plus oscilloscope for different settings of the oscilloscope's input attenuator. Output level from the probe is a maximum of 2.6V.

The specifications for the P5200 are shown in Table 1.

We used a sample P5200 in our


laboratory and found that it does all that is claimed for it. It enables safe and accurate measurements when the source is not referenced to ground, particularly where mains voltage signals are concerned. In addition, it offers a much higher common mode rejection ratio than any typical dual channel oscilloscope when used in the "Add" mode – an important advantage.

The Tektronix P5200 is priced at \$658 plus sales tax where applicable. For further information, contact Tektronix Australia Pty Ltd, 80 Waterloo Rd, North Ryde, NSW 2113. Phone (02) 888 7066 or fax (02) 888 0125.
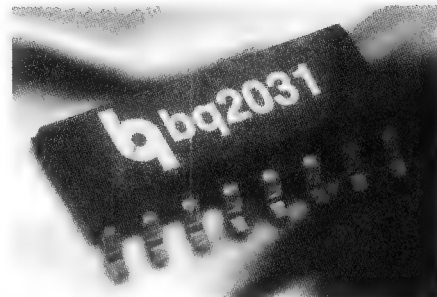
## Fast-charger IC for lead-acid batteries

Reptechnic has introduced the Benchmarq bq2031 lead acid fast charge IC. This incorporates current and voltage regulation with fast charge control to produce a highly cost effective fast charge system.

Available in a 16-pin narrow DIP or SOIC package, the bq2031 is designed for controlling constant voltage and constant current charging of lead acid



batteries in emergency lighting, backup power, industrial equipment and consumer electronics applications. It can be configured for linear or gated current regulation applications.

The bq2031 meets the battery manufacturers' charge recommendations for both cyclic and float/maintenance charge. It includes a flexible pulse width modulation regulator which is suitable for high efficiency switch-mode designs. Direct LED control outputs are featured for displaying charge status and fault conditions.

Pre-charge qualification tests have been performed on the device for shorted, open or damaged cells, allowing it to condition the battery for fast charge. Charging is also qualified by selectable temperature and voltage

## KITS-R-US

PO Box 314 Blackwood SA 5051 Ph 018 806794

### TRANSMITTER KITS

- FMTX1 \$49: a simple to build 2.5 watt free running CD level input, FM band runs from 12-24VDC.
- FMTX2B \$49: the best transmitter on the market, FM-Band XTAL locked on 100MHz. CD level input 3 stage design, very stable up to 30mW RF output.
- FMTX2A \$49: a universal digital stereo encoder for use on either of our transmitters. XTAL locked.
- FMTX5 \$99: both FMTX2A & FMTX2B on one PCB.
- FMTX10 \$599: a complete FMTX5 built and tested, enclosed in a quality case with plugpack, DIN input connector for audio and a 1/2mtr internal antenna, also available in 1U rack mount with balanced cannon input sockets, dual VU meter and BNC RF \$1299. Ideal for cable FM or broadcast transmission over distances of up to 300 mtrs, i.e. drive-in theatres, sports arenas, football grounds up to 50mW RF out.
- FMTX10B \$2599: same as rack mount version but also includes dual SCA coder with 67 & 92kHz subcarriers.

### AUDIO

- DIGI-125 Audio Power Amp: this has been the most popular kit of all time with some 24,000 PCBs being sold since 1987. Easy to build, small in size, high power, clever design, uses KISS principle. Manufacturing rights available with full technical support and PCB CAD artwork available to companies for a small royalty. 200 Watt Kit \$29, PCB only \$4.95.
- AEM 35 Watt Single Chip Audio Power Amp \$19.95: this is an ideal amp for the beginner to construct; uses an LM1875 chip and a few parts on a 1 inch square PCB.
- Low Distortion Balanced Line Audio Oscillator Kit \$69: designed to pump out line up tone around studio complexes at 400Hz or any other audio frequency you wish to us. Maximum output +21dBm.
- MONO Audio DA Amp Kit, 15 splits: \$69.
- Universal BALUN Balanced Line Converter Kit \$69: converts what you have to what you want, unbalanced to balanced or vice versa. Adjustable gain. Stereo.

### COMPUTERS

- Max I/O Card for PCs Kit \$169: originally published in Silicon Chip, this is a real low cost way to interface to the outside world from your PC, 7 relays, 8 TTL inputs, ADC & DAC, stepper motor drive/open collector 1 amp outputs. Sample software in basic supplied on disk.
- IBM PC 8255 24 Line I/O Card Kit \$69, PCB \$39: described in ETI, this board is easy to construct with only 3 chips and a double sided plated through hole PCB. Any of the 24 lines can be used as an input or output. Good value.
- Professional 19" Rack Mount PC Case: \$999.
- All-In-One 486SLC-33 CPU Board \$799: includes dual serial, games, printer floppy & IDE hard disk drive interface, up to 4Mb RAM 1/2 size card.
- PC104 486SLC CPU Board with 2Mb RAM included: 2 serial, printer, floppy & IDE hard disk \$999; VGA PC104 card \$399.

### KIT WARRANTY – CHECK THIS OUT!!!

If your kit does not work, provided good workmanship has been applied in assembly and all original parts have been correctly assembled, we will repair your kit FREE if returned within 14 days of purchase. Your only cost is postage both ways. Now, that's a WARRANTY!

KITS-R-US sell the entire range of designs by Graham Dicker. The designer has not extended his agreement with the previous distributor, PC Computers, in Adelaide. All products can be purchased with Visa/ Bankcard by phone and shipped overnight via Australia EXPRESS POST for \$6.80 per order. You can speak to the designer Mon-Fri direct from 6-7pm or place orders 24 hours a day on: PH 018 80 6794; FAX 08 270 3175.

## NOT COMING TO A NEWSAGENT NEAR YOU!



The new 1996 AV-COMM SATELLITE TV CATALOGUE, contains up to the minute information on all available satellites and equipment needed to receive them.

Contains detailed information on over 200 products covering all aspects of Satellite Television Reception.

For your FREE copy of the new 1996 AV-COMM CATALOGUE simply complete the coupon and send to: AV-COMM PTY. LTD, P.O. Box 225, Balgowlah NSW 2093.

### AV-COMM PTY LTD

A.C.N. 002 174 478

198 Condamine Street,  
Balgowlah NSW 2093

Tel: (02) 9949 7417/9948 2667  
Fax: (02) 9949 7095

YES Garry, please send me a FREE copy of the 1996 AV-COMM Satellite TV Catalogue.

Name: \_\_\_\_\_

Address: \_\_\_\_\_


Postcode: \_\_\_\_\_

Phone: ( ) \_\_\_\_\_



## PCB POWER TRANSFORMERS

1VA to 25VA

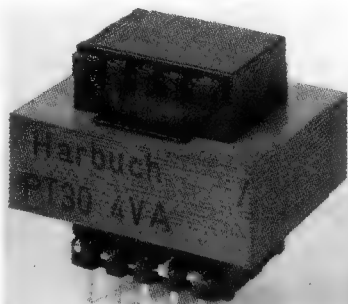

Manufactured in Australia  
**Harbuch Electronics Pty Ltd**  
 9/40 Leighton Pl. HORNSBY 2077  
 Ph (02) 476-5854 Fx (02) 476-3231

limits. Key specifications include temperature, float voltage reference, pin selectable charge and maintenance modes, and pin selectable charge termination by maximum threshold voltage, minimum current and maximum time.

A switchmode development system, the DV2031S1, is available to allow

designers to experiment with the bq2031. For further information, contact Reptechnic, 3/36 Bydown St, Neutral Bay, NSW 2089. Phone (02) 9953 9844.

## Jaycar kits now made under AS9002

The head office, warehouse and kit department of Jaycar Electronics has successfully passed all requirements and has been accredited to AS/NZ ISO 9002:1994.

"We realised that sooner or later we would have to seek this level of quality of management, documentation and quality control," commented Managing Director, Gary Johnston. "As it turned out, our existing organisation was close to the high standards required anyway, so achieving the AS9002 level of quality was not particularly difficult. Our kits have always been very high quality. Now we have independent proof that they are."

According to Mr Johnston, the quality accreditation is part of an ongoing commitment by Jaycar to provide a high standard of service in the industry.

## Pocket-sized fax machine & organiser

Now available at Dick Smith Electronics, the Handifax 1000 is a 256K electronic personal organiser and fax machine in one. In a lightweight, compact 72 x 198mm unit, Handifax 1000 gives you the capability of faxing your colleagues and clients anywhere, any time, by simply using it in conjunction with a standard touch tone telephone or analog mobile phone.

Simply type the message you want to fax, place the handset of the telephone or mobile phone on the acous-

tic coupler speaker and microphone, dial the fax machine you are calling and press SEND.

Handifax 1000 can communicate with any standard fax machine at speeds of up to 9600 bps. Quick and simple to use, it will hold up to 120 faxable pages and its auto dialling facility ensures that there is no need to manually dial numbers or access codes. The unit has built-in fax cover pages and the ability to customise fax headers, standard orders, invoices, etc.


With a 256K memory, Handifax 1000 also doubles as a personal organiser, capable of storing more than 3500 entries. A 7-digit password can be used to protect all data. An optional PC interface allows users to back up and store information on any standard IBM compatible PC.

The Handifax comes complete with an operation manual, an instruction video and is available at all Dick Smith Electronics stores for just \$699. **SC**


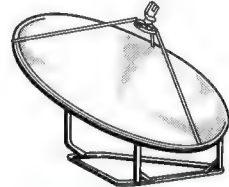
# YOU CAN NOW AFFORD YOUR OWN SATELLITE TV SYSTEM

For many years you have probably looked at satellite TV systems and thought "one day"



Your own K-band system from only:

**\$995**

## HERE'S WHAT YOU GET:

- Prime focus dish configured to your location.
- Super low noise LNB/feedhorn.
- 25m low loss coaxial cable.
- DYNALINK 50 channel stereo satellite receiver, with remote control. Pre-programmed to Optus frequencies.
- Pointing co-ordinates for your location.

## BEWARE OF IMITATORS

**Direct Importer: AV-COMM PTY. LTD.**

PO BOX 225, Balgowlah NSW 2093  
 Tel: (02) 9949 7417 Fax: (02) 9949 7095

Ask about our regular newsletters and Customer BBS. Send coupon for your free info pack, listing all items and prices.

**YES GARRY, please send me more information on K-band satellite systems.**

Name: \_\_\_\_\_

Address: \_\_\_\_\_

\_\_\_\_\_  
 P'code: \_\_\_\_\_

Phone: \_\_\_\_\_

ACN 002 174 478



# ALTRONICS COMPONENTS

Fax Order Line: (09) 328 3487



## ALTRONICS

**For Ultra Quick delivery.**

Phone Order on 1-800 999 007.


JetService Delivery - next day all capital cities and suburbs, please add 24 - 48 hours for country clients.

Regards, Jack O'Donnell, Managing Director

### EPROM Emulator Kit

(See EA Dec '95) This EPROM emulator allows you to do away with EPROM's whilst in the prototyping stage of product development. The emulator is connected to a spare parallel port on your computer and also the 'target' board. The EPROM file (that is normally downloaded into the EPROM), is then transferred into the emulator by copying the file to the parallel port. This process saves repetitively "blowing" new EPROM's with each modification to the program. Emulates 2764, 27128, 27256 and 27512 EPROM's.

K 9530 **Just \$149**

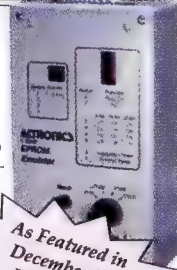

As Featured in  
December '95  
Electronics  
Australia

### Sub-Woofer Controller Kit

**Add Incredible Bass to Your Hi-Fi or Home Theatre System!**

(See SC Dec '95) A very exciting subwoofer adaptor design published in Silicon Chip Magazine. **High level inputs** enables simple parallel connection to either left or right stereo speaker. **Low level inputs** allows connection to surround sound subwoofer output or standard stereo signal, eg CD, VCR etc. **Other features** of this excellent design includes: • Variable filter output frequency • Inbuilt compressor/limiter prevents over-drive clipping • Subsonic filter (below 15Hz) • Auto input signal sensing and 24V power up facility for external sub power amplifier • "In Phase" and "Out of Phase" outputs enable bridge mode output if desired. Very compact, only 200W x 160D x 70H mm. Two versions available, PCB and components kit only (K 5562), or complete with a case, power supply and PCB (K 5563).

K 5562 Short Form Version (PCB & Parts Only) **\$49**

M 9120 12V AC Pluggack to Suit K 5562 **\$12.95**

K 5563 Full Version (Includes PCB, Components, Case & Power Supply) **\$99**

### Impedance Meter Kit

Measuring a transformer with a standard ohm meter will not give accurate results because it is measuring with a DC signal, not AC. This invaluable unit is fantastic for checking transformers and speaker impedances. For those people dealing in PA equipment, the built in tone generator enables an entire PA system to be checked before the amplifiers are connected. Uses one 9 Volt battery. (Not supplied). Three ranges enable accurate measurement of 2 - 20,000 ohms. Accuracy mid range typically  $\pm 5\%$ .



**Great for measuring:**  
• Speaker impedances  
• Line transformer / audio transformer impedance and reflected impedance  
etc • Speaker circuit total impedance & more.

K 2550 Kit Version **\$99**

K 2551 Fully Built & Tested Version **\$159**

### High Efficiency Fluoro Inverter Kit

(See SC Nov '93) Ideal for camping, fixing cars etc. This circuit will drive a standard 40 Watt fluoro tube from a 12 volt source. Being a fluoro light, it draws less current than an incandescent globe. Features flicker free starting/running, reverse polarity protection and faulty tube protection. Globe and housing not included. Requires 11 to 14V DC power source. Suitable for 18, 20 36 and 40W globes. Low EMF radiation.

K 6370 **\$69.00**



### Signal Comparator Kit

(See EA Aug '93) If you have ever tried to fix a circuit without a circuit diagram you will know how frustrating it can be. If you have an operational unit this can ease the pain but still, difficulties can be incurred. This kit could help. It can compare two circuits point to point and will indicate any difference between them.

K 2563 Normally \$39.95

This Month Only **\$29**



### PC Based EPROM Programmer Kit

(See EA Sept '93) This is a great new kit for programming EPROM's from 2716 to 27256. Compares favourably against commercial units costing \$55 more. This kit puts you in the driving seat for under \$100. It is flexible enough to be able to program 12.5, 21 and 25V EPROM's/EEPROM's.

K 9525 **\$97.50**

K 9526 3.5" PC Software to Suit **\$19.95**

A must for the  
Experimenter!



### 50W Mosfet Amp Module Kit

This great module features moderate power output at low harmonic distortion. Simple to build and compact in size this unit makes a great replacement module for your old Hi-Fi or buy two and make your own stereo amplifier. Requires  $\pm 50V$  DC supply.

Power Output: .....50W into 8 $\Omega$   
Freq. Response: .....25Hz-20KHz,  $\pm 1dB$

Input Sensitivity: .....1V RMS  
T.H.D.: .....0.05%

K 5115 **\$54.95**



Ultra  
Compact  
Design!

### Ignition Killer Kit

(See SC Dec '95) There are many ways of theft prevention for your vehicle. Disabling the ignition is perhaps one of the better methods, as it can totally immobilise the car. This ignition killer will help prevent your car from being stolen by producing erratic behaviour in the ignition system. The thief will suspect a problem with the car and leave it.

K 4380 **\$29.95**



**NEW**

### Digital Announcement Recorder Kit

(See EA Feb '95) This kit is an extremely flexible microprocessor controlled eight channel digital voice recorder.

Requires no battery back up for memory. Will record up to 8 different messages, with a total time up to 16 seconds. Each message can be individually triggered. Features chime function, an on-board 2 watt amplifier, negative or positive trigger, once only or recycling announcement function etc.

K 9580 **\$109**



1000's Uses Include  
Car Warning Alert, Alarm  
Systems, Door Bell etc.

### Auxiliary Battery Manager

(See EA Jan '96) Ideal for four wheel drives, trucks or any lead acid battery application. This is a 'smart' manager for an auxiliary lead acid 12V battery. Charges the auxiliary cell after the main cell has been recharged. Unit features controlled current charging for flat auxiliaries and full current charging when its terminal voltage rises above 11V. Also, this unit isolates the auxiliary battery from the electrical system when the ignition is off.

K 4330 **\$49.95**



**NEW**

### Guitar Headphone Amplifier Kit

(See SC May '95) Now you can practice your guitar at any time by using this low cost amplifier. It provides ample power for headphones so that you can play to your heart's content without disturbing the rest of the household or your neighbours. Simply plug in your guitar, headphones and a 12V AC power supply (not included).



K 5537 Normally \$29.95 Now **\$25**  
M 9120 12V AC Pluggack to Suit **\$12.95**

### Digital Storage C.R.O.

### Adaptor Kit for P.C.'s

(See EA Jan '93)

This great kit enables a P.C. user to capture a waveform and zoom in to segments of interest then save them to disc. The unit has 32K of storage memory and a sampling rate of over 600K samples per second. Input level of up to 2.5 Volt. Full sampling rate between 15K s/s to over 600K s/s. Input impedance of 1M ohm.


K 2805 Normally \$63.50

This Month Only **\$55**

K 2812 PC 3.5" Disk Software to Suit **\$29.95**
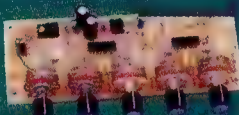
### 5 Band Graphic Equaliser Kit

(See SC Dec '95) Liven up your keyboard, guitar or



music system with this 5 band graphic equaliser. It uses only a few low cost parts and will vastly improve the versatility of your sound system. Bands are centred at 63Hz, 250Hz, 1kHz, 4kHz and 18kHz, with a  $\pm 12dB$  boost/cut adjustable level on each band. Requires  $\pm 15V$  power supply (not included).

K 5305 **\$39.95**

**1-800 999 007 PERTH (09) 328 1599**



# OVERNIGHT DELIVERY

## The Powerhouse 600W & 1200W Inverters

(See EA Feb '92) These Power Inverters will provide all your power requirements from a heavy duty 12 or 24V battery. Using the latest Mosfet output stage and toroidal transformer the inverters are both efficient and will deliver high surge currents. The Powerhouse has been designed not only for rugged operation but for ease of construction. The kits come to you in a fully drilled, pre punched chassis complete with silk screened front panel. Assembly of the kit is simplified as the majority of components mount on a single PCB. Thus virtually eliminating all external terminations. Suitable for use in camping, boating, fishing, mining, farming, remote settlements etc.

**Now with Improved Circuitry!**

K 6776 12V Input, 600W Kit Version **\$535**  
K 6778 24V Input, 600W Kit Version

K 6796 1200W Kit Version **\$799**  
K 6798 1200W Kit Version

## At Last - An Accurate Digital LCR Meter

In the past multimeters including inductance and capacitance ranges have been relatively mediocre in their performance. This new model will measure inductance, capacitance and AC resistance with great accuracy! Ideally suited for speaker crossover design and transformer/coil manufacture.

Supplied complete with two sets of leads and inbuilt sockets for direct measurement of inductors, capacitors or resistors. Includes integral bench stand.

**Resistance Ranges:** .....20, 200, 2k, 20k, 200k, 2M, 20M

**Capacitance Ranges:** .....200pF, 2nF, 20nF, 200nF, 2µF, 20µF, 200µF

**Inductance Ranges:** 2mH, 20mH, 200mH, 2H, 20H, 200H

**Accuracy:** .....Better than 5%

Q 1010 Normally \$199, Now Only **\$149**

## True RMS Digital Multimeter with RS-232

Supplied with high quality hard carry case and silicon test leads. This 3.75 digit 4000 count digital multimeter would have to be one of the best meters we have seen. Features include menu driven functions (no complicated instructions to remember), large backlit display, timer function, 20 amp current scale and many more. Other Features: • RS-232 Mode • True RMS mode • Large display includes main and sub displays with bargraph • 10 Location memory • Stop watch/pre-settable count down timer • Minimum, maximum, average and relative modes • Decibel measurement • Capacitance and inductance measurement • Temperature mode (°C and °F) • Pulse signal generator for logic and audible testing etc • Continuity and diode test • Logic test • Auto power "off" and "keep on" mode • 20A current range • Warning buzzer sounds when leads are incorrectly inserted in the 20A current mode • Back lit display • Data hold and run mode • Low battery indication • Overload protection • Safety design in compliance with UL 1244 and VDE0411

**Specifications & Ranges Available:**

DC Volt: .....400mV, 4V, 40V, 400V, 1000V  
AC Volt: .....4V, 40V, 400V, 750V  
DC Current: .....400µA, 400mA, 20A  
AC Current: .....400µA, 400mA, 20A  
Frequency: .....10kHz, 100kHz, 1MHz, 10MHz  
Resistance: 400Ω, 4kΩ, 40kΩ, 400kΩ, 4MΩ, 40MΩ  
Capacitance: .....100µF  
Inductance: .....100H  
Temperature: .....-17° - 1093° C (0° - 2000° F)  
Display: .....3.75 digit, 4000 count LCD

Q 1098 **\$299**

Q 1092 K Type Temperature Probe to Suit \$22.00

Q 1093 Protective Carry Holster to Suit \$13.50



**Includes Heavy Duty Battery Leads!**



## PCB Spacers

We are massively over-stocked with incorrectly supplied PCB spacers - incorrect because they have an odd UNC4/40 thread. Although perfectly fine with the correct bolt, we are unable to sell them separately. So out they go at never to be repeated prices. All are quality heavy duty nickel plated brass.

**All are supplied in packs of 100 spacers with 200 6mm bolts.**

HX1391 10mm Spacer **\$7.50**

HX1394 15mm Spacer **\$10**

HX1397 25mm Spacer **\$15**

**Massive Savings on Regular Prices. Save Up to 60%**



**Highly Recommended for Scientific Research & Development Work**

**Includes Software for DOS & Windows. Will Graph, Sample, Display all Multimeter Functions!**

## Famous Labtech 20MHz Dual Trace Oscilloscope

This model is a dual trace, 20MHz oscilloscope with a high brightness CRT. The vertical amplifiers have high sensitivity of 5mV/div and a frequency characteristic response with a smooth roll off exceeding 20MHz. The TV sync. signal operator circuit is provided to ensure stable observation of video signals. Triggering is obtained by sampling the AC power waveform, external waveform or internally generated trigger.

Q 0156 Normally **\$729.00**

**This Month Only \$649**

Q 0175 Cro Probes to Suit **\$39.95** Each

## Polypropylene Speakers

These fantastic speakers are ideal replacement speakers or for your own speaker design. The lightweight plastic cones offer levels of performance above that of conventional cardboard cones. The cone is more rigid and does not "break-up" (flex) as much as its counterparts.

	Watts RMS	Watts Max	Normally	This Month
C 3055 6.5" Woofer/Midrange	30W	50W	\$29.95	\$22.50
C 3060 8" Woofer	60W	100W	\$59.95	\$44.95
C 3065 10" Woofer	60W	100W	\$79.95	\$59.95
C 3070 12" Woofer	100W	150W	\$99.00	\$73.95
C 3075 15" Woofer	120W	200W	\$139.95	\$104.95

## High Performance 2 Way Flush Mount Ceiling Speaker System

Designed to be installed into ceilings or walls, this slim profile attractive speaker system/grill assembly will compliment any sound system. Installation is simplified by use of mounting frame (which could be installed during construction) which the speaker assembly attaches to. Full mounting kit supplied, including fixing screws. Employs a 165mm (6.5") latex covered driver and a high efficiency polymylar tweeter coupled with a high quality crossover. The grill and exposed surround can be painted to match existing decor.

**Specifications:** • Impedance: 8 Ohm • Power Input: 30W RMS • Frequency Response: 50Hz - 20kHz • Colour: Ivory White • Dimensions: 306L x 220W x 86H mm

C 0884 Normally **\$250 Per Pair**,

**This Month Only \$199 Per Pair**

## 24 Hour Timer

**These Timers Are Made by the Same Manufacturer as Those Sold by Major Hardware Stores & Supermarkets!**

Programming is done by simply inserting the supplied pins into the appropriate time slots. On and off times are in multiples of 30 minutes. Includes manual on/off switch.

A 0301 Normally **\$26.50**, This Month Only **\$16.50**


**These Timers Can be Used for Security, Pool Pumps & Heaters, Electric Blankets, Lights, Radios, Reticulation etc.**

## 7 Day Electronic Timer

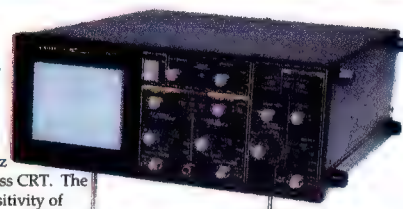**This Month Save 30%**

Excellent for home security. 6 different programs can be set to activate any specified day of the week. All 6 programs operate independent of each other. With normal operation the in-built LCD digital display clearly shows the current time and day of the week. Internal rechargeable backup battery will maintain all program settings and current time for up to approximately 100 hours in the event of a power failure. Simple to program. Includes manual on/off/automatic control. 16 amp at 240V AC maximum current rating.

A 0303 Normally **\$49.50**, This Month Only **\$34.50**



**Now With Component Test Function! New Over 2000 in service throughout Australia including many 100's in Universities, Research Establishments and Industry**

**Fax Us on (09) 328 3487 Altronics for Full Specifications.**

**Save 25%**



**Ideal for Home Theatre Surround Sound or Hi-Fi Extension Speakers!**

**Save Over \$50 a Pair**

**Highly Recommended. I found it difficult to pick the difference between the Altronics C 0884, the American Sonance and Boston Acoustic Systems both costing around \$600.00 a pair John Negus - Leading WA Audiophile**



**ALTRONICS Fax Order Line: (09) 328 3487**

**1-800 999 007**

**PERTH (09) 328 1599**



# ALTRONICS COMPONENTS

## Multi-Function Remote Car Alarm

S 5205 **\$199**

*Easily the Best Car Alarm We Have Ever Evaluated!*

This amazing model features just about everything you could imagine. Multi-function key ring remote control will arm and disarm alarm (and activate central locking if fitted), panic and even open the boot (if actuator fitted). Other features include starter inhibitor, valet mode, central locking interface, flashes car indicators when tripped, auto reset, user programmable options plus much more. Also includes two spare electric outputs which are operated by the key ring remote control, these can be used to chirp the horn, turn on the car headlights or a myriad of other functions! Can be configured to automatically re-arm if a door is not opened within 22 seconds after disarming (avoids accidental disarming). Full battery backup siren includes built-in batteries, charging circuit, siren and key on/off switch.

**Features:** • Supplied complete with two miniature remote controls • Remote arming and disarming • Super Loud 127dB siren • Remote panic function • Full battery backup and tamper proof siren • Child proofing and anti intrusion alert while driving • User selectable exit delay and automatic re-arming • User selectable arming/disarming chirp • User selectable auto arming • Starter disable • Valet mode can be activated by remote or glove box switch • Automatic shunt of any defective entry zone • Turns on interior lights for 20 seconds when alarm is disarmed • Alarm memory indicates which zone (1-3) triggered • 60 second siren with auto reset • Two colour LED status indicator • Can be interfaced with central locking (where fitted) • 3 extra channels on remote to control other vehicle features such as boot release, etc.



**Exclusive to Altronics & Dealers!**

## 14,400bps Internal Fax/Modem with Internet Access Software

Connect to the information super-highway on the Internet and explore the world!

Using the latest in digital signal processing, this internal fax/modem will give you years of service. Supplied with WinFax Lite for Windows, and DoxFax Lite for DOS, this software will let you send/receive faxes direct from your PC. Features 5 year warranty. Austel approved.

\* Service charges apply.

D 1650 **\$199**

**Turn Your PC into a Fax!**

**Amazing Value! 14.4bps Fax/Modem for Under \$200. Includes Software to Access the Internet\***

## Professional 8 Zone Digital Alarm System with Auto Dialler


*This alarm panel is the same type as used by many commercial alarm companies to protect both residential and commercial properties.*

Incorporating an inbuilt Austel approved auto-dialler, this great alarm can be configured to automatically dial two preset numbers in the event of an alarm, i.e. could be configured to automatically ring a neighbour or an alarm monitoring company. The main controller circuitry is housed in a sturdy steel cabinet. Provision is made to house an optional back up battery. The keypad control unit is generally located at the front door for easy access to arming and disarming of the system. The entire system is controlled and programmed via this keypad. Virtually any type of sensor can be used with this system. A combination of normally open and normally closed sensors can be used on any zone. Each zone is monitored by end of line resistors to maintain system integrity, i.e. if someone interferes with the system wiring the alarm will sound immediately.

**Features:** • microprocessor controlled • 8 fully programmable supervised zones • supervised fire zone • 1 auxiliary normally open zone • 3 keypad activated zones • two master codes, one installer code and 16 user codes • monitor function which tests features like battery backup and mains failure • eight individually and fully programmable zones with a large array of functions available • all eight sectors utilise extensive noise protection circuitry and end of line resistors for added security • once triggered, the alarm has the option of a silent alarm, and dialling a friend or monitoring company • quick arming option • zone bypassing for sectors which are false triggering • bell test - to test the external sirens without dialling out • door chime mode for entry/exit paths • battery backup • home or away operation • accessible alarm memory for confirming which sectors were triggered • separate instruction and installation manuals • 12 months warranty • system information can be down-loaded to a printer

S 5495 **\$389**

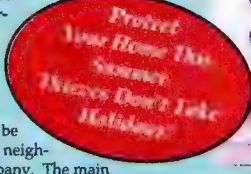M 9140 16V AC Plug Pack with Earth to Suit \$32  
S 5069 12V 4AH Backup Battery to Suit \$49.95



**NEW**

## PIR Movement Detector

**5 Year Warranty**

Small and sleek this detector is ideal for the home or the office. Range up to 13 x 13m.

**Features:** • LED On/Off Jumper • Vertical Adjustment • Wall/Corner Mounting • Small Size - 62w x 88h x 48d mm • 5 Year Warranty

S 5307 **\$49**

### Amazing Bonus Package

Over \$100 Value of Installation Accessories Including Cable, Strobe & Siren Free with Each Alarm System Purchase!

50 Metres of High Quality 6 Core Security Cable (Sufficient for average 4 bedroom house). W 0303



High Intensity Strobe S 5455



Siren Horn S 6130



2 Large Alarm Stickers - S 5400  
Plus 4 Window Stickers - S 5410



174 Roe St. Perth W.A. 6000  
Phone (09) 328 1599, Fax (09) 328 3487  
MAIL ORDERS C/- P.O. Box 8350  
Perth Business Centre, W.A. 6849



**Standard Delivery & Packing Charge:** \$4.00 to 500gms, \$5.50 500gms-1 kg, \$8.00 1kg-5kg. Where possible we process your order the day received and despatch via Australia Post. Allow approx 9 days from day you post order to when you receive goods.

**Overnight JetService:** Up to 3kg is \$9.50, 3kg to 5kg is \$18.00—We will process your order the day received (if placed before 2.00PM WST) and despatched for delivery the next day. Country areas please allow an additional 24-48 hours.

supplier, we send goods at consignee's risk. Should you require insurance cover against loss or damage please add \$1.00 per \$100 of order value (minimum charge \$1). When phone ordering please request "Insurance". **Altronics Resellers:** Chances are there is an Altronics Reseller right near you—check this list or phone us for details of the nearest dealer. Blue Ribbon Dealers are highlighted with a ●. These dealers generally carry a comprehensive range of Altronics products and kits or will order any required item for you.

### WA - COUNTRY

**ALBANY** BP Electronics ● (098) 412681  
Micro Electronics (098) 412077  
**BUNBURY** Micro Electronics (097) 216222  
**BUSSELTON** Mark's Music (097) 523522  
**ESPERANCE** Esperance Comm. (090) 713344  
**KALGOORLIE** Golden Mile Electronics (090) 215212  
**PORT HEDLAND** Ivan Tomek Electronics (091) 732531  
**ROCKINGHAM** TV Joe's (09) 5271806  
**VIC - CITY** All Electronic Comp. (03) 96623506  
TECS ● (03) 96706474  
**CHELTENHAM** Talking Electronics (03) 95842386  
TECS ● (03) 95629501  
**CLAYTON** Truscott Electronics ● (03) 97233860  
**CROYDON** G.B. Telespares (03) 93266035  
**FOOTSCRAY** Preston Electronics ● (03) 94840191  
**PRESTON**

### COUNTRY

**BALLARAT** Ballarat Electronics (053) 311947  
**BENDIGO** Sumner Electronics (054) 431977  
**MILDURA** Truscott Electronics ● (050) 238138  
**SHEPPARTON** Andrew Guyatt Elect. (058) 219497  
**QLD - CITY** Delsound PL ● (07) 38396155  
E.C.Q. (07) 32541153  
**NEWSTEAD** B.A.S. Audiotronics (07) 38447566  
**WEST END** David Hall Elect. ● (07) 38082777  
**WOODRIDGE** Gladstone Elect. Services (079) 724459  
**COUNTRY** Mals Electronics ● (074) 436119  
**GLADSTONE** Super Solex ● (077) 724466  
**MAROOCHYDORE** G.H.E. Electronics ● (002) 342233  
**TOWNSVILLE** G.H.E. Electronics ● (003) 316533  
**TAS**  
**HOBART**  
**LAUNCESTON**

### NT ALICE SPRINGS KATHERINE SA - CITY

Farmer Electronics (089) 522388  
Logicware (089) 723030  
Astronics ● (08) 2126212  
Force Electronics ● (08) 2125505  
Force Electronics ● (08) 3770512  
Force Electronics ● (08) 3743346  
Astronics ● (08) 3496340  
Force Electronics ● (08) 3471188  
Force Electronics ● (08) 2617088  
Force Electronics ● (08) 3322299  
Force Electronics ● (08) 3260901  
Force Electronics ● (08) 2830755  
David Reid Elect. ● (02) 2671385  
Chantronics (02) 6097218  
Coffs Harbour Elect. (066) 525684  
Novocastrian Elect. Supplies (049) 621358  
Vilec Distributors (049) 566792  
Newtek Electronics ● (042) 271620  
Vimcom Electronics (042) 284400

**1-800 999 007 PERTH (09) 328 1599**



### BACK ISSUES

MONTH	YEAR	MONTH	YEAR	PRICE EACH (includes p&p)	TOTAL
				Australia (by return mail) \$A7; NZ & PNG (airmail) \$A7; Overseas (airmail) \$A10. Note: Nov 87-Aug 88; Oct 88-Mar 89; Jun 89; Aug 89; May 90; Feb 92; & Nov-Dec 92 are sold out. All other issues are currently in stock.	\$A
<b>BINDERS</b>					
				Please send me _____ SILICON CHIP binder(s) at \$A14.95 each (incl. postage within Australia). NZ & PNG orders please add \$A5.00 each for postage. Not available elsewhere.	\$A

### SUBSCRIPTIONS

☐ New subscription – month to start \_\_\_\_\_

☐ Renewal – Sub. No. \_\_\_\_\_ ☐ Gift subscription 

**RATES (please tick one)**    **2 years (24 issues)**    **1 year (12 issues)**

Australia	<input type="checkbox"/> \$A99	<input type="checkbox"/> \$A54
Australia with binder(s)*	<input type="checkbox"/> \$A123	<input type="checkbox"/> \$A66
NZ & PNG (airmail)	<input type="checkbox"/> \$A145	<input type="checkbox"/> \$A77
Overseas surface mail	<input type="checkbox"/> \$A145	<input type="checkbox"/> \$A77
Overseas airmail	<input type="checkbox"/> \$A250	<input type="checkbox"/> \$A125

\* 1 binder with 1-year subscription; 2 binders with 2-year subscription

#### GIFT SUBSCRIPTION DETAILS

Month to start \_\_\_\_\_

Message \_\_\_\_\_

Gift for:  
Name \_\_\_\_\_

(PLEASE PRINT)

Address \_\_\_\_\_

State \_\_\_\_\_ Postcode \_\_\_\_\_

#### YOUR DETAILS

Your Name \_\_\_\_\_  
(PLEASE PRINT)

Address \_\_\_\_\_

Postcode \_\_\_\_\_

Daytime Phone No. \_\_\_\_\_ Total Price \$A \_\_\_\_\_

☐ Cheque/Money Order    ☐ Bankcard    ☐ Visa Card    ☐ Master Card

Card No.

Signature \_\_\_\_\_

Card expiry date \_\_\_\_/\_\_\_\_/\_\_\_\_

**Phone (02) 9979 5644**  
9am-5pm Mon-Fri.  
Please have your credit card  
details ready

OR

**Fax (02) 9979 6503**  
Fax the coupon with your  
credit card details  
24 hours 7 days a week

OR

**Mail coupon to:**

Reply Paid 25  
Silicon Chip Publications  
PO Box 139, Collaroy 2097  
No postage stamp required in Australia





# IR remote control for the Railpower Mk.2

***This remote control gives you complete freedom of operation for the Railpower Mk.2 train controller. It has pushbutton control for everything & pulls negligible current when not in use.***

By RICK WALTERS

As presented in the September & October 1995 issues, the Railpower Mk.2 is a walkaround throttle. It allows you to follow your trains as they go around the layout. As such, it performs very well. But perhaps you don't like being tethered by a remote control cable. If so, you will want this infrared remote control. It operates just like any other remote and is based

on the same microprocessor used in the Railpower Mk.2.

The remote control handpiece has six pushbuttons but does not have the meter which was included in the walkaround hand control. Instead, we have designed a small PC board which has an array of 10 LEDs, to give an indication of train speed. This is mounted inside the main unit, along


with a small PC board for the infrared receiver.

The remote control uses the same plastic case as for the walkaround hand control. It contains a small PC board (coded 09101961) and a battery. The board contains six pushbuttons, three transistors, one IC, one crystal and a few other components.

As you can see from the circuit of Fig.1, the battery is connected all the time, as is standard practice in all infrared remote controls. But instead of a dedicated IC as found in most remote controls, we have used a Z86E08 microprocessor.

To conserve the battery, we have used a feature which was not previously exploited. The Z86E08 is a CMOS device and normally does not draw much current but for battery operation, it can be put into a "sleep" mode, whereby the current it draws is



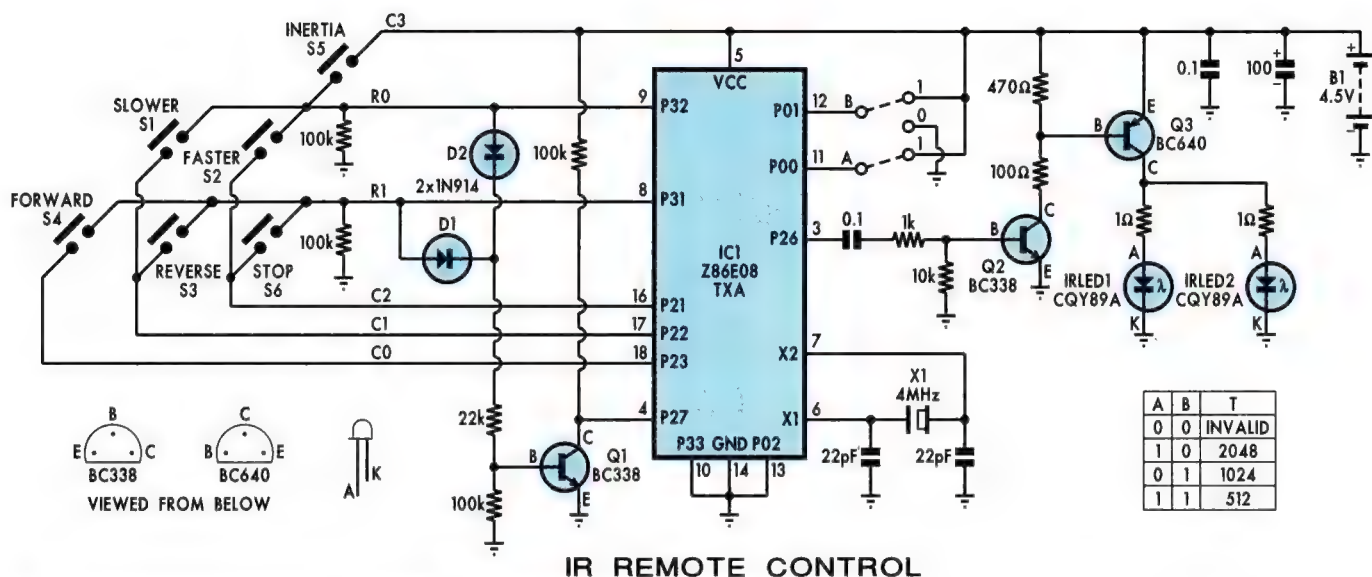

**Fig.1: the transmitter circuit. This uses a Z86E08 microprocessor to produce coded IR pulses when the buttons are being pressed. When the buttons are not being pressed, the microprocessor goes into sleep mode to conserve the battery.**

only 10µA. This greatly increases the battery life.

When IC1 is put to sleep, it takes pins 16, 17 & 18 high (ie, to the battery positive line, +4.5V). Later, when any button is pressed, R0 or R1 (ie, row zero or row one of the pushbutton matrix) will go high, turning on transistor Q1 via diode D1 or D2. Q1 pulls pin 4 of IC1 low, to "wake it up", after which it takes pins 16, 17 & 18 low and scans the buttons to see which one was pressed.

C3 (column 3), the input to the INERTIA button, is high and if this is pressed, pin 9 of IC1 will go high. If

this button is not pressed the processor then takes pin 16 (C2) high. As you can see from the circuit, the STOP or FASTER button, if pressed, will take pin 8 or pin 9 of IC1 high and the code for this button will be sent. Pins 17 and 18 are taken high in sequence and if any of the remaining buttons are pressed, their code will be transmitted.

The pulse code appears on pin 3 of IC1 and turns Q2 and thus Q3 on and off. Q3 pulses two infrared LEDs (LED1 and LED2).


Remember, only one button is pressed at a time and the code for this

button will be sent many times before you can release it. With the jumpers set on 1,1 a burst of code takes 20 milliseconds to be sent.


Each time the processor finishes a scan, it takes all column outputs high (C0-C3) and looks at the collector of Q1. If it is low, indicating a button is pressed, it will scan the buttons again; if high, it will go into sleep mode to conserve the batteries.

The RATE links A and B must be the same in the transmitter and the

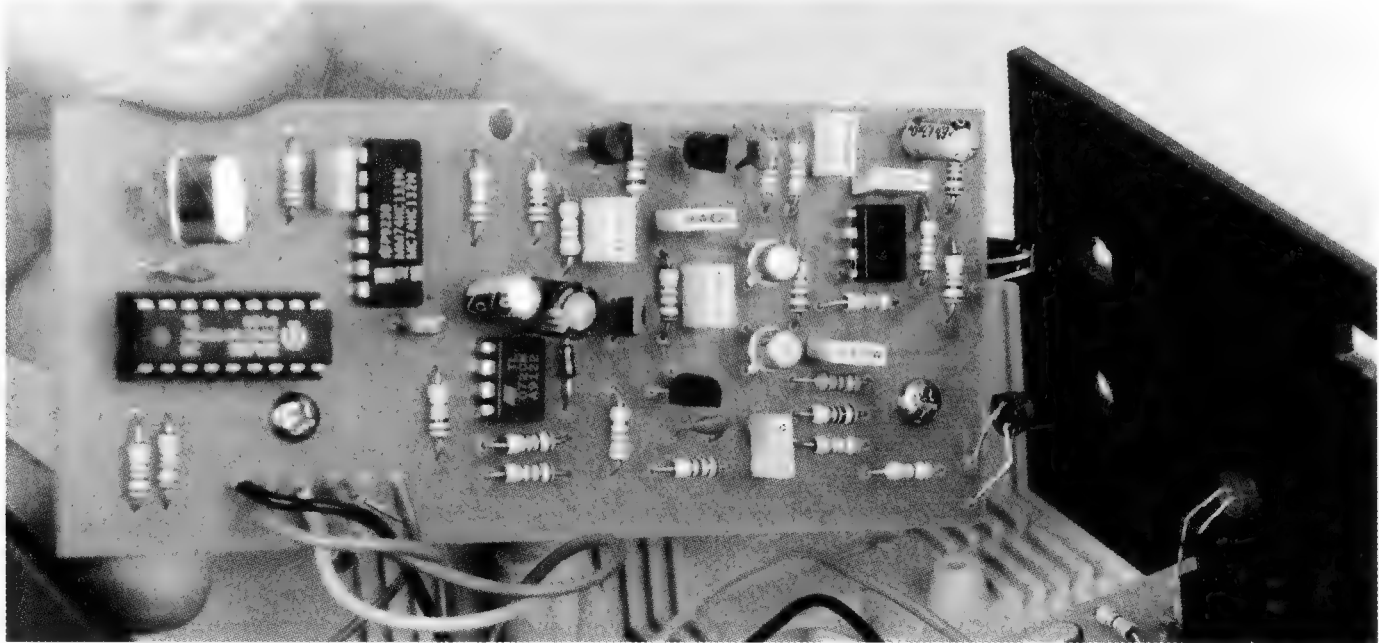**Below: this photo shows the completed IR receiver board being installed in the Railpower case. Note the mounting details for the Acknowledge LED and the LT536 infrared diode (PD1).**





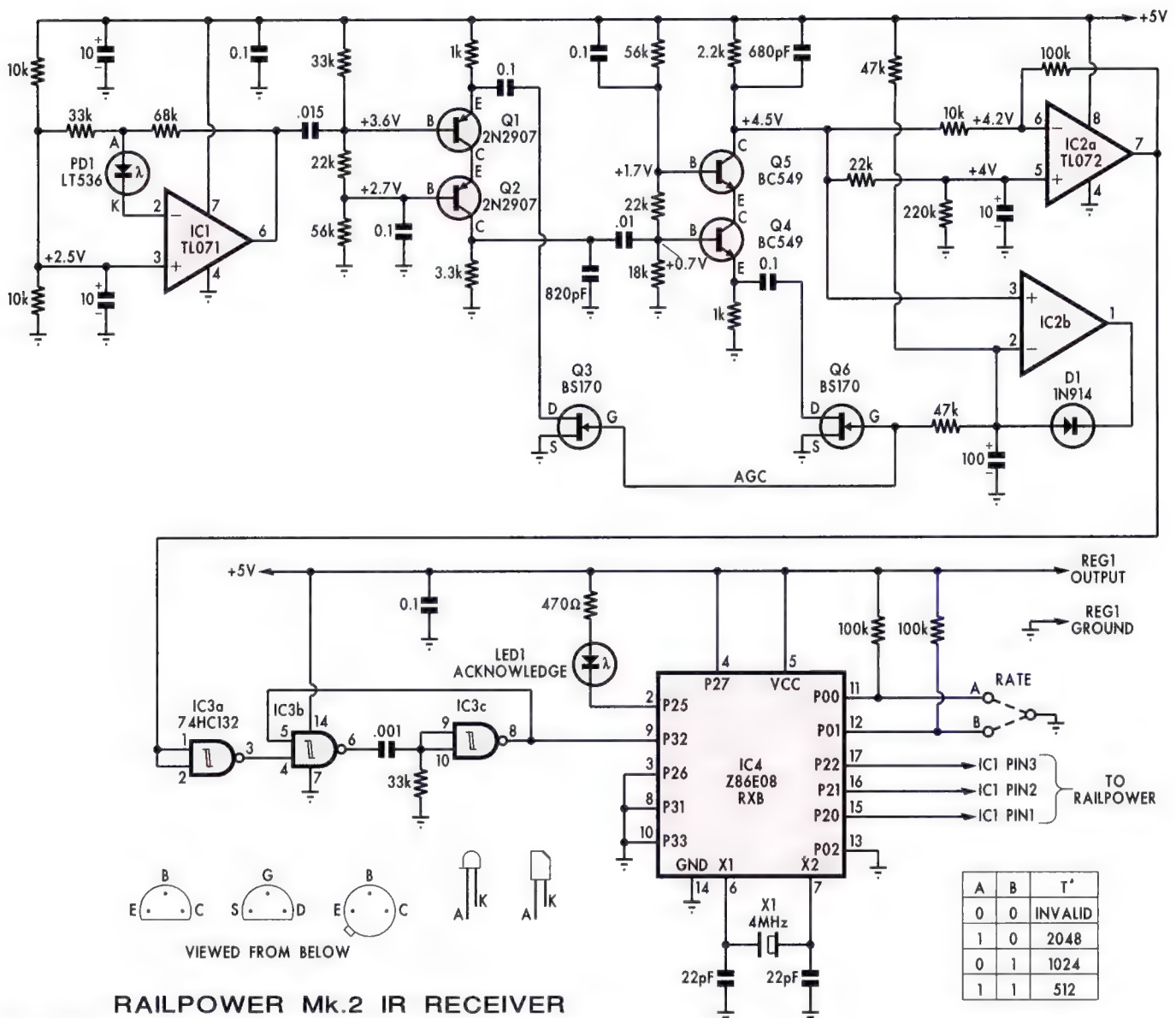

RAILPOWER Mk.2 IR RECEIVER

Fig.2: the IR receiver circuit. This uses two cascode transistor stages (Q1, Q2 and Q4, Q5) with AGC to provide the necessary large gain for the photodiode signal. The signal decoding is done by IC4, a Z86E08 microcontroller programmed for this purpose.

receiver. These links could allow you to have one hand control with a 3-position selector switch and this could control three Railpower IR receivers, each with a different rate setting.

### Infrared receiver

The infrared receiver consists of photodiode PD1, current-to-voltage converter IC1, two cascode transistor amplifiers (Q1, Q2 and Q4, Q5) with AGC (automatic gain control), a comparator and AGC detector (IC2), a pulse stretcher (IC3) and a data decoder, IC4. These are all mounted on a PC board (coded 09101962) which is housed in the case of the Railpower

controller. The circuit is shown in Fig.2.

Photodiode PD1 sees the IR pulses emitted by the remote control and varies its current accordingly. This variation in current is converted to voltage pulses by op amp IC1 which drives the base of Q1 via a .015μF capacitor.

The pulses from IC1 can vary from around 0.2V peak-peak when the remote control is close to PD1 to being lost in the noise when it is some distance away. For this reason, we need a lot of gain for weak signals but not very much for the stronger ones. We obtain lots of gain by using cascode

circuits and then we use automatic gain control (AGC) on both to cope with large signals.

### Gain control

The two cascode circuits are similar, the first using PNP transistors Q1 & Q2, the second using NPN transistors Q4 & Q5. AGC is applied to the first pair by FET Q3, while FET Q6 applies AGC to the second cascode pair.

The gain of the first cascode stage, with Q3 turned off, is around 3.3 while the gain of the second stage, with Q6 turned off, is 2.2 giving an overall gain of 7.3 (3.3 x 2.2). With Q3 & Q6 turned on fully, the gain of each cascode stage can be in excess of 200, giving an overall gain of 40,000 or more for very small input signals.



## PARTS LIST

### Remote Control Transmitter

- 1 PC board, code 09101961, 85 x 50mm
- 1 plastic case (Jaycar HB-6032 or equivalent)
- 1 4MHz crystal (HC18, HC49)
- 2 yellow PC mount momentary switches (Jaycar SP-0722 or equivalent)
- 1 red PC mount momentary switch (Jaycar SP-0720 or equivalent)
- 1 black PC mount momentary switch (Jaycar SP-0721 or equivalent)
- 1 white PC mount momentary switch (Jaycar SP-0723 or equivalent)
- 1 green PC mount momentary switch (Jaycar SP-0722 or equivalent)
- 1 single AA cell holder (see text)
- 3 L1154 alkaline batteries
- 1 18 pin IC socket (optional)
- 4 #8 x 10mm self-tapping screws
- 4 5mm untapped spacers
- 1 100mm-length red wire
- 1 100mm-length black wire
- 1 50mm-length 1mm sleeving

### Semiconductors

- 1 Z86E08 programmed TXA (IC1)
- 2 1N914 signal diodes (D1,D2)
- 2 BC338 NPN transistors (Q1,Q2)
- 1 BC640 PNP transistor (Q3)
- 2 CQY89A LED (or equivalent)

### Capacitors

- 1 100 $\mu$ F 16VW electrolytic
- 2 0.1 $\mu$ F 50VW monolithic
- 2 22pF ceramic

### Resistors (0.25W, 1%)

- 4 100k $\Omega$       1 470 $\Omega$
- 1 22k $\Omega$         1 100 $\Omega$
- 1 10k $\Omega$         2 1 $\Omega$
- 1 1k $\Omega$

### IR Receiver Board

- 1 PC board, code 0911X951, 120 x 50mm
- 1 4MHz crystal (HC18,HC49)
- 1 18-pin IC socket (optional)
- 2 3mm x 15mm threaded spacer
- 2 3mm x 10mm screw
- 2 3mm x 6mm screw
- 1 200mm-length black hook-up wire
- 1 200mm-length red hook-up wire
- 1 200mm-length orange hook-up wire
- 1 200mm-length yellow hook-up wire
- 1 200mm-length green hook-up wire

### Semiconductors

- 1 TL071 op amp (IC1)
- 1 TL072 dual op amp (IC2)
- 1 74HC132 quad 2-input NAND gate (IC3)
- 1 Z86E08 programmed RXB (IC4)
- 2 2N2907 PNP transistors (Q1,Q2)
- 2 BC549 NPN transistors (Q4,Q5)
- 2 BS170 FET (Q3,Q6)
- 1 LT536 photodiode (PD1)
- 1 1N914 signal diode (D1)
- 1 5mm red LED (LED1)

### Capacitors

- 1 100 $\mu$ F 16VW electrolytic
- 3 10 $\mu$ F 50VW electrolytic

- 6 0.1 $\mu$ F 50VW monolithic
- 1 .015 $\mu$ F 100VW MKT polyester
- 1 .01 $\mu$ F 100VW MKT polyester
- 1 .001 $\mu$ F 100VW MKT polyester
- 1 820pF disc ceramic
- 1 680pF disc ceramic
- 2 22pF capacitors

### Resistors (0.25W, 1%)

- 1 220k $\Omega$       1 18k $\Omega$
- 3 100k $\Omega$       3 10k $\Omega$
- 1 68k $\Omega$         1 3.3k $\Omega$
- 2 56k $\Omega$         1 2.2k $\Omega$
- 2 47k $\Omega$         2 1k $\Omega$
- 3 33k $\Omega$         1 470 $\Omega$
- 3 22k $\Omega$

### Speed Display Board

- 1 PC board, code 09101963, 65 x 50mm
- 1 5k $\Omega$  horizontal trimpot (VR1)
- 1 1k $\Omega$  horizontal trimpot (VR2)

### Semiconductors

- 1 LM3914 bargraph driver (IC1)
- 1 10-LED display (Jaycar ZD-1700)

### Capacitors

- 1 10 $\mu$ F 50VW electrolytic
- 1 1 $\mu$ F 16VW electrolytic
- 1 0.1 $\mu$ F monolithic

### Resistors (0.25W, 1%)

- 1 100k $\Omega$       1 4.7k $\Omega$
- 1 15k $\Omega$         1 820 $\Omega$
- 1 15k $\Omega$  9-resistor array (10-pin SIP)

### Miscellaneous

- Hookup wire, PC stakes.

In practice, the output signal from the collector of Q5 is monitored by IC2b which is connected as a peak rectifier. With no input signal present, pin 2 of IC2b is pulled high by the 47k $\Omega$  resistor connected to the +5V rail. Negative-going pulse signals at the collector of Q5 cause IC2b and its associated diode D1 to pull pin 2 towards 0V and hence discharge the 100 $\mu$ F capacitor. Thus, the gates of Q3 & Q6 tend to be taken high for small signals, to increase the gain. Conversely, large signals tend to result in the gates of Q3 & Q6 going toward 0V,

to turn them off and reduce the gain.

In practice, the circuit continuously varies its gain so that the signal amplitude at the collector of Q5 is more or less constant.

Q3 & Q6 are connected to the emitters of their respective cascode stages via 0.1 $\mu$ F capacitors. This means that the gain of the cascodes increases at high frequencies but not at 50Hz or 100Hz, to reduce any interference from incandescent or fluorescent lights.


IC2a is connected as a comparator and compares the signal from the collector of Q5 with the DC voltage at its

pin 5. It effectively squares up the signal pulses and removes any residual noise. IC2a drives IC3, a CMOS quad NAND gate which is used as a pulse stretcher. This allows us to supply a consistent pulse width to IC4, regardless of the output of IC2a.

### Data decoder

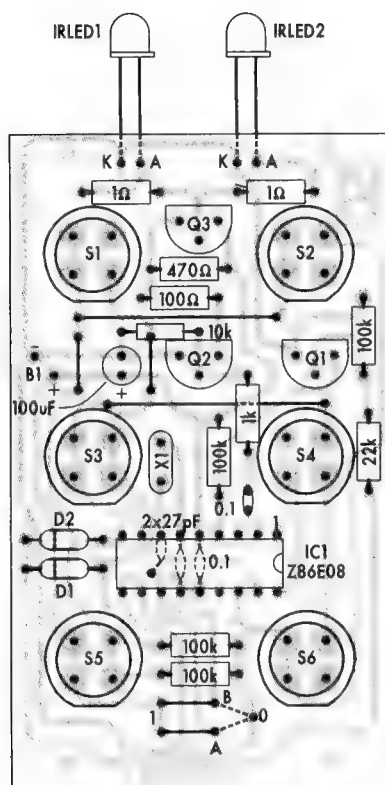IC4 is another Z86E08 microprocessor which has been programmed to accept the IR data transmitted by the hand control and convert it to the correct code on pins 15, 16 & 17 to operate the Railpower functions. The

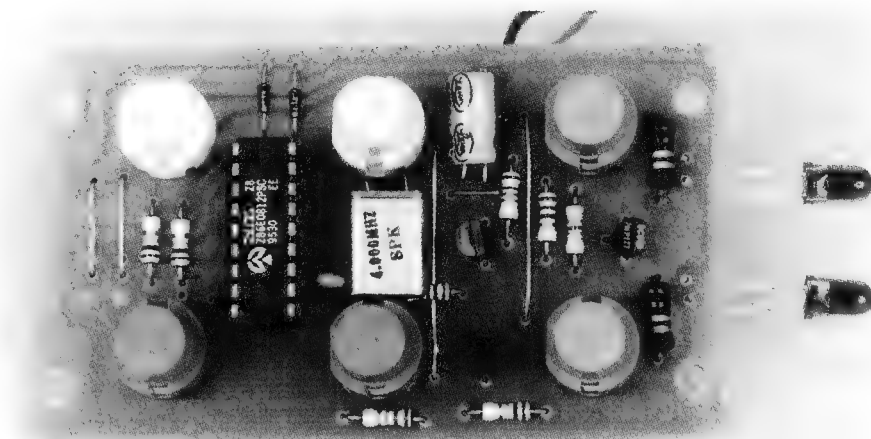





**Fig.3: the component layout for the transmitter PC board. Note the three capacitors mounted on the underside of the board. These are shown dotted within the outline for IC1.**

microprocessor stores two consecutive codes from the transmitter and compares them. If they are identical, it will send the information to the Railpower; if they differ, it will ignore them and compare the next two codes received. As mentioned previously, the rate links on the receiver must be the same as those on the transmitter.


The three output lines from IC4 are



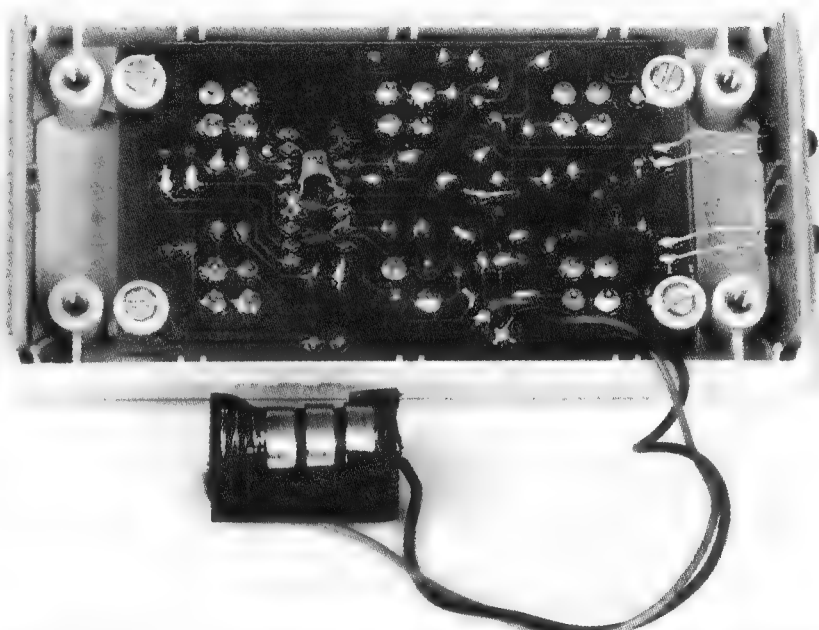**This topside view of the remote control transmitter board shows how the crystal is laid flat. Make sure that the two IR LEDs are correctly oriented.**




**This view inside the completed transmitter shows the mounting details for the three capacitors on the copper side of the board. Note the modified AA cell holder for the three button cells.**

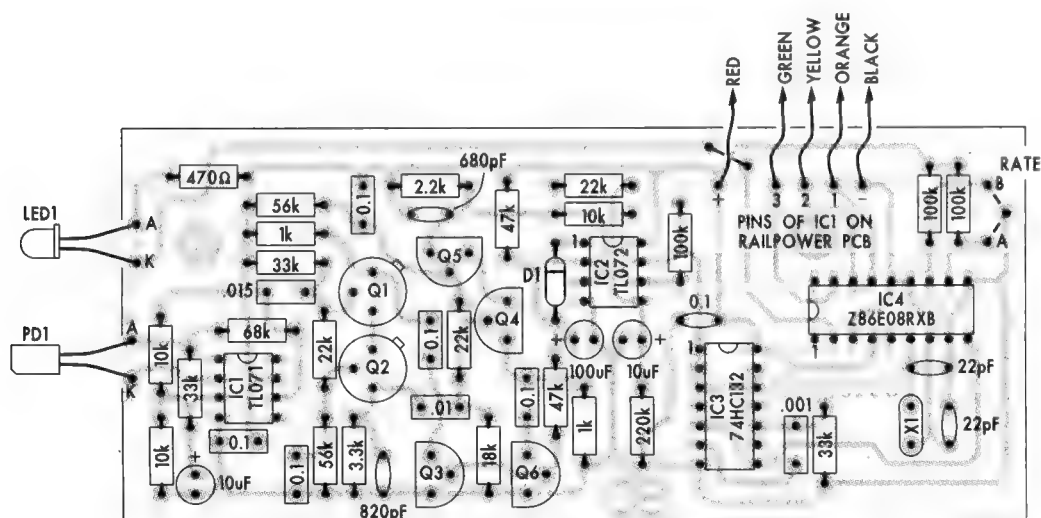

**Fig.4: the component overlay for the IR receiver board. Note that the rate links on this board must match the rate link settings on the transmitter PC board.**



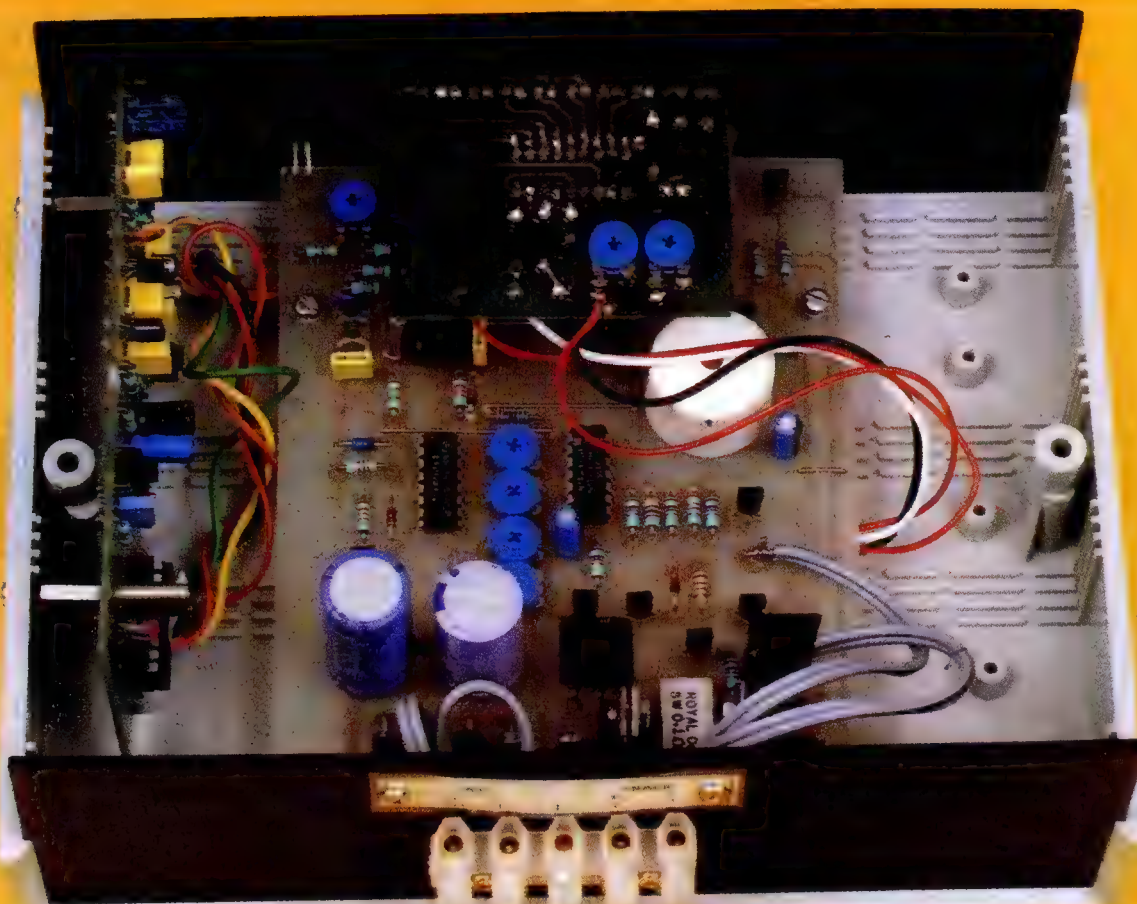


This view shows how the IR receiver board is mounted vertically along one side of the Railpower Mk.2 case, while the speed board is mounted upside down, with the LEDs protruding through the front panel.

### RESISTOR COLOUR CODES

	No.	Value	4-Band Code (1%)	5-Band Code (1%)
☐	1	220kΩ	red red yellow brown	red red black orange brown
☐	8	100kΩ	brown black yellow brown	brown black black orange brown
☐	1	68kΩ	blue grey orange brown	blue grey black red brown
☐	2	56kΩ	green blue orange brown	green blue black red brown
☐	2	47kΩ	yellow violet orange brown	yellow violet black red brown
☐	3	33kΩ	orange orange orange brown	orange orange black red brown
☐	4	22kΩ	red red orange brown	red red black red brown
☐	1	18kΩ	brown grey orange brown	brown grey black red brown
☐	1	15kΩ	brown green orange brown	brown green black red brown
☐	4	10kΩ	brown black orange brown	brown black black red brown
☐	1	4.7kΩ	yellow violet red brown	yellow violet black brown brown
☐	1	3.3kΩ	orange orange red brown	orange orange black brown brown
☐	1	2.2kΩ	red red red brown	red red black brown brown
☐	3	1kΩ	brown black red brown	brown black black brown brown
☐	1	820Ω	grey red brown brown	grey red black black brown
☐	2	470Ω	yellow violet brown brown	yellow violet black black brown
☐	1	100Ω	brown black brown brown	brown black black black brown
☐	2	1Ω	brown black gold gold	brown black black silver brown


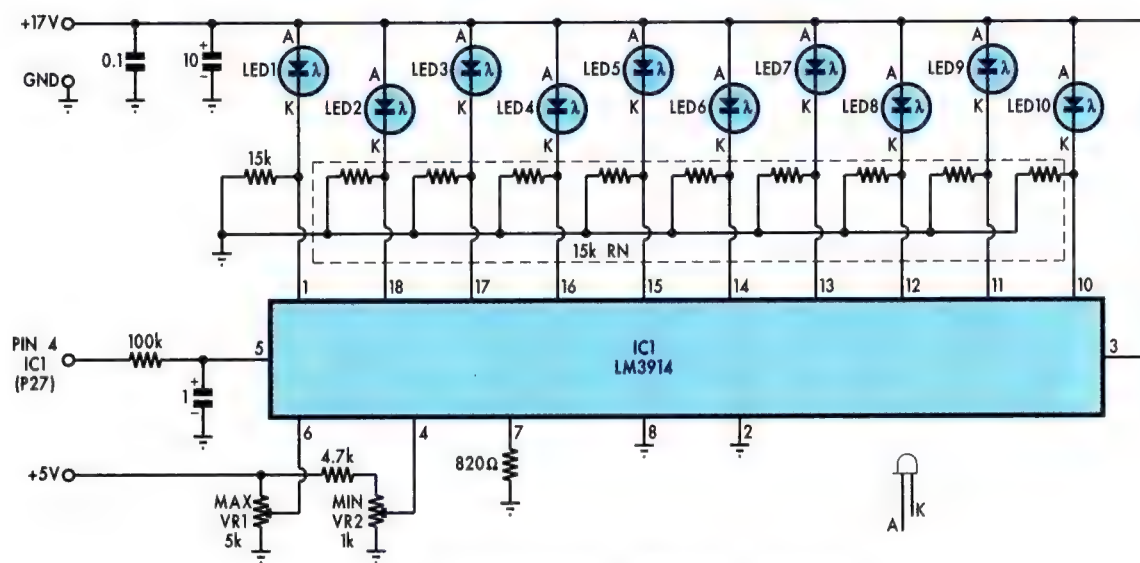
# Adding A Speed Meter To The Railpower Mk.2



**RAILPOWER SPEED METER**

**Fig.5: the speed meter is a conventional LM3914 LED bargraph circuit. It takes the place of the analog meter in the original walkaround control for the Railpower Mk.2.**

If you wish to add a speed meter to the Railpower Mk.2, then use the LED bargraph display we have designed. It sits above the LED indicators on the front panel of the main unit and consists of a bar of 10 red LEDs. It is a standard circuit employing an LM3914 LED bargraph display driver. The two preset potentiometers on this board are adjusted in a similar manner to the meter setup in the hand control. The circuit is shown in Fig.5

while the component overlay for the PC board (coded 09101963) is shown in Fig.6.

Fit the IC, SIP and resistors, then the capacitors and potentiometers. If you wish, you can solder the potentiometers on the copper side of the board, as we have done, to make them easy to adjust.

Connect a red wire to the +17V, orange to the +5V, black to the ground and yellow to the input terminal, as shown on the layout.

The other end of the red wire connects to +17V on the main board (REG1 input), the orange to +5V (REG1 output) and the black wire to ground. The other end of the yellow wire should be soldered to pin 4 of IC1 (top of VR5).

## Calibration

Once the maximum and minimum speeds have been set satisfactorily on the main Railpower PC board, FORWARD should be se-

connected to IC1 in the Railpower unit.

## Construction

In discussing the construction, we will assume that you have already built the Railpower Mk.2, as described in the September & October 1995 issues. We will also assume that you have built up the original wired hand control and have made everything function as described in the setup procedure.

To add the infrared remote control, you need to build the remote control


handpiece and the IR receiver board. As mentioned previously, we have also designed an optional LED bargraph speed indicator which takes the place of the speed meter in the original walkaround hand control.

Let's start with the remote control transmitter PC board. Its component layout is shown in Fig.3. Check the board for open circuit tracks or shorts, especially the track that passes between pins 7 and 8 of IC1. While you're at it, check the other two boards for any etching problems and make any fixes as required.


The first step is to mount the blank board in the plastic case. It goes in the half with the brass inserts (the front), with the copper side of the PC board facing up. A small hole has been drilled at the centre of each group of four pushbutton pads to allow you to drill pilot holes through into the case front for the six pushbuttons. When you have drilled them, remove the board from the case. (By the way, these pilot holes are not present in the photo of our prototype).

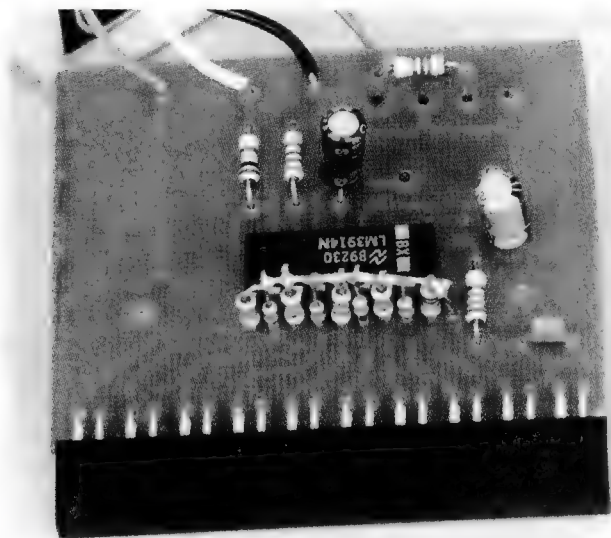Fit the two long and two short links at the LED end of the board and the





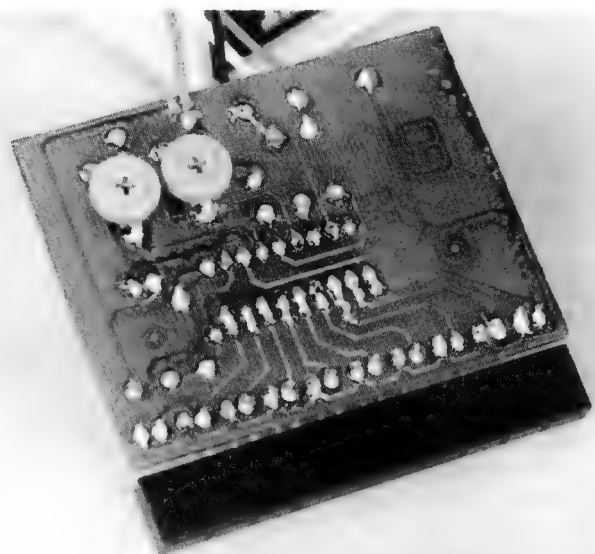This assembled speed meter shows nine discrete resistors instead of the specified SIP resistor array.




The two adjustment pots are mounted on the underside of the speed meter board for easy access.

lected and the minimum pot (VR2) on this board set so that the first LED lights. The controller should then be taken to full speed and the maximum pot (VR1) adjusted so that LED number 10 is lit. There is a small amount of interaction and the adjustments may have to be made several times to get it right.

As an alternative to the speed bargraph, there is no reason why you could not mount the original walkaround control meter in the front panel, fitting a meter zero adjust control the same as in the handpiece and taking the positive meter wire to pin 2 on the DIN socket.

Fig.6 (right): install the parts on the speed meter PC board as shown in this wiring diagram. Check that all the LEDs are correctly oriented and note the mounting details for VR1 and VR2 (see photo above right).

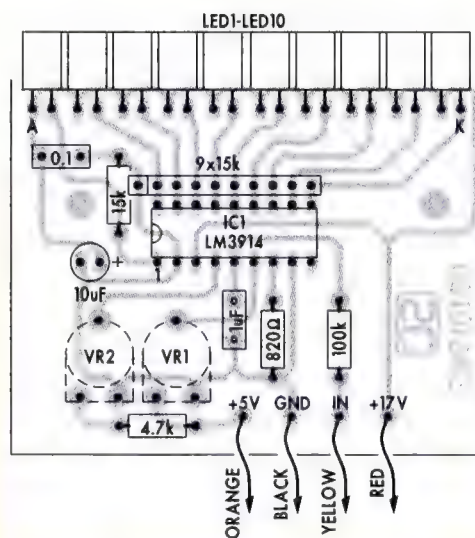

two rate links. We suggest you initially code it 1,1 as shown on the overlay, as this gives the fastest transmission rate. Next, fit and solder the diodes and resistors, followed by the transistors, capacitors and crystal. Push the transistors well down so that they are only about 2mm off the board. Bend the crystal's leads at right angles and lie it down flat. The electrolytic capacitor should also lie flat on the board.

Lastly, fit the pushbuttons, noting that all the flats face in the same direction (towards the rate links). Do not fit

the LEDs as this will be done later. If you elected not to use an IC socket, fit and solder the IC marked TXA (this Z86E08 has been programmed as the transmitter); otherwise, solder in the IC socket. In either case, be sure to check the orientation of pin 1.

As the PC board is rather small, we elected to mount three capacitors on the copper side. These can be fitted now. The 0.1µF monolithic type is soldered from pin 5 to pin 14, then laid flat against the board towards the pin 1 end. The two 22pF capacitors are soldered from pin 6 to pin 13 and

from pin 7 to the pad on the copper track between pin 13 and pin 10. Both are laid flat, facing towards the other end of the socket. These details can be checked in the relevant photo.

## Battery holder

The battery consists of three 1.5V button cells in series. These are held in a half-sized holder made out of a single AA cell holder. Cut the battery holder in half with a saw or sharp knife about 28mm from the spring end. Our holder had a moulded ridge at this point. Carefully cut the non-



spring plastic end out of the holder and locate it in the piece with the spring to make a half-size unit. The easiest way to retain the end is to melt the plastic with your soldering iron. If you do this inside and out, the end will be held firmly in place. Alternatively, you can do a neater job if you have access to ACC adhesive as used in plastic model making). Solder a red wire to the spring end and a black wire to the other end, then connect the red to the positive supply terminal on the PC board and the black wire to the negative terminal.

Now drill one of the case end pieces to take the IR LEDs. Drill two 5mm holes on the horizontal centreline and 7.5mm either side of the vertical centreline. Slip 10mm of 1mm-dia. sleeving over each long LED lead, sit the PC board and LEDs in the case and bend the leads so that 2-3mm of each LED protrudes through the end piece. The longer sleeved lead should be on the right when viewed from the component side.

Once you are satisfied, solder in the LEDs, insert the IC if you used a socket and fit the board in the case using the self-tapping screws and spacers. The battery holder can be kept in place with a dab of BLU-TACK® adhesive.

## Receiver board

The component layout for the receiver board is shown in Fig.4. Start by fitting the one link and the resistors. Next, fit the ICs, using a socket for IC4 if you prefer. Make sure that all the ICs are correctly oriented. This done, solder in the MKT capacitors, the transistors, electrolytic capacitors and finally the crystal. Don't mount PD1 or the acknowledge LED yet.

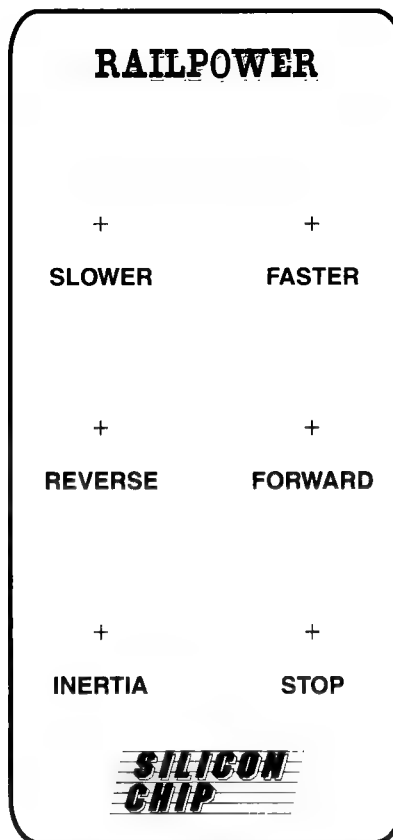


Fig.7: the full-size artwork for the remote control front panel.

Fit 200mm lengths of hook-up wire to the board, in the wire colours as shown in Fig.4, for the signal output and supply connections. This done, mount the PC board in the righthand side of the Railpower case, using two tapped metal spacers.

Drill two 5mm holes in the front panel for the photodiode and acknowledge LED. File the hole for the photodiode to a 5 x 7.5mm rectangle, then replace the panel and bend the LED

leads so that it protrudes satisfactorily through the front panel. Locate the sensor centrally behind the rectangular cutout. Both anodes (longer lead) are towards the top of the PC board. When you are satisfied with their positions, solder them both in place.

Solder the black wire to the centre pin of REG1 (ground) and the red wire to the output pin of REG1 (+5V). The orange wire should be soldered to pin 1 of IC1, the yellow to pin 2 and the green to pin 3. Reassemble the unit and after applying power, check that the walkaround control still operates. If it doesn't, the most likely cause is a short between pins 1, 2 or 3 on IC1.

## Testing

Clip the three cells into the holder on the IR remote control unit, observing their polarity. They are back-to-front compared to standard cells, the small cap being the negative connection. Point the remote control at the receiver and press a button. If all is well, the acknowledge LED on the Railpower should light and the corresponding function should be indicated by the Railpower LED.

If it doesn't work, the problem is knowing which unit is not operating correctly, the transmitter or the receiver.

First, check that the battery voltage is around 4.5V on the transmitter. If you have an oscilloscope, hold a button down and check pin 7 of IC1 to see that the crystal is oscillating at 4MHz. Now check at the anode of one of the transmitter LEDs. There should be a pulse train output whenever a button is pressed. If the pulses are being sent continuously, then one of



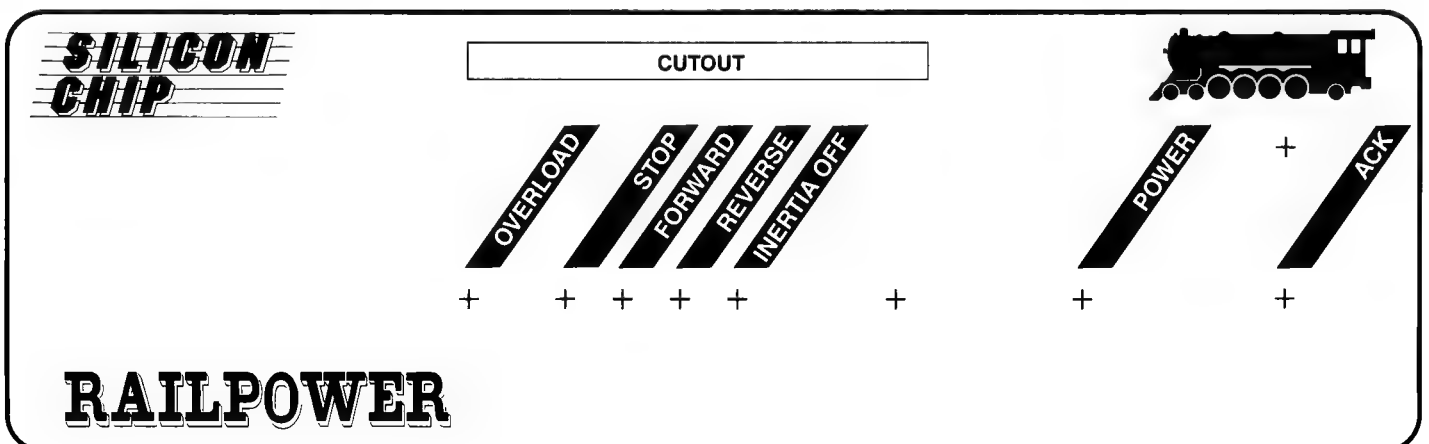
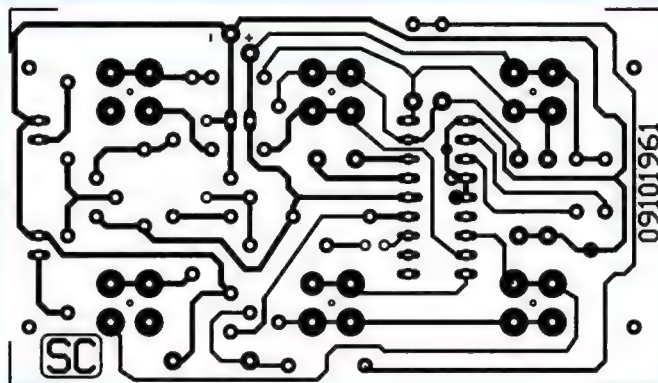


Fig.8: this is the full-size front panel artwork for the remote control version of the Railpower Mk.2.

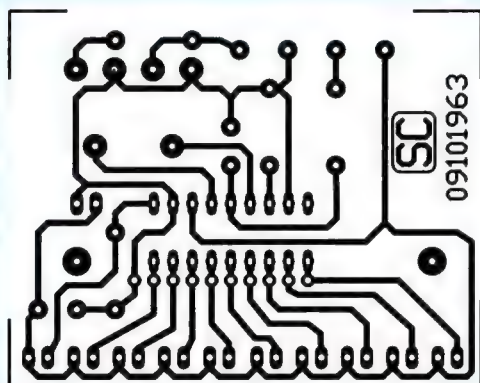

Fig.9: here are the full size etching patters for the IR receiver board (right), transmitter PC board (bottom right) and the speed meter PC board (below). Check the etched boards carefully before installing any of the parts.

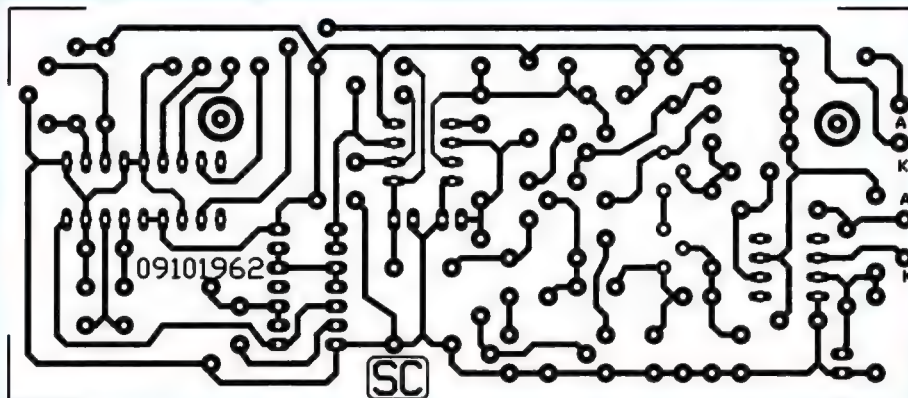


the pushbuttons has been inserted incorrectly.

If an oscilloscope is not available, remove the batteries and connect a DC power supply set to 4.5V. When a button is pressed, the current should be around 9mA. As soon as the button is released, the current should drop to about 5mA and after one second drop to 100μA. If this occurs, you can assume that the transmitter is working satisfactorily. If not check the capacitors on the crystal pins.
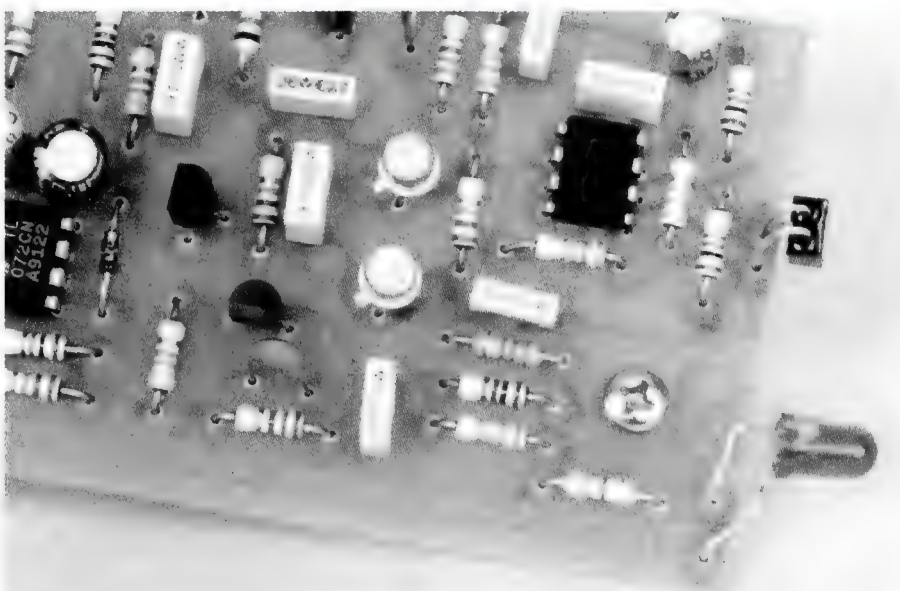
### IR receiver board

On the receiver, check that pin 14 of IC3 is at +5V with respect to pin 7. If you have an oscilloscope, check pin 7 of the processor to confirm that the crystal is oscillating at 4MHz. Hold the transmitter close to the receiver with a button pressed. The output at pin 6 of IC1 should be a negative-going pulse of several hundred millivolts. It should be positive-going at Q2's collector and 3-4V negative-going at Q5's collector.

The output of IC2a (pin 7) should be positive-going, while the signal into pin 9 of IC4 should be a negative-going 5V pulse 33μs wide.



This close-up view shows how the leads of the infrared photodiode (PD1) on the receiver are bent over, so that the active surface of the device faces the hole in the front panel.

If you don't have an oscilloscope, the best approach is to compare the DC voltages measured in your receiver with those shown on the circuit. They should be within 10% of each other. If there is a discrepancy, check the com-

ponent values around the relevant stage and also your soldering.

Check also that the A and B rate links on the transmitter and receiver match each other. If they don't, the remote control won't work. **SC**



# SERVICEMAN'S LOG

## The complaint seemed simple enough

**Yes, it did sound simple. And, relatively speaking, it was. The trouble was, it didn't stop there – it had brought all its gremlin mates along with it. By the time I'd knocked them all over, it was a major exercise.**

This story concerns a Sanyo colour TV set, model 6627 (79P chassis), which lead me a merry dance with a succession of faults – these in addition to the original complaint.

The set belongs to a pensioner, one of several among my regular customers, and whom I regard as being in something of a special category. In general, their equipment tends to be older than average, for the very simple reason that, for many, the cost of new equipment is almost prohibitive. So they keep their old units and call on me to keep them going for as long as possible.

Of course, I do my best to help them, even though at times it taxes one's ingenuity and patience. (After all, I'll be old myself someday – and no editorial comment, please). Anyway, this case was a classic example of this sort of job and, as is typical, involved a set that was over 10 years old.

But the owner's complaint seemed simple enough – distorted sound. And a quick check while he was there confirmed the complaint; the distortion was quite bad. Even so, I reckoned it should be a snack; that I would be able to knock the job over in no time. And that, as the reader has doubtless guessed, was where I came a gutser.

### Sound circuitry

The sound section in this set is quite straightforward – see Fig.1. It consists of a sound IF amplifier and demodulator IC (IC151), the latter feeding two output transistors, Q151 and Q152. These are both specified as 2SC2568 or 2SC2456.

My first step was to check the 220V main HT rail, which came up spot on, as did several secondary rails derived from it. OK, so where to in the sound section? My first inclination was to suspect one of the two output transistors and, with more haste than wisdom, I whipped them out and tested them.

They both tested OK, which served me right for rushing in. I then did what I should have done first – checked the voltages around these transistors. And, yes there was something wrong. The base voltage of Q151 is shown on the circuit as "80V-106V", which seemed an unusually large spread. But that was largely academic anyhow, because the actual voltage was way down on even the lower figure.

And this was where I encountered the first of several discrepancies between the set on the bench and the circuit. And I don't meant bodgie repairs; I'm referring to original components. The bias resistor for Q151 (R151) is shown as 39k $\Omega$  but the one in the set was 27k $\Omega$ . Or, more correctly, it was coded 27k $\Omega$ . In fact, it measured over 100k $\Omega$ .

Well that seemed like the answer and I promptly fitted a new 27k $\Omega$  resistor. That brought the voltages back to within tolerance of those on the circuit and wiped out most of the distortion. And I say "most" because there remained a niggling level. It was nothing like the original but it was enough to

indicate that there was still something wrong.

And that's just about the nastiest kind of fault I can imagine. It was at such a level that, at times, on certain program material, one could kid oneself that it wasn't there. Then the program would change and it was all too obvious. There was nothing for it; it had to be found.

So, with all the stage's operating voltages restored to normal, where should I go from here? The IC seemed the next most likely culprit. I had one on hand and changing it was not a particularly difficult job. But, alas, I drew another blank.

### Down to basics

It was time to really get down to basics. I went right over the output



THE SERVICEMAN  
40 YEARS AGO



stage and, by one means or another, checked each component in turn. And in the process, I encountered another circuit discrepancy; a diode, D153, which was in the set but not on the circuit. It has been drawn in on the circuit shown here.

I paid particular attention to electrolytic capacitors C151 (1 $\mu$ F) and C157 (2.2 $\mu$ F on the circuit, 4.7 $\mu$ F in the set). Low value electrolytics are always suspect. But these and all the other components, except one, were cleared.

That one component was C153, a 5600pF capacitor connecting to pin 13 of the IC. And I had left it until last because, initially, I couldn't identify it. I had been looking for a small ceramic capacitor or something similar but without success. In the end, I had to trace the copper pattern and, when I found it, it was quite a surprise.

It wasn't a ceramic capacitor and it wasn't 5600pF. It was an electrolytic and it was 0.47 $\mu$ F; the biggest change from the original circuit I had found so far. More to the point, being an electrolytic – and of very low value to boot – it was a prime suspect and I lost no time in reefing it out and fitting a new one.

And that was the answer, with the set now producing clean sound. And to confirm it, the suspect electrolytic showed substantial leakage when tested. So that looked like the end of the exercise. I gave the set the usual once over for general performance and minor adjustments, then set it up on the end of the bench and let it run.

### The set carks it

Initially, it ran for several hours and then, suddenly, I was aware that it was completely dead, with no picture and no sound. Well, I took another punt: the horizontal output transistor (2SD838 on the circuit, 2SD621L in the set). And I picked it in one; it was short circuit.

This failure, in itself, did not present any real problem, except that the 2SD838 was cheaper – at around \$30 – than the 2SD621L (\$42) but was no longer available. It was something of a slug for a pensioner but that's life.

More importantly, I was concerned as to why the transistor had failed. It has a pretty hard life in this set. The waveform shown on the collector is 1900V p-p which is high by any standards. That means that the stage is vulnerable to any spikes or rubbish on


the driving waveform. And from experience, the most likely cause is a failure in C483, a 1 $\mu$ F electrolytic, which decouples the 220V rail to the horizontal drive transistor, Q481.

Again, experience has shown that this capacitor dries out, allowing all kinds of rubbish to reach the driver. So I pulled it and replaced it. And, as an attempt at insurance, I upped the value to 10 $\mu$ F. I can't guarantee how much it will help but it won't do any harm.

When I switched the set on again, there was sound but no picture. So what on earth could be wrong now? My first reaction was to suspect the operating voltages on the picture tube. I fished out the probe and checked the EHT. There were plenty of volts there, something over 25kV, and so I checked the screen voltage, focus voltage and the RGB drive transistors. All seemed OK.

I have experienced trouble in the past around transistor Q191. This forms part of the ACL (Automatic Contrast Limiter) circuit and the problem concerns resistor R197 (220k $\Omega$ ) which goes high. And while the trouble had never been anything like this, I checked it, found it somewhat high

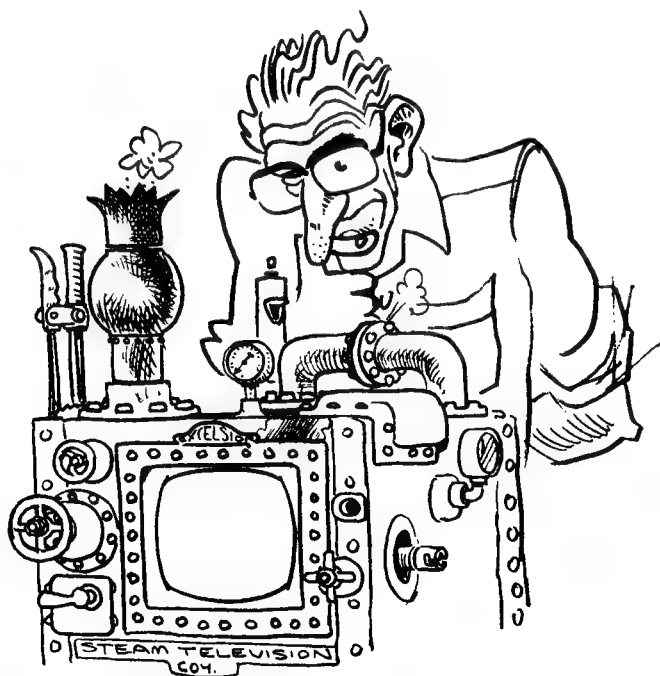AFTER ALL, I'LL BE OLD  
MYSELF, SOMEDAY...




THE SERVICEMAN  
20 YEARS AGO



THE SERVICEMAN  
TODAY



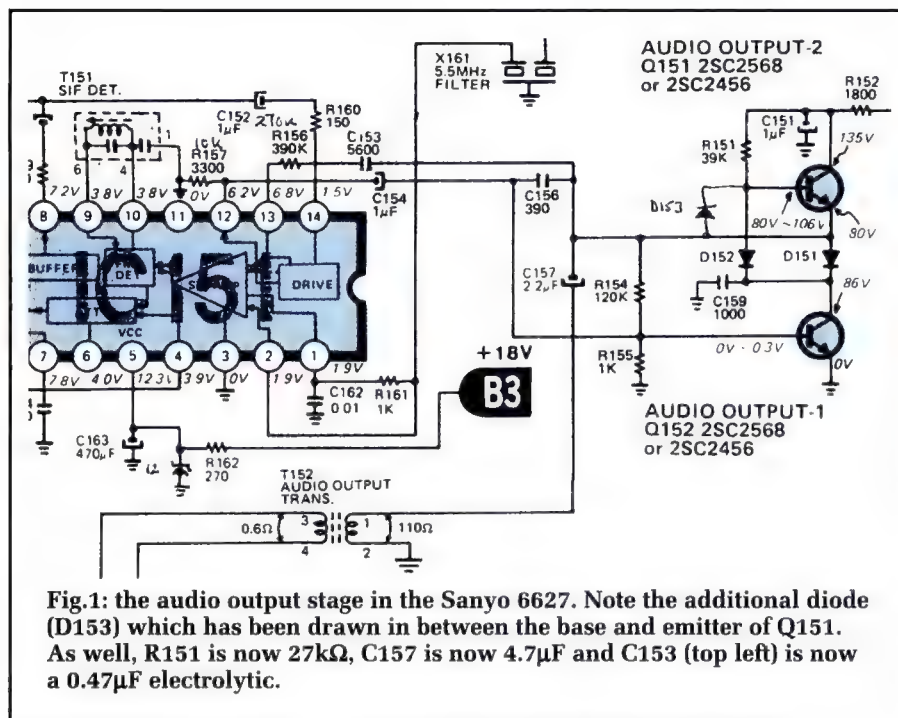

although it was a trifle grotty in places. And so I let myself be saddled with the monster.

It was quite an elaborate set, with most of the modern features: a very impressive remote control system, Teletext, and so on. As with any dead set, the first thing to check is the rail voltages and, by implication, the power supply. So I went straight to the power supply. And, yes, it was completely dead.

The supply itself is a fairly standard switchmode arrangement, the main difference being that, in order to accommodate the remote control on-off function, the supply runs continuously while ever the power point is on. The set itself is turned on or off via its 12V rail and this comes from IP61, an LM317T adjustable 3-terminal regulator. This regulator is in turn controlled by a signal from pin 7 of IR25.

In addition to the aforementioned 12V rail, there is also a 13V rail, a 22V rail and a 90V rail, the latter being the main supply rail. And, at first glance, there also appears to be a 17V rail emanating from the chopper transformer (UP40).

In fact, this is something of a furphy; the 17V rail is actually generated at pin 10 of the horizontal output transformer and this apparently takes over from the 13V rail (which feeds the regulator) once the horizontal stage fires up. (Note the arrow configuration on the 17V block).

## No voltage

More to the point, there was no voltage on any of these rails. I moved over to the primary side of the chopper transformer (UP40). There was voltage out of the bridge rectifier and, in fact, this was applying some 350V across the main filter capacitor (CP11 – 100µF). I traced this through the primary winding, pins 9 & 1, of the transformer to the collector of the chopper transistor, TP32.

I subsequently spent some time checking likely components around this stage but could find nothing wrong. But I did make one useful observation. With the CRO connected to the waveform points indicated on the circuit, I found that, at the moment of switching on, there was a very brief indication of activity but the waveforms vanished almost immediately. The stage was trying to oscillate but couldn't continue.

and replaced it. But I wasn't surprised when it had no effect.

Next I did a waveform check, right through the video chain, but could find nothing wrong. I stopped and had a think and a caffeine fix and went over the checks I had made.

And suddenly I became suspicious. I realised that all the voltages I had measured – EHT, screen, focus, RGB, etc – had all been marginally high. I hadn't taken as much notice of this as I should have, the complete picture failure suggesting a total loss of voltage somewhere.

Now I went back to taws – the main HT rail. And there was the answer, or part of it. Instead of the previous spot-on 220V, it was now 275V. It was only a symptom but it was a start. I went straight to the power supply and, after a few preliminary checks, attacked Q901, the power regulator. And that was it; it was short circuit.

I fitted a new one and switched on. And everything came up roses; 220V on the HT rail and a picture on the screen.

And that was the end of the drama. But why did the excessive HT rail voltage create the effect it did? Frankly, I don't know. I considered a number of likely reasons – including the possible action of an over-voltage protection circuit somewhere in the system – but I'm afraid I was too fed up with

the set to want to spend any more time trying to find out. I let it run for another day or so, then called the customer to come and collect it. And I was glad to see the back of it.

Granted, I was lucky in one way. At least those secondary faults occurred while the set was still on the bench. If I had returned the set immediately after fixing the first fault – as I might have done had the customer been in hurry – then I would have had it bounce. And that can generate bad will on the part of the customer.

So let's be thankful for small mercies.

## The crook Telefunken

My next story is about a Telefunken colour set. It used an ICC4 chassis and while it had its problems, it wasn't quite the headache of the previous story.

The set came from a colleague. He passed it over to me for a couple of reasons. First, he is not particularly keen on servicing European sets and, second, he was rather snowed under at the time and didn't want to be caught with something that might take up a lot of time. And I gathered that it had been through several other organisations before it came to him.

The complaint was quite straightforward; it was completely dead. Fortunately, my colleague had a circuit,



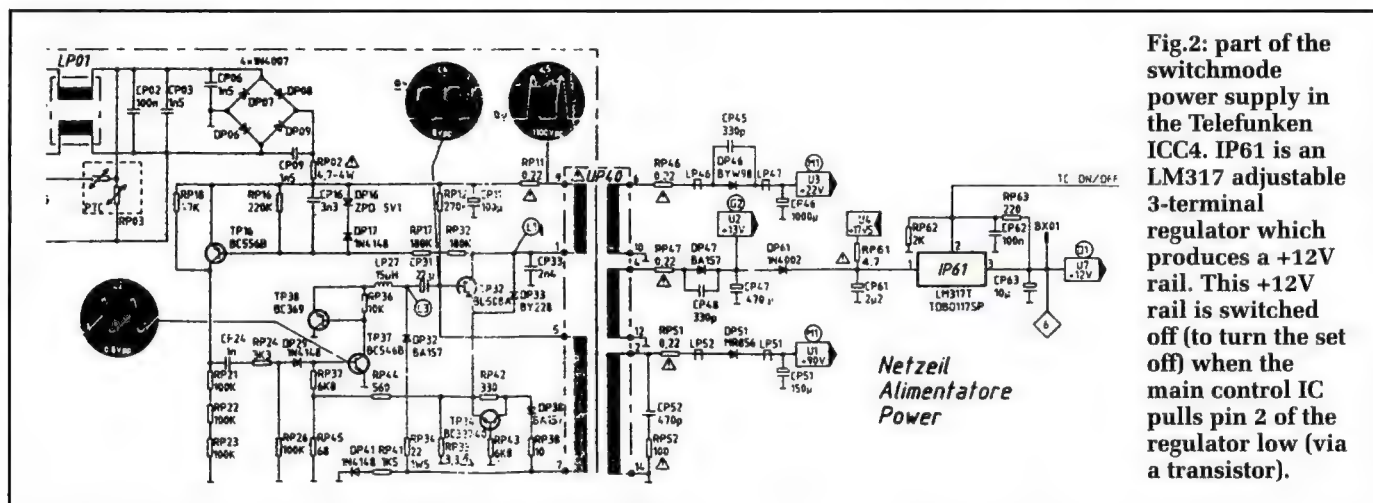


Fig.2: part of the switchmode power supply in the Telefunken ICC4. IP61 is an LM317 adjustable 3-terminal regulator which produces a +12V rail. This +12V rail is switched off (to turn the set off) when the main control IC pulls pin 2 of the regulator low (via a transistor).

This started a different train of thought. Perhaps there was a short circuit or overload on one of the rails which was placing an unacceptable load on the power supply?

First, I checked each rail with the ohmmeter but found nothing suspicious. This was not conclusive of course – there could still be a breakdown or leakage at the operating voltage, which would not show up with an ohmmeter check. I also checked the diodes supplying each of the rails. Again I drew a blank.

Next, I checked the horizontal output transistor, TL37 (BU508A), which connects to pin 2 of the horizontal output transformer (UL65) and thence

to the 90V rail via pin 6. This checked out OK.

On the basis of all these tests, and assuming that the overload theory was still a valid suspicion, the next obvious step was to disconnect each of the rails in turn. I started with the 90V rail by disconnecting the 0.22Ω safety resistor, RP51, at pin 2 of UP40.

As it turned out, this was the wrong way to do the right thing. It was right because the power supply now showed signs of life. Each of the other rails now came up, partially and briefly, and then died away. (On reflection, I suspect that the aforementioned weird 17V rail configuration had something to do with this strange behaviour).

Unfortunately, disconnecting the rail at that point was the wrong way to do it, because it was directly on the transformer pin and did not allow me to check the 90V rail itself.

I restored the 0.22Ω resistor and went back to the horizontal stage. This is a very complex arrangement and difficult to follow, both in the set and on the circuit. But the 90V rail goes to a choke (LL54), through diode DL56, and thence to pin 6 of the horizontal output transformer via LL57. And LL54 provided a convenient place to break the 90V rail and check it.

In fact, it did come good, in a similar manner to the way the other rails had responded. The rail was getting

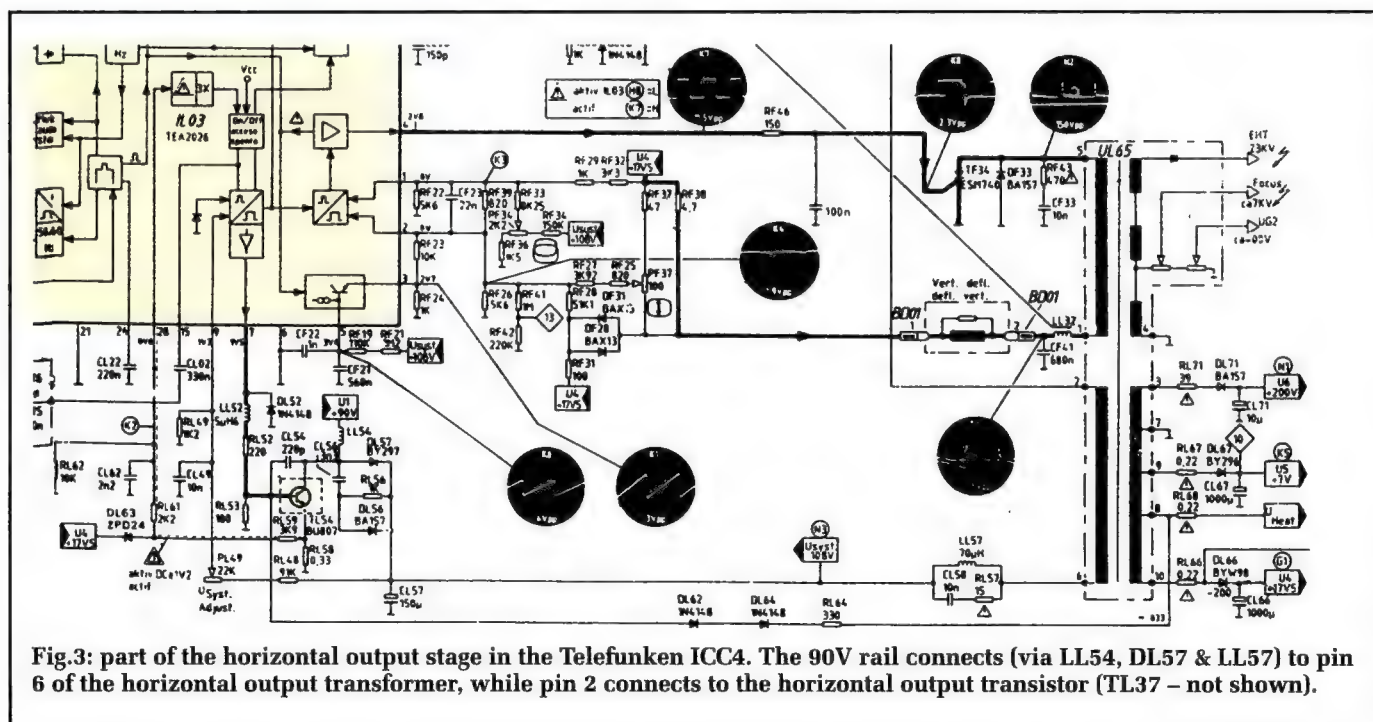


Fig.3: part of the horizontal output stage in the Telefunken ICC4. The 90V rail connects (via LL54, DL57 & LL57) to pin 6 of the horizontal output transformer, while pin 2 connects to the horizontal output transistor (TL37 – not shown).





**I NEEDED A NEW TRANSFORMER...**

warmer now. I restored the connection at LL54, then disconnected the rail at pin 6 of the transformer – same result.

So the fault was either somewhere on the other side of this transformer

all intact individually but when I happened to check between winding 2-6 and winding 1-5, I struck oil; there was a dead short between them.

Naturally, there was only one answer to a fault like that; I needed a

winding, in a circuit connected to one of the other windings, or in the winding itself. I restored the pin 6 connection and lifted the pin 2 connection. And it was a different story this time. I was now back to the original fault, with no voltage on any of the rails.

By now, I was becoming more and more suspicious of the transformer itself – so much so that I went for broke and pulled it out. My idea was to check it for shorted turns, which I felt was the most likely explanation.

But first I made a routine check of each winding with an ohmmeter. Well, they were

new transformer. But that had me worried initially because I knew of no current Australian agency for Telefunken. Fortunately, a few enquiries revealed that Hitachi use the same transformer, a type 243445. In fact, as I understand it, they actually make it and Telefunken buys it from them. Anyway, they are readily available, and one was obtained and fitted.


End of story? Not quite. Oh, the switchmode supply leapt into life alright at switch-on but there was one little snag – the set was still dead.

A quick check with the voltmeter provided the first clue; all the rails were up and spot on, at least out of the power supply. But there was no 12V rail out of pin 3 of regulator IP61. The reason wasn't hard to track down.

As mentioned earlier, IP61 is controlled by pin 7 of the remote control IC, IR25. This control signal is fed to pin 2 of IP61 via transistor TR74 (BC547B). And TR74 was shot – it was as simple as that.

A replacement BC547B was fitted and I finally had everything running at full bore. And a very nice result it was too. I gave the set the usual routine adjustment check, let it run for a day or so, and then passed it back to my colleague to return to his customer.

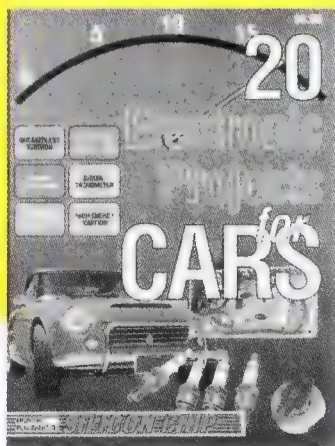It wasn't going to be cheap, of course, taking into account the new transformer. But that's the way it goes and I hope he was happy. **SC**



**Price:** \$8.95 plus \$3 for postage. Order by phoning (02) 9979 5644 & quoting your credit card number; or fax the details to (02) 9979 6503; or mail the coupon to Silicon Chip Publications, PO Box 139, Collaroy, NSW 2097.

## 20 Electronic Projects For Cars

**Yes!** Please send me \_\_\_ copies of **20 Electronic Projects For Cars**

Enclosed is my cheque/money order for \$\_\_\_\_\_ or please debit my

☐ Bankcard

☐ Visa Card

☐ Master Card

Card No.

Signature \_\_\_\_\_ Card expiry date \_\_\_\_/\_\_\_\_/\_\_\_\_

Name \_\_\_\_\_ Phone No (\_\_\_\_) \_\_\_\_\_

PLEASE PRINT

Street \_\_\_\_\_

Suburb/town \_\_\_\_\_ Postcode \_\_\_\_\_



# SILICON CHIP BOOK SHOP

## Newnes Guide to Satellite TV

*Installation, Reception & Repair. By Derek J. Stephenson. First published 1991, reprinted 1994 (3rd edition).*

This is a practical guide on the installation and servicing of satellite television equipment. The coverage of the subject is extensive, without excessive theory or mathematics. 371 pages, in hard cover at \$55.95.

## Servicing Personal Computers

*By Michael Tooley. First published 1985, 4th edition 1994.*

Computers are prone to failure from a number of common causes & some that are not so common. This book sets out the principles & practice of computer servicing (including disc drives, printers & monitors), describes some of the latest software diagnostic routines & includes program listings. 387 pages in hard cover at \$59.95.

## The Art of Linear Electronics

*By John Linsley Hood. Published 1993.*

This is a practical handbook from one of the world's most prolific audio designers, with many of his designs having been published in English technical magazines over the years. A great many practical circuits are featured - a must for anyone interested in audio design.

336 pages, in paperback at \$49.95.

## Optoelectronics: An Introduction

*By J. C. A. Chaimowicz. First published 1989, reprinted 1992.*

This particular field is about to explode and it is most important for engineers and technicians to bring themselves up to date. The subject is comprehensively covered, starting with optics and then moving into all aspects of fibre optic communications. 361 pages, in paperback at \$55.95.

## Digital Audio & Compact Disc Technology

*Produced by the Sony Service Centre (Europe). 3rd edition, published 1992.*

Prepared by Sony's technical staff, this is the best book on compact disc technology that we have ever come across. It covers digital audio in depth, including PCM adapters, the Video8 PCM format and R-DAT. If you want to understand digital audio, you need this reference book. 305 pages, in paperback at \$55.95.

## Power Electronics Handbook

*Components, Circuits & Applications, by F. F. Mazda. Published 1990.*

Previously a neglected field, power electronics has come into its own, particularly in the areas of traction



and electric vehicles. F. F. Mazda is an acknowledged authority on the subject and he writes mainly on the many uses of thyristors & Triacs in single and three phase circuits. 417 pages, in soft cover at \$59.95.

## Surface Mount Technology

*By Rudolph Strauss. First published 1994.*

This book will provide informative reading for anyone considering the assembly of PC boards with surface mounted devices. Includes chapters on wave soldering, reflow soldering, component placement, cleaning & quality control. 361 pages, in hard cover at \$99.00.

## Electronics Engineer's Reference Book

*Edited by F. F. Mazda. First published 1989, 6th edition 1994.*

This just has to be the best reference book available for electronics engineers. Provides expert coverage of all aspects of electronics in five parts: techniques, physical phenomena, material & components, electronic design, and applications. The sixth edition has been expanded to include chapters on surface mount

technology, hardware & software design, semicustom electronics & data communications. 63 chapters, in paperback at \$140.00.

## Radio Frequency Transistors

*Principles & Practical Applications. By Norm Dye & Helge Granberg. Published 1993.*

This timely book strips away the mysteries of RF circuit design. Written by two Motorola engineers, it looks at RF transistor fundamentals before moving on to specific design examples; eg, amplifiers, oscillators and pulsed power systems. Also included are chapters on filtering techniques, impedance matching & CAD. 235 pages, in hard cover at \$85.00.

## Newnes Guide to TV & Video Technology

*By Eugene Trundle. First published 1988, reprinted 1990, 1992.*

Eugene Trundle has written for many years in *Television* magazine and his latest book is right up date on TV and video technology. 432 pages, in paperback, at \$39.95.

Your Name \_\_\_\_\_  
PLEASE PRINT

Address \_\_\_\_\_

Postcode \_\_\_\_\_

Daytime Phone No. \_\_\_\_\_ Total Price \$A \_\_\_\_\_

☐ Cheque/Money Order ☐ Bankcard ☐ Visa Card ☐ MasterCard

Card No.

Signature \_\_\_\_\_ Card expiry date \_\_\_\_/\_\_\_\_/\_\_\_\_

Return to: Silicon Chip Publications, PO Box 139, Collaroy NSW, Australia 2097.  
Or call (02) 9979 5644 & quote your credit card details; or fax to (02) 9979 6503.

✓ Title	Price
<input type="checkbox"/> Newnes Guide to Satellite TV	\$55.95
<input type="checkbox"/> Servicing Personal Computers	\$59.95
<input type="checkbox"/> The Art Of Linear Electronics	\$49.95
<input type="checkbox"/> Optoelectronics: An Introduction	\$55.95
<input type="checkbox"/> Digital Audio & Compact Disc Technology	\$55.95
<input type="checkbox"/> Power Electronics Handbook	\$59.95
<input type="checkbox"/> Surface Mount Technology	\$99.00
<input type="checkbox"/> Electronic Engineer's Reference Book	\$140.00
<input type="checkbox"/> Radio Frequency Transistors	\$85.00
<input type="checkbox"/> Newnes Guide to TV & Video Technology	\$39.95
Postage: add \$5.00 per book. Orders over \$100 are post free within Australia. NZ & PNG add \$10.00 per book; elsewhere add \$15 per book.	
TOTAL \$A	



# VINTAGE RADIO

By JOHN HILL



## Anode bend to diode detection

**During the early to mid-1930s era, the low priced 5-valve superhet console radio was very popular. Many employed anode bend detection but they can be easily converted to diode detection for improved audio performance.**

The early '30s were the tough times of the Great Depression years, when about 25% of the workforce was out of work. And, of course, they were without the back-up support that the unemployed have today. This meant that any radio manufacturer who wanted to stay in business had to produce a range of receivers that were

affordable. The formula, in most cases, was to keep things fairly basic.

The usual format for these cheaper radios was the autodyne superhet – a 5-valve receiver with an autodyne mixer, IF stage, anode bend detector and a single output stage. Some designs used a 175kHz IF and this necessitated a pre-selector stage, using a

3-gang tuning capacitor, in order to control the double spot problem created by of such a low value.

Other makers chose a 455kHz IF, which was rapidly gaining popularity, and which solved the double spot problem automatically. This allowed the use of a cheaper 2-gang capacitor.

Either way, this broad design concept was a compromise between price and quality and while these sets worked reasonably well, they had several disadvantages.


### Design drawbacks

One problem was the lack of automatic gain control. This circuit innovation came into existence in the early 1930s but was only found on the more up-market receivers.


Another difficulty with the autodyne setup was that, while it worked OK on broadcast band frequencies, its performance on shortwave was not so good.

And finally, the anode bend detector used in these sets created a level of audio distortion that left something to be desired. While this distortion may have been acceptable in the 1930s, by today's standards it is not very good and can be quite distracting. It may have been fairly distracting in the 1930s too, because by the middle of that decade most manufacturers had changed to diode detection.

Some of those old receivers with anode bend detection sound better than others and in many instances the loudspeaker must play a part. The moving coil loudspeaker had been in existence for only a few years at that stage of radio development and there were still things to learn and manufacturing techniques to master. While an early '30s moving coil loudspeaker was a remarkable improvement on a '20s horn speaker, there was still quite

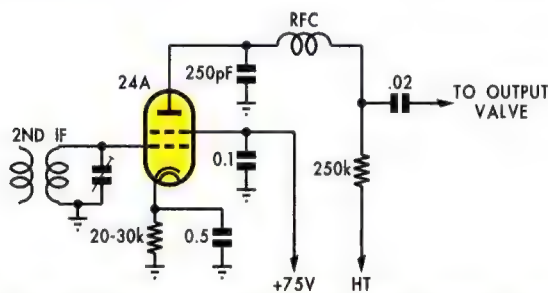

**Fig.1: the circuit of a typical anode bend detector. The valve type shown is a 24A tetrode or similar sharp cutoff tetrode. Later circuits used a type 57 pentode, although the basic arrangement remained the same.**

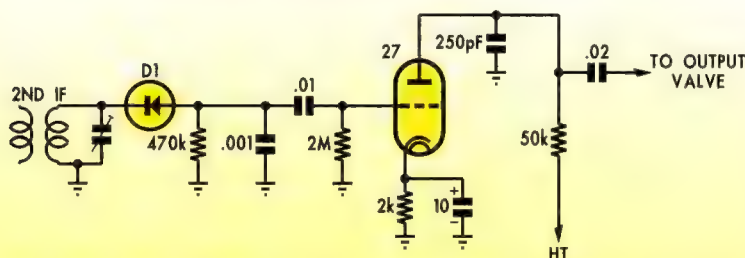

**Fig.2: this is what the circuit looked like after conversion to diode detection. The original type 24A tetrode was replaced by a type 27 triode valve.**



a lot of developmental work ahead of it.

### Basic circuit

Fig.1 shows the circuit of a typical anode bend detector. The valve type shown is a 24A or similar sharp cutoff tetrode. When the type 57 valve (a pentode) was developed, it replaced the radio frequency tetrode, although the circuit arrangements for anode bend detection were still the same.

The main aspect of the anode bend detection method is the very high cathode bias resistor, which operates the valve at close to cutoff. The term "cut-off" simply means that the anode or plate current will be at or near zero when no signal is being received.

When a modulated radio frequency (RF) signal is applied to the control grid, there will be pulses of anode current during the positive half cycles and little or no anode current during the negative half cycles. Therefore, the anode current is a rectified version of the signal waveform at the grid.

Filtering of the RF component after detection is achieved by a small plate bypass capacitor (typically around 250pF) to chassis and an RF choke in series with the plate load.

Anode bend detection has some odd characteristics and the distortion it produces can be minimised by varying the value of the cathode bias resistor.

However, if the cathode bias is selected to give good low distortion sound with a strong signal at the control grid, then the performance is not as good on a weak signal and vice versa. So, after much experimenting, the cathode circuit is often returned to its original form, as the manufacturer's setup was probably a reasonable compromise.

### Detector conversion

I have quite a number of old auto-dyne/anode bend console radios and I find some of them quite irritating due to their high levels of distortion. There are times I like to listen to my radios for hours on end and if they sound crook, there is no listening pleasure at all.

The last of these receivers to come off the restoration assembly line was an old 1932 Darelle (see June 1995). While the Darelle was no more annoying to listen to than any of the



Shown here is the Darelle 5-valve superhet cabinet. It is affectionately known as the "tea chest on legs". The Darelle's chassis was converted from anode bend detection to diode detection and this simple modification gave a significant improvement in sound quality.

others, it was the one I selected to see if the sound reproduction could be improved by converting the set to diode detection. The experiment produced a surprisingly good result, so allow me to fill you in on the details.

There are several choices when it comes to converting a set to diode detection. One can use either a valve with diodes in it, a triode connected as a diode, or do the unforgivable and use a germanium signal diode.


As the old Darelle used tetrode valves, there was no applicable diode type valve apart from the 55 duo-diode triode. The use of this valve would

require a valve socket change from 5-pin to 6-pin.

Using a triode connected as a diode was not an option either because there was insufficient room to accommodate it. So that left the unthinkable – a germanium signal diode.

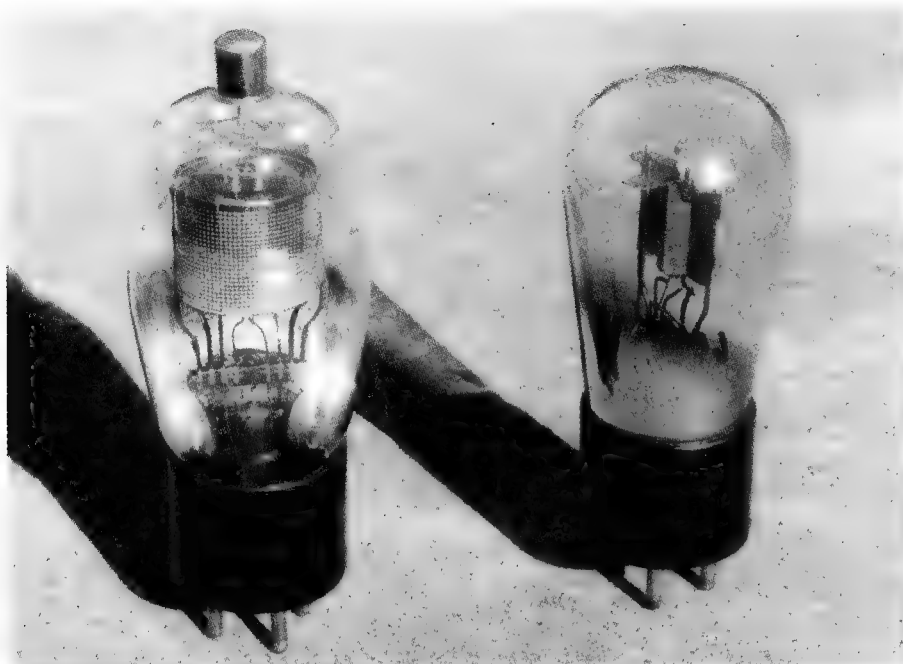Not being a modern electronics man, I was not really sure how to incorporate a solid state diode into a valve circuit. I mentioned what I planned to do to young David (a collector friend) and he drew up a circuit of what he thought I needed to make a solid state diode detector work in a valve receiver – see Fig.2. I might add that





The original anode bend detector valve was a 24A, as shown at left. This was replaced with a 27 triode (right) and this worked well as an audio amplifier, something that the 24A could not do.

David's circuit was a little more involved than what I had in mind.

Another aspect of my conversion was to retain the existing 24A anode bend detector valve and use it as an audio amplifier – if that was at all possible. David was not confident that this could be done but as I wanted to keep the original valve line-up, I would try to do it anyway. Whether or not it would be successful was in doubt at that stage.

Many radio frequency valves (the 57 and the 6J7 for example) can be used as audio valves when connected as either pentodes or triodes. Hopefully, the 24A would perform likewise, although there is no mention of audio frequency application in the valve manual. (Editorial comment: the 24A, being a tetrode – as distinct from the above mentioned pentodes – is

less suitable for use as a resistance/capacitor coupled audio amplifier. When it was used as an audio amplifier, it was usually in the choke/capacitor coupling mode. This permits a much greater plate voltage signal swing without distortion).

The detector circuit was made up on a small piece of tagstrip to form a compact detector module (see photo). This module was then bolted to a convenient part of the chassis and wired to the second IF transformer and the control grid of what was the anode bend detector. But while the set worked, one could not say that it was working well.

Actually, the sound quality was really good at moderate volume levels, but distorted badly as the volume increased.

Various alterations were made to

the 24A audio amplifier. It was tried as a tetrode, a triode, with high and low plate voltages, and with a variety of cathode bias setups. None proved to be really satisfactory, although the triode connection wasn't too bad except for a drop in overall volume. It had to be considered unsatisfactory for that reason alone.

## Valve replacement

It was time to do what should have been done in the first place and that is fit a valve that was more suitable for audio frequency work than a 24A. A 27 was a logical choice as its 5-pin base was compatible with the existing valve socket. Rewiring the socket to suit the triode valve required a couple of alterations, as the 27 has no top-cap grid connection.

After fitting the 27, all the previous problems associated with the diode detection modification suddenly disappeared. Triode audio amplifiers were all the go in the early 1930s and a triode also proved to be most successful with this particular circuit arrangement.


Once everything was working OK, it was time to experiment a little. The detection module was disconnected and another signal diode substituted. This setup used no grid leak, no coupling capacitor or anything else – just the diode between the IF transformer and the grid of the valve. It made little difference apart from an ever so slight increase in volume.

So it would appear as though there are many ways to incorporate a signal diode into a valve circuit – and they will all probably work. However, if one decides to do this modification, remember that the second IF transformer will require realignment. That would be about the only inconvenience incurred.

After this little experiment, the original detector module was reconnected into the circuit.

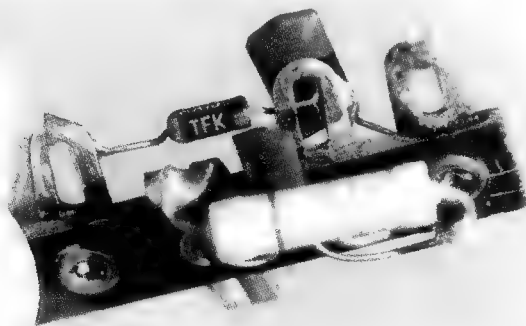
## Practicality vs originality

No doubt some readers will have difficulty in understanding why I would want to modify an existing circuit and ruin the set's originality! Well, in this case, I want to listen to the radio and not be annoyed by it. It is as simple as that! What's more, if a receiver can be significantly improved by implementing such a simple modification, then why not do it? In this




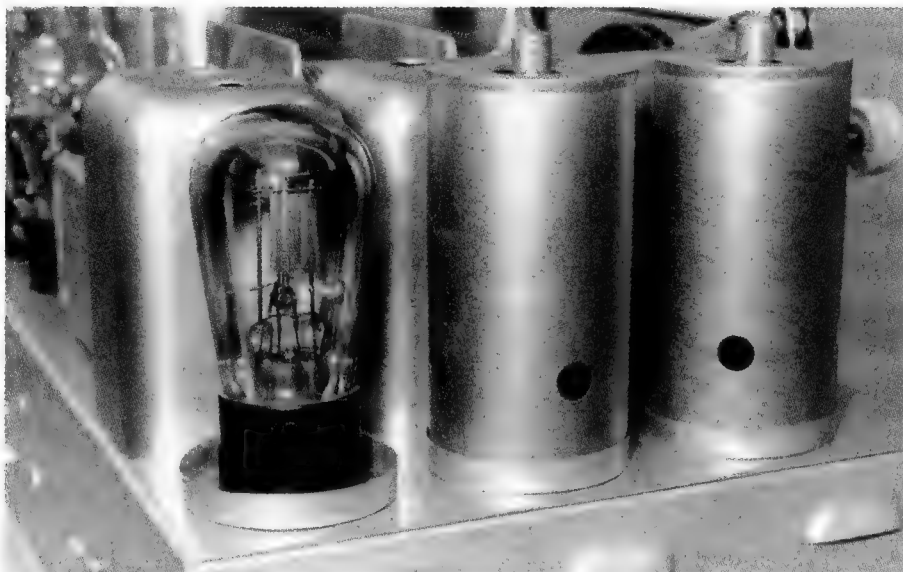The diode detector module was built from miscellaneous components mounted on a tagstrip. The small size of the module allows it to be mounted in some out-of-sight location if so desired.





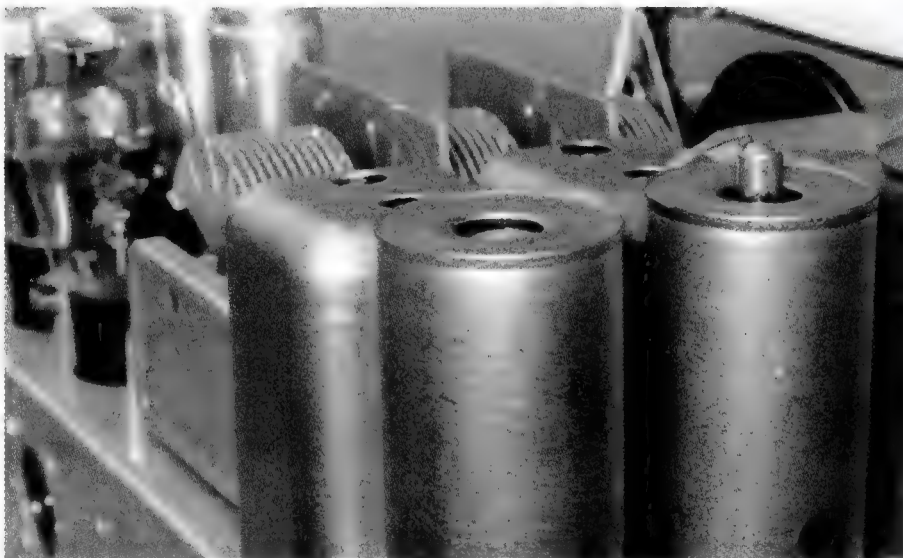Efforts to use the original 24A valve failed miserably. Substituting the 27 involved some socket rewiring and the removal of the top-cap connector. It was worth the effort, as it solved the problem of trying to use the 24A in a role for which it was never intended.



The missing top-cap and connector may look a bit odd but so be it! Removing the anode bend detector and replacing it with diode detection was an experiment that paid off with a cleaner audio output.

instance, the improvement was well worth the effort.


Should a future owner wish to convert the receiver back to original, it can easily be returned to its anode bend state. Why someone would want to do this I don't know, but if they did, they may not be happy with the distortion that this detection method produces.

The diode detector described here can be a completely invisible modification if so desired. Although I chose to mount the diode and accompanying components on a small tag strip

underneath the chassis, there is no reason why it cannot be housed inside the second IF transformer shield can or positioned in some other out-of-the-way place where it is out of sight.

As far as I'm concerned, if everything looks OK then that's all that matters. A few devious modifications here and there don't upset me in the least, especially if they improve the set's performance. The fact that the old Darelle sounds a bit better than most radios from that era must be worth something! **SC**

## RESURRECTION RADIO

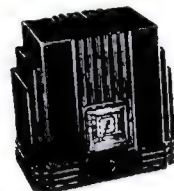

**VALVE EQUIPMENT SPECIALISTS**  
**Repairs to valve radios, guitar**  
**and audio amplifiers.**

### Books for holiday reading:

Golden Age of Radio In the Home .....	\$42.95
More Golden Age of Radio .....	\$49.95
Old Time Radios Restoration & Repair .....	\$36.95
70 Years of Radio Tubes & Valves .....	\$42.95
Crystal Sets 'n' Such .....	\$19.95
In Marconi's Footsteps .....	\$49.95
The Complete Talking Machine .....	\$39.95
An Approach to Audio Frequency Design ..	\$39.95
The Audio Designer's Tube Register .....	\$36.95

**Send SSAE for Catalogue**

**Visit our Showroom at**  
**242 Chapel Street (PO Box**  
**2029) PRAHRAN, VIC 3181**

**Tel: (03) 9510 4486; Fax (03) 9529 5639**

## Silicon Chip Binders



These beautifully-made binders will protect your copies of SILICON CHIP. They are made from a distinctive 2-tone green vinyl & will look great on your bookshelf.

Price: \$A11.95 plus \$3 p&p each (NZ \$8 p&p). Send your order to:

**Silicon Chip Publications**  
**PO Box 139**  
**Collaroy Beach 2097**

Or fax (02) 9979 6503; or ring (02) 9979 5644 & quote your credit card number.



# Silicon Chip BACK ISSUES

**September 1988:** Hands-Free Speakerphone; Electronic Fish Bite Detector; High Performance AC Millivoltmeter, Pt.2; Build The Vader Voice.

**April 1989:** Auxiliary Brake Light Flasher; What You Need to Know About Capacitors; 32-Band Graphic Equaliser, Pt.2; LED Message Board, Pt.2.

**May 1989:** Build A Synthesised Tom-Tom; Biofeedback Monitor For Your PC; Simple Stub Filter For Suppressing TV Interference; LED Message Board, Pt.3.

**July 1989:** Exhaust Gas Monitor (Uses TGS812 Gas Sensor); Extension For The Touch-Lamp Dimmer; Experimental Mains Hum Sniffers; Compact Ultrasonic Car Alarm.

**September 1989:** 2-Chip Portable AM Stereo Radio (Uses MC13024 and TX7376P) Pt.1; High Or Low Fluid Level Detector; Studio Series 20-Band Stereo Equaliser, Pt.2; Auto-Zero Module for Audio Amplifiers (Uses LMC669).

**October 1989:** FM Radio Intercom For Motorbikes Pt.1; GaAsFet Preamp For Amateur TV; 1Mb Printer Buffer; 2-Chip Portable AM Stereo Radio, Pt.2; Installing A Hard Disc In The PC.

**November 1989:** Radfax Decoder For Your PC (Displays Fax, RTTY & Morse); FM Radio Intercom For Motorbikes, Pt.2; 2-Chip Portable AM Stereo Radio, Pt.3; Floppy Disc Drive Formats & Options; The Pilbara Iron Ore Railways.

**December 1989:** Digital Voice Board; UHF Remote Switch; Balanced Input & Output Stages; Data For The LM831 Low Voltage Amplifier IC; Index to Volume 2.

**January 1990:** High Quality Sine/Square Oscillator; Service

Tips For Your VCR; Speeding Up Your PC; Phone Patch For Radio Amateurs; Active Antenna Kit; Speed Controller For Ceiling Fans; Designing UHF Transmitter Stages.

**February 1990:** 16-Channel Mixing Desk; High Quality Audio Oscillator, Pt.2; The Incredible Hot Canaries; Random Wire Antenna Tuner For 6 Metres; Phone Patch For Radio Amateurs, Pt.2.

**March 1990:** 6/12V Charger For Sealed Lead-Acid Batteries; Delay Unit For Automatic Antennas; Workout Timer For Aerobics Classes; 16-Channel Mixing Desk, Pt.2; Using The UC3906 SLA Battery Charger IC.

**April 1990:** Dual Tracking  $\pm 50V$  Power Supply; Voice-Operated Switch (VOX) With Delayed Audio; 16-Channel Mixing Desk, Pt.3; Active CW Filter For Weak Signal Reception; How To Find Vintage Receivers From The 1920s.

**June 1990:** Multi-Sector Home Burglar Alarm; Low-Noise Universal Stereo Preamp; Load Protection Switch For Power Supplies; A Speed Alarm For Your Car; Fitting A Fax Card To A Computer.

**July 1990:** Digital Sine/Square Generator, Pt.1 (Covers 0-500kHz); Burglar Alarm Keypad & Combination Lock; Simple Electronic Die; Low-Cost Dual Power Supply; Inside A Coal Burning Power Station.

**August 1990:** High Stability UHF Remote Transmitter; Universal Safety Timer For Mains Appliances (9 Minutes); Horace The Electronic Cricket; Digital Sine/Square Generator, Pt.2.

**September 1990:** Remote Control Extender For VCRs; Power Supply For Burglar Alarms; Low-Cost 3-Digit Counter Module; Simple Shortwave Converter For The 2-Metre Band.

**October 1990:** Low-Cost Siren For Burglar Alarms; Dimming Controls For The Disc Light; Surf Sound Simulator; DC Offset For DMMs; Using The NE602 In Home-Brew Converter Circuits.

**November 1990:** How To Connect Two TV Sets To One VCR; A Really Snazzy Egg Timer; Low-Cost Model Train Controller; Battery Powered Laser Pointer; 1.5V To 9V DC Converter; Introduction To Digital Electronics; Simple 6-Metre Amateur Transmitter.

**December 1990:** DC-DC Converter For Car Amplifiers; The Big Escape - A Game Of Skill; Wiper Pulsar For Rear Windows; A 4-Digit Combination Lock; 5W Power Amplifier For The 6-Metre Amateur Transmitter; Index To Volume 3.

**January 1991:** Fast Charger For Nicad Batteries, Pt.1; Have Fun With The Fruit Machine; Two-Tone Alarm Module; LCD Readout For The Capacitance Meter; How Quartz Crystals Work; The Dangers When Servicing Microwave Ovens.

**February 1991:** Synthesised Stereo AM Tuner, Pt.1; Three Inverters For Fluorescent Lights; Low-Cost Sinewave Oscillator; Fast Charger For Nicad Batteries, Pt.2; How To Design Amplifier Output Stages

**March 1991:** Remote Controller For Garage Doors, Pt.1; Transistor Beta Tester Mk.2; A Synthesised AM Stereo Tuner, Pt.2; Multi-Purpose I/O Board For PC-Compatibles; Universal Wideband RF Preamp For Amateur Radio & TV.

**April 1991:** Steam Sound Simulator For Model Railroads; Remote Controller For Garage Doors, Pt.2; Simple 12/24V Light Chaser; Synthesised AM Stereo Tuner, Pt.3; A Practical Approach To Amplifier Design, Pt.2.

**May 1991:** 13.5V 25A Power Supply For Transceivers; Stereo Audio Expander; Fluorescent Light Simulator For Model Railways; How To Install Multiple TV Outlets, Pt.1.

**June 1991:** A Corner Reflector Antenna For UHF TV; 4-Channel Lighting Desk, Pt.1; 13.5V 25A Power Supply For Transceivers; Active Filter For CW Reception; Tuning In To Satellite TV, Pt.1.

**July 1991:** Battery Discharge Pacer For Electric Vehicles; Loudspeaker Protector For Stereo Amplifiers; 4-Channel Lighting Desk, Pt.2; How To Install Multiple TV Outlets, Pt.2; Tuning In To Satellite TV, Pt.2.

## ORDER FORM

Please send me a back issue for:

- |   |   |
|---|---|
| <input type="checkbox"/> July 1989      | <input type="checkbox"/> September 1989 |
| <input type="checkbox"/> January 1990   | <input type="checkbox"/> February 1990  |
| <input type="checkbox"/> July 1990      | <input type="checkbox"/> August 1990    |
| <input type="checkbox"/> December 1990  | <input type="checkbox"/> January 1991   |
| <input type="checkbox"/> May 1991       | <input type="checkbox"/> June 1991      |
| <input type="checkbox"/> October 1991   | <input type="checkbox"/> November 1991  |
| <input type="checkbox"/> April 1992     | <input type="checkbox"/> May 1992       |
| <input type="checkbox"/> September 1992 | <input type="checkbox"/> October 1992   |
| <input type="checkbox"/> April 1993     | <input type="checkbox"/> May 1993       |
| <input type="checkbox"/> September 1993 | <input type="checkbox"/> October 1993   |
| <input type="checkbox"/> February 1994  | <input type="checkbox"/> March 1994     |
| <input type="checkbox"/> July 1994      | <input type="checkbox"/> August 1994    |
| <input type="checkbox"/> December 1994  | <input type="checkbox"/> January 1995   |
| <input type="checkbox"/> May 1995       | <input type="checkbox"/> June 1995      |
| <input type="checkbox"/> October 1995   | <input type="checkbox"/> November 1995  |

- |   |
|---|
| <input type="checkbox"/> September 1988 |
| <input type="checkbox"/> October 1989   |
| <input type="checkbox"/> March 1990     |
| <input type="checkbox"/> September 1990 |
| <input type="checkbox"/> February 1991  |
| <input type="checkbox"/> July 1991      |
| <input type="checkbox"/> December 1991  |
| <input type="checkbox"/> June 1992      |
| <input type="checkbox"/> January 1993   |
| <input type="checkbox"/> June 1993      |
| <input type="checkbox"/> November 1993  |
| <input type="checkbox"/> April 1994     |
| <input type="checkbox"/> September 1994 |
| <input type="checkbox"/> February 1995  |
| <input type="checkbox"/> July 1995      |
| <input type="checkbox"/> December 1995  |

- |  |
|--|
| <input type="checkbox"/> April 1989    |
| <input type="checkbox"/> November 1989 |
| <input type="checkbox"/> April 1990    |
| <input type="checkbox"/> October 1990  |
| <input type="checkbox"/> March 1991    |
| <input type="checkbox"/> August 1991   |
| <input type="checkbox"/> January 1992  |
| <input type="checkbox"/> July 1992     |
| <input type="checkbox"/> February 1993 |
| <input type="checkbox"/> July 1993     |
| <input type="checkbox"/> December 1993 |
| <input type="checkbox"/> May 1994      |
| <input type="checkbox"/> October 1994  |
| <input type="checkbox"/> March 1995    |
| <input type="checkbox"/> August 1995   |

- |   |
|---|
| <input type="checkbox"/> May 1989       |
| <input type="checkbox"/> December 1989  |
| <input type="checkbox"/> June 1990      |
| <input type="checkbox"/> November 1990  |
| <input type="checkbox"/> April 1991     |
| <input type="checkbox"/> September 1991 |
| <input type="checkbox"/> March 1992     |
| <input type="checkbox"/> August 1992    |
| <input type="checkbox"/> March 1993     |
| <input type="checkbox"/> August 1993    |
| <input type="checkbox"/> January 1994   |
| <input type="checkbox"/> June 1994      |
| <input type="checkbox"/> November 1994  |
| <input type="checkbox"/> April 1995     |
| <input type="checkbox"/> September 1995 |

Enclosed is my cheque/money order for \$\_\_\_\_\_ or please debit my: ☐ Bankcard ☐ Visa Card ☐ Master Card

Card No. \_\_\_\_\_

Signature \_\_\_\_\_ Card expiry date \_\_\_\_/\_\_\_\_/\_\_\_\_

Name \_\_\_\_\_ Phone No (\_\_\_\_) \_\_\_\_\_

PLEASE PRINT

Street \_\_\_\_\_

Suburb/town \_\_\_\_\_ Postcode \_\_\_\_\_

**Note: all prices include post & packing**

Australia (by return mail) ..... \$A7  
NZ & PNG (airmail) ..... \$A7  
Overseas (airmail) ..... \$A10

**Detach and mail to:**

**Silicon Chip Publications, PO Box 139,  
Collaroy, NSW, Australia 2097.**

Or call (02) 979 5644 & quote your credit card details or fax the details to (02) 979 6503.





**August 1991:** Build A Digital Tachometer; Masthead Amplifier For TV & FM; PC Voice Recorder; Tuning In To Satellite TV, Pt.3; Step-By-Step Vintage Radio Repairs.

**September 1991:** Studio 3-55L 3-Way Loudspeaker System; Digital Altimeter For Gliders & Ultralights, Pt.1; The Basics Of A/D & D/A Conversion; Windows 3 Swapfiles, Program Groups & Icons.

**October 1991:** Build A Talking Voltmeter For Your PC, Pt.1; SteamSound Simulator For Model Railways Mk.II; Magnetic Field Strength Meter; Digital Altimeter For Gliders & Ultralights, Pt.2; Getting To Know The Windows PIF Editor.

**November 1991:** Colour TV Pattern Generator, Pt.1; Battery Charger For Solar Panels; Flashing Alarm Light For Cars; Digital Altimeter For Gliders & Ultralights, Pt.3; Build A Talking Voltmeter For Your PC, Pt.2.

**December 1991:** TV Transmitter For VCRs With UHF Modulators; Infrared Light Beam Relay; Solid-State Laser Pointer; Colour TV Pattern Generator, Pt.2; Index To Volume 4.

**January 1992:** 4-Channel Guitar Mixer; Adjustable 0-45V 8A Power Supply, Pt.1; Baby Room Monitor/FM Transmitter; Experiments For Your Games Card.

**March 1992:** TV Transmitter For VHF VCRs; Studio Twin Fifty Stereo Amplifier, Pt.1; Thermostatic Switch For Car Radiator Fans; Telephone Call Timer; Coping With Damaged Computer Directories; Valve Substitution In Vintage Radios.

**April 1992:** IR Remote Control For Model Railroads; Differential Input Buffer For CROs; Studio Twin Fifty Stereo Amplifier, Pt.2; Understanding Computer Memory; Aligning Vintage Radio Receivers, Pt.1.

**May 1992:** Build A Telephone Intercom; Low-Cost Electronic Doorbell; Battery Eliminator For Personal Players; Infrared Remote Control For Model Railroads, Pt.2; Aligning Vintage Radio Receivers, Pt.2.

**June 1992:** Multi-Station Headset Intercom, Pt.1; Video Switcher For Camcorders & VCRs; Infrared Remote Control For Model Railroads, Pt.3; 15-Watt 12-240V Inverter; A Look At Hard Disc Drives.

**July 1992:** Build A Nicad Battery Discharger; 8-Station Automatic Sprinkler Timer; Portable 12V SLA Battery Charger; Multi-Station Headset Intercom, Pt.2.

**August 1992:** Build An Automatic SLA Battery Charger; Miniature 1.5V To 9V DC Converter; Dummy Load Box For Large Audio Amplifiers; Troubleshooting Vintage Radio Receivers.

**September 1992:** Multi-Sector Home Burglar Alarm; Heavy-Duty 5A Drill Speed Controller (see errata Nov. 1992); General-Purpose 3½-Digit LCD Panel Meter; Track Tester For Model Railroads; Build A Relative Field Strength Meter.

**October 1992:** 2kW 24VDC To 240VAC Sinewave Inverter; Multi-Sector Home Burglar Alarm, Pt.2; Mini Amplifier For Personal Stereos; Build A Regulated Lead-Acid Battery Charger.

**January 1993:** Peerless PSK60/2 2-Way HiFi Loudspeakers; Flea-Power AM Radio Transmitter; High Intensity LED Flasher For Bicycles; 2kW 24VDC To 240VAC Sinewave Inverter, Pt.4; Speed Controller For Electric Models, Pt.3.

**February 1993:** Three Projects For Model Railroads; Low Fuel Indicator For Cars; Audio Level/VU Meter (LED Readout); An Electronic Cockroach; MAL-4 Microcontroller Board, Pt.3; 2kW 24VDC To 240VAC Sinewave Inverter, Pt.5.

**March 1993:** Build A Solar Charger For 12V Batteries; Alarm-Triggered Security Camera; Low-Cost Audio Mixer For Camcorders; A 24-Hour Sidereal Clock For Astronomers.

**April 1993:** Solar-Powered Electric Fence; Build An Audio Power Meter; Three-Function Home Weather Station; 12VDC To 70VDC Step-Up Voltage Converter; Digital Clock With Battery Back-Up.

**May 1993:** Nicad Cell Discharger; Build The Woofer Stopper; Remote Volume Control For HiFi Systems, Pt.1; Alpha-numeric LCD Demonstration Board; The Microsoft Windows Sound System.

**June 1993:** Build An AM Radio Trainer, Pt.1; Remote Control For The Woofer Stopper; Digital Voltmeter For Cars; Remote Volume Control For HiFi Systems, Pt.2.

**July 1993:** Single Chip Message Recorder; Light Beam Relay Extender; AM Radio Trainer, Pt.2; Quiz Game Adjudicator; Programming The Motorola 68HC705C8 – Lesson 1; Antenna Tuners – Why They Are Useful.

**August 1993:** Low-Cost Colour Video Fader; 60-LED Brake Light Array; A Microprocessor-Based Sidereal Clock; The Southern Cross Z80-Based Computer; A Look At Satellites & Their Orbits.

**September 1993:** Automatic Nicad Battery Charger/Discharger; Stereo Preamplifier With IR Remote Control, Pt.1; In-Circuit Transistor Tester; A +5V to ±15V DC Converter; Remote-Controlled Cockroach.

**October 1993:** Courtesy Light Switch-Off Timer For Cars; Wireless Microphone For Musicians; Stereo Preamplifier With IR Remote Control, Pt.2; Electronic Engine Management, Pt.1; Programming The Motorola 68HC705C8 – Lesson 2.

**November 1993:** Jumbo Digital Clock; High Efficiency Inverter For Fluorescent Tubes; Stereo Preamplifier With IR Remote Control, Pt.3; Siren Sound Generator; Electronic Engine Management, Pt.2; Experiments For Games Cards.

**December 1993:** Remote Controller For Garage Doors; Low-Voltage LED Stroboscope; Low-Cost 25W Amplifier Module; Build A 1-Chip Melody Generator; Electronic Engine Management, Pt.3; Index To Volume 6.

**January 1994:** 3A 40V Adjustable Power Supply; Switching Regulator For Solar Panels; Printer Status Indicator; Mini Drill Speed Controller; Stepper Motor Controller; Active Filter Design; Electronic Engine Management, Pt.4.

**February 1994:** 90-Second Message Recorder; Compact & Efficient 12-240VAC 200W Inverter; Single Chip 0.5W Audio Amplifier; 3A 40V Adjustable Power Supply; Electronic Engine Management, Pt.5; Airbags – How They Work.

**March 1994:** Intelligent IR Remote Controller; Build A 50W Audio Amplifier Module; Level Crossing Detector For Model Railroads; Voice Activated Switch For FM Microphones; Simple LED Chaser; Electronic Engine Management, Pt.6.

**April 1994:** Remote Control Extender For VCRs; Sound & Lights For Model Railway Level Crossings; Discrete Dual Supply Voltage Regulator; Low-Noise Universal Stereo Preamplifier; Build A Digital Water Tank Gauge; Electronic Engine Management, Pt.7.

**May 1994:** Fast Charger For Nicad Batteries; Induction Balance Metal Locator; Multi-Channel Infrared Remote Control; Dual Electronic Dice; Two Simple Servo Driver Circuits; Electronic Engine Management, Pt.8; Passive Rebroadcasting For TV Signals.

**June 1994:** 200W/350W Mosfet Amplifier Module; A Coolant Level Alarm For Your Car; An 80-Metre AM/CW Transmitter For Amateurs; Converting Phono Inputs To Line Inputs; A PC-Based Nicad Battery Monitor; Electronic Engine Management, Pt.9.

**July 1994:** Build A 4-Bay Bow-Tie UHF Antenna; PreChomp 2-Transistor Preamplifier; Steam Train Whistle & Diesel Horn Simulator; Portable 6V SLA Battery Charger; Electronic Engine Management, Pt.10.

**August 1994:** High-Power Dimmer For Incandescent Lights; Microprocessor-Controlled Morse Keyer; Dual Diversity Tuner For FM Microphones, Pt.1; Build A Nicad Zapper; Simple Crystal Checker; Electronic Engine Management, Pt.11.

**September 1994:** Automatic Discharger For Nicad Battery Packs; MiniVox Voice Operated Relay; Image Intensified Night Viewer; AM Radio For Aircraft Weather Beacons; Dual Diversity Tuner For FM Microphones, Pt.2; Electronic Engine Management, Pt.12.

**October 1994:** Dolby Surround Sound – How It Works; Dual Rail Variable Power Supply (±1.25V to ±15V); Talking Headlight Reminder; Electronic Ballast For Fluorescent Lights; Temperature Controlled Soldering Station; Electronic Engine Management, Pt.13.

**November 1994:** Dry Cell Battery Rejuvenator; A Novel Alphanumeric Clock; 80-Metre DSB Amateur Transmitter; Twin-Cell Nicad Discharger (See May 1993); Anti-Lock Braking Systems; How To Plot Patterns Direct To PC Boards.

**December 1994:** Dolby Pro-Logic Surround Sound Decoder, Pt.1; Easy-To-Build Car Burglar Alarm; Three-Spot Low Distortion Sinewave Oscillator; Clifford – A Pesky Electronic Cricket; Cruise Control – How It Works; Remote Control System For Models, Pt.1; Index to Vol.7.

**January 1995:** Sun Tracker For Solar Panels; Battery Saver For Torches; Dolby Pro-Logic Surround Sound Decoder, Pt.2; Dual Channel UHF Remote Control; Stereo Microphone Preamplifier; The Latest Trends In Car Sound; Pt.1.

**February 1995:** 50-Watt/Channel Stereo Amplifier Module; Digital Effects Unit For Musicians; 6-Channel Thermometer With LCD Readout; Wide Range Electrostatic Loudspeakers, Pt.1; Oil Change Timer For Cars; The Latest Trends In Car Sound; Pt.2; Remote Control System For Models, Pt.2.

**March 1995:** 50W/Channel Stereo Amplifier, Pt.1; Subcarrier Decoder For FM Receivers; Wide Range Electrostatic Loudspeakers, Pt.2; IR Illuminator For CCD Cameras; Remote Control System For Models, Pt.3; Simple CW Filter.

**April 1995:** Build An FM Radio Trainer, Pt.1; Photographic Timer For Darkrooms; Balanced Microphone Preamplifier & Line Filter; 50W/Channel Stereo Amplifier, Pt.2; Wide Range Electrostatic Loudspeakers, Pt.3; 8-Channel Decoder For Radio Remote Control.

**May 1995:** Introduction To Satellite TV; CMOS Memory Settings – What To Do When The Battery On Your Motherboard Goes Flat; Mains Music Transmitter & Receiver; Guitar Headphone Amplifier For Practice Sessions; Build An FM Radio Trainer, Pt.2; Low Cost Transistor & Mosfet Tester For DMMs; 16-Channel Decoder For Radio Remote Control.

**June 1995:** Build A Satellite TV Receiver; Train Detector For Model Railroads; A 1W Audio Amplifier Trainer; Low-Cost Video Security System; A Multi-Channel Radio Control Transmitter For Models, Pt.1; Build A \$30 Digital Multimeter.

**July 1995:** Low-Power Electric Fence Controller; How To Run Two Trains On A Single Track (Plus Level Crossing Lights & Sound Effects); Setting Up A Satellite TV Ground Station; Build A Door Minder; Adding RAM To A Computer.

**August 1995:** Vifa JV-60 2-Way Bass Reflex Loudspeaker System; A Fuel Injector Monitor For Cars; Gain Controlled Microphone Preamp; The Audio Lab PC Controlled Test Instrument, Pt.1; The Mighty-Mite Powered Loudspeaker; An Easy Way To Identify IDE Hard Disc Drive Parameters.

**September 1995:** A Keypad Combination Lock; The Incredible Vader Voice; Railpower Mk.2 Walk-Around Throttle For Model Railroads, Pt.1; Build A Jacob's Ladder Display; The Audio Lab PC Controlled Test Instrument, Pt.2; Automotive Ignition Timing, Pt.1.

**October 1995:** Build A Compact Geiger Counter; 3-Way Bass Reflex Loudspeaker System; Railpower Mk.2 Walk-Around Throttle For Model Railroads, Pt.2; Fast Charger For Nicad Batteries; Digital Speedometer & Fuel Gauge For Cars, Pt.1; Automotive Ignition Timing, Pt.2.

**November 1995:** LANsmart – A LAN For Home Or A Small Office; Mixture Display For Fuel Injected Cars; CB Transverter For The 80M Amateur Band, Pt.1; Low Cost PIR Movement Detector; Dolby Pro Logic Surround Sound Decoder Mk.2, Pt.1; Digital Speedometer & Fuel Gauge For Cars, Pt.2.

**December 1995:** Engine Immobiliser For Cars; Five Band Equaliser For Musicians; CB Transverter For The 80M Amateur Band, Pt.2; Build A Subwoofer Controller; Dolby Pro Logic Surround Sound Decoder Mk.2, Pt.2; Knock Sensing In Cars; RAM Doubler Reviewed; Index To Volume 8.

**PLEASE NOTE:** November 1987 to August 1988, October 1988 to March 1989, June 1989, August 1989, May 1990, February 1992, November 1992 and December 1992 are now sold out. All other issues are presently in stock. For readers wanting articles from sold-out issues, we can supply photostat copies (or tearsheets) at \$7.00 per article (includes p.&p.). When supplying photostat articles or back copies, we automatically supply any relevant notes & errata at no extra charge.



# ASK SILICON CHIP

Got a technical problem? Can't understand a piece of jargon or some technical principle? Drop us a line and we'll answer your question. Write to: Ask Silicon Chip, PO Box 139, Collaroy Beach, NSW 2097.

## Sins of omission in a preamplifier

I recently constructed the Low Noise Universal Preamplifier as described in April 1994, for use with a pair of unbalanced binaural microphones. During construction, I decided to omit all components between the input pins and the op amp, as these seemed to relate largely to the phono preamp version. Any comments? It seems to work perfectly well. Would the omitted part of the circuit have made any difference or improvement?

As part of the same project, I intend to build balanced outputs. The December 1989 issue of SILICON CHIP gives a design utilising a pair of LM833s per channel to provide balanced ins and outs. Is the PC board for this available anywhere? I also came across a design in "ETI" in the December 1982 issue for a Balanced Input Differential Preamp. This used a pair of 5534 op amps, one for each of the balanced line conductors, feeding a TL071. Any comments on the pros and cons of the two different approaches to producing balanced inputs? (D. M., Canton Beach, NSW).

- Omitting all the components between the input pins and the op amp

is not good practice, even though, as you have observed, the circuit will still work. The RF suppression components, consisting of the inductor L1, 150Ω resistor and the 100pF capacitors, are desirable in order to prevent pickup of interference, particularly AM radio stations. Second, the 100kΩ resistor on the op amp side of the 47μF capacitor should be retained so that, if the microphone is unplugged, the op amp continues to be correctly biased; otherwise there will be a loud 'pop' whenever the microphone is plugged in or out.

The 47μF capacitor is desirable to prevent the bias current of the LM833, typically around 0.5μA, from flowing through the microphone. This could lead to non-linearity or possibly demagnetisation, over a long period. Finally, the second 100kΩ resistor is required to make sure that the 47μF capacitor is always charged and does not charge via the microphone when it is plugged in; if this happened, a loud 'pop' would result.

The PC board for the balanced output circuit is available from RCS Radio Pty Ltd, 651 Forest Road, Bexley, NSW 2207. Phone (02) 587 3491.

The ETI circuit for balanced inputs would certainly work but a superior

circuit using the special purpose SSM2017 was published in the April 1995 issue of SILICON CHIP. A kit for this project is available from Altronics, in Perth.

## Altering timer for burglar alarm

I have just completed wiring up your Multi-Sector Home Burglar Alarm from the June 1990 edition and thankfully (for me) it worked straight away. My question is what do I alter to get a five minute alarm instead of the 10-minute period? And just as a query, why did you put the sector switches with the off position down? Thanking you for a really good magazine for novices as well as the brighter boys! (H. M., Ballina, NSW).

- The 10-minute timer comprises IC4, IC6 & IC7. Halving the 10-minute period is simply a matter of using the Q5 output (pin 5) of IC6 to drive IC7. So disconnect pin 6 of IC6 and connect pin 5 instead.

We're not sure what you mean by your question about the sector switches being down in the Off position. The design was presented in the form of PC boards so the way in which it was built was up to the constructor.

## Speed controller for a 2hp router

Have you produced a speed control for a 2hp router. I am using it with some large diameter bits and the recommendation is to reduce the speed for safety. I know you produced a 5A speed controller but I obviously need something bigger.

By the way, the current rating for the router is 10A. Could I upgrade your 5A design by just using a bigger Triac? (N. M., Seymour, Vic).

- The 5A speed controller is the

highest rating we have produced and it already uses a 40A Triac. As it stands, you could use the 5A design for your 2hp router provided you change the 10A fuse to a "slow-blow" type and you arrange for better heatsinking for the Triac. This would most easily be done by using a reasonable size diecast aluminium box.

Note that at the full speed setting with any half-wave speed control, the maximum speed of the router will be reduced by about 20%. So a 20,000 RPM router would immediately be reduced to a maximum of 16,000 RPM.

## Combination AM/FM radio trainer wanted

Could the AM Radio Trainer (June/July 1993) and the FM Radio Trainer (April/May 1995) be combined to make an AM/FM Radio Trainer? Over the years I have built AM valve radio sets and AM transistor sets. I did not make the FM Radio Trainer because it only had the one section.

Completely designing a radio trainer would be desirable so that a person could obtain experience aligning the AM/FM coils using a cheap oscilloscope, sweep generator or FM-AM generator. It would be a good idea if a sweep generator kit was developed for alignment of the FM section.

By this method, one would learn



## Coolant alarm for plastic radiators

I refer to the very successful coolant alarm project from the June 1994 issue. I have just purchased a new Mitsubishi Magna sedan and to my surprise, I find that the radiator appears to be of composite manufacture, with plastic head and bottom tanks moulded on to a metal heat exchanger.

The metal heat exchanger is earthed to the car body, according to my ohmmeter, and as the plastic header tank is an insulator, it would appear that a suitable sensor probe could be made by just drilling and tapping a 1/8-inch brass metal thread into the header tank. However, I would like your comments please. (B. P., Port Macquarie, NSW).

• A large number of modern cars now use radiators with plastic header tanks. While a bolt attachment to the top tank would be a simple addition, we're not keen on the idea of drilling and tapping the tank to fit a brass screw. A screw might work its way out after a time and then you really would have a loss of coolant. Nor are we keen on the idea of fitting a brass screw in close proximity to the aluminium radiator core. That seems like asking for corrosion problems.

We think it would be preferable to fit a stainless steel bolt and nut to this type of radiator, together with flat washers and a lockwasher. Naturally, this would need to be installed close to the radiator cap, in order to attach the nut and washers to the bolt.

more alignment procedures experimentally. If possible, rather than IC1-IC4 of the FM side being integrated circuits they should be completely transistorised. Then one could learn the internal structure of each circuit on the FM side. (L. F., North Bondi, NSW).

• Although FM/AM radios and tuners are standard commercial products, frequently using only one or two ICs, there is no easy way of combining our radio trainer circuits onto one PC board. These discrete circuits are quite difficult to produce on a freestanding PC board and our final versions were only arrived at after quite a few prototypes had been built.

## Car burglar alarm malfunction

I'm hoping you can help with a number of problems I'm having with the Car Burglar Alarm featured in December 1994. I've obviously botched something somewhere and anything you can suggest to get the alarm working properly would be appreciated.

After assembling the kit carefully and doing a neat soldering job, I installed it in the car and no matter what I do to the trimpots it doesn't seem to work properly at all. The car it is fitted in is a Volkswagen Beetle,

not a very complicated car in terms of wiring, so installation was easy, even for an amateur like me. About the only extra items fitted to the kit are two pin switches under the bonnet and boot which are connected to the "Immediate Sense" circuit of the alarm and a key switch as opposed to the toggle switch included in the kit.

When I arm the alarm with the key switch the LED doesn't "continuously light" as described in the assembly instructions. But after the set exit delay period, the LED starts flashing to indicate the alarm is set. When I then open a door or the bonnet or boot to set off the alarm/horn siren, the LED continues to flash instead of turning itself off to indicate it is going to sound the horn siren. However, the horn siren fails to go off at all. The LED continues to flash and switching the keyswitch to "disarm", fails to have any effect on the LED (and obviously the alarm as well) and the only way to turn it off is to push in the door pin switch of the open door. So it appears I can arm the alarm (sort of) but not disarm it. (J. C., Melbourne, Vic).

• As far as we can tell from your description, IC2 and the LED are operating normally. The LED does not start to flash until after the exit period. We suggest that you carefully check the voltages around the circuit

# AVICO

## SAFETY PRODUCTS

**Avico Electronics** markets a range of protection devices designed for use with office and household equipment such as fax machines, photocopiers, printers, computers, Hi Fi's, TVs, VCR's, FAXTAM's and others.

• AC OUTLET SURGE PROTECTOR  
• AC LINE EMI/RFI FILTER & SURGE PROTECTOR • AC/TELEPHONE LINE



### SurgePlus MSD15

#### AC OUTLET SURGE PROTECTOR

Metal Oxide Varistors (MOV's) connected to each wire provide total protection.

• Load Rating: 240Vac 50Hz 10Amps  
• Clamping Voltage: 275 Volts RMS  
• Peak Surge Current: 4500A (8/20 nano sec)  
• Response Time: <10 nano sec  
• Protection Modes: Act>Neutral, Act > Earth  
• Energy Absorption: 75 joules

### FilterPlus MSD18

#### AC LINE FILTER AND SURGE PROTECTOR

Protected by Metal Oxide Varistors (MOV's) and toroidal coils.

• Load Rating: 240Vac 50Hz 10Amps  
• Clamping Voltage: 275 Volts RMS  
• Peak Surge Current: 4500A (8/20 nano sec)  
• Response Time: <10 nano sec  
• Energy Absorption: 75 Joules  
• Filtering Characteristics:  
3KHz - 10KHz 20dB minimum rejection  
10KHz - 100KHz 30dB minimum rejection  
100KHz - 1MHz 60dB minimum rejection

### ComPlus MSD20

#### AC/TELEPHONE LINE

#### SURGE PROTECTOR

Protected by Metal Oxide Varistors (MOV's) and Gas Arrestors.

• Load Rating: 240Vac 50Hz 10Amps  
• Clamping Voltage: 275 Volts RMS  
• DC Strike Voltage: 500 VDC  
• Surge Current: 4500A (8/20 nano sec)  
• Surge MOV response Time: <10 nano sec  
• Gas Arrestor response Time: <100 nano sec  
• Energy Absorption: 75 joules

### ComPlus<sup>PRO</sup> MSD22

#### AC FILTER & SURGE PROTECTION

This is our pro model with the ability to provide both filtration and surge protection on the AC line whilst still have surge protection for your phone line.

Protected by Metal Oxide Varistors (MOV's) and Gas Arrestors with filtration on AC line.  
• Surge specifications are equal to the MSD20  
• Filtration characteristics same as MSD18



Imported and distributed by  
AVICO ELECTRONIC PTY LTD  
PHONE: (02) 624-7977  
FAX: (02) 624-7143  
Trade Enquiries Only

ASK FOR AVICO PRODUCTS AT YOUR FAVOURITE ELECTRONICS RETAIL STORE



## Door minder is insensitive

I have recently assembled the "Door Minder" kit as published in the July 1995 issue of SILICON CHIP. I find that it is not very sensitive and it only works in a small room with the windows shut and if I give the door a hefty pull. I would be most grateful if you could tell me how to make it more sensitive; the preset pot is adjusted to the most sensitive it will go. The article says it works with open windows in an adjoining room.

Also, where can I purchase the Philips ETD49/25/16 transformer components and the TEA100 nicad monitor IC for the Fast Nicad Charger, as published in the September 1995 issue?

I refer to the letter on page 7 of the April 1995 issue, on making PC boards by photocopying the original back to front and rubbing with thinners mixture on the back. I have had limited success and find it is best if the photocopy is removed whilst still moist. I say moist and not wet, as too much thinners gets underneath and smudges the pattern. When dry, doing it a second time darkens the picture but use a fresh, new photocopy.

However, the result produces a porous copper surface which has to be heavily layered with solder. An improvement can be made by going over the whole pattern with a fine felt tip pen which is water resistant. (D. S., Caloundra, Qld).

- We are surprised that your Door Minder is so insensitive. You should check that the  $0.1\mu\text{F}$  and  $1\mu\text{F}$  capacitors on IC1a's input are the correct values and that the  $1\mu\text{F}$  capacitor is inserted with the correct polarity. Also confirm that the two resistors around IC1a are  $47\text{k}\Omega$  and  $3.9\text{M}\Omega$  – a wrong value may have been fitted. Also, did you ground the case of the electret insert?

Check that the regulated DC is about 8V and the voltage on pin 1 of IC1a is 3.3V. As the circuit has a gain of 80 it only needs 10mV from the microphone to trigger the chimes. It should not be necessary to increase the gain of the circuit, as it is quite adequate. Perhaps the microphone insert is faulty.

You can get some extra gain by decreasing the  $47\text{k}\Omega$  input resistor to  $39\text{k}\Omega$  but any more variation could alter the passband of the filter.

Regarding the parts for the Fast Nicad Charger, these can be purchased from Jaycar Electronics.

and also monitor the output of IC1 to see that it delivers the correct signal from its output in response to the arm/disarm switch.

## How to reduce preamp gain

I recently put together the preamp section of your 50W amplifier design and find it very satisfactory. My amplifier and speakers are of very high sensitivity so I need much less gain than is provided. Would you please advise the correct way of changing the feedback components around IC1 to achieve closer to unity gain? I prefer to do this rather than use attenuators. (K. A., Moss Vale, NSW).

- The gain of IC1 can be reduced by increasing the  $4.7\text{k}\Omega$  resistor at pins 6 & 2. To halve the gain, increase the

$4.7\text{k}\Omega$  resistor to  $10\text{k}\Omega$ . To obtain unity gain, omit the  $4.7\text{k}\Omega$  resistor.

## Frigid remote control won't respond

I have just built the UHF remote switch from the December 1989 issue of SILICON CHIP. It is operating perfectly from a distance of 10 metres but only when the temperature is over  $20^\circ\text{C}$ . Can you advise how to overcome this problem as the temperature in Victoria is generally under  $20^\circ\text{C}$ . (P. L., Springvale North, Vic).

- Ever thought of moving to warmer climes? It appears as though one or more of the transistors or possibly one of the ICs is temperature sensitive. As a first step, we suggest you check all voltages in the circuit. Second, check all soldering on the PC boards. Cold

solder joints can be temperature sensitive. Third, with a can of freezer spray, freeze each semiconductor component to see if it causes the problem. Alternatively, replace the transistors one by one to see if you can effect a cure.

## Extended leads for a digital thermometer

Recently, I bought a digital thermometer with indoor/outdoor display from Jaycar (Cat QM-7210). I intended to extend the outdoor twin lead by a further 12 metres to enable the probe to be sited in the foliage of a bushy tree for a genuine outdoor reading. Doing this increased the leads' total resistance by about  $0.3\Omega$  which, in turn, increased the readout figure by  $7^\circ\text{C}$ . I tried counteracting this by adding  $0.3\Omega$  in parallel with the probe but then the readout for this probe disappears.

I cannot see any internal adjustment to compensate for extra lead length. Have any readers had similar experience along these lines? (M. B., Taree, NSW).

- We doubt whether the additional resistance in the probe leads has caused the increase in temperature reading. We are more inclined to think that the long leads may be picking up hash which is adding to the reading. Try connecting a  $0.1\mu\text{F}$  greencap or MKT capacitor across the probe leads where they enter the case.

## Note & Errata

**Dolby Pro Logic Surround Sound Decoder, Pt.1, November 1995:** the anode of diode D12 is shown incorrectly joined to the junction of the cathode of D14 and an associated  $10\text{k}\Omega$  resistor. Instead, D14 and the  $10\text{k}\Omega$  resistor should connect directly to push-button switch S7.

**Dolby Pro Logic Surround Sound Decoder, Pt.2, December 1995:** the resistor connected to pin 21 of IC2 is marked "300" on the layout diagram (Fig.4, p71). The correct value of this resistor is  $30\Omega$ .

**Five-Band Equaliser, December 1995:** the supply pins for IC2 on the circuit diagram (Fig.5, p24) are shown reversed. Pin 4 should go to the +15V rail, while pin 11 should go to -15V. The parts layout diagram (Fig.6, p25) is correct.

SC



# MARKET CENTRE

Cash in your surplus gear. Advertise it here in Silicon Chip.

## FOR SALE

**BUSINESS FOR SALE:** electronic service and repair business for sale in the fastest growing inland city in NSW.

Plenty of fresh air, sunshine and country hospitality. At present servicing mainly audio gear, specialising in car audio. Service agent for leading car audio brands. Regular, wide customer base. Plenty of room to expand in

premises and business, including into retail. Good lease available. This business is offered for genuine urgent sale due to the owner's ill health. Price \$45,000 WIWO. Enquiries phone (068) 84 1158.

## CLASSIFIED ADVERTISING RATES

Advertising rates for this page: Classified ads: \$10.00 for up to 12 words plus 50 cents for each additional word. Display ads (casual rate): \$25 per column centimetre (Max. 10cm). Closing date: five weeks prior to month of sale.

To run your classified ad, print it clearly in the space below or on a separate sheet of paper, fill out the form & send it with your cheque or credit card details to: Silicon Chip Classifieds, PO Box 139, Collaroy, NSW 2097. Or fax the details to (02) 979 6503.


Enclosed is my cheque/money order for \$\_\_\_\_\_ or please debit my

☐ Bankcard ☐ Visa Card ☐ Master Card

Card No.

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

Signature\_\_\_\_\_ Card expiry date\_\_\_\_\_/\_\_\_\_

Name\_\_\_\_\_

Street\_\_\_\_\_

Suburb/town\_\_\_\_\_ Postcode\_\_\_\_\_


**MicroZed** are supplying BS2 upgrade kits free with purchase of BS2 and carrier, regardless of where you bought your legit BS1. Proof of purchase required.

**NEW SPRINKLER CONTROLLER KITS:** RAIN BRAIN version uses 'C8 and switch mode supply. Features galore!! Contact **Mantis Micro Products**, 38 Garnet St, Niddrie 3042. Phone/fax (03) 337 1917.

**EDUCATIONAL ELECTRONIC KITS:** Easy to build. Guaranteed to work. Good quality. Latest technology. Cheap. Good selection. **LESSON PLANS FOR TEACHERS.** Send \$2 stamp for catalogue and price list. Log onto our bulletin board for full details. **DIY Electronics**, 22 McGregor St, Numurkah 3636. Ph/Fax (058) 62 1915. E-Mail: laurie.c@cnl.com.au BBS (058) 62 3303.

**SATELLITE DISHES:** international reception of Intelsat, Panamsat, Gorizont, Rimsat. Warehouse Sale - 4.6m Dish & Pole \$1499; LNB \$50; Feed \$75. All accessories available. Videosat, 2/28 Salisbury Rd, Hornsby. Phone (02) 482 3100 8.30-5.00 M-F.

## RCS RADIO PTY LTD

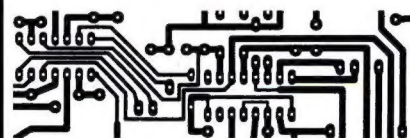

RCS Radio Pty Ltd is the only company that manufactures and sells every PC board and front panel published in SILICON CHIP, ETI and EA.

**RCS Radio Pty Ltd,**  
651 Forest Rd, Bexley 2207.  
Phone (02) 587 3491



## MicroZed Computers

Specialist in controllers with on-chip interpreters  
Boards, Software, Chipsets, Books.  
Easy to learn. Fast prototyping  
Low cost. Chipsets available for volume production  
Easy to use – get going in hours, not months  
Raw PIC chips available too, JW & OTP

Send 2 x 45c postage stamps for information package.

**PO Box 634 (296 Cook's Rd), ARMIDALE 2350.**  
Ph (067) 722 777 Fax (067) 728 987  
Mobile (014) 036 775

## PARALLAX

BASIC Stamp I 8 I/O; and BSII 16 I/O

### Scott Edwards Electronics

Accessories for Stamp and second source for Stamp I

### Versa Tech

TICKIT – a 21 I/O PIC based controller

### NEW Micro

68HC11 F1 boards with resident FORTH. Other languages  
supplied, ASM. Small C & BASIC

## MEMORY \* DRIVES \* MODEMS

**SPECIAL!** (Incl Tax)  
1Mbx9 – 70ns Simm \$52  
1Mbx9 – 80ns Simm \$38

SIMMS	(Parity/No Parity)		
4MB 30 PIN-70	\$210	\$196	
4MB 72 PIN-70	\$217	\$193	
8MB 72 PIN-70	\$435	\$364	
16MB 72 PIN-70	\$834	\$728	
32MB 72 PIN-70	\$1663	\$1428	
<b>EDO SIMMS</b>			
4MB (1Mbx32)-70ns	\$215		
8MB (2Mbx32)-70ns	\$425		
<b>MAC</b>			
8MB PBOOK	\$435		
<b>VIDEO MEMORY</b>			
256KX16 70ns (SOJ)	\$30		
256KX16 70ns (ZIP)	\$57		

LASER PRINTER MEMORY	
HP 2MB UPGRADE	\$158
CO-PROCESSORS	
80387SX/DX to 40MHz	\$90
COMPAQ	
8MB CONTURA AERO	\$445
TOSHIBA PORTEGE/SATELLITE	
8MB / 16MB	\$650 / \$1200
DRIVES SEAGATE	
545MB EIDE 14ms 3yr	\$264
850MB EIDE 11ms 3yr	\$308
1080MB EIDE 11ms 3yr	\$365
2150MB SCSI 9ms 5yr	\$1250
MODEMS (Includes Sales Tax)	
14,400 BANKSIA 5yr W	\$283
14,400 SPIRIT 2yr W	\$229
28,800 BANKSIA V.F.C	\$385
28,800 SPIRIT V.34/V.F.C	\$410

### EX TAX PRICING AS AT NOVEMBER '95

Sales Tax 22%, O/Night Delivery \$8. Ring For Latest Prices.  
Credit Cards Welcome. We Also Buy And Trade-In Memory.

**PELHAM**

Ph: (02) 980 6988  
Fax: (02) 980 6991

Suite 6, 2 Hillcrest Rd, Pennant Hills, 2120.

**ETI PIC Basic Interpreter:** BASIC57/  
XT/P \$45, BASIC84/04/P \$45. 2K  
EEPROM \$8, 8K EEPROM \$16. PC  
serial port driven. 18 and 28-pin PCB  
\$20, 4MHz Xtl \$5. Windows Software  
free. InfoFax: Voice then Fax, (03) 9338  
2935 Password '# 1111'. Don McKenzie,  
29 Ellesmere Crescent, Tullamarine  
3043. Phone (03) 9338 6286.

**MICROCRAFT PRESENTS:** Dunfield  
(DDS) products are now available ex-  
stock at a new low price; please ask for  
our catalogue. Micro C, the affordable  
"C" compiler for embedded applications.  
Versions for 8051/52, 8086, 8096,  
68HC08, 6809, 68HC11 or 68HC16  
\$139.95 each + \$3 p&h • Now on spe-  
cial is the SDK, a package of ALL the  
DDS "C" compilers for \$399 + \$6 p&h •  
EMILY52 is a PC based 8051/52 high  
speed simulator \$69.95 + \$3 p&h • DDS  
demo disks \$7 + \$3 p&h • VHS VIDEO  
from the USA (PAL) "CNC X-Y-Z using  
car alternators" (uses car alternators as  
cheap power stepper motors!) \$49.95 +  
\$6 p&h (includes diagrams) • Device  
programming EPROMs/PALs etc from

## Printed Circuit Board Manufacture

Best Prices on Prototypes and  
Production Quantities.  
**INSTANT PCB's**  
P O Box 448 Avalon Beach 2107  
Ph (02) 974 1189 Fax (02) 974 5491

## SPEAKER PARTS DIRECT

**vifa Peerless DYNAUDIO**

Send \$10 cheque, money order or fax with  
credit card details for our book of complete  
specifications on every speaker driver we  
stock, as well as specials list and details  
on Solen and Bennic capacitors, inductors,  
terminals, flared ports and other speaker  
parts. *Bulk Vifa buyers: We are always  
much cheaper than anyone else. Call us!*

**SCAN AUDIO** Pty Ltd Ph: (03) 9429 2199  
P.O. Box 242, Hawthorn VIC 3122 Fx: (03) 9429 9309

\$1.50 • Fixed price electronic design  
and PCB layout • Credit cards accepted  
• All goods sent certified mail • Call Bob  
for more details. MICROCRAFT, PO  
Box 514, Concord NSW 2137. Phone  
(02) 744 5440 or fax (02) 744 9280.

**COMPLETE WORKSHOP PROGRAM:**  
suit IBM compatible 386 or better com-  
puter. Handles: Stock Control, Sales,  
Service Records, Debits, Credits, Faults,  
Service Manuals and Phone Directory.  
Full price \$399.00. For demo disk, phone  
or fax your details to (045) 71 1640.  
Jack Albers Electronics & Software  
Development.

**C COMPILERS:** Dunfield compilers are  
now even better value. Everything you  
need to develop C and ASM software for  
68HC08, 6809, 68HC11, 68HC16,  
8051/52, 8080/85, 8086 or 8096:  
\$140.00 each. Macro CrossAssemblers  
for these CPUs + 6800/01/03/05 and  
6502: \$140 for the set. Debug monitors:

## Advertising Index

Altronics .....	66-68
Av-Comm .....	64,65
Avico Electronics .....	93
Car Projects Book .....	OBC
Dick Smith Electronics .....	18-21
Harbuch Electronics .....	65
Instant PCBs .....	96
Jaycar .....	45-52
Kits-R-US .....	64
L & M Satellite Supplies .....	3
MicroZed Computers .....	96
Oatley Electronics .....	8-9
Pelham .....	96
Railway Projects Book .....	IFC
RCS Radio .....	95
Resurrection Radio .....	89
Rod Irving Electronics .....	35-39
Scan Audio .....	96
Silicon Chip Back Issues .....	90
Silicon Chip Bookshop .....	85
Silicon Chip Walchart .....	IBC

## PC Boards

Printed circuit boards for SILICON  
CHIP projects are made by:

- RCS Radio Pty Ltd, 651 Forest Rd, Bexley, NSW 2207. Phone (02) 587 3491.
- Marday Services, PO Box 19-189, Avondale, Auckland, NZ. Phone (09) 828 5730.

\$70 for 6 CPUs. All compilers, XASMs  
and monitors: \$400. 8051/52 or 80C320  
simulator (fast): \$70. Demo disk: FREE.  
All prices + \$5 p&p. GRANTRONICS  
PTY LTD, PO Box 275, Wentworthville  
2145. Ph/Fax (02) 631 1236 or Internet:  
lgrant@mpx.com.au.


**HC11s AND ICs** - <http://worf.albany-is.com.au/bobhome.html>.

**SOUND TECHNOLOGY** 3100A/3200A  
programmable transmission/audio test  
system, operating manual, \$9500. (03)  
9499 1524.


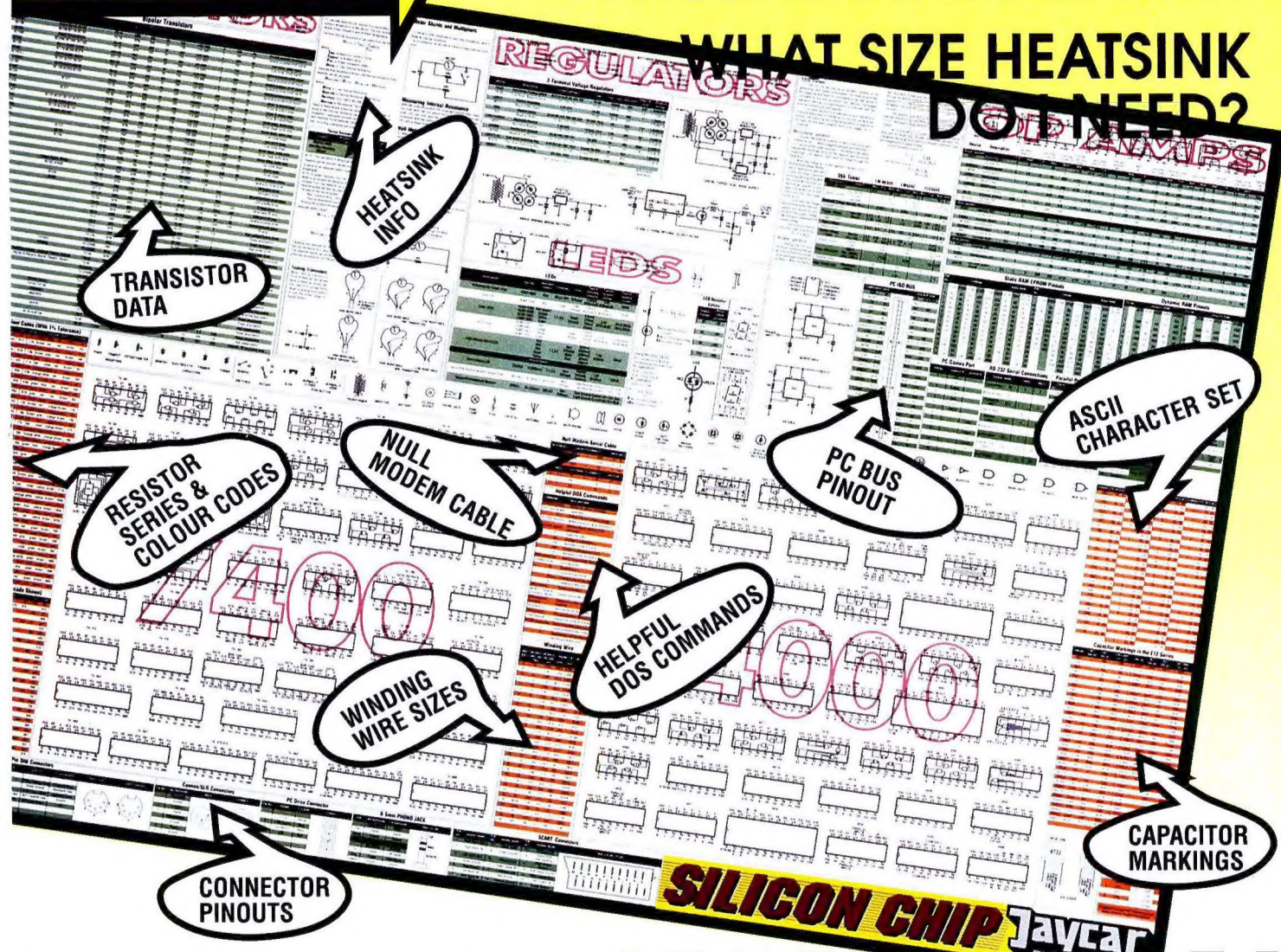
# QUICK INFO

WHAT'S THE PINOUT  
OF A 74H138?  
WHICH PIN OF A BC547  
IS THE BASE?  
HOW DO YOU WIRE UP  
A NULL MODEM CABLE?  
WHAT SIZE HEATSINK  
DO I NEED?



This giant wallchart (850 x 580mm) has been specially prepared by Silicon Chip & Jaycar. Absolutely jam packed with info on the most frequently asked questions by hobbyists, technicians, servicemen & engineers.

Folded: \$8.95 + \$2 p&p. Unfolded (in mailing tube): \$9.95 + \$4.50 p&p

**Yes!** Please send me \_\_\_\_ copies of the Silicon Chip/Jaycar Wallchart. Enclosed is my cheque for \$\_\_\_\_ or please debit my: ☐ Bankcard ☐ Visa Card ☐ Master Card

Card No. \_\_\_\_\_

Signature \_\_\_\_\_ Card expiry date \_\_\_\_/\_\_\_\_


Name \_\_\_\_\_ Phone No. (\_\_\_\_) \_\_\_\_\_

Street \_\_\_\_\_

Suburb/town \_\_\_\_\_ Postcode \_\_\_\_\_

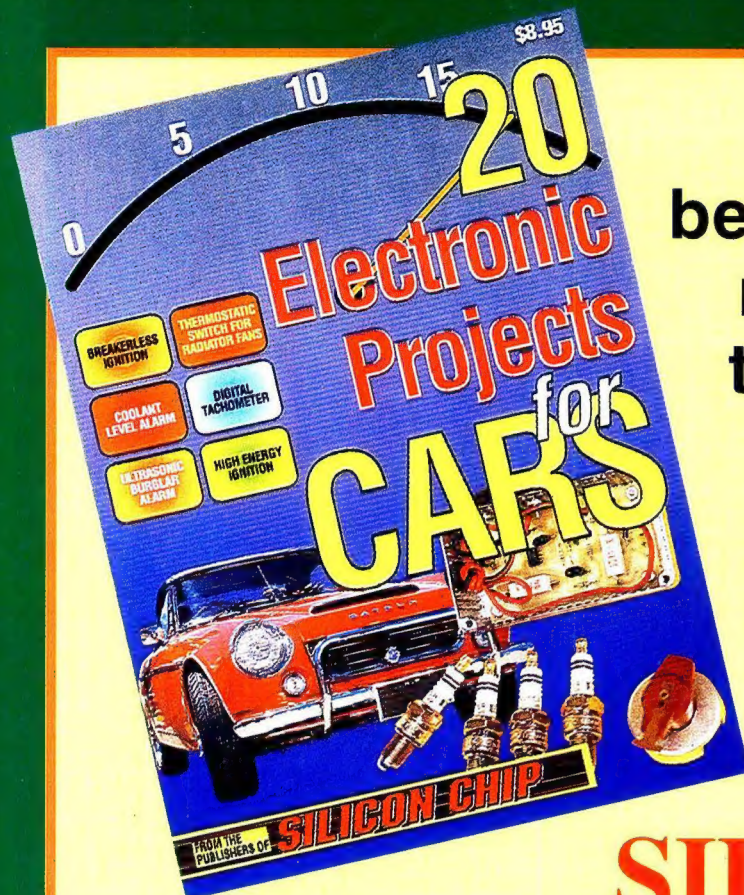Please supply: ☐ Folded (\$10.95) ☐ Unfolded (\$14.45)





**SILICON CHIP'S 20  
best car projects are  
now all together in  
this 112-page book**

**ORDER  
DIRECT  
FROM  
SILICON CHIP**

This book has 20 electronic projects for cars, including high energy & breakerless ignition systems, an ultrasonic alarm, a digital tachometer, a coolant level alarm, a flashing alarm light, a talking headlight reminder, a UHF remote switch & a thermostatic switch for electrically operated radiator fans. And there are eight quick circuit ideas as well.

**Price: \$8.95 (plus \$3 p&p if ordering from Silicon Chip)**

*Yes!* Please send me \_\_\_\_\_ copies of **20 Electronic Projects For Cars**

Enclosed is my cheque/money order for \$\_\_\_\_\_ or please debit my

☐ Bankcard    ☐ Visa Card    ☐ Master Card

Card No.

Signature \_\_\_\_\_ Card expiry date \_\_\_\_/\_\_\_\_/\_\_\_\_

Name \_\_\_\_\_ Phone No (\_\_\_\_) \_\_\_\_\_

PLEASE PRINT

Street \_\_\_\_\_

Suburb/town \_\_\_\_\_ Postcode \_\_\_\_\_

**Or fill in & mail  
or fax this  
easy-order form**

Order today by phoning  
(02) 9979 5644 & quoting  
your credit card number;  
or fill in the coupon & fax  
it to (02) 9979 6503; or mail  
the coupon to: Silicon  
Chip Publications, PO Box  
139, Collaroy, NSW 2097.